

EQUAȚII DE DIMENSIONARE $\left\{ \begin{array}{l} R_{IN} \geq R_4 \Rightarrow AVEG R_4 = 6K\Omega \\ R_{TH} \geq 6K\Omega \end{array} \right.$

$$\left\{ \begin{array}{l} R_3 + R_2 + R_1 + R_0 = 4 R_4 \quad (1) \\ R_2 + R_1 + R_0 = 2(R_4 + R_3) \quad (2) \\ R_1 + R_0 = R_4 + R_3 + R_2 \quad (3) \\ R_0 = 0.5 \times (R_4 + R_3 + R_2 + R_1) \quad (4) \end{array} \right. \quad |A_V| = \frac{R_0}{R_F}$$

(4) - (2)

$$R_3 = 2R_4 - 2R_3 \Rightarrow R_3 = \frac{2}{3} R_4 = \frac{4}{6} R_4 \quad ; \quad R_3 = 4K\Omega$$


(2) - (3)

$$R_2 = R_4 + R_3 - R_2 \Rightarrow R_2 = \frac{1}{2} \cdot \frac{5}{3} R_4 = \frac{5}{6} R_4 \quad ; \quad R_2 = 5K\Omega$$

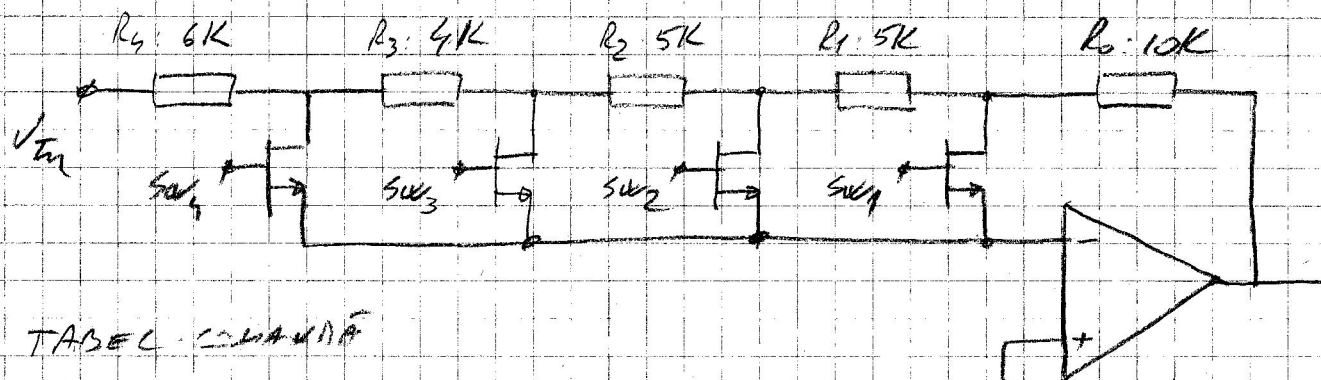(3) - (4)

$$R_1 = 0.5 \times (R_4 + R_3 + R_2) - 0.5 \times R_1 \Rightarrow R_1 = \frac{5}{6} R_4 \quad R_1 = 5K\Omega$$

$$(4) \quad R_0 = \frac{1}{2} \times \left(R_4 + \frac{4}{6} R_4 + \frac{5}{6} R_4 + \frac{5}{6} R_4 \right) \Rightarrow R_0 = \frac{10}{6} R_4 \quad R_0 = 10K\Omega$$



TABEL COMBINAȚII

SW4	SW3	SW2	SW1	R _G	R _F	A _V [%]	A _V [dB]	R _{IN}	V _{out} ?
VDD	0	0	0	6K	24K	4	12	6K	
0	VDD	0	0	10K	20K	2	6	10K	
0	0	VDD	0	15K	15K	1	0	15K	
0	0	0	VDD	20K	10K	0,5	-6	20K	