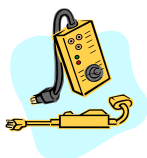


SWITCHING DC TWO-PORT NETWORKS



I. OBJECTIVES

- To understand the link between the structure and the functions of two-port DC networks.
- To understand the way to build up the voltage multipliers (double and triple) using simple two-port DC networks.



II. COMPONENTS AND INSTRUMENTATION

You will use a breadboard, two semiconducting diodes of 1N4184 type (the stripe indicates the cathode) and two 330 nF capacitors. Because you will apply and measure both dc and ac voltages you will need a dc regulated voltage supply, a signal generator, a digital multimeter and a dual channel oscilloscope.



III. THEORETICAL ASPECTS

The DC two-port networks are switching circuits which containing diodes and capacitors. They have the same circuit configurations as the RD two-port networks, but instead of R they have C.

1. TEMPORAL EXTREME (MAXIMUM/MINIMUM) DC TWO-PORT NETWORKS

We will consider the DC two-port network in Fig.1.

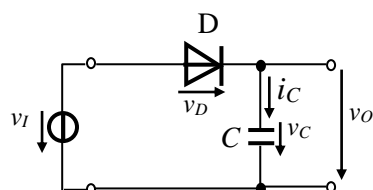


Fig. 1. Positive peak detector.

To analyze this circuit let the input signal be a triangular waveform and let the capacitor be initially discharged. We want to find out the output voltage $v_O(t)$, which is the same with the one across the capacitor $v_O(t) = v_C(t)$, and the voltage across the diode $v_D(t)$. To start with, let us also assume the diode to be ideal.

The potentials at both terminals of the diode can be changed in time. As long as v_D tends to a positive value, the diode conducts, $v_D=0V$, the capacitor charges up to the instantaneous value of the input voltage and $v_C(t)$ increases. A current $i_C > 0$ flows through the circuit, whose value is determined only by the value of the capacitor and the rate of increase of the input voltage:

$$i_C = C \frac{dv_I}{dt}$$

Due to the ideal diode, the output voltage will be equal to the input voltage.

As long as $v_D < 0V$, the diode is cutoff, so there is no current through the circuit, which makes the voltage across the capacitor to remain unmodified: $v_C(t) = \text{constant}$.

According to KVL we have:

$$v_D(t) = v_I(t) - v_O(t)$$

The waveforms of the output voltage and of the voltage across the capacitor can be visualized in Fig. 2.

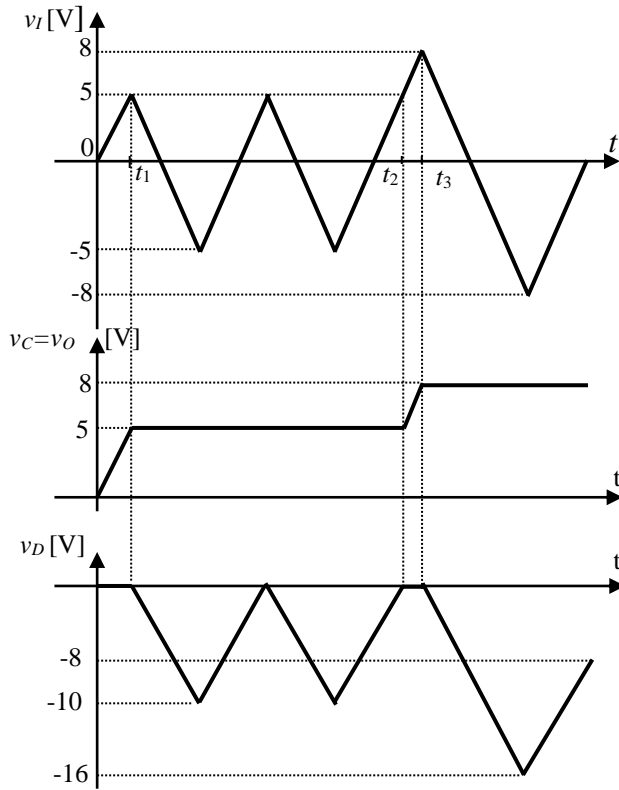


Fig. 2. Waveforms for the positive peak detector

We can notice that at each moment of time the value of the output voltage v_O is equal to the greatest positive value taken by the input voltage at every previous time moment. For this reason the circuit is called a **maximum two-port or positive peak detector**.

If we consider a voltage drop of 0.7V across the conducting diode, for $t \in [t_1, t_2]$; $v_O = 4.3V$ and for $t > t_3$, $v_O = 7.3V$.

To obtain a **minimum two-port network** we can use a circuit similar to the one for the maximum, but reversing the orientation of the diode.

2. TRANSLATION DC TWO-PORT NETWORKS

For the circuit in Fig. 1, if we consider the output across the diode, we can re-draw the circuit as in Fig. 3.

The voltage waveforms remain as in Fig. 2, only that the output voltage will be considered across the diode, $v_O(t) = v_D(t)$.

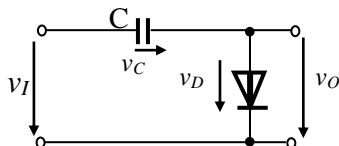


Fig. 3. Downward translation circuit

As the relationship $v_O(t) = v_I(t) - v_C(t)$ shows us, at every moment of time the output voltage results by translating downward the voltage v_I , with the voltage across the capacitor. Because $v_C(t) \geq 0$, v_I is always translated towards negative values, and that is why the circuit is called a **downward**

translation DC two-port network. Please note that in this circuit the voltage across the capacitor is always positive and the output voltage is always smaller than or equal to zero.

The circuit shown in Fig.4 is an **upward translation DC two-port network**:

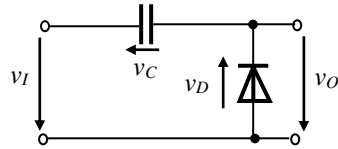


Fig.4. Upward translation circuit.

Its corresponding waveforms are plotted in Fig.5 with a full line for the ideal diode and with a broken line for diodes with 0.7V voltage drop across for conducting diodes. The output voltage v_O is given by the equation:

$$v_O(t) = v_I(t) + v_C(t)$$

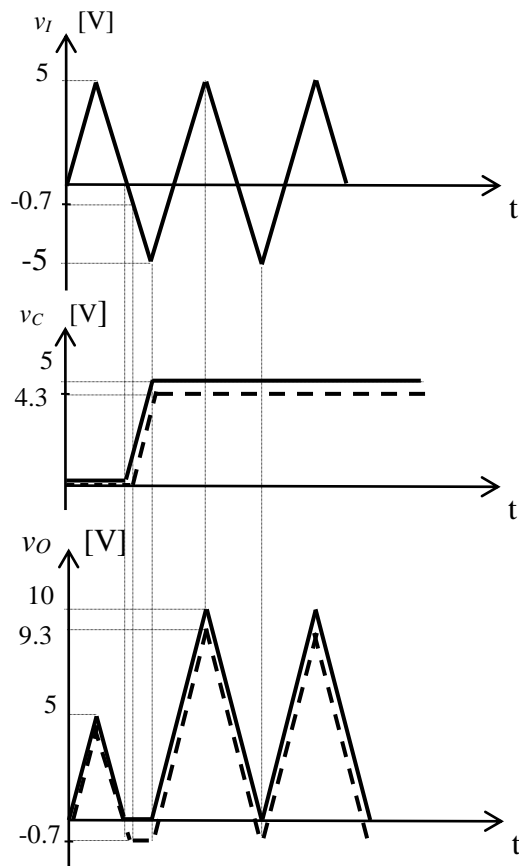


Fig. 5. Waveforms of the upward translation two-port network in two cases:
 D ideal; ———
 0.7 V across D in conduction - - -

Because $v_C \geq 0$; v_I is translated upwards, at every moment, with a value equal to the voltage across the capacitor v_C , that is the absolute value of the negative input voltage peak until that moment.



IV. PREPARATION

The exercises in this paragraph will be solved using the constant voltage drop diode model.

1.P. TEMPORAL EXTREME (MAXIMUM/MINIMUM) DC TWO-PORT NETWORKS

WAVEFORMS AND OPERATION OF THE CIRCUIT

- How do the waveforms for $v_O(t)$ and $v_D(t)$ look like, in steady state, for the circuits shown in Fig. 8 and Fig. 9 if $v_I(t)=5V$ d.c. (Fig.8) and $v_I(t)=-5V$ d.c. (Fig.9)?
- How do the waveforms for $v_O(t)$ and $v_D(t)$ look like, in steady state, for the circuits shown in Fig. 8 and Fig. 9 if $v_I(t)$ is a sinusoidal voltage with 0.3V amplitudes?
- How do the waveforms for $v_O(t)$ and $v_D(t)$ look like, in steady state, for the circuits shown in Fig. 8 and Fig. 9 if $v_I(t)$ is a sinusoidal voltage with 10V amplitudes?

2.P. TRANSLATION TWO-PORT DC NETWORK (UPWARD/DOWNWARD)

WAVEFORMS AND OPERATION OF THE CIRCUIT

- How do the waveforms for $v_O(t)$ and $v_C(t)$ look like, in steady state, for the circuits shown in Fig. 10 and Fig. 11 if $v_I(t)$ is a sinusoidal voltage with 0.3V amplitudes?
- How do the waveforms for $v_O(t)$ and $v_C(t)$ look like, in steady state, for the circuits shown in Fig. 10 and Fig. 11 if $v_I(t)$ is a sinusoidal voltage with 10V amplitudes?

V. EXPLORATIONS AND RESULTS

1. TEMPORAL EXTREME (MAXIMUM/MINIMUM) DC TWO-PORT NETWORKS

1.1 TEMPORAL MAXIMUM TWO-PORT NETWORK - WAVEFORMS AND THE OPERATION OF THE CIRCUIT



Exploration

Build the circuit shown in Fig. 8.

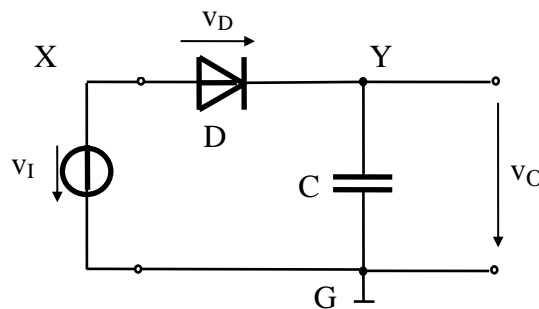


Fig. 8. Temporal maximum two-port

- You will apply at the input a 5V d.c. voltage from dc regulated voltage supply.
- V_D and V_O are measured using a digital multimeter.
- At the input of the circuit apply a sinusoidal voltage with 500 Hz frequency of and 0.3V amplitude obtained from the signal generator.
- The signals v_I and v_O are displayed on the oscilloscope set in Y-t mode, both of the channels being directly coupled and having 0V in the centre of the screen. The two leads are connected in the points X, Y and the ground in the point G.
- The measurements are done again for 10V amplitude of v_I .



Results

- The values of v_O and v_D for $v_I=5V$ d.c.
- The waveforms for $v_I(t)$, $v_O(t)$ and $v_D(t)$ considering 0.3V and 10V amplitude for the sinusoidal input voltage; $v_D(t)$ is obtained from the difference between $v_I(t)$ and $v_O(t)$.

1.2 TEMPORAL MINIMUM TWO-PORT NETWORK - WAVEFORMS AND THE OPERATION OF THE CIRCUIT



Exploration

Build the circuit shown in Fig. 9.

- You will apply at the input a - 5V d.c. voltage from dc regulated voltage supply.
- V_D and V_O are measured using a digital multimeter.
- At the input of the circuit apply a sinusoidal voltage with 500 Hz frequency of and 0.3V amplitude obtained from the signal generator.
- The signals v_I and v_O are displayed on the oscilloscope set in Y-t mode, both of the channels being directly coupled and having 0V in the centre of the screen. The two leads are connected in the points X, Y and the ground in the point G.
- The measurements are done again for 10V amplitude of v_I .

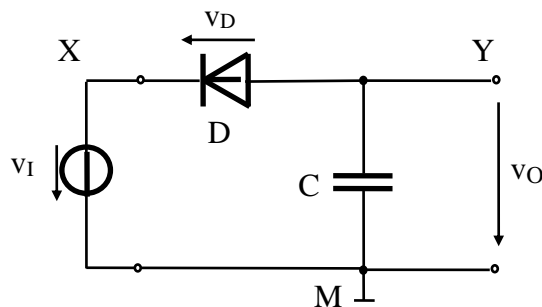


Fig. 9. Temporal minimum two-port



Results

- The values of v_O and v_D for $v_I= -5V$ d.c.
- The waveforms for $v_I(t)$, $v_O(t)$ and $v_D(t)$ considering 0.3V and 10V amplitude for the sinusoidal input voltage; $v_D(t)$ is obtained from the difference between $v_I(t)$ and $v_O(t)$.

2. TRANSLATION TWO-PORT DC NETWORK (UPWARD/DOWNWARD)

2.1 UPWARD TRANSLATION DC TWO-PORT NETWORK – WAVEFORMS AND THE OPERATION OF THE CIRCUIT



Exploration

Build the circuit shown in Fig. 10.

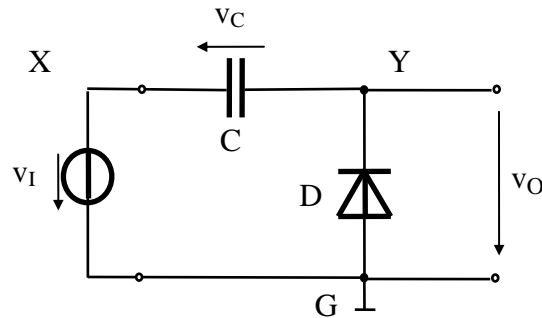


Fig. 10. Upward translation two-port

- At the input of the circuit it is applied a sinusoidal voltage with frequency of 500 Hz and amplitude of 0.3V obtained from the signal generator.
- The signals v_I and v_O are visualized on the calibrated oscilloscope set in Y-t mode, both of the channels being directly coupled and having 0V in the centre of the screen. The two leads are connected in the points X, Y and the ground in the point G.
- The measurements are done again for 10V amplitude of v_I .



Results

- The waveforms for $v_I(t)$, $v_O(t)$ and $v_D(t)$ considering the following values for the amplitude of the sinusoidal input voltage: 0.3V and 10V. $v_C(t)$ is computed as the difference between $v_I(t)$ and $v_O(t)$.

2.2 DOWNWARD TRANSLATION DC TWO-PORT NETWORK – WAVEFORMS AND THE OPERATION OF THE CIRCUIT



Exploration

Build the circuit shown in Fig. 11.

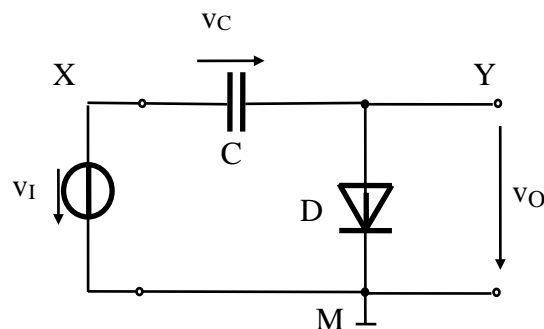


Fig. 11. Downward translation two-port

- At the input of the circuit it is applied a sinusoidal voltage with frequency of 500 Hz and amplitude of 0.3V obtained from the signal generator.
- The signals v_I and v_O are visualized on the calibrated oscilloscope set in Y-t mode, both of the channels being directly coupled and having 0V in the centre of the screen. The two leads are connected in the points X, Y and the ground in the point G.

- The measurements are done again for 10V amplitude of v_i .



Results

- The waveforms for $v_i(t)$, $v_o(t)$ and $v_D(t)$ considering the following values for the amplitude of the sinusoidal input voltage: 0.3V and 10V. $v_C(t)$ is computed as the difference between $v_i(t)$ and $v_o(t)$.

REFERENCES

1. Oltean, G., Electronic Devices, Editura U.T. Pres, Cluj-Napoca, ISBN 973-662-220-7, 2006
2. Sedra, A. S., Smith, K. C., Microelectronic Circuits, Fifth Edition, Oxford University Press, ISBN: 0-19-514252-7, 2004
3. <http://www.bel.utcluj.ro/dce/didactic/ed/ed.htm>