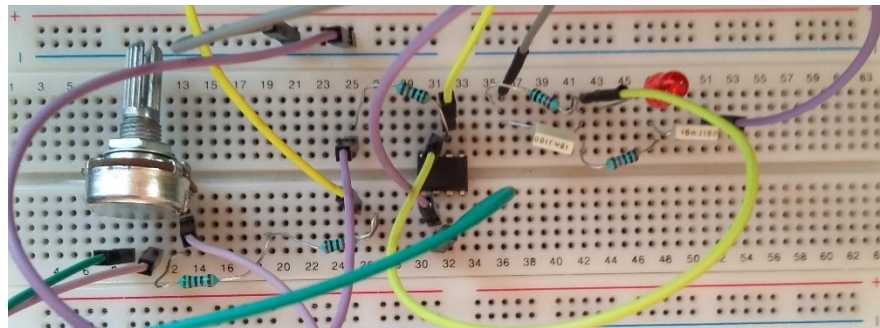




ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C1 – Introduction. Fundamentals.



Contents

- Course presentation
- Desired outcome. Evaluation.
- Fundamentals

Course presentation

Fundamentals

- Electrical signals
- Relations and laws for electrical circuits
- RC circuits – time and frequency response

Diodes (D)

- Types, operating principle, characteristic, parameters
- Diode circuits
- Zener diodes, LEDs


Operational Amplifiers (OpAmps)

- Ideal OpAmp, operating principle, characteristics, parameters, operating modes
- OpAmp comparators
- OpAmp amplifiers
- Applications with OpAmp


Transistors (T)

- Types, operating principles, characteristics, parameters
- Bipolar junction transistors (BJTs)
- Field-effect transistors (MOSFET)

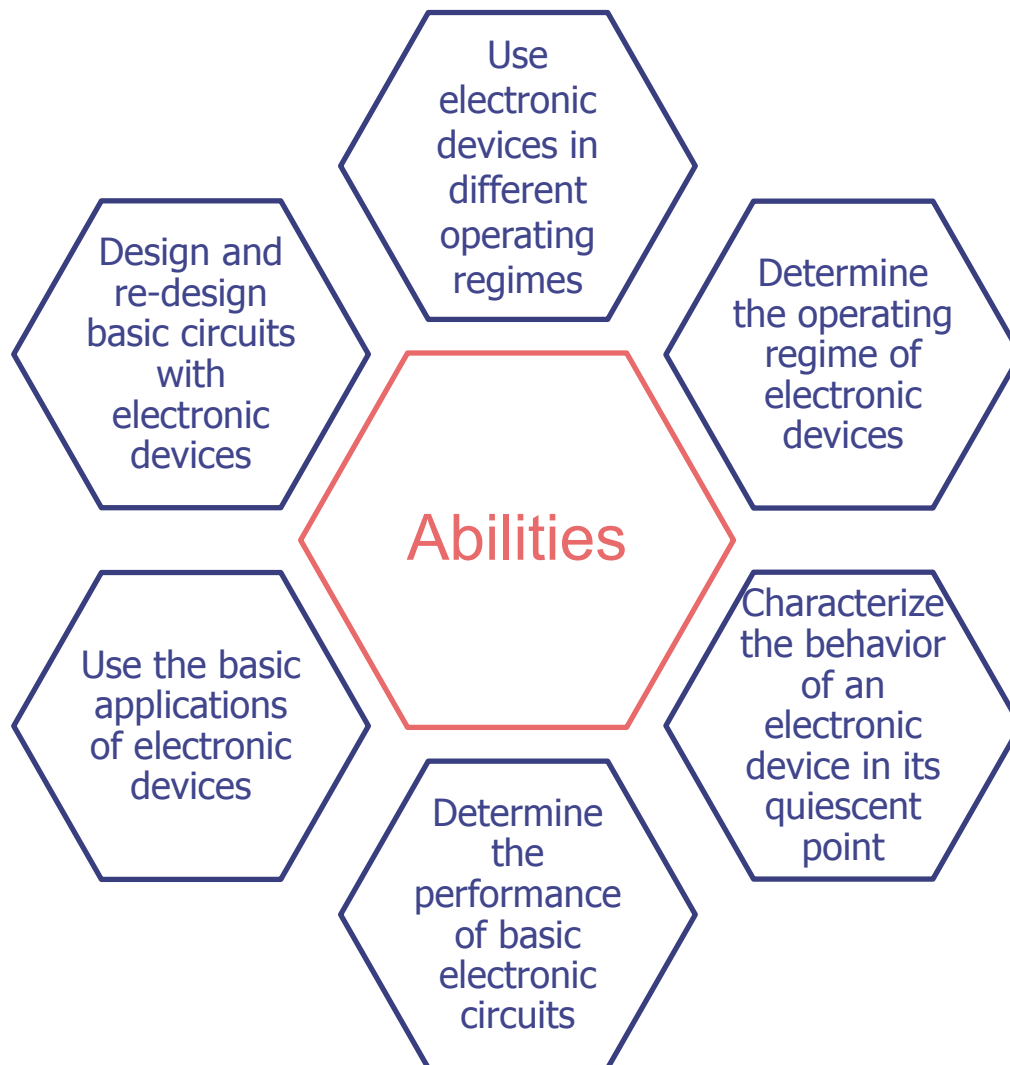At the end of the semester, you will be able to



Provided that you spend

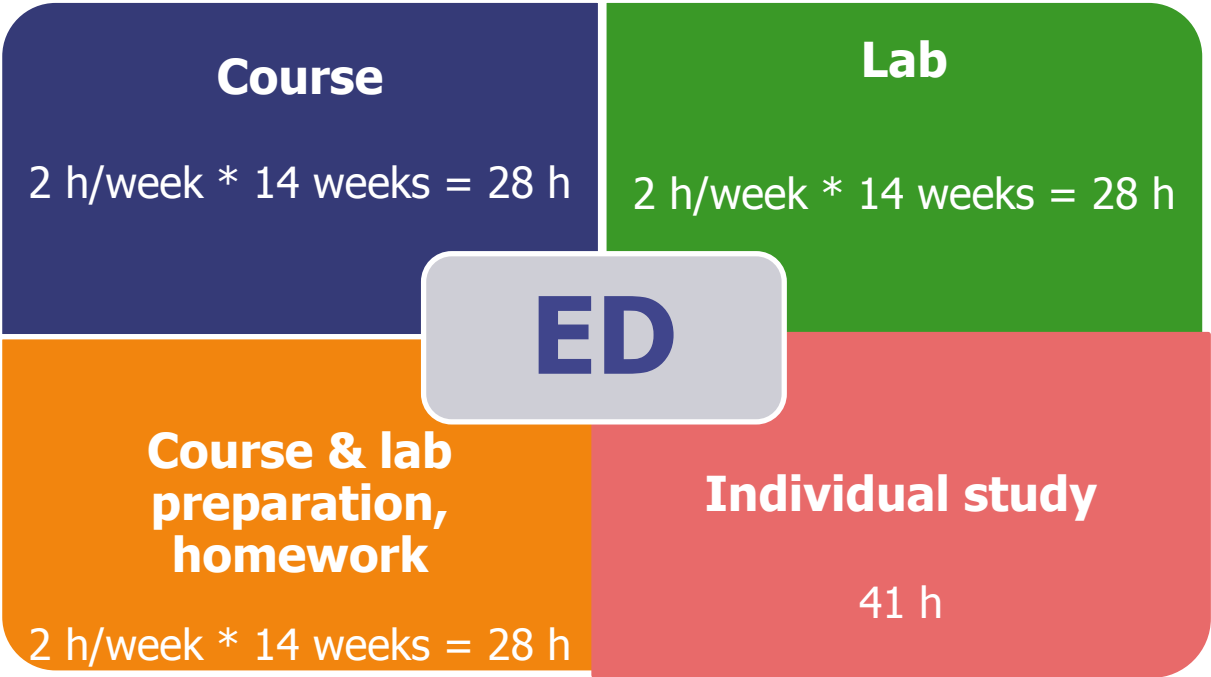

www.bel.utcluj.ro/dce/didactic/ed/

Evaluation

Written exam (**E**)
0...10 points


- problem solving

Laboratory (**L**)
0...10 points

- full attendance
- activity
- practical test


Course homeworks (**H**)
0...10 points

- 10 homeworks - optional

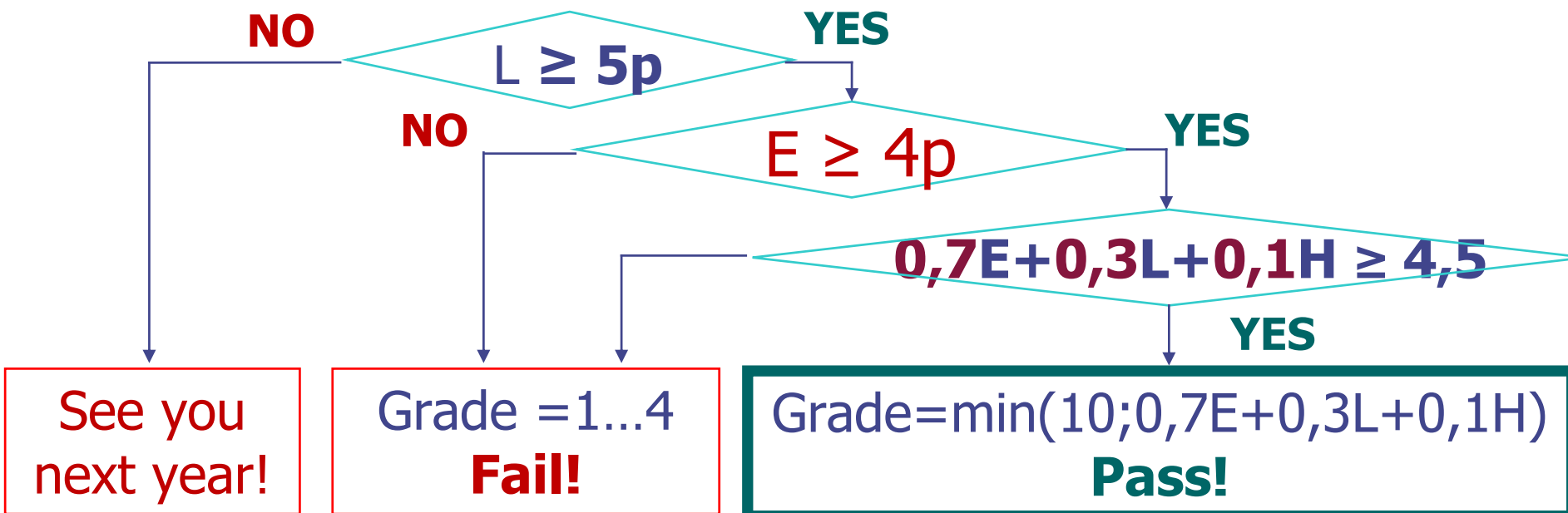


Fundamentals

➤ Electrical signals

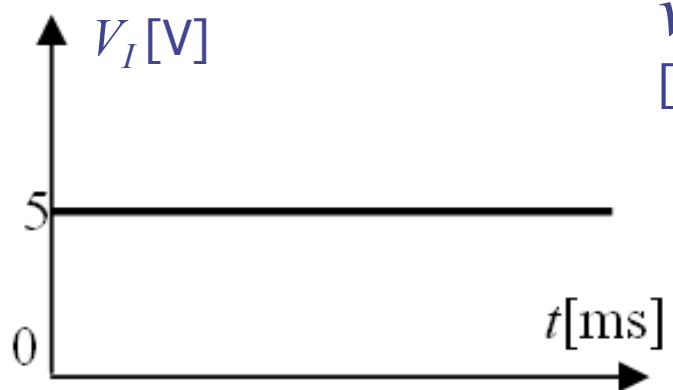

a)

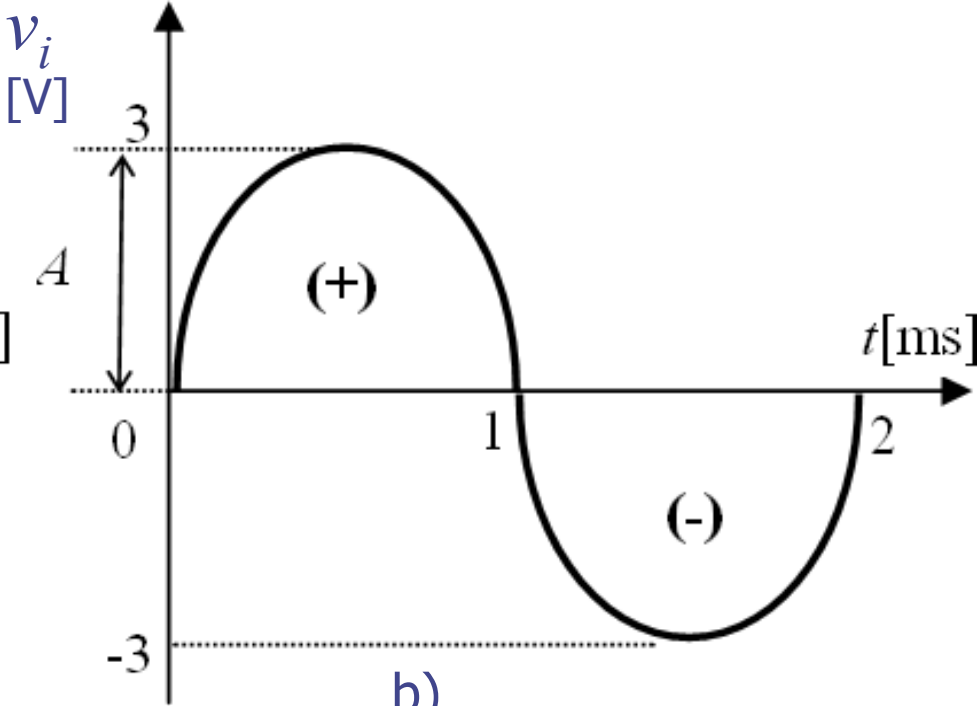

b)


Time variation of a:

a) continuous voltage (dc);


b) sinusoidal voltage (ac)

Fundamentals


➤ Sources. Notations.

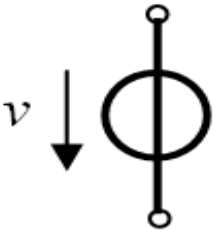


ac voltage

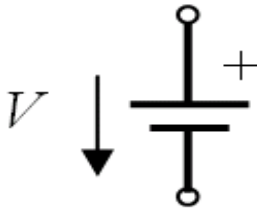

dc voltage

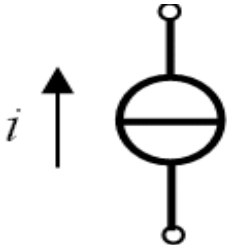


current

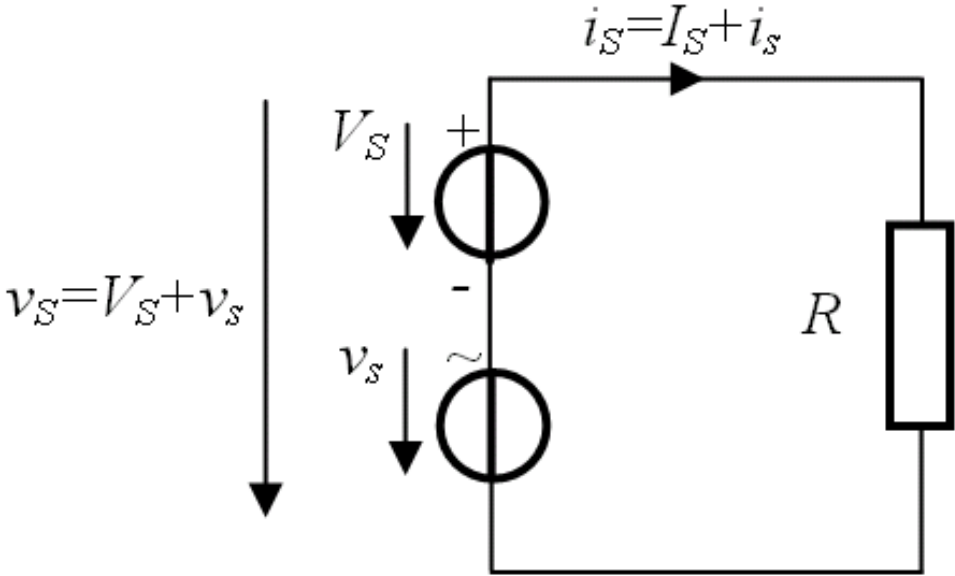

Fundamentals

- Ohm's law. Kirchhoff's laws.

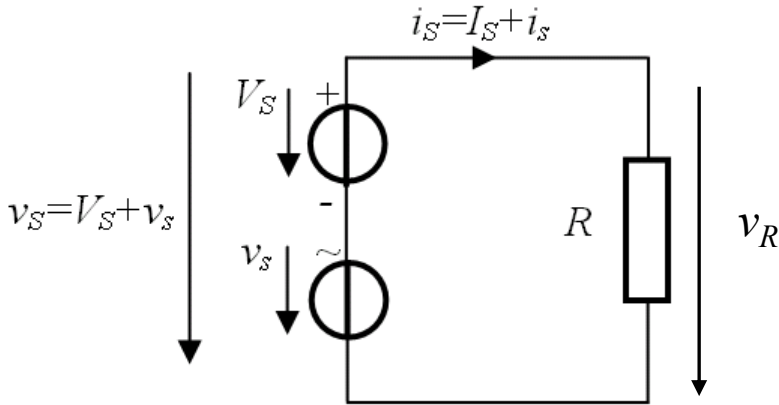

Ohm's law


$$v_R = i_S R$$

Kirchhoff's voltage law (KVL)

$$v_S - v_R = 0$$

Fundamentals

➤ Resistive divider

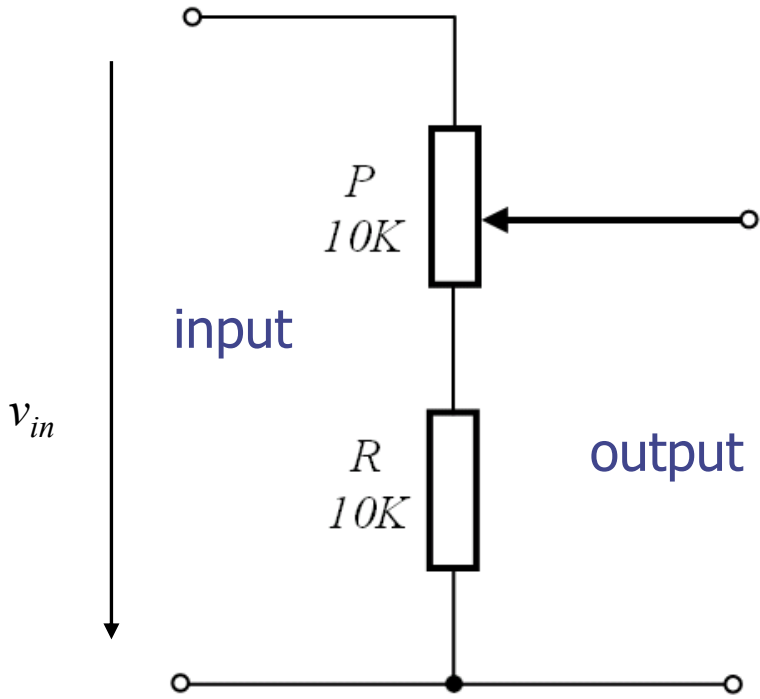


$$v_{out} = \frac{R + kP}{R + P} v_{in}$$

Adjustable voltage divider


Fundamentals

➤ Superposition method

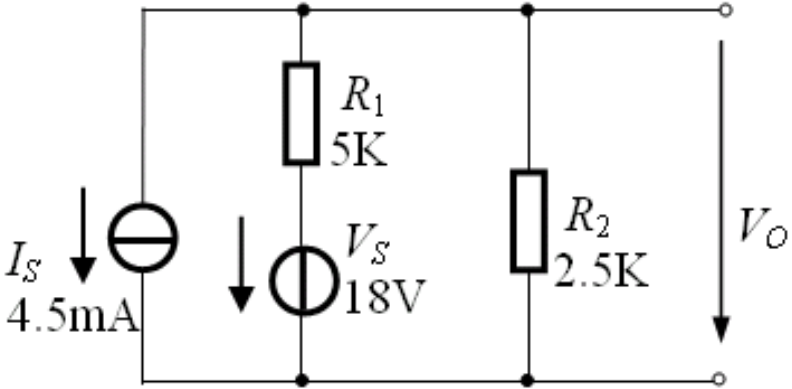


$$V_O = V_{O1} + V_{O2}$$

a)

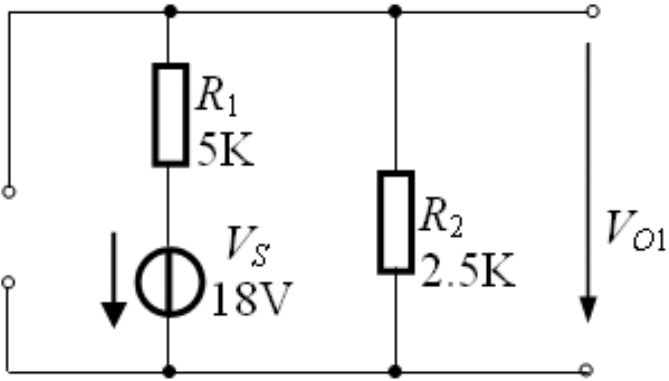


b)

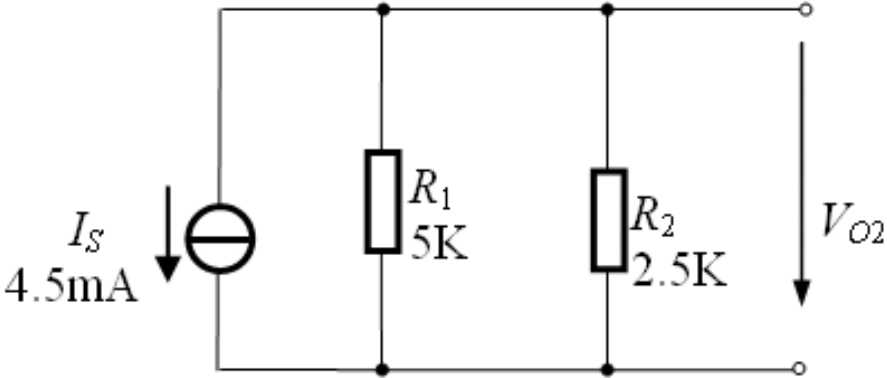

c)

Fundamentals

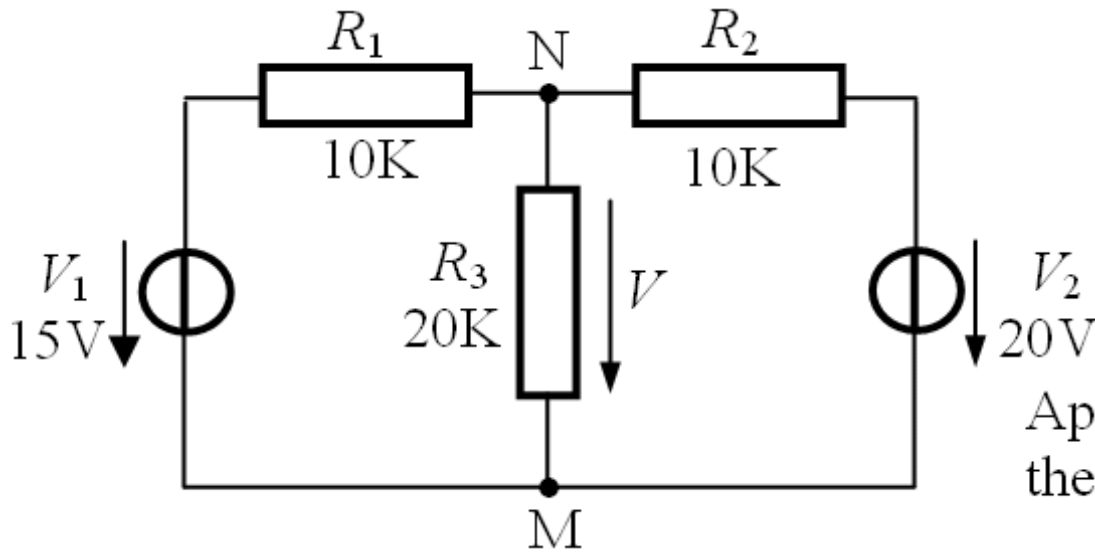➤ Millman's theorem (nodes potential theorem)




Application of Millman's theorem.

M - the reference point (ground)

$$V_N = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} = \frac{\frac{15}{10} + \frac{20}{20}}{\frac{1}{10} + \frac{1}{20} + \frac{1}{20}} = 12.5 \text{ V}$$

Fundamentals

➤ Power. Power transfer.

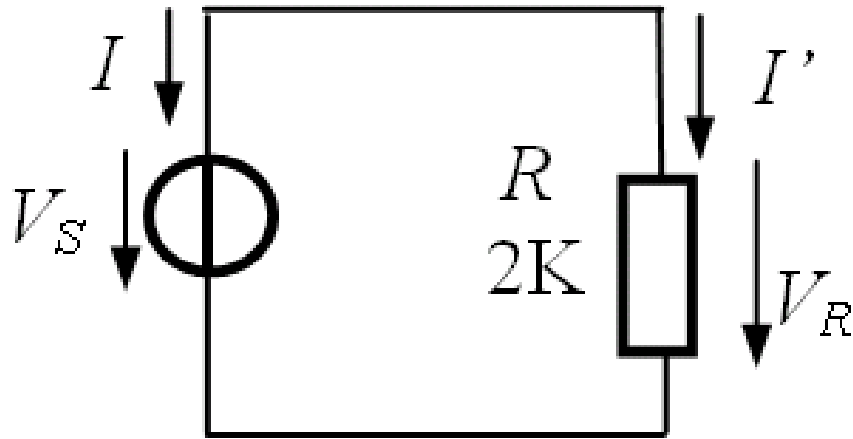


$$I = -\frac{V_S}{R} = -5 \text{ mA}; \quad I' = -I = 5 \text{ mA}$$

$P_S = V_S I = 10V \cdot (-5mA) = -50mW$; the power is **generated** by the source.

$P_R = V_R I' = 10V \cdot 5mA = 50mW$; the power is **dissipated** by the resistor.

Fundamentals

➤ RC circuits

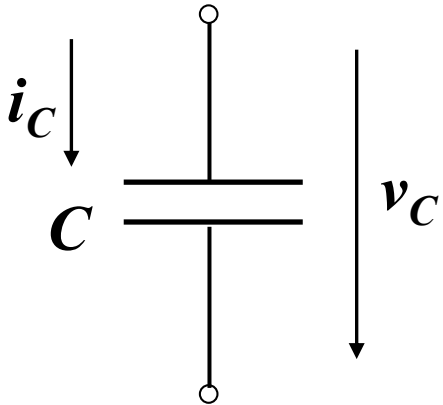

Relation between current and voltage:

$$C dv_C(t) = i_C(t) dt$$


Assuming finite variations:

$$C \Delta v_C = i_C \Delta t$$

Fundamentals

➤ RC circuits – time domain analysis

RC circuit with a dc voltage source

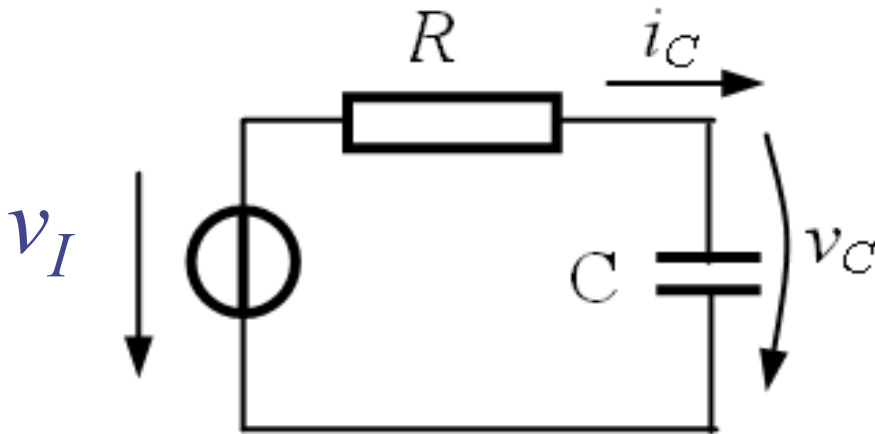

$$Ri_C(t) + v_C(t) = v_I(t)$$

$$Cdv_C(t) = i_C(t)dt$$

$$i_C(t) = C \frac{dv_C(t)}{dt}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = v_I(t)$$


$\tau = RC$ time constant of the circuit

$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$



Fundamentals

➤ RC circuits – time domain analysis

RC circuit with a dc voltage source

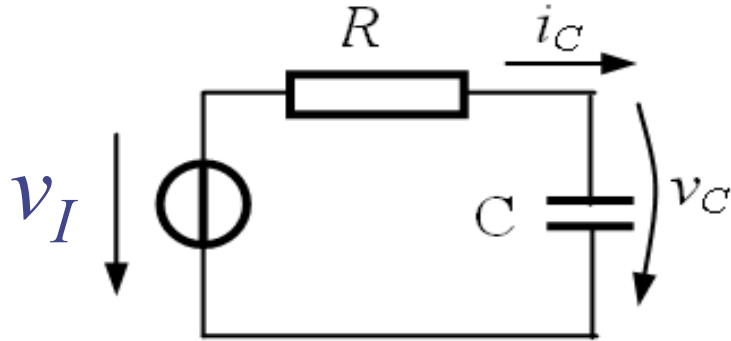

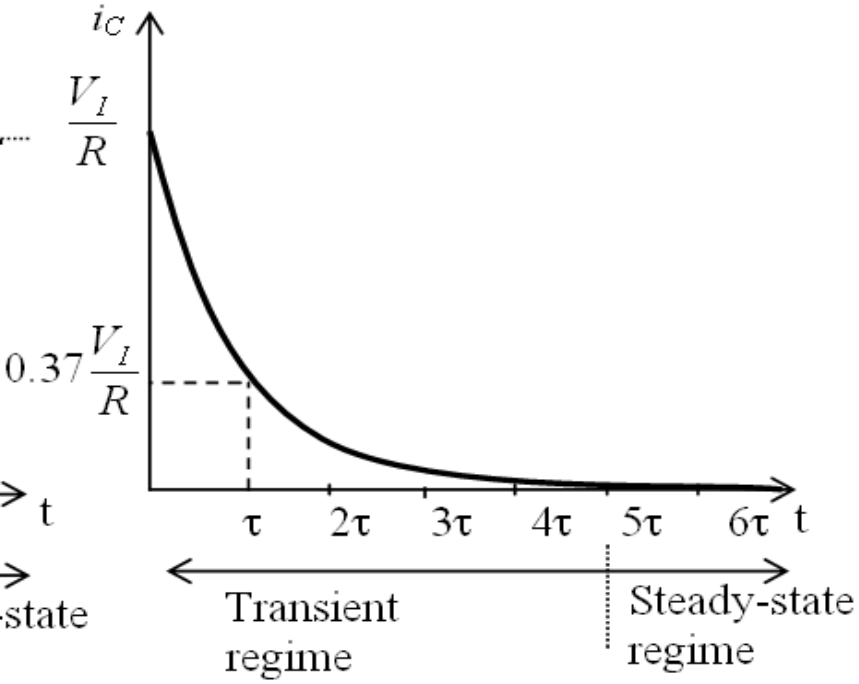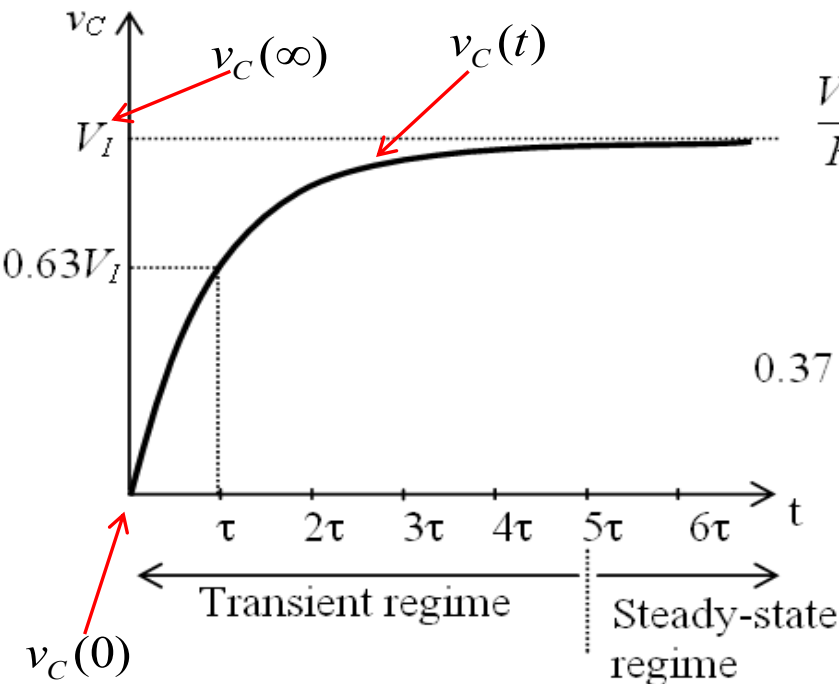
$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$




Fundamentals

➤ RC circuits – time domain analysis

RC circuit with an ac voltage source

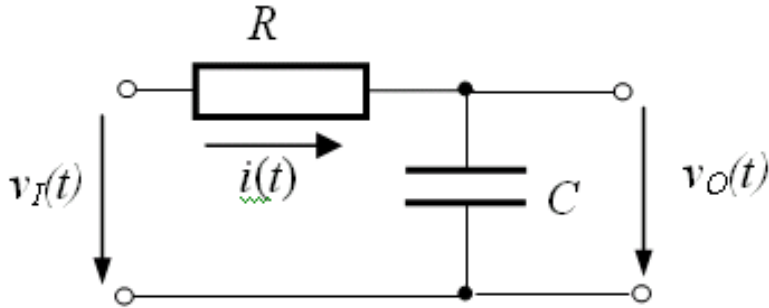
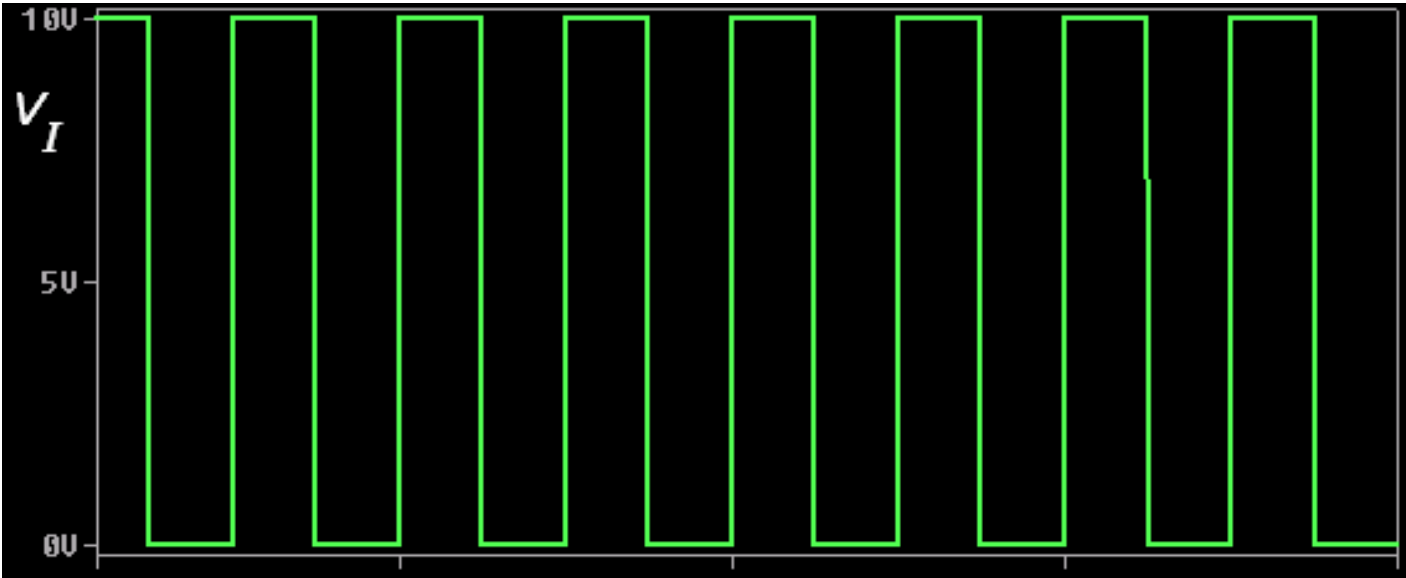
$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$




$$v_O(t) = ?$$

Fundamentals

➤ RC circuits – time domain analysis



RC circuit with an ac voltage source

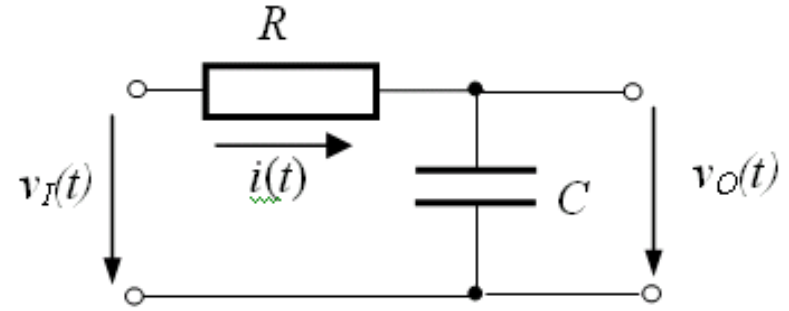

$$v_C(t) = v_C(0)e^{\frac{-t}{\tau}} + (1 - e^{\frac{-t}{\tau}})v_C(\infty)$$

$$5\tau \ll \frac{T}{2}; \quad \tau \ll \frac{T}{10}$$

$$\frac{T}{2} \approx 5\tau$$

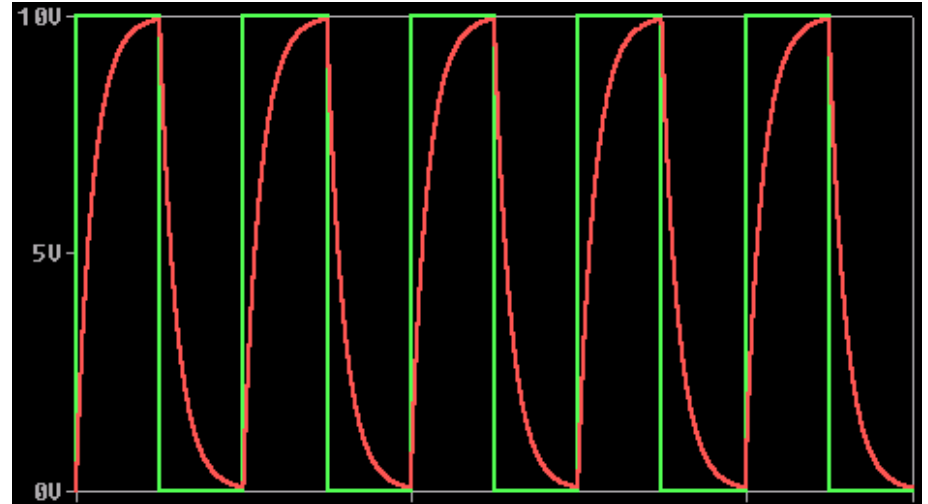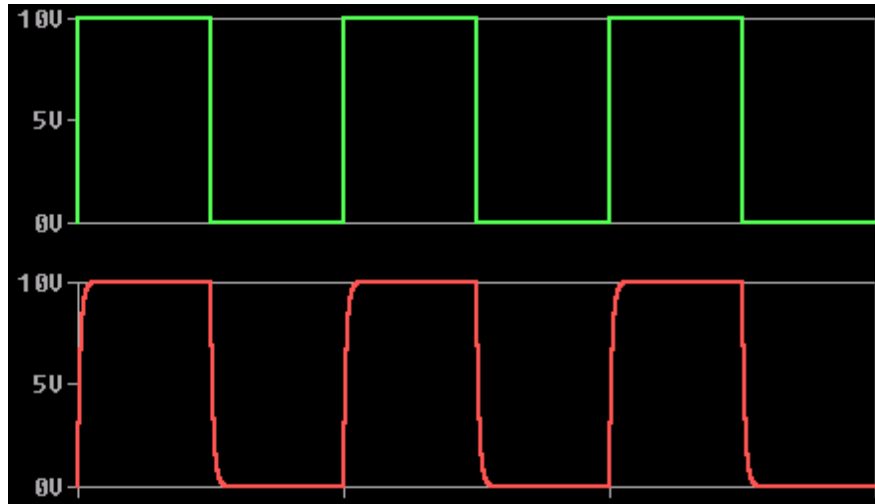


Fundamentals

- Capacitor charging under a constant current

$$Cdv_c(t) = i_c(t)dt$$


$$v_c(t) = \frac{1}{C} \int_0^t i_c(t)dt + v_c(0)$$

$$v_c(t) = \frac{1}{C} It + v_c(0)$$

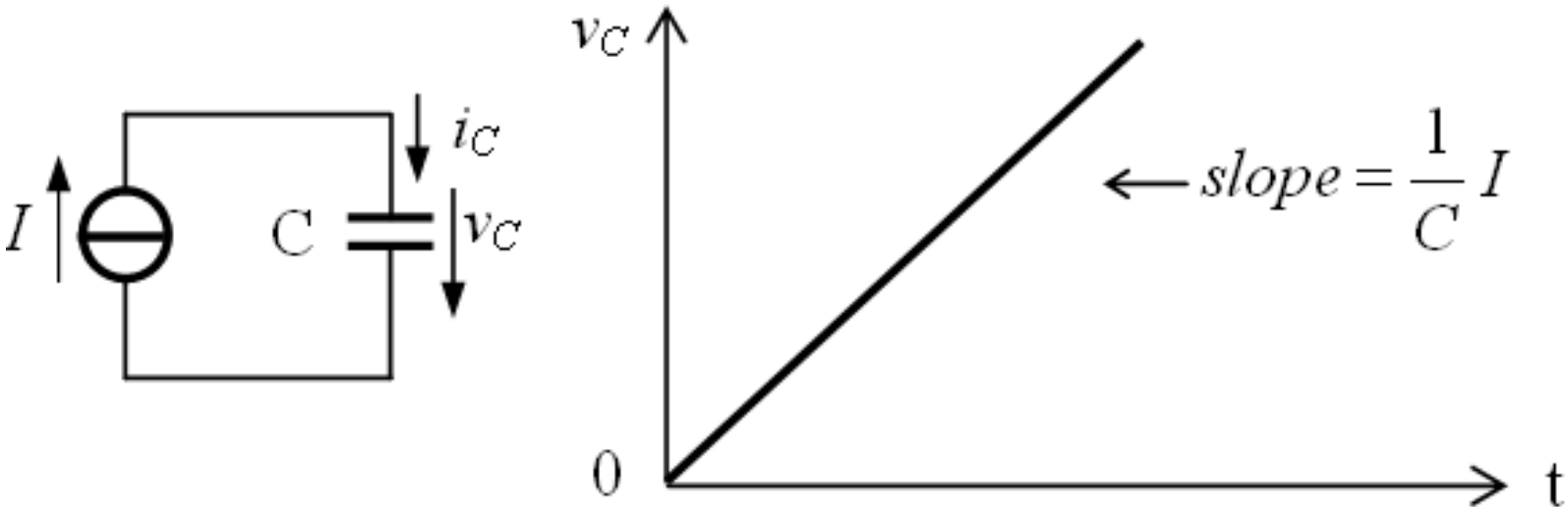

Fundamentals

➤ RC circuit – frequency response

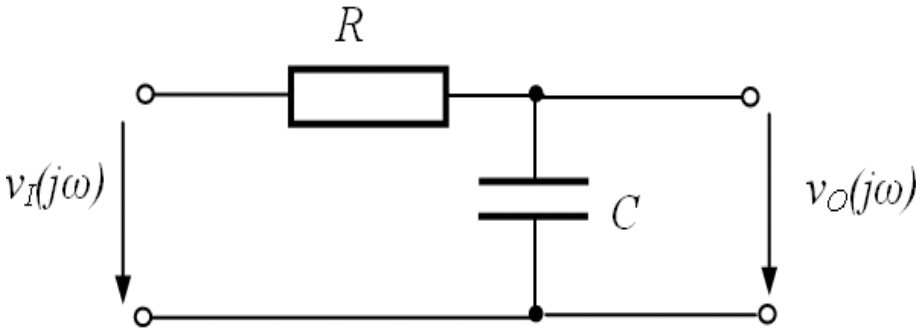

$$Z_C = \frac{1}{j\omega C}$$

Low frequency:

$f \rightarrow 0$; $Z_C \rightarrow \infty$; output \rightarrow open circuit; $v_O(j\omega) \rightarrow v_I(j\omega)$ **pass**


High frequency:

$f \rightarrow \infty$; $Z_C \rightarrow 0$; output \rightarrow short - circuit; $v_O(j\omega) \rightarrow 0$ **don't pass (reject)**

First order, passive, low-pass filter (LPF)

Fundamentals

➤ RC circuit – frequency response

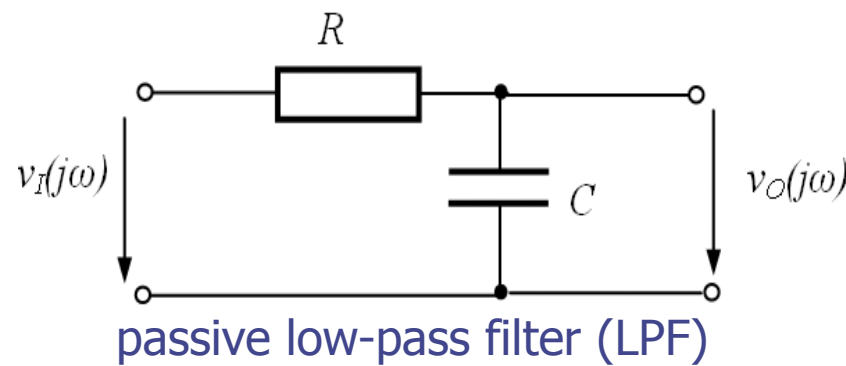

Transfer function

$$F(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{1}{1 + j\omega RC}$$

$$\Phi(\omega) = -\text{arctg}(\omega RC)$$

$$|F(j\omega)| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$

f – very low; $|F(j\omega)| \approx 1$

f – high; $|F(j\omega)| \approx \frac{1}{\omega RC}$



$$1 = \frac{1}{\omega_0 RC} \Rightarrow \omega_0 = \frac{1}{RC} \Rightarrow$$

$$f_0 = \frac{1}{2\pi RC}$$


Cut-off frequency

Fundamentals

➤ RC circuit – frequency response

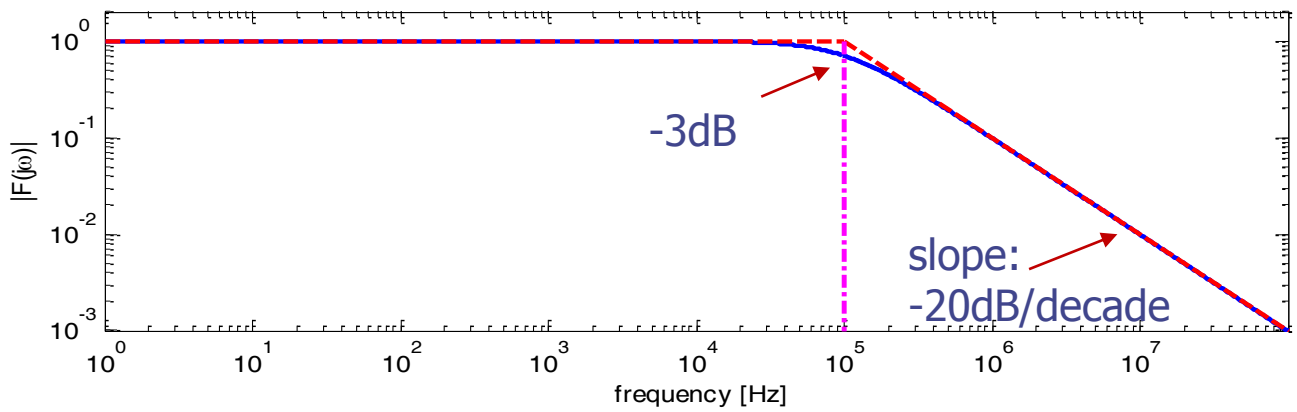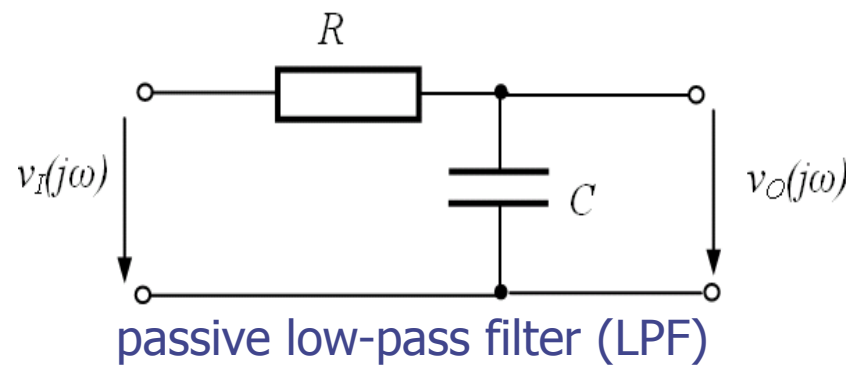


magnitude response (log-log plot)

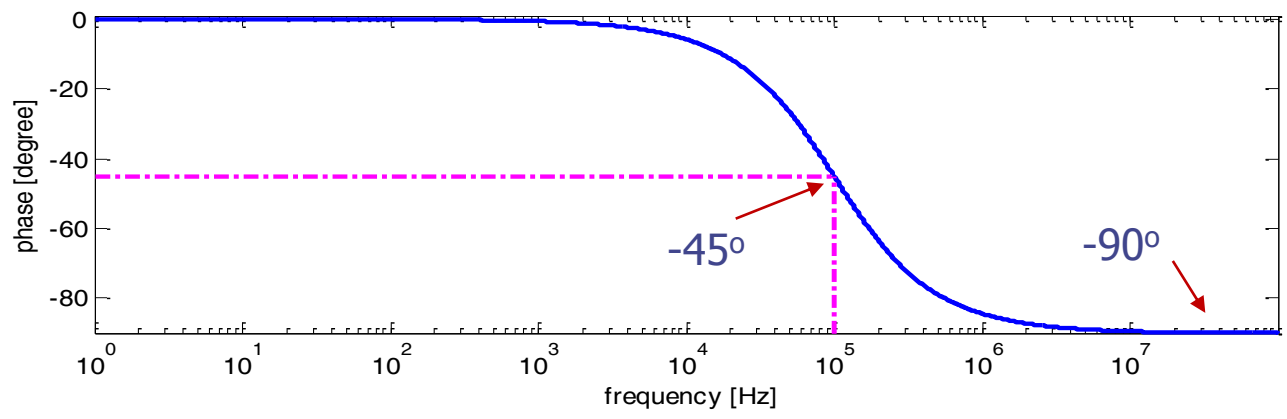

phase response (lin-log plot)

Fundamentals

➤ RC circuit – frequency response

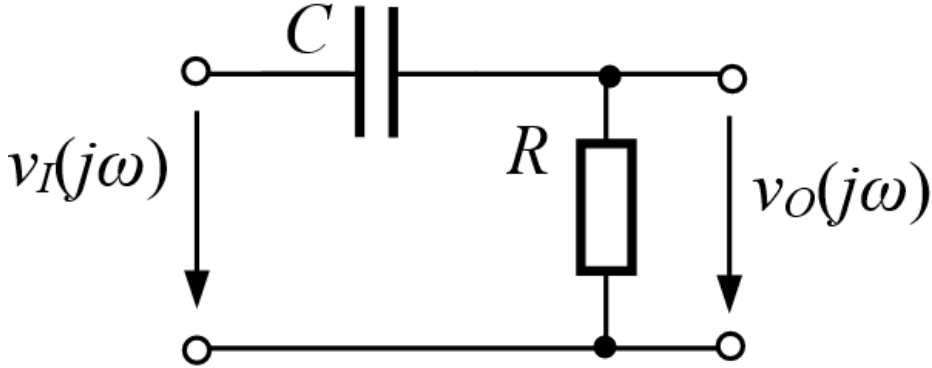

$$Z_C = \frac{1}{j\omega C}$$

Low frequency:

$f \rightarrow 0$; $Z_C \rightarrow \infty$; input – output \rightarrow open circuit; $v_O(j\omega) \rightarrow 0$ **don't pass (reject)**


High frequency:

$f \rightarrow \infty$; $Z_C \rightarrow 0$; input – output \rightarrow short - circuit; $v_O(j\omega) \rightarrow v_I(j\omega)$ **pass**

First order, passive, high-pass filter (HPF)

Fundamentals

➤ RC circuit – frequency response

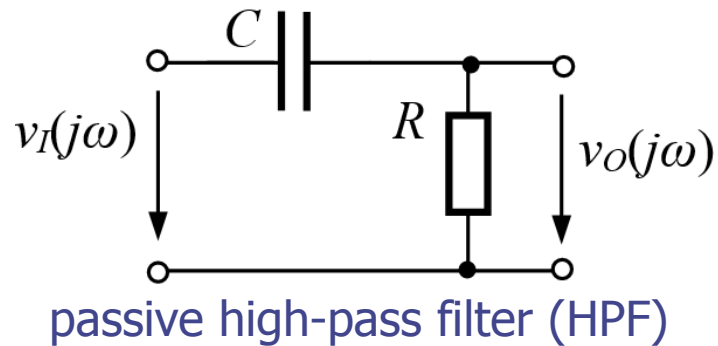

Transfer function

$$F(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{j\omega RC}{1 + j\omega RC}$$

$$|F(j\omega)| = \frac{\omega RC}{\sqrt{1 + (\omega RC)^2}}$$

$$\Phi(\omega) = 90^\circ - \text{arctg}(\omega RC)$$

f – very low; $|F(j\omega)| \approx \omega RC$

f – high; $|F(j\omega)| \approx 1$



$$\omega_0 RC = 1 \Rightarrow \omega_0 = \frac{1}{RC} \Rightarrow$$

$$f_0 = \frac{1}{2\pi RC}$$


Cut-off frequency

Fundamentals

➤ RC circuit – frequency response

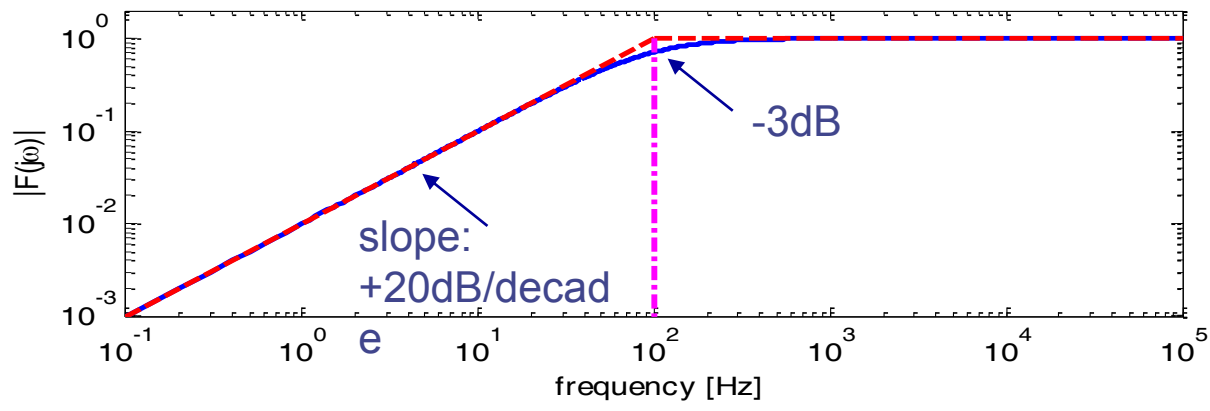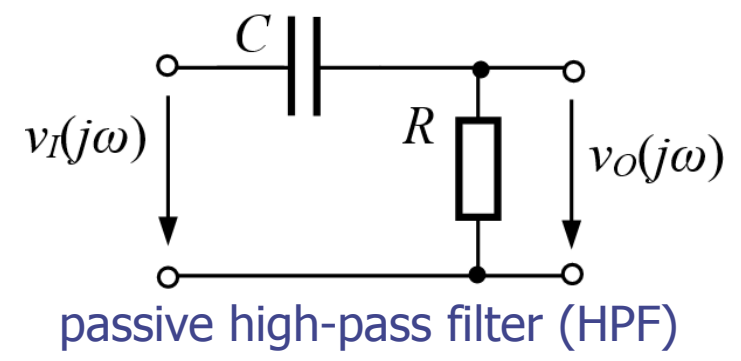


magnitude response (log-log plot)

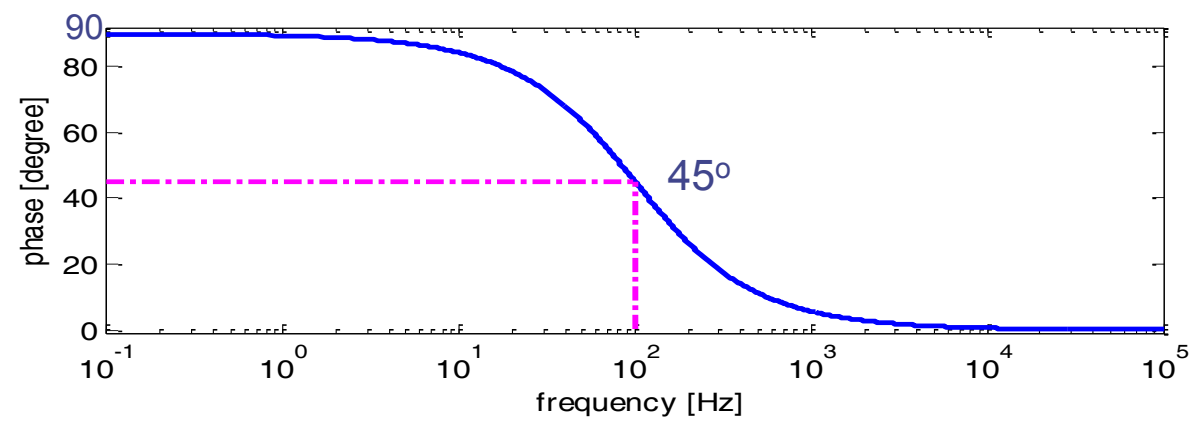

phase response (lin-log plot)

Fundamentals

➤ RC circuit – frequency response

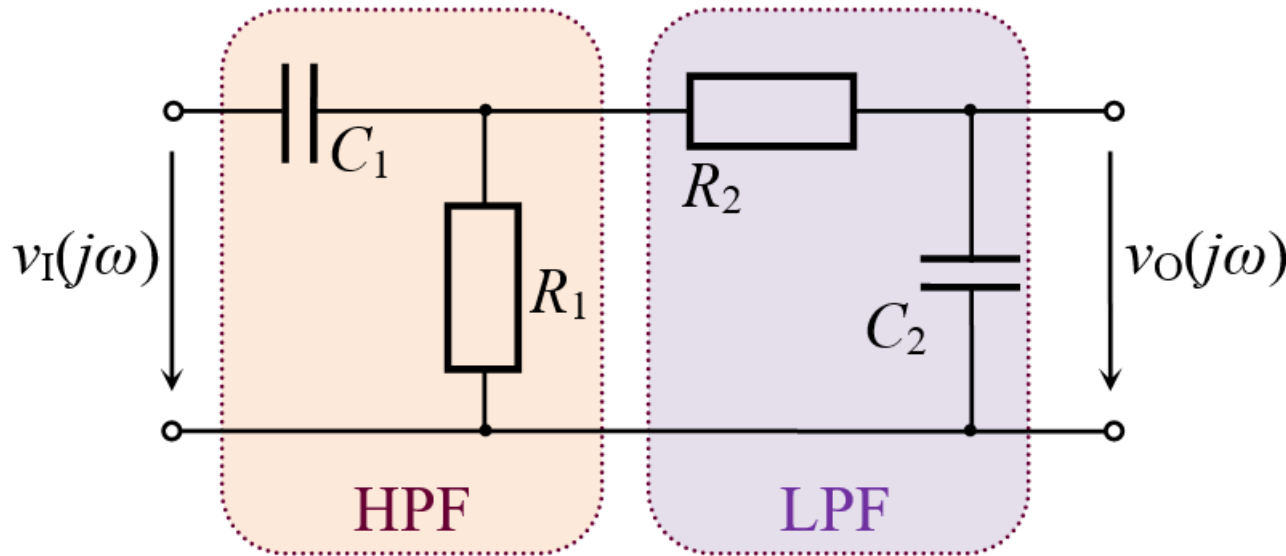


$$Z_C = \frac{1}{j\omega C}$$

Second order, passive, band-pass filter (HPF)

Fundamentals

➤ RC circuit – frequency response

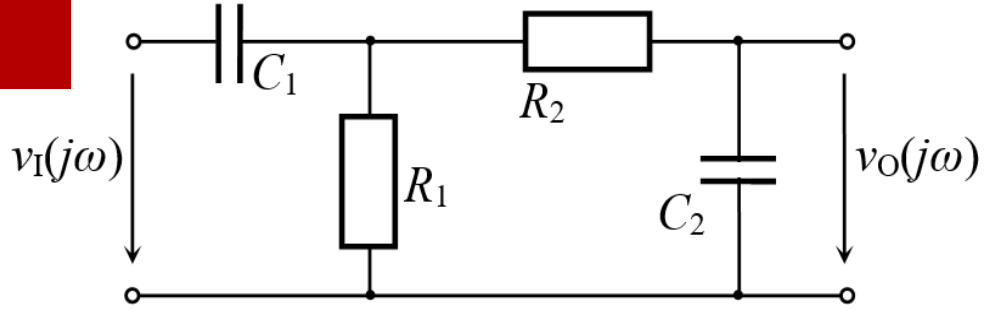

passive band-pass filter (BPF)

Transfer function

$$F(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = \frac{j\omega R_1 C_1}{(1 + j\omega R_1 C_1)(1 + j\omega R_2 C_2)}$$

$$|F(j\omega)| = \frac{\omega R_1 C_1}{\sqrt{1 + (\omega R_1 C_1)^2} \sqrt{1 + (\omega R_2 C_2)^2}}$$

$$\Phi(\omega) = 90^\circ - \text{arctg}(\omega R_1 C_1) - \text{arctg}(\omega R_2 C_2)$$

Cut-off frequencies


$$f_L = \frac{1}{2\pi R_1 C_1} \quad f_H = \frac{1}{2\pi R_2 C_2}$$

Bandwidth


$$B = f_H - f_L$$

Fundamentals


➤ RC circuit – frequency response

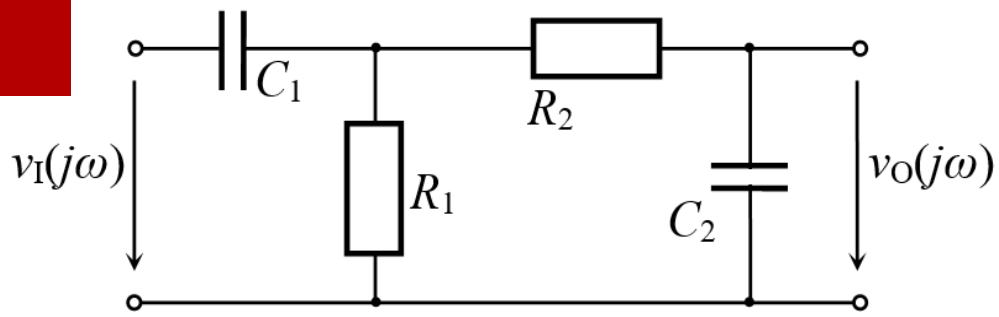

passive band-pass filter (BPF)

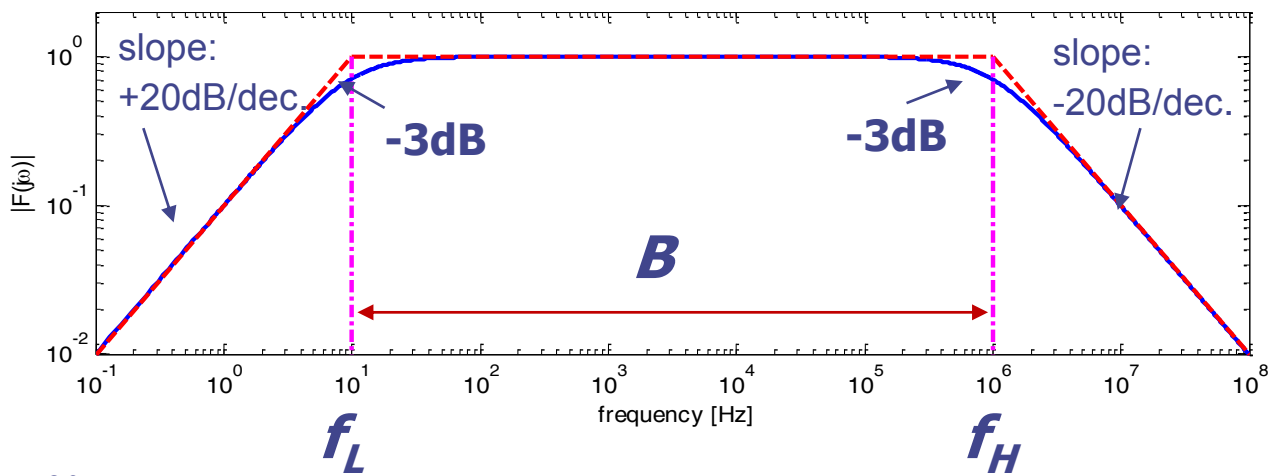

magnitude response (log-log plot)

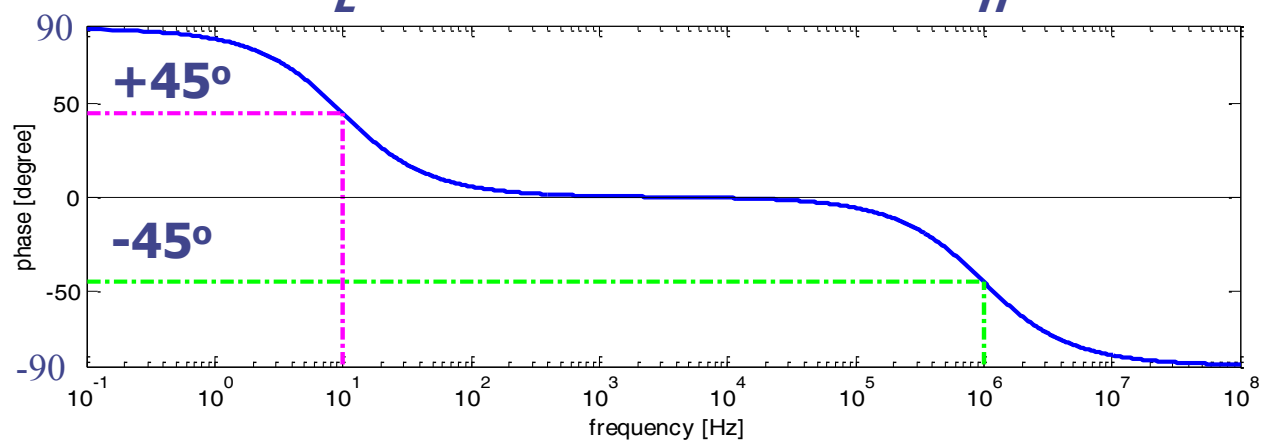

phase response (lin-log plot)

Summary

The trip down memory lane revived knowledge about:

- Electrical signals, sources
- Ohm's law
- Kirchhoff's law
- Resistive divider
- Superposition method
- Millman's theorem
- RC circuits – time and frequency domain behaviors, filters

Next week: Diodes. DR circuits.