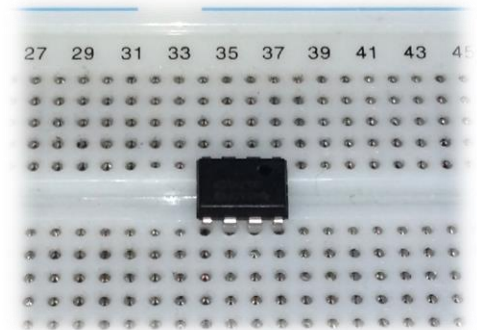




# ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.


## C10 – Applications with OpAmp



# Contents

- Voltage domain conversion circuits
- Capacitively coupled amplifiers
- Op-amp amplifiers operated from a single power supply
- Integrators and differentiators – active filters

**Previously on ED:**

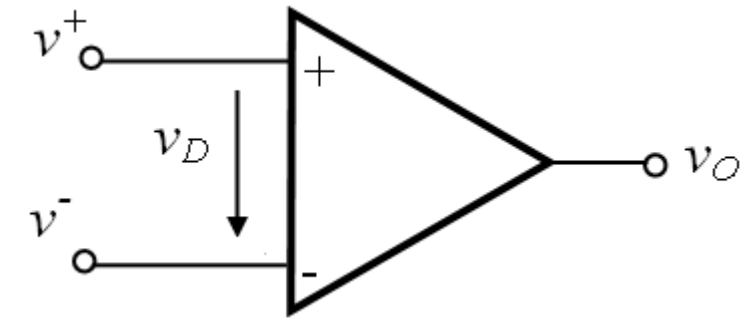

Type of feedback	$v_I$ goes to	Application	We compute	$v_O$
No feedback	NI	Simple comparator, non-inverting	$V_{Th}$	$v_O \in \{V_{OL}; V_{OH}\}$
	II	Simple comparator, inverting		
Positive feedback	NI	Hysteresis comparator, non-inverting	$V_{ThL}$ $V_{ThH}$	$v_O \in \{V_{OL}; V_{OH}\}$
	II	Hysteresis comparator, inverting		
Negative feedback	NI	Amplifier, non-inverting	$A_v$	$v_O \in (V_{OL}; V_{OH})$
	II	Amplifier, inverting		

### Basic applications of OpAmps with negative feedback

- Inverting/non-inverting amplifier **(C8, L11)**
- Differential amplifier **(C9, L11)**
- Summing amplifier (inverting/non-inverting) **(C9)**

### Other applications of OpAmps with negative feedback:

- Voltage domain conversion circuits
- Capacitively coupled amplifiers
- Op-amp amplifiers operated from a single power supply
- Integrators and differentiators – active filters
- Half-wave and full-wave precision rectifiers
- Precision peak detectors
- Current sources
- Logarithmic and exponential amplifiers
- Circuits for multiplication and division

## Linear conversion of the voltage domain

$$v_{cd} \in [v_{cd_{\min}} ; v_{cd_{\max}}] \longrightarrow v_O \in [v_{O_{\min}} ; v_{O_{\max}}]$$

- inverting amplifier

$$v_{cd_{\min}} \longrightarrow v_{O_{\max}}$$

$$v_{cd_{\max}} \longrightarrow v_{O_{\min}}$$

- non-inverting amplifier

$$v_{cd_{\max}} \longrightarrow v_{O_{\max}}$$

$$v_{cd_{\min}} \longrightarrow v_{O_{\min}}$$


Circuits?

### Linear conversion of the voltage domain

- inverting amplifier

$$v_{cd_{min}} \rightarrow v_{O_{max}}$$


$$v_{cd_{max}} \rightarrow v_{O_{min}}$$

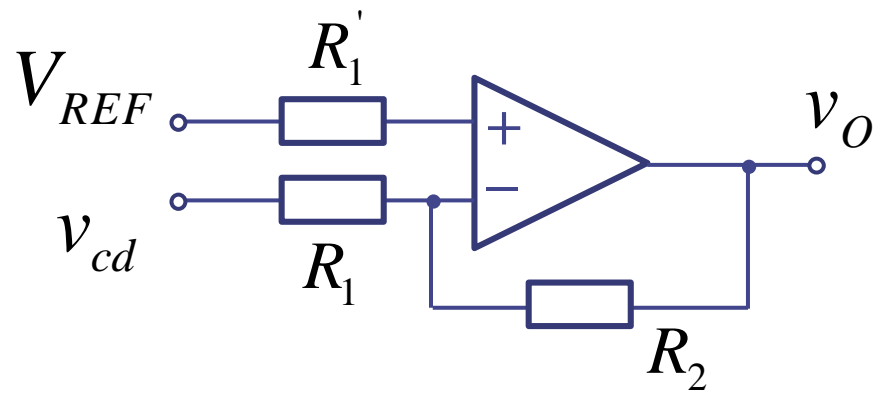

- non-inverting amplifier



$$v_{cd_{max}} \rightarrow v_{O_{max}}$$

$$v_{cd_{min}} \rightarrow v_{O_{min}}$$

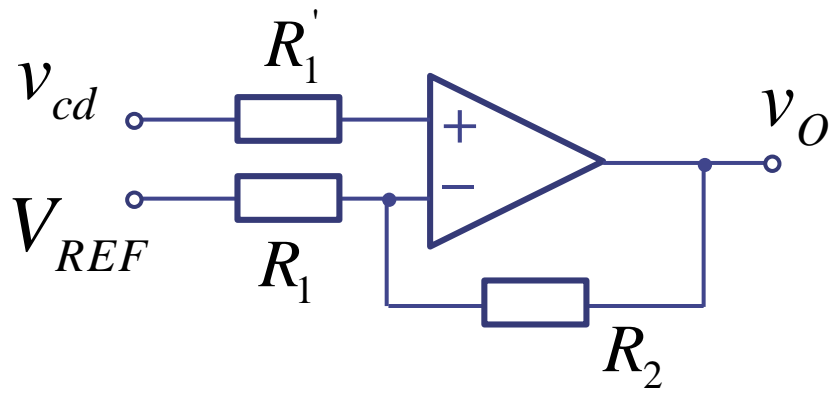


Why is  $V_{REF}$  necessary?

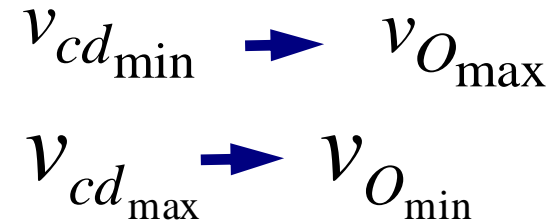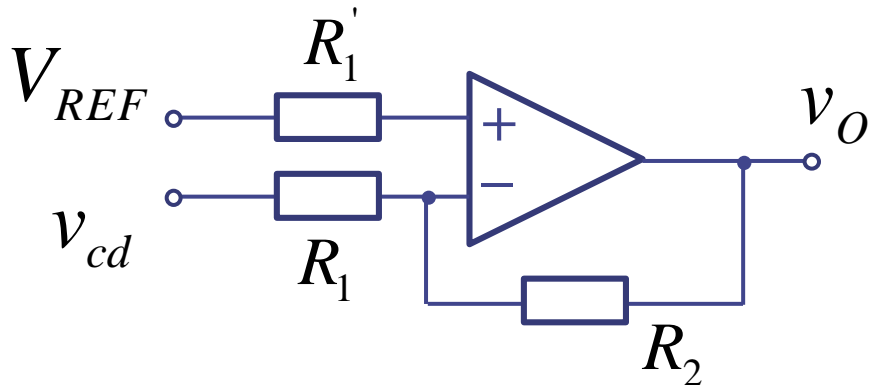➤ Inverting voltage domain conversion amplifier





$$v_O = -\frac{R_2}{R_1} v_{cd} + \left(1 + \frac{R_2}{R_1}\right) V_{REF}$$
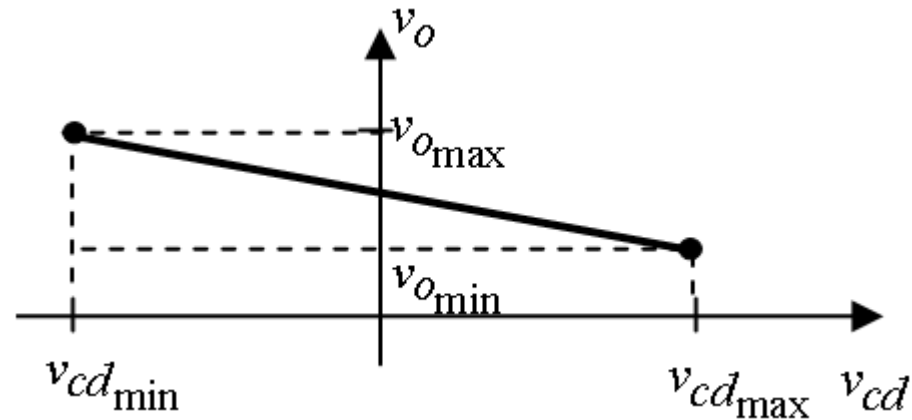
$$V_{REF} = \frac{v_{O_{min}} + \frac{R_2}{R_1} v_{cd_{max}}}{1 + \frac{R_2}{R_1}}$$



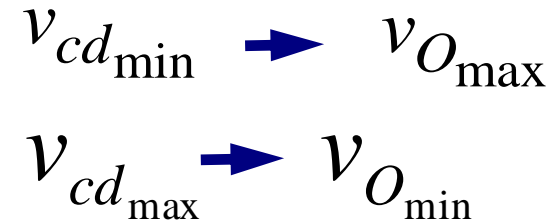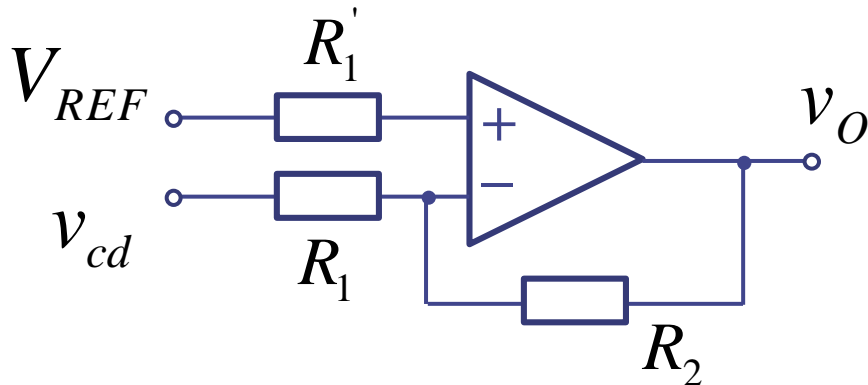➤ Inverting voltage domain conversion amplifier



$$v_O = -\frac{R_2}{R_1} v_{cd} + \left(1 + \frac{R_2}{R_1}\right) V_{REF}$$

$$\frac{R_2}{R_1} = \frac{v_{Omax} - v_{Omin}}{v_{cdmax} - v_{cdmin}}$$

$$R_1' = R_1 \parallel R_2$$

$$V_{REF} = \frac{v_{Omin} + \frac{R_2}{R_1} v_{cdmax}}{1 + \frac{R_2}{R_1}}$$

$$v_{Omin} = -\frac{R_2}{R_1} v_{cdmax} + \left(1 + \frac{R_2}{R_1}\right) V_{REF}$$


$$v_{Omax} = -\frac{R_2}{R_1} v_{cdmin} + \left(1 + \frac{R_2}{R_1}\right) V_{REF}$$



➤ Inverting voltage domain conversion amplifier

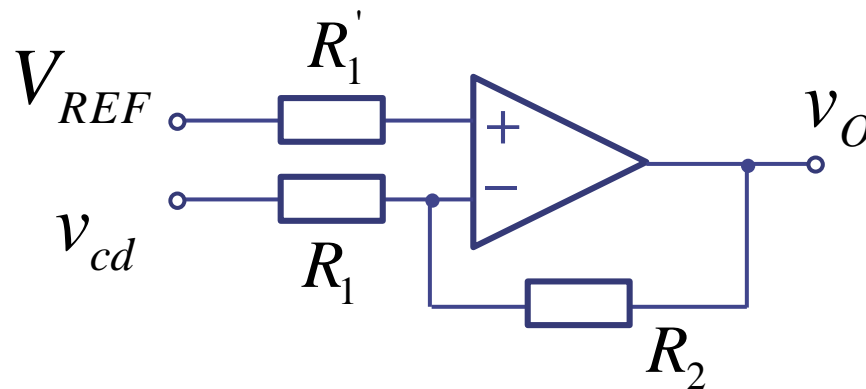
### Example

$$v_{cd} \in (2; 7)V \quad v_O \in (-1; 6)V$$



- VTC
- Values for resistors
- $V_{REF}$

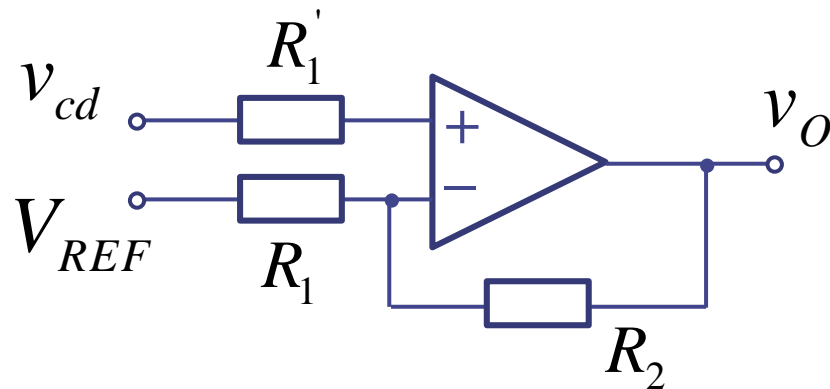➤ Non-inverting voltage domain conversion amplifier



$$v_{cd_{\min}} \rightarrow v_{O_{\min}}$$
$$v_{cd_{\max}} \rightarrow v_{O_{\max}}$$


- VTC
- Values for resistors
- $V_{REF}$

$$v_I(t) = V_I + v_i(t)$$

**To do:** amplify only the variable signal,  $v_i(t)$

**Solution:** differential amplifier (C9)



capacitively coupled amplifier

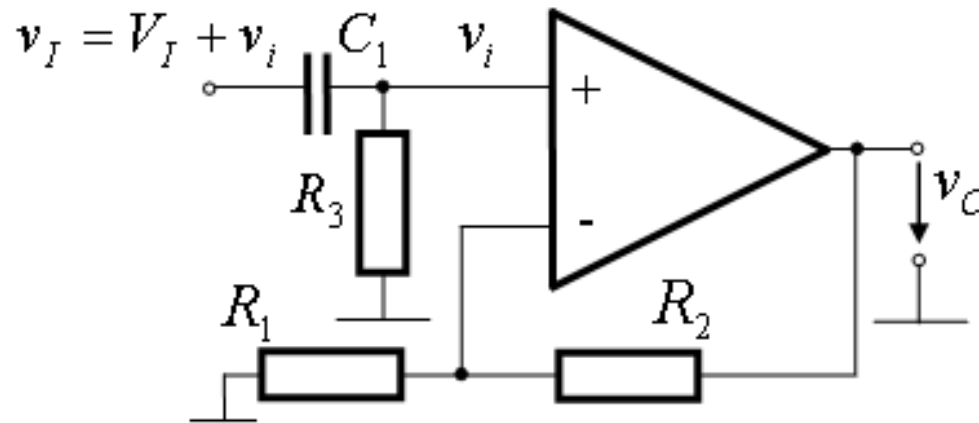

$$v_o(t) = v_i(t) \left( 1 + \frac{R_2}{R_1} \right)$$

Role of  $R_3$ ?



➤ Non-inverting configuration

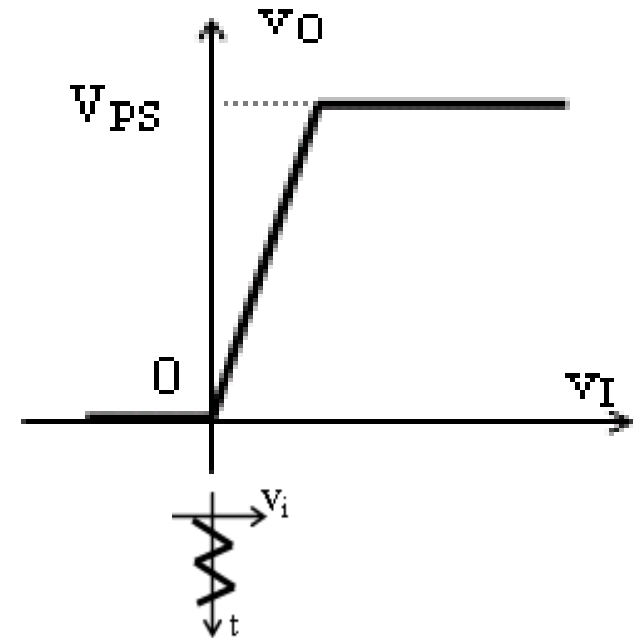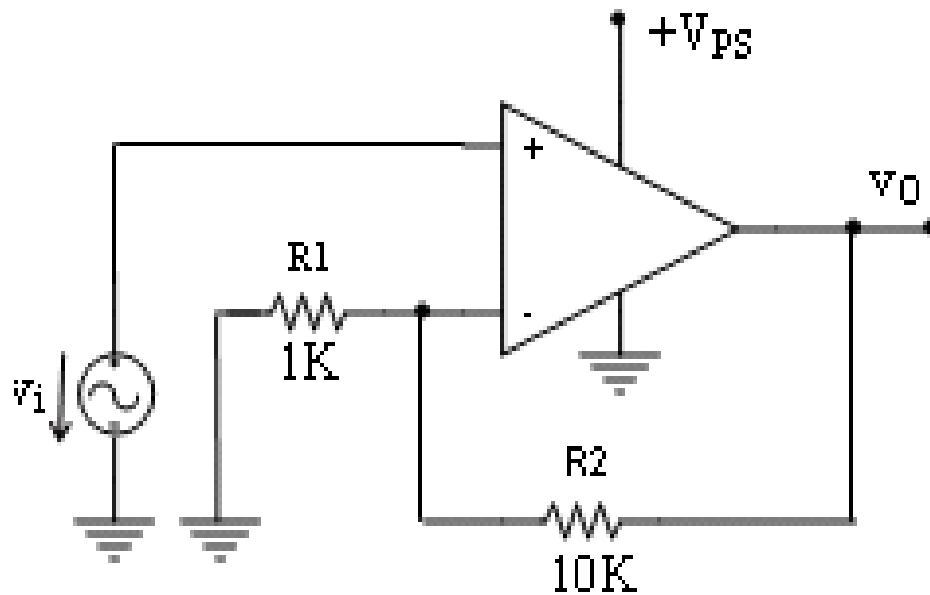

How can we amplify the **entire**  $v_i(t)$  (not just the positive halfwave), in the case of unipolar supply?

➤ Non-inverting configuration


Solution: translate the VTC

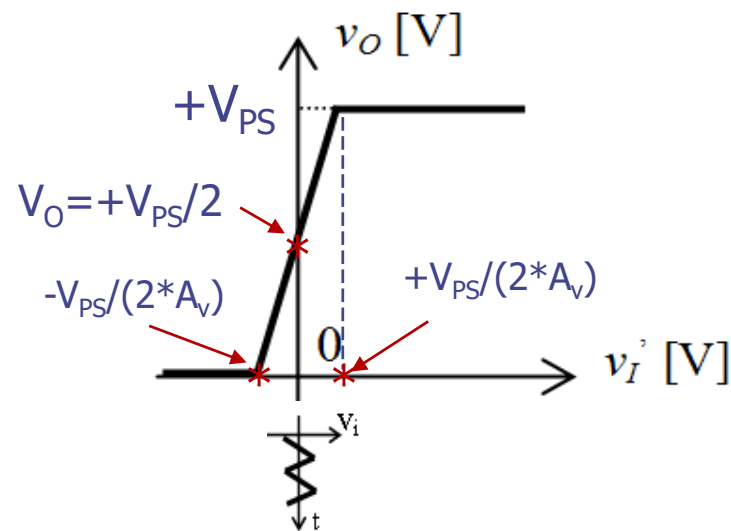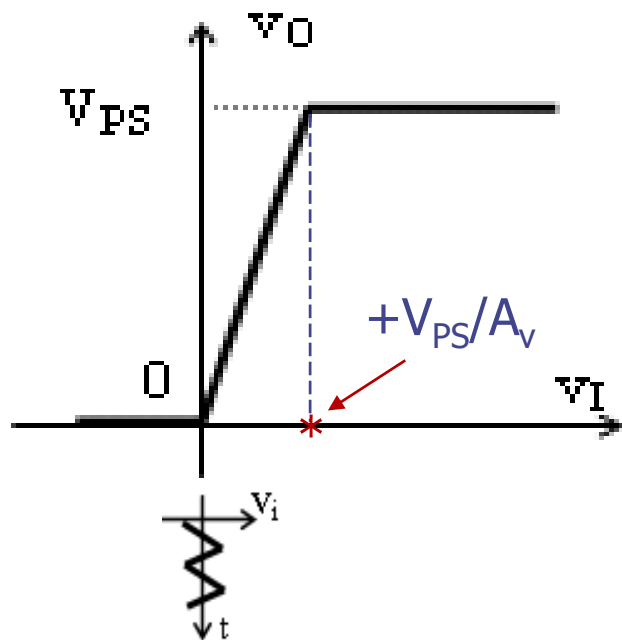



$$v_i' = v_i - V_{BIAS}$$

➤ Non-inverting configuration

Solution: translate the VTC

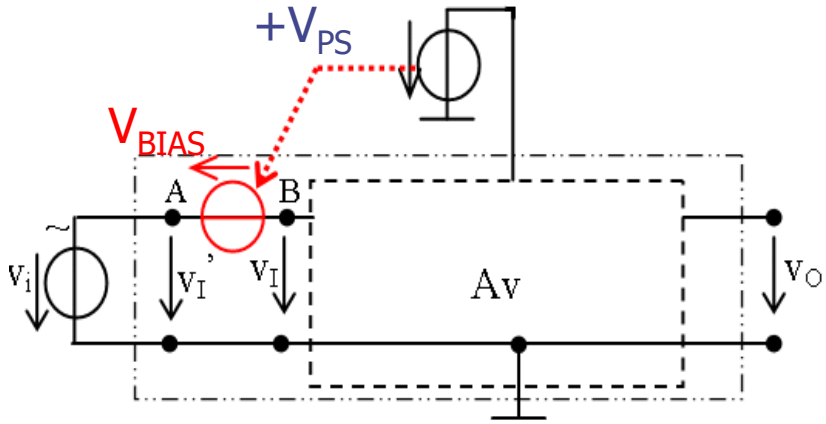


- obtaining  $V_{BIAS}$

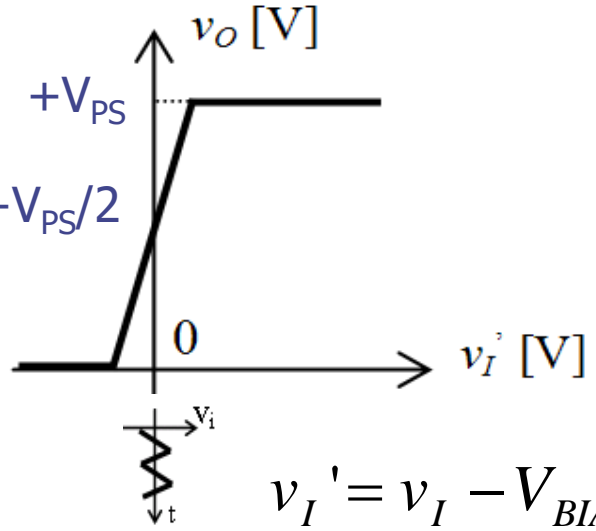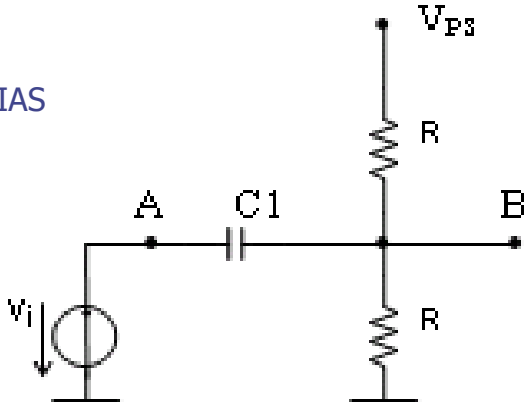


$$v_I' = v_I - V_{BIAS}$$

- equivalence in steady-state regime

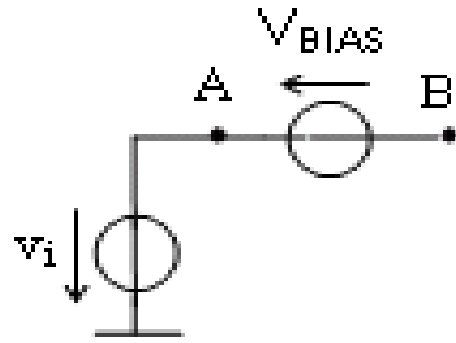

➤ Non-inverting configuration

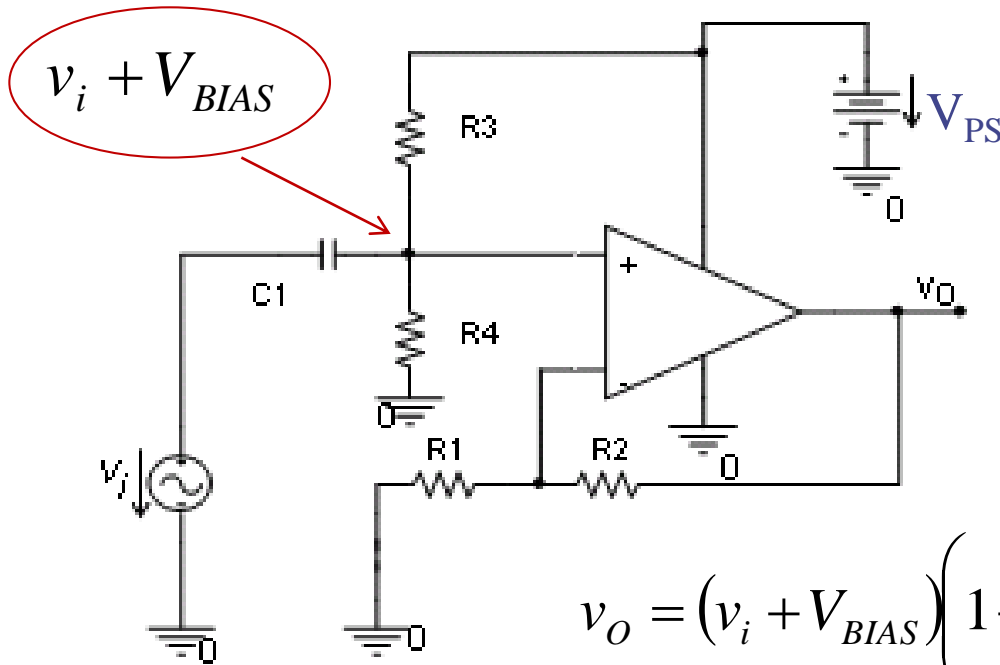

$$V_{BIAS} = \frac{R_4}{R_4 + R_3} V_{PS}$$

$$v_O = (v_i + V_{BIAS}) \left( 1 + \frac{R_2}{R_1} \right) = v_i \left( 1 + \frac{R_2}{R_1} \right) + V_{BIAS} \left( 1 + \frac{R_2}{R_1} \right)$$



**Problem:**  $V_{BIAS}$  is also amplified (dc gain is too high)

**Possible solution:** to implement

$$v_O = v_i \left( 1 + \frac{R_2}{R_1} \right) + V_{BIAS} \left( 1 + \frac{R_2}{R_1} \right) - V_{BIAS} \frac{R_2}{R_1}$$

➤ Non-inverting configuration

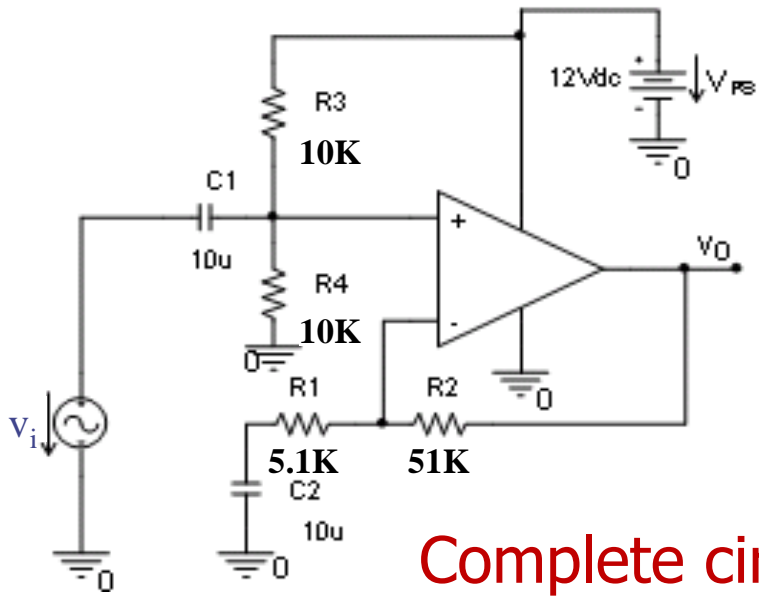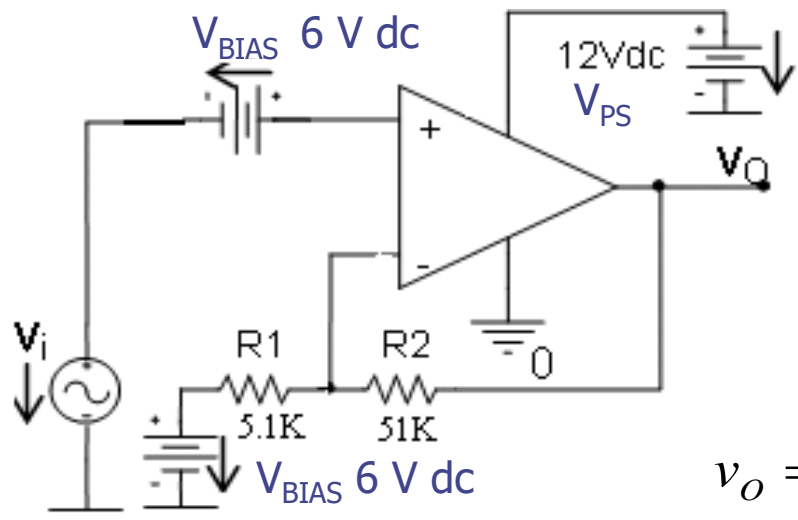Equivalent circuit in steady-state regime



Complete circuit

$$v_O = (v_i + V_{BIAS}) \left( 1 + \frac{R_2}{R_1} \right) - V_{BIAS} \frac{R_2}{R_1}$$

$$v_O = v_i \left( 1 + \frac{R_2}{R_1} \right) + 1 * V_{BIAS}$$

$A_{V, ac}$  →


←  $A_{V, dc}$

$A_{V, ac} = 1 + R_2/R_1$

$A_{V, dc} = 1$



➤ Non-inverting configuration

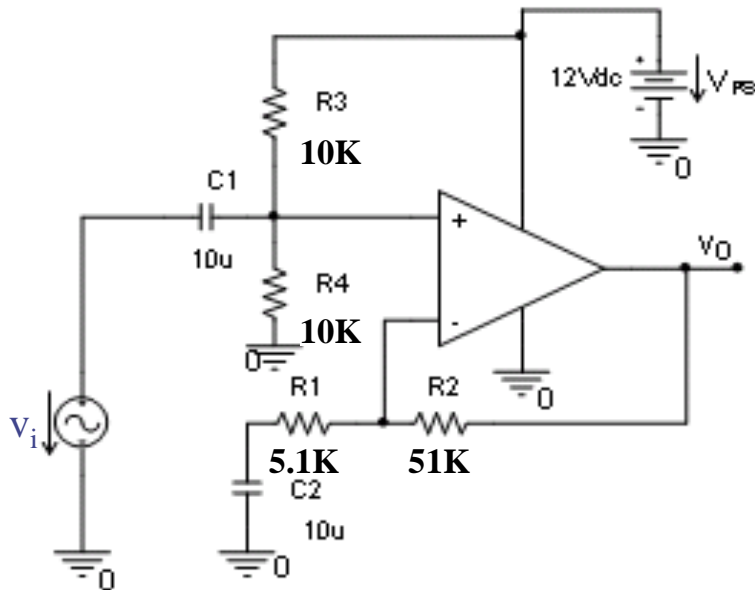

$$v_O = (v_i + V_{BIAS}) \left( 1 + \frac{R_2}{R_1} \right) - V_{BIAS} \frac{R_2}{R_1}$$

$$v_O = v_i \left( 1 + \frac{R_2}{R_1} \right) + 1 * V_{BIAS}$$

$A_{V, ac}$

$A_{V, dc}$

$$A_{V, ac} = 1 + R_2/R_1$$

$$A_{V, dc} = 1$$

- Equivalent ac circuit?
- Equivalent dc circuit?
- Inverting configuration?

➤ Integrator – active LPF

Time domain analysis

$$i(t) = \frac{v_I(t)}{R} \quad Cdv_c = -idt$$

$$v_o(t) = v_c(t) = -\frac{1}{C} \int_0^t i(t) dt + v_c(0) \quad v_o(t) = -\frac{1}{C} \int_0^t \frac{v_I(t)}{R} dt + v_c(0)$$


$$v_o(t) = -\frac{1}{RC} \int_0^t v_I(t) dt + v_c(0)$$

RC – time constant, integrating constant

**Problem:** The op-amp can become saturated due to the dc offset voltage and / or biasing currents, because there is **no NF** in dc

**Solution:** Introduce a NF path in dc


**OPTIONAL**

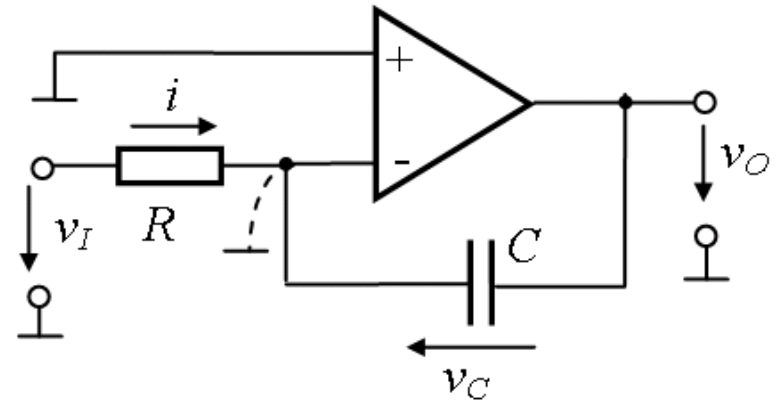

**OPTIONAL**

## ➤ Integrator – active LPF

Integrator with NF in dc (lossy integrator)

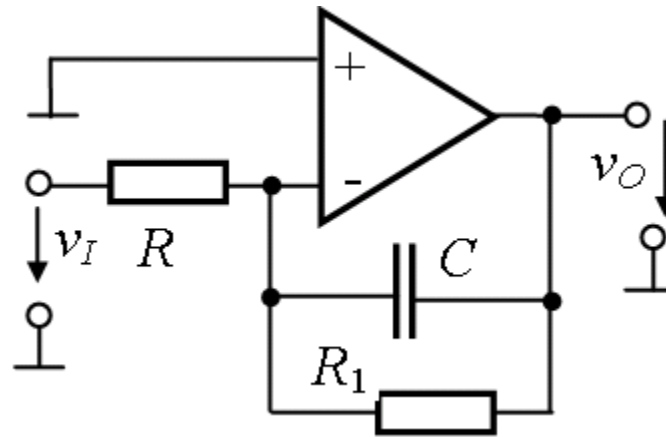
 $R_1$  - large enough to be neglected when compared to  $Z_C$  @working frequency

!To be used in practical applications!

**OPTIONAL**

➤ Integrator – active LPF

Frequency domain analysis

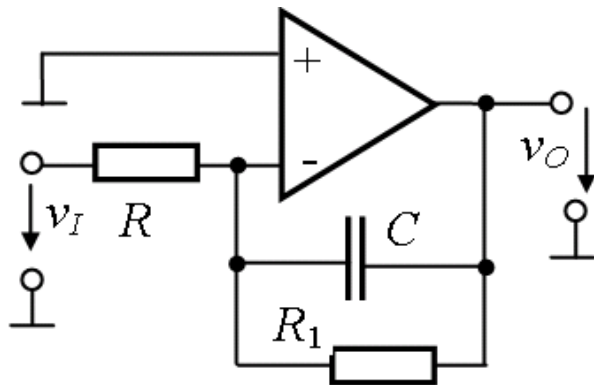

$$A_v(j\omega) = -\frac{R_1}{R} \frac{1}{1 + j\omega R_1 C}$$

Example:


$$R = 1 \text{ k}\Omega$$

$$R_1 = 100 \text{ k}\Omega$$

$$C = 100 \text{ pF}$$


$$A_v(j\omega) = \frac{v_o(j\omega)}{v_I(j\omega)} = -\frac{Z_{ech}}{R}$$
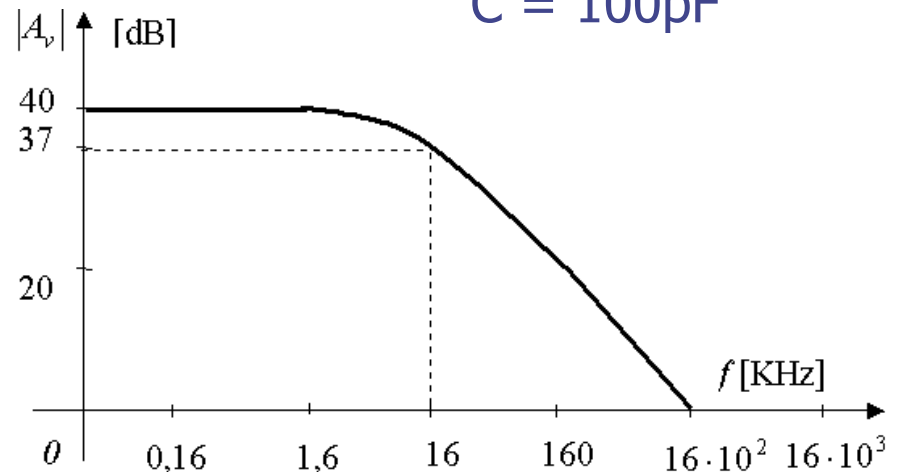
$$Z_{ech} = R_1 \parallel \frac{1}{j\omega C} = \frac{R_1}{1 + j\omega R_1 C}$$



**OPTIONAL**

➤ Differentiator – active HPF

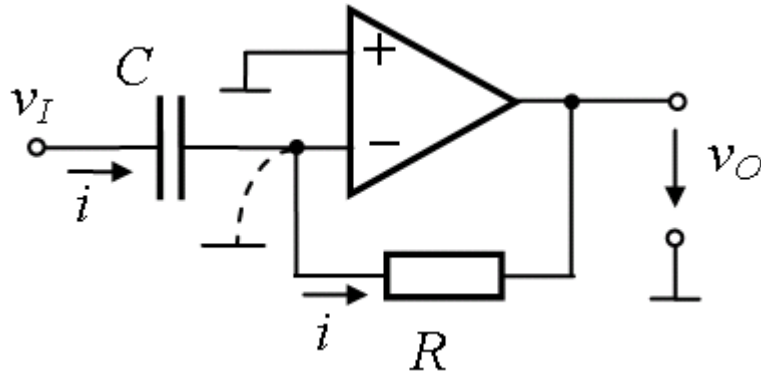

$$i(t) = C \frac{dv_I(t)}{dt}$$

$$v_O(t) = -Ri = -RC \frac{dv_I(t)}{dt}$$


$$A_v(j\omega) = \frac{v_O(j\omega)}{v_I(j\omega)} = \frac{R}{Z_C} = j\omega RC$$

$$|A_v(j\omega)| = \omega RC$$

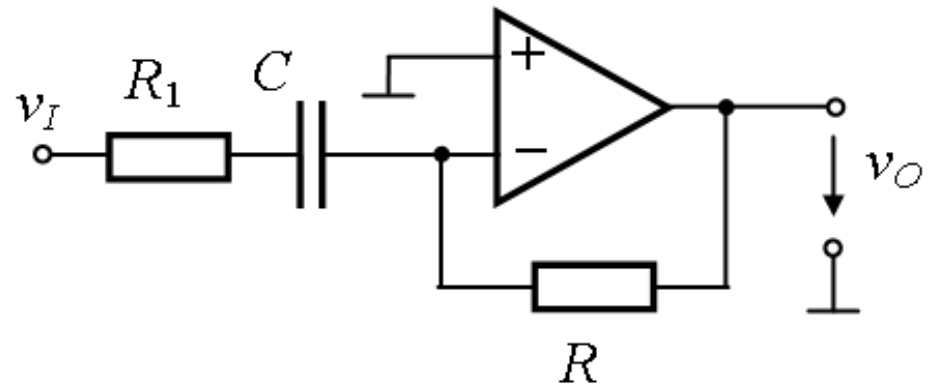**Active high-pass filter**

$$f_0 = \infty \quad f_0 = \frac{1}{2\pi R_1 C}$$


The circuit acts as a “noise amplifier” because of the derivation of the input signal.



$R_1$  – small, in series with C, used in practical applications

**Previously on ED (C3)**

## Half-wave rectifier

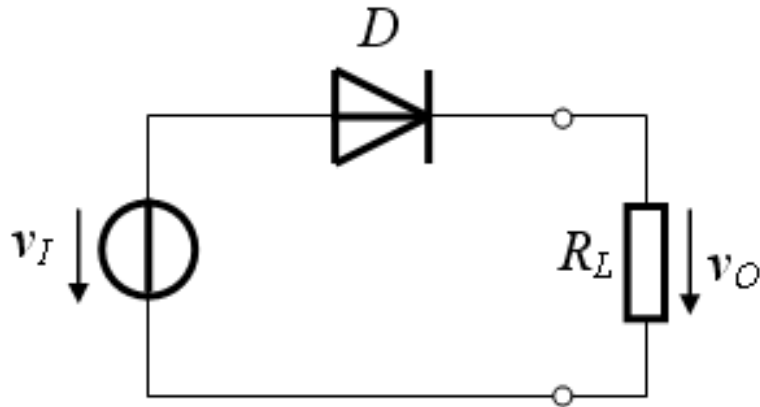**Problems:**

- small signals can't be rectified (D - off)
- some voltage (0.7 V) is wasted across the conducting diode


**Solution:**

**Precision rectifier:**  $v_O = v_I$

**Superdiode** – (almost) zero voltage drop across the conducting superdiode

Circuit?

➤ Half-wave precision rectifier

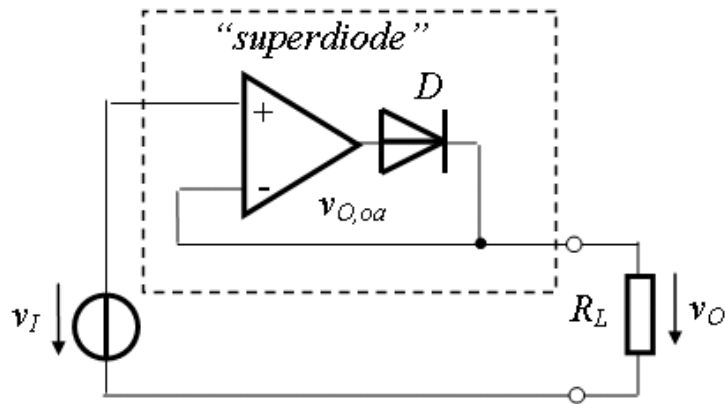

$v_O$  cannot become negative

$$i_D \geq 0$$

Operating principle:

$v_I > 0$

$v_{O,oa} > 0.6 \text{ V}$ , (D) – on, **NF**

$v_O = v_I$  for  $v_I > 0$

Circuit for rectifying the negative half-wave?

$v_I < 0$



$v_{O,oa} < 0$ , (D) – off

**No NF** -> OpAmp works as a **simple comparator**, non-inverting

$v_{O,oa} = V_{OL}$ ,  $v_O = 0$  (no current through  $R_L$ ) for  $v_I < 0$

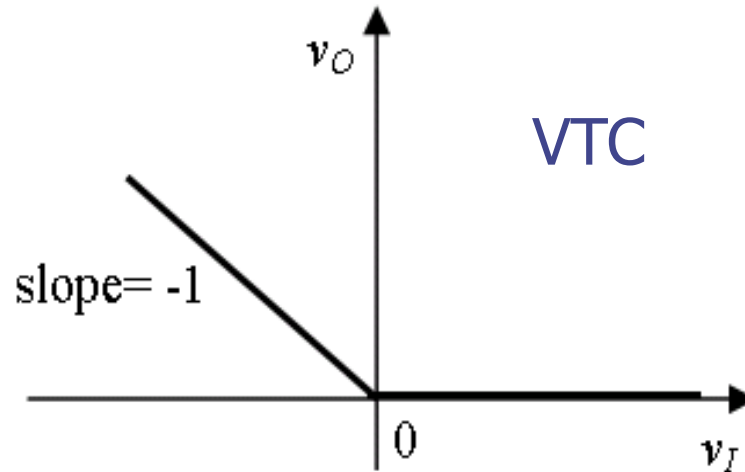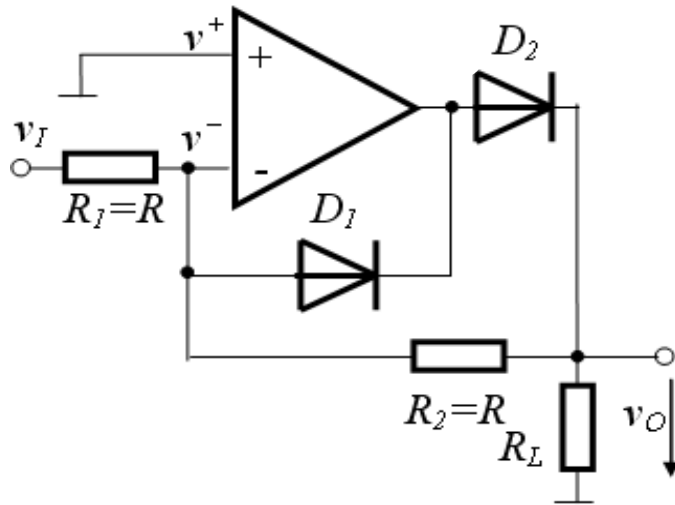**OPTIONAL**

➤ Inverting half-wave precision rectifier avoiding saturation



$v_I < 0$ ;  $D_2$  – (on);  $D_1$  – (off) NF through  $D_2$  and  $R_2$ ;  $v_O = -v_I$


$v_{O,oa} = v_O + 0.7V$  OpAmp – active region

$v_I > 0$ ;  $D_2$  – (off);  $D_1$  – (on) NF through  $D_1$ ;  $v^- = v^+ = 0$ ;  $v_O = 0$

$v_{O,oa} = -0.7V$  OpAmp – active region



➤ Full-wave precision rectifier

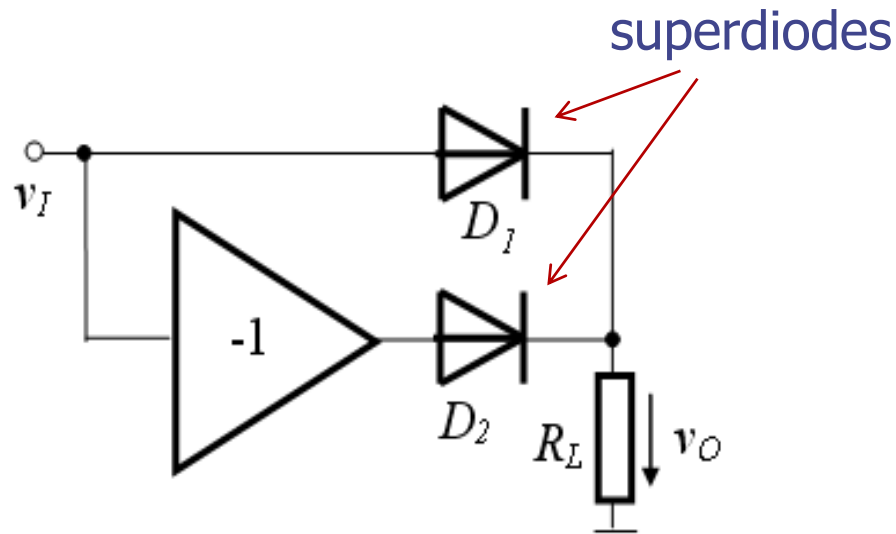

Operating principle

$$v_I > 0, D_1\text{-}(\text{on}), D_2\text{-}(\text{off}) \quad v_O = v_I$$

$$v_I < 0, D_1\text{-}(\text{off}), D_2\text{-}(\text{on}) \quad v_O = -v_I$$

Circuit?

**OPTIONAL**


➤ Full-wave precision rectifier

$v_I > 0$ ,  $D_1$  - (on),  $D_2$  - (off)

NF only for OA1,  $v_O = v_I$


$v_I < 0$ ,  $D_1$ -(off),  $D_2$ -(on)

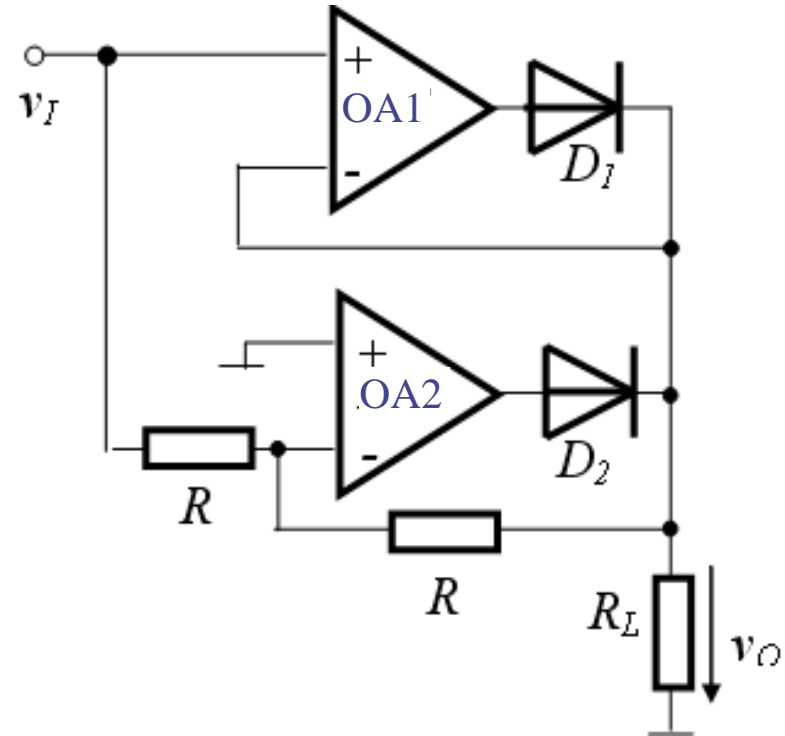NF only for OA2,  $v_O = -(R/R) \cdot v_I$        $v_O = -v_I$



**OPTIONAL**

## ➤ Precision positive peak detector

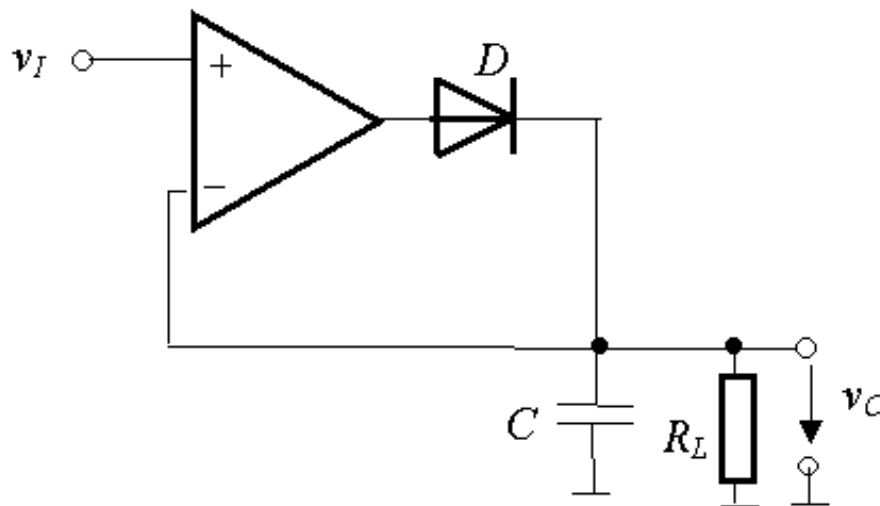


The diode from the common peak detector is replaced with a superdiode.

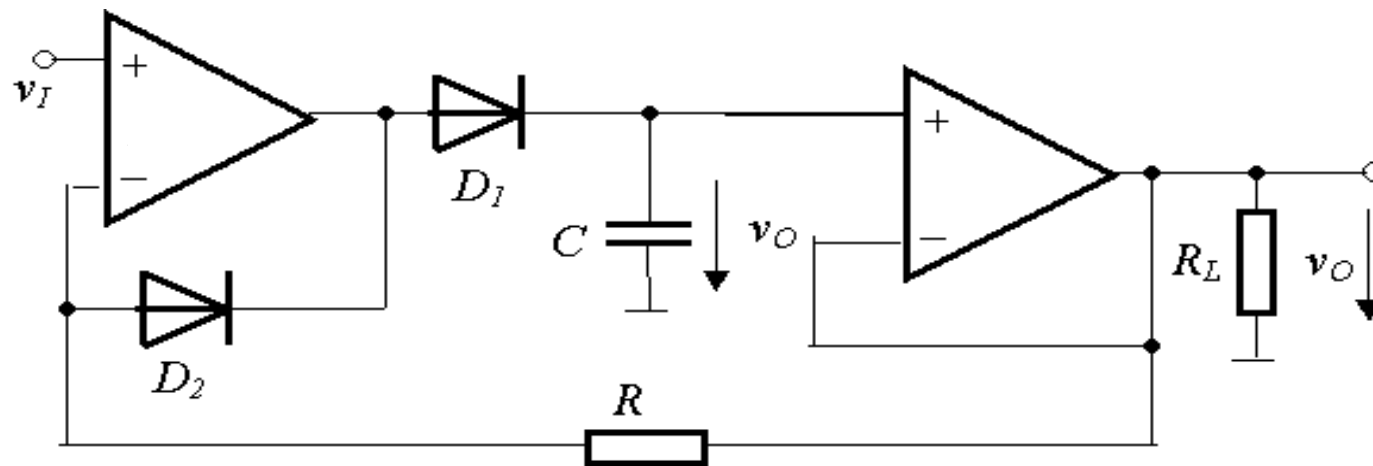**OPTIONAL**

➤ Precision positive peak detector


Precision positive peak detector that holds the voltage



- $D_2$  prevents negative saturation of OA1
- OA2 – voltage follower (buffer)
- OA1 – local NF, when  $D_2$  - (on),  $v_{O, OA1}$  is limited to  $v_I - 0.7\text{ V}$
- $R$  provides a small current through  $D_2$

➤ Voltage controlled current source

**OPTIONAL**

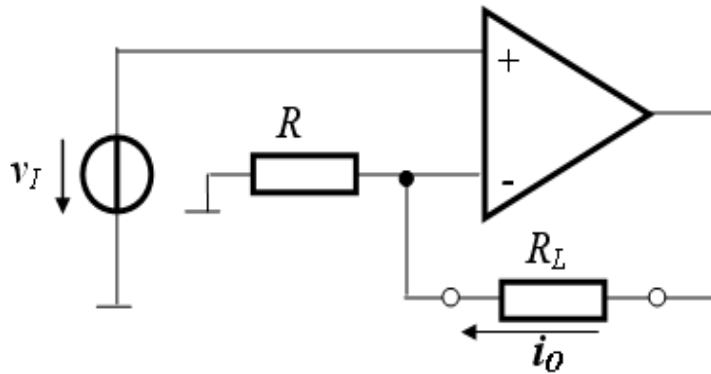

$$i_o = \frac{v_I}{R}$$

- $i_o$  does not depend on the value of  $R_L$
- adjustable  $i_o$  - replace  $R$  with  $(R + P)$


Circuit? Why can't  $R$  be replaced only with  $P$ ?

- value of  $i_o$  is **controlled** by the value of  $v_I$
- $R_L$  is not connected to ground -> **floating load**

?Circuit with non-floating load?

➤ Current source with non-floating load

**OPTIONAL**

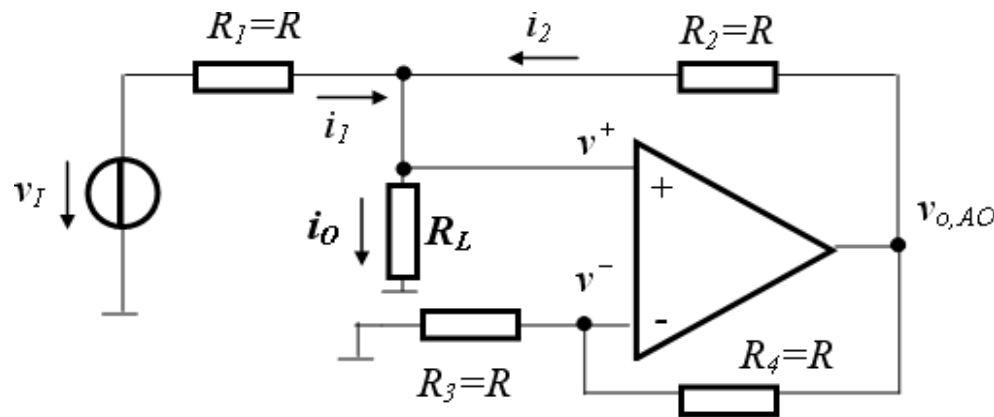

Howland source

NF and PF, NF is dominant

$$K^- = \frac{R_3}{R_3 + R_4} = \frac{R}{R + R} = \frac{1}{2}$$

$$K^+ = \frac{R_1 \parallel R_L}{R_1 \parallel R_L + R} = \frac{R \parallel R_L}{R \parallel R_L + R}$$

$$i_o = i_1 + i_2 = \frac{v_I - v^+}{R_1} + \frac{v_{o,OA} - v^+}{R_2}$$

$$v^+ = v^- = \frac{R_3}{R_3 + R_4} v_{o,OA} = \frac{1}{2} v_{o,OA}$$

$$v_{o,OA} = 2i_o R_L$$


$$i_o = \frac{v_I}{R}$$

Since  $R \parallel R_L < R$ ,

$K^- > K^+ \rightarrow$  **NF**

$$v^+ = v^-$$

**OPTIONAL**

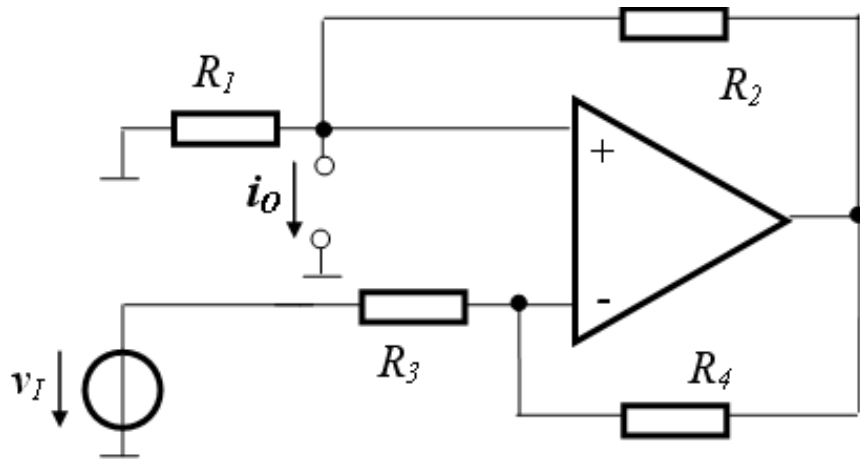


For  $\frac{R_1}{R_2} = \frac{R_3}{R_4}$

$$i_O = -\frac{v_I}{R_1}$$

The pairing of the resistors should be very accurate, in order to obtain a perfect current source (infinite output resistance).

Practical solution: current source using OpAmp and BJT/MOS

## ➤ Current follower

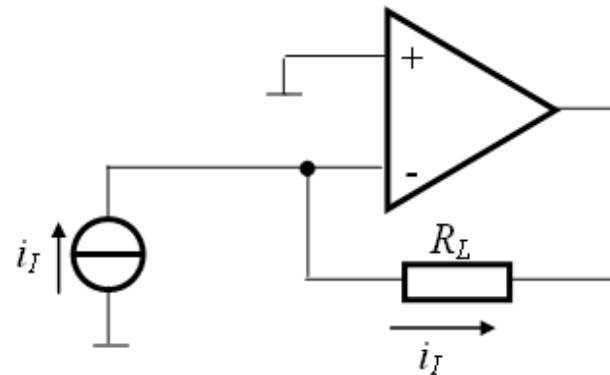
**OPTIONAL**

- The current source does not generate power
- The power in the load resistor,  $R_L$ , is obtained from the power supplies of the OpAmp



➤ Logarithmic amplifier

**OPTIONAL**

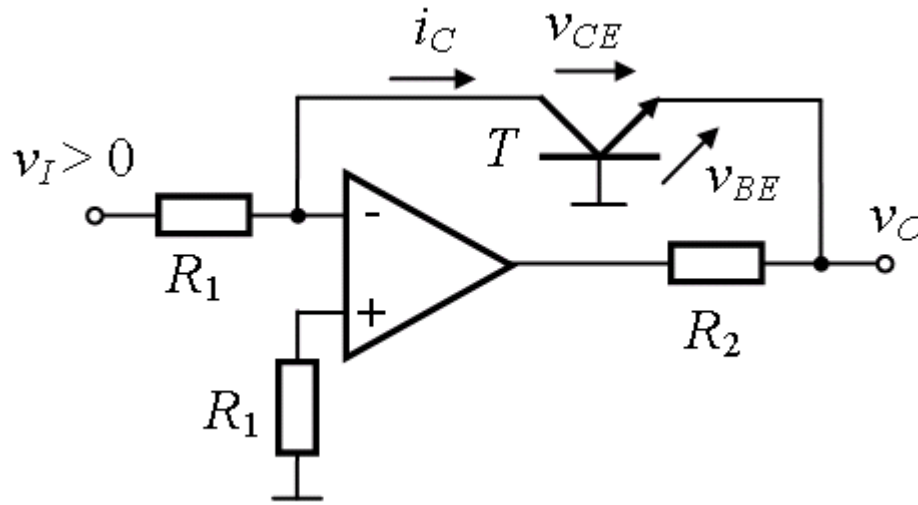

$$v_O = -v_{BE}$$

$$i_C = I_S e^{\frac{v_{BE}}{V_T}}$$

$$i_C = \frac{v_I}{R_1} \quad v_{BE} = V_T \ln \frac{i_C}{I_S}$$

$$v_O = -V_T \ln \frac{v_I}{R_1 I_S}$$


For  $v_I < 0$  - use *pnp* transistor

Limitations of the circuit:

- the range of the output voltage is narrow, hundreds of mV ( $v_O$  is a base to emitter voltage);
- temperature dependence of the output voltage ( $V_T$  and  $I_S$ )

➤ Exponential amplifier

**OPTIONAL**

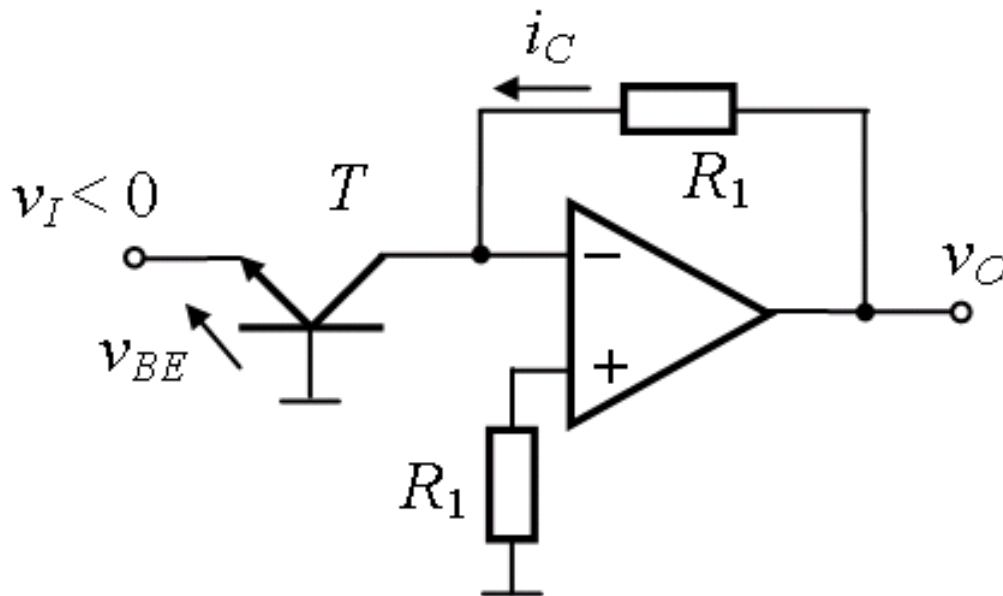

$$v_O = R_1 i_C$$


$$v_{BE} = -v_I$$

$$i_C = I_S e^{\frac{v_{BE}}{V_T}} = I_S e^{-\frac{v_I}{V_T}}$$

$$v_O = R_1 I_S e^{-\frac{v_I}{V_T}}$$

➤ Multiplication circuit

**OPTIONAL**

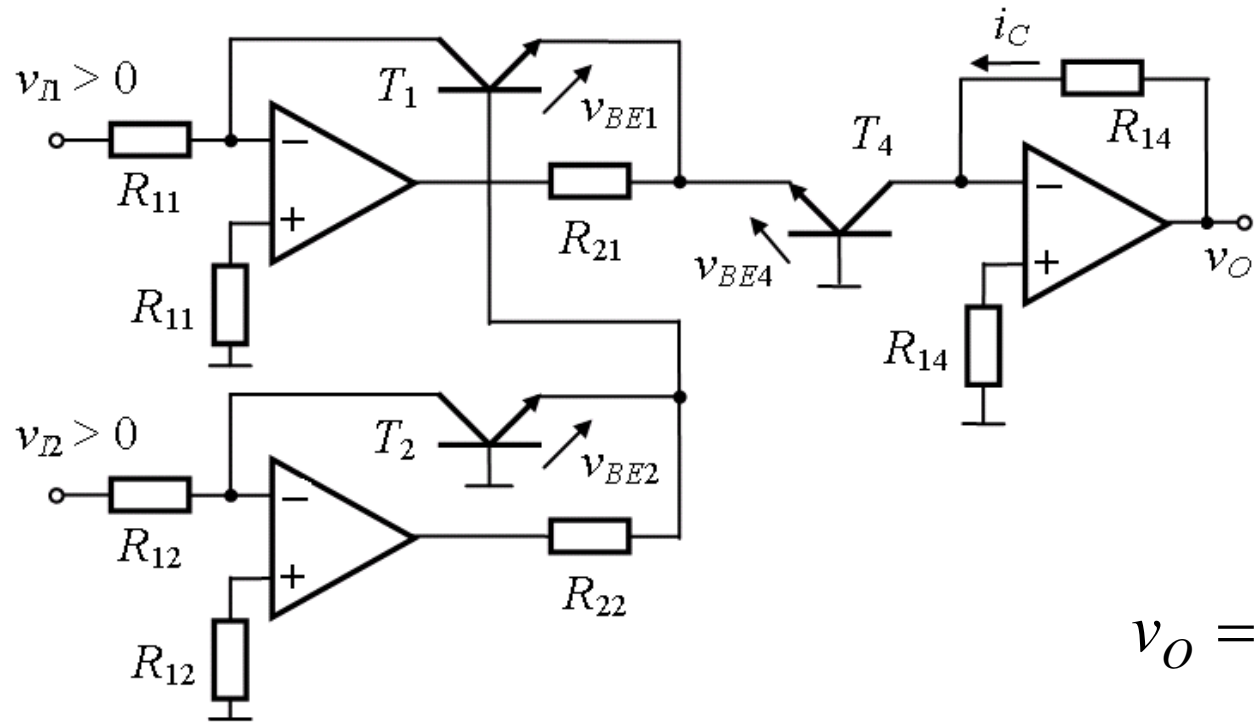

$$v_{BE1} = V_T \ln \frac{v_{I1}}{R_{11} I_S}$$

$$v_{BE2} = V_T \ln \frac{v_{I2}}{R_{12} I_S}$$

$$v_{BE4} = v_{BE1} + v_{BE2}$$


$$v_O = R_{14} I_S e^{\frac{v_{BE4}}{V_T}}$$

$$v_{I1} v_{I2} = e^{\ln(v_{I1} v_{I2})} = e^{(\ln v_{I1} + \ln v_{I2})}$$

$$v_O = \frac{R_{14}}{R_{11} R_{12} I_S} v_{I1} v_{I2}$$

➤ Multiplication and division circuit

**OPTIONAL**

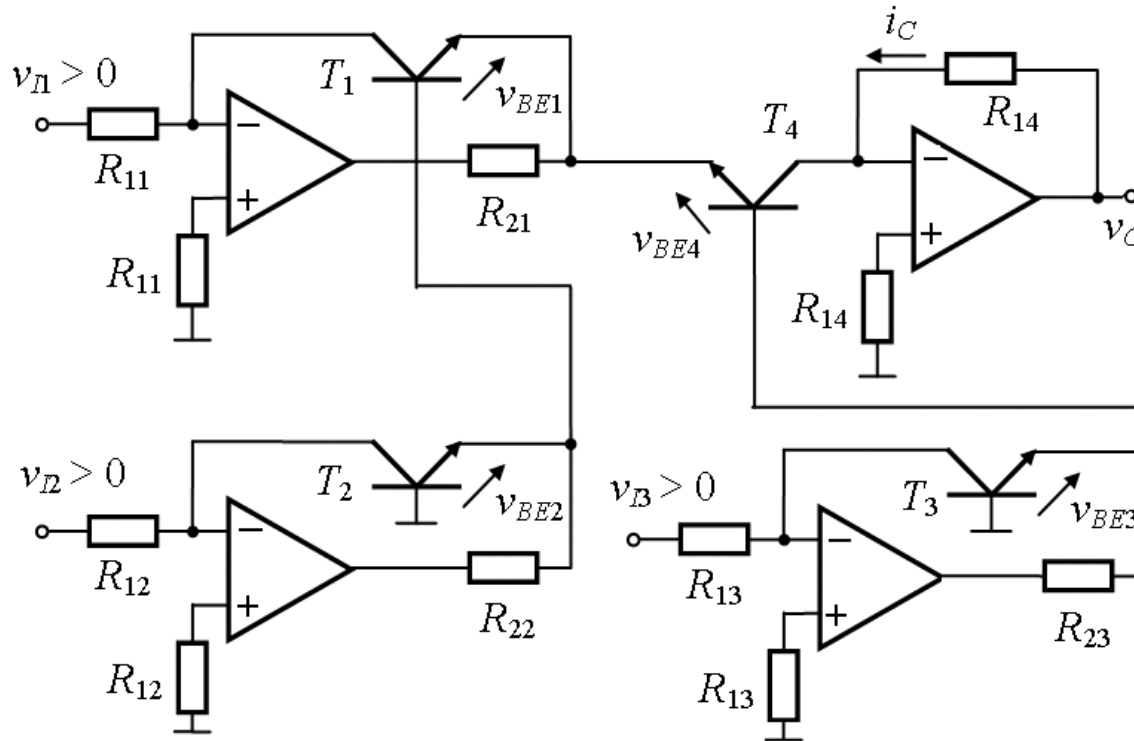

$$v_{BE1} = V_T \ln \frac{v_{I1}}{R_{11} I_S}$$

$$v_{BE2} = V_T \ln \frac{v_{I2}}{R_{12} I_S}$$

$$v_{BE3} = V_T \ln \frac{v_{I3}}{R_{13} I_S}$$

$$v_{BE4} = v_{BE1} + v_{BE2} - v_{BE3}$$

$$v_O = R_{14} I_S e^{\frac{v_{BE4}}{V_T}}$$

$$v_O = \frac{R_{14} R_{13}}{R_{11} R_{12}} \frac{v_{I1} v_{I2}}{v_{I3}}$$

For equal resistances:

$$v_O = \frac{v_{I1} v_{I2}}{v_{I3}}$$

No temperature dependence!

# Summary

Our last encounter with the OpAmp (this semester) showed us how it can be used to obtain more specialized applications.

New challenges await.

Next week: Transistors. BJTs.

**To do: Homework 8**