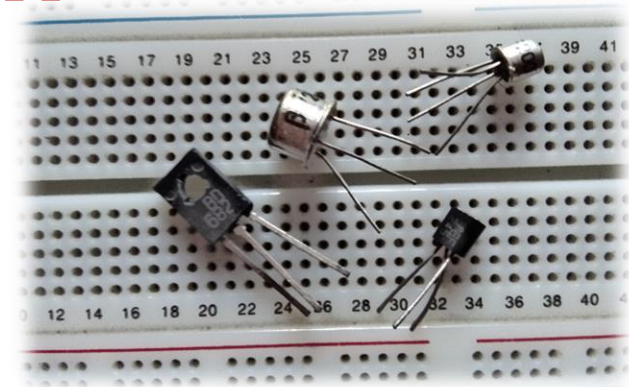




ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C13 – MOSFET operation



Contents

- Symbols
- Structure and physical operation
- Operating principle
- Transfer and output characteristics
- Quiescent point
- Operating regions
- Examples

Previously on ED (C11):

Transistors

= **active** semiconductor devices, with three terminals

- used to amplify or switch signals
- essential components of electronic circuits
- discrete or integrated

Operating principle:



The **voltage** applied between two terminals (command) controls the **current** through the third terminal

Metal-oxide-semiconductor field effect transistors (MOSFETS)


general symbols
(w/ B substrate terminal)

n-channel enhancement-type



p-channel enhancement-type

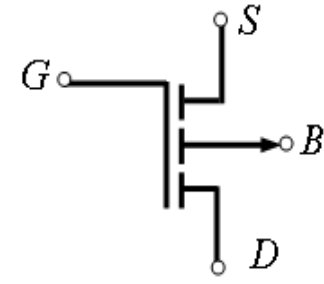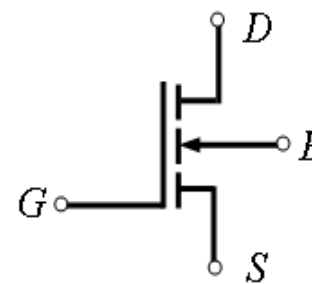

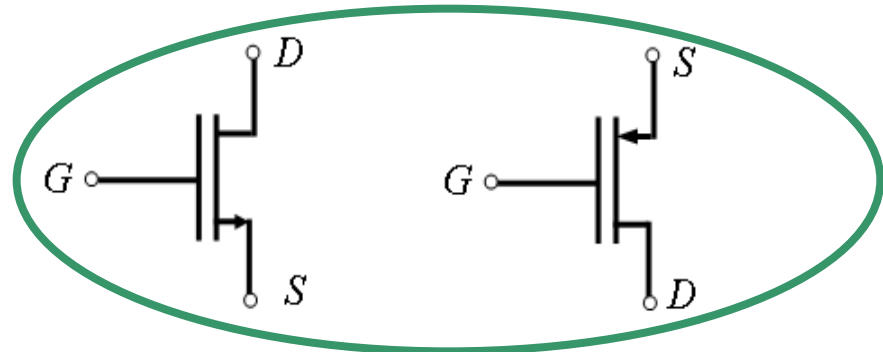simplified symbols
(B internally connected to S)





other symbols

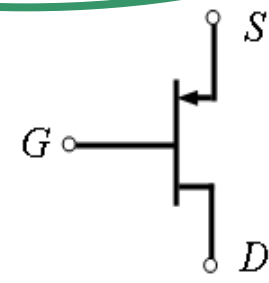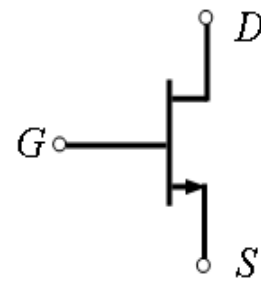



Metal-oxide-semiconductor field effect transistors (MOSFETS)

n-channel enhancement-type p-channel enhancement-type

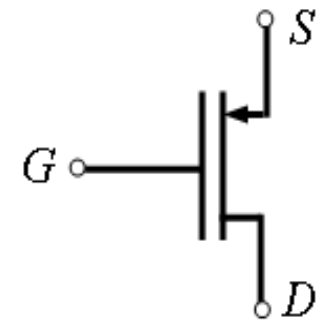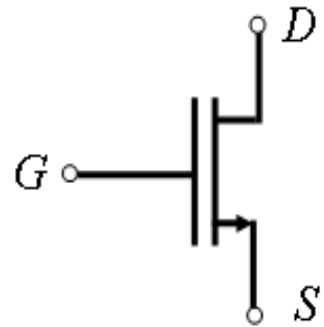- D – drain (similar to C)
- G – gate (similar to B)
- S – source (similar to E)




Structure and physical operation

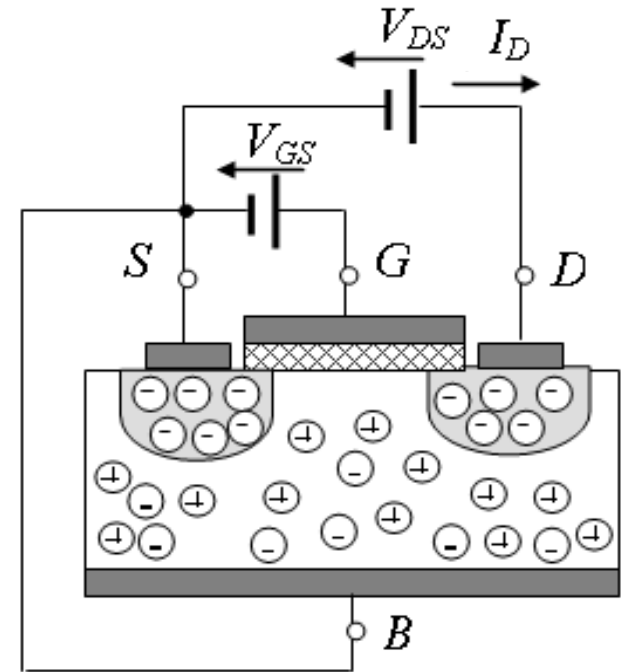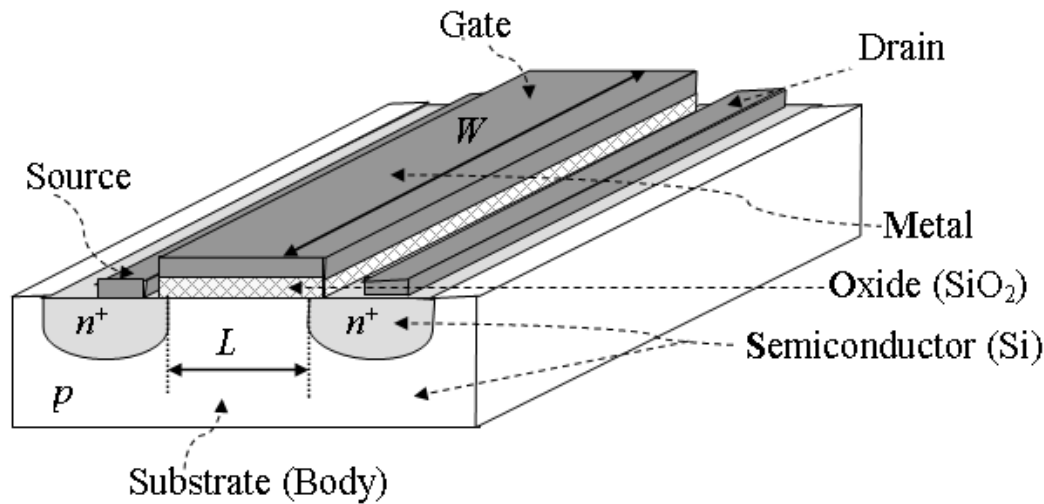

In order to have a drain-to-source current, two conditions must be fulfilled:

- creation of an n -type channel between the drain and source terminals
- existence of a positive potential difference between the drain and source to move the carriers

OPTIONAL

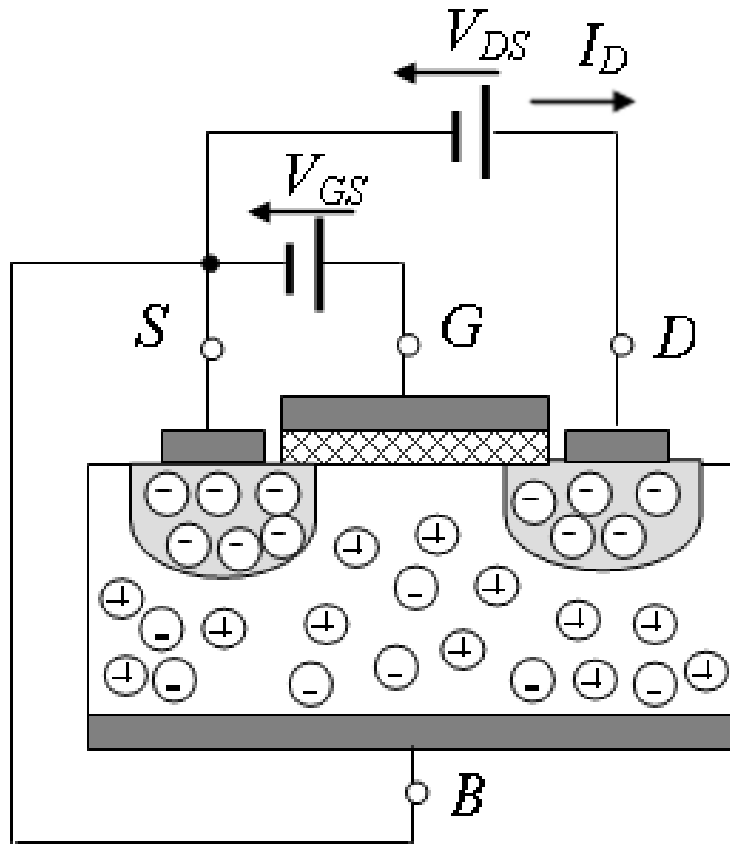


V_{Th} – threshold voltage

$$\begin{aligned}
 V_{GS} &< V_{Th} \\
 V_{DS} &= 0 \\
 I_D &= 0
 \end{aligned}$$

No possibility for the current to flow from drain to source

No channel

OPTIONAL

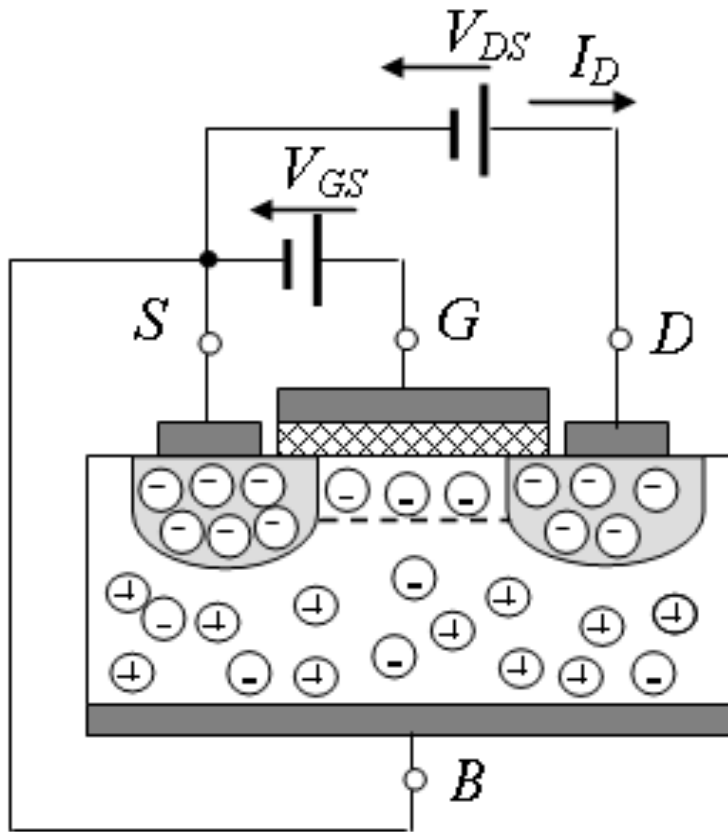

Due to the electric field created by $V_{GB} > 0$ ($V_{GS} > 0$), the electrons in the substrate will be attracted and accumulated just under the oxide (gate region).

When V_{GS} is increased further, the electron concentration becomes larger than the hole concentration; this process is called **population inversion**.

Inversion creates a conducting **n-channel** between the drain and the source.


The gate voltage V_{GS} at which inversion produces an n concentration equal to the unbiased p concentration is called the **threshold voltage V_{Th}** .

$$V_{GS} > V_{Th}$$

$$V_{DS} = 0$$

$$I_D = 0$$

OPTIONAL

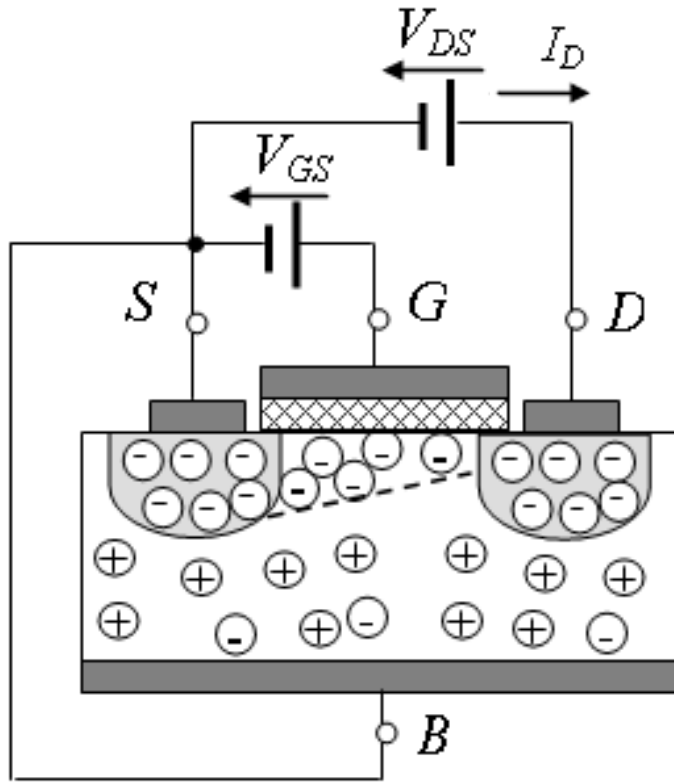

The current flows through the channel under the action of $V_{DS} > 0$. The transistor operates in the **linear region**.

The channel will become shallower at the drain end, because the electrons from the close vicinity of the drain region are attracted by the positive drain region.

$$I_D = \beta \left[2(V_{GS} - V_{Th})V_{DS} - V_{DS}^2 \right]$$

$$I_D = \frac{K}{2} \frac{W}{L} \left[2(V_{GS} - V_{Th})V_{DS} - V_{DS}^2 \right]$$

β – constructive parameter [$\mu\text{A}/\text{V}^2$]

K – transconductance parameter [$\mu\text{A}/\text{V}^2$]

W, L – physical dimensions of channel [μm]


$$V_{GS} > V_{Th}$$

$$0 < V_{DS} < V_{DSsat}$$

$$I_D > 0$$

The current depends **linearly** on V_{GS} , but also depends on V_{DS} .

OPTIONAL

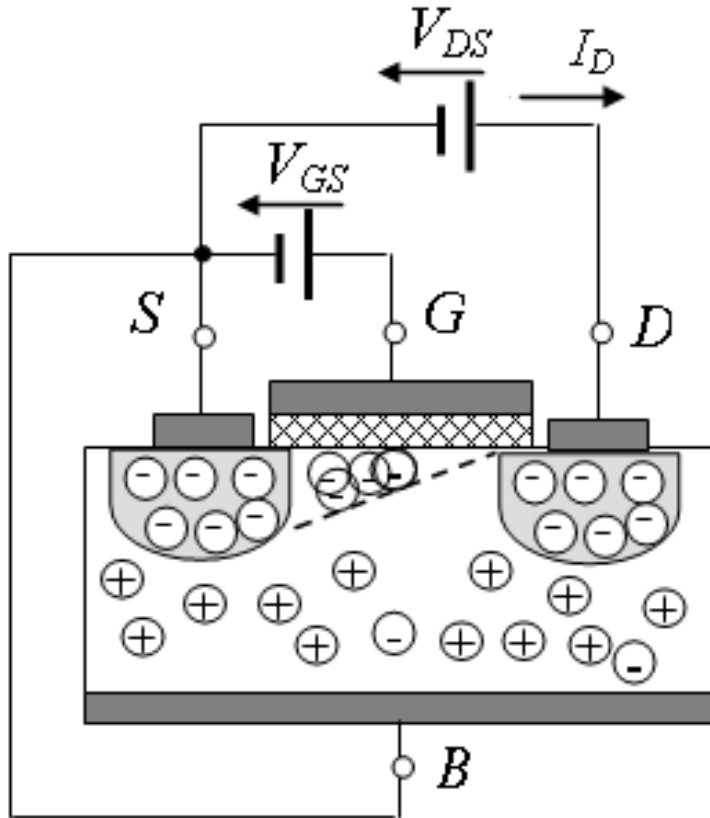

$$\begin{aligned}
 V_{GS} &> V_{Th} \\
 V_{DS} &> V_{DSsat} \\
 I_D &> 0
 \end{aligned}$$

The V_{DS} voltage is greater than the V_{DSsat} voltage.

All the electrons from the close vicinity of the drain region are attracted by the more positive drain region.

The channel depth becomes zero at the drain end. The transistor is now in the **pinch-off region**, or **saturation region** or **active region**.

I_D is almost independent of the V_{DS} . Conduction from the source to drain still occurs with current passing through the depletion region next to the drain.


$$I_D = \beta(V_{GS} - V_{Th})^2 \left(1 + \frac{V_{DS}}{V_A} \right) \cong \beta(V_{GS} - V_{Th})^2$$

$$I_D = \frac{K}{2} \frac{W}{L} (V_{GS} - V_{Th})^2 \left(1 + \frac{V_{DS}}{V_A} \right) \cong \frac{K}{2} \frac{W}{L} (V_{GS} - V_{Th})^2$$

The current depends **non-linearly (quadratic)** on V_{GS}

➤ The current through MOSFET

$$I_D = f(V_{GS}, V_{DS})$$

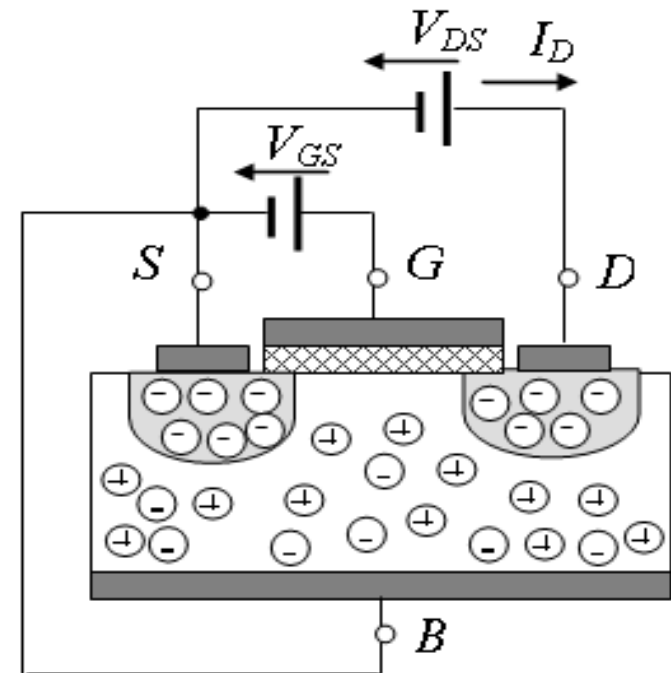

The current depends on

- V_{GS} - conducting channel building (enhancement)
- V_{DS} – controlled movement of the carriers (free electrons between D and S terminals)


➤ n-channel enhancement type MOSFET

- Family of transfer characteristics

$$i_D(v_{GS}), v_{DS} \text{ as parameter}$$

- Family of output characteristics
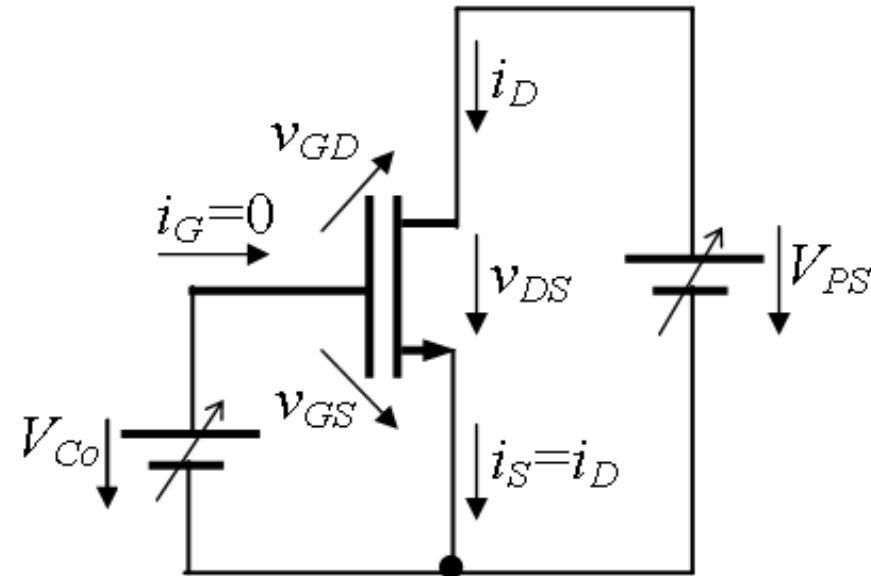
$$i_D(v_{DS}), v_{GS} \text{ as parameter}$$



$$v_{GS} = v_{Co}$$

$$v_{DS} = V_{PS}$$

$$i_D + i_G = i_S$$

$$i_G = 0$$

$$i_D = i_S$$

➤ Transfer characteristics

$i_D(v_{GS})$, v_{DS} as parameter

$V_{DSsat} = v_{GS} - V_{Th}$ drain-source saturation voltage

• Saturation region (a_F)

$$v_{DS} > V_{DSsat} \quad i_D = \beta(v_{GS} - V_{Th})^2$$



i_D – quadratic dependence on v_{GS}

• Linear region (exc)

$$v_{DS} < V_{DSsat} \quad i_D = \beta[2(v_{GS} - V_{Th})v_{DS} - v_{DS}^2]$$

i_D – linear dependence on v_{GS}

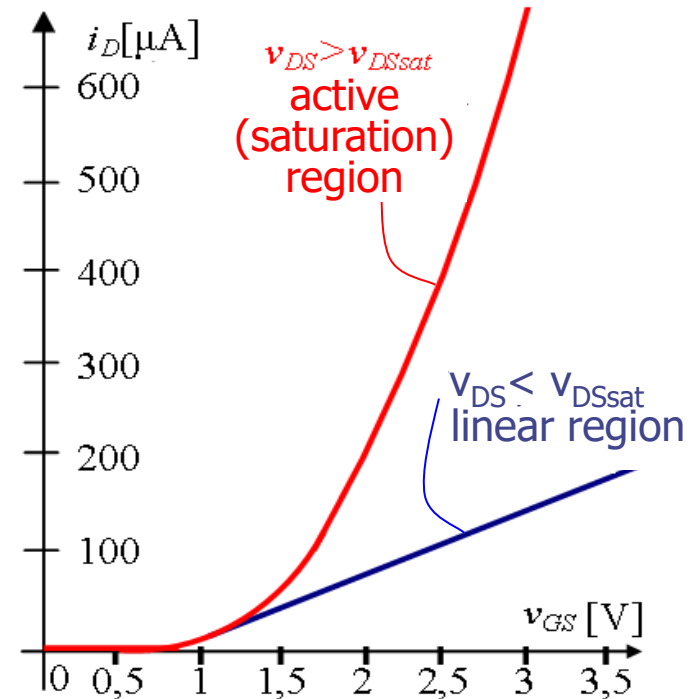
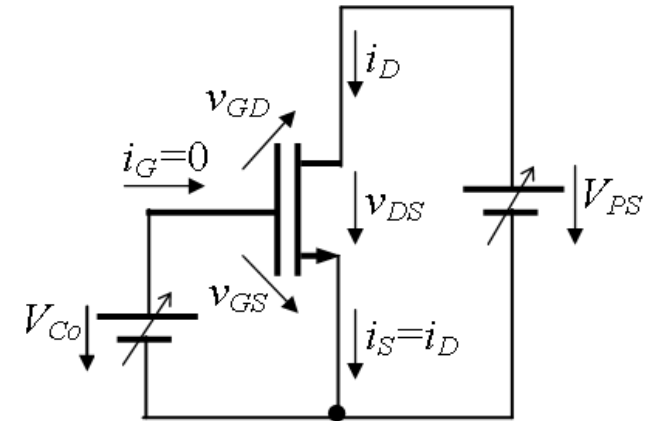
- also influenced by the output voltage v_{DS}



$$V_{Th} = 0.58 \text{ V}, \quad \beta = 104 \text{ } \mu\text{A/V}^2$$

➤ Output characteristics

$i_D(v_{DS}), v_{GS}$ as parameter

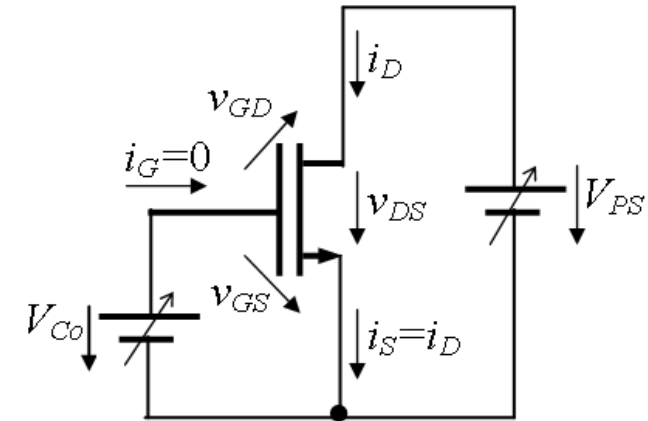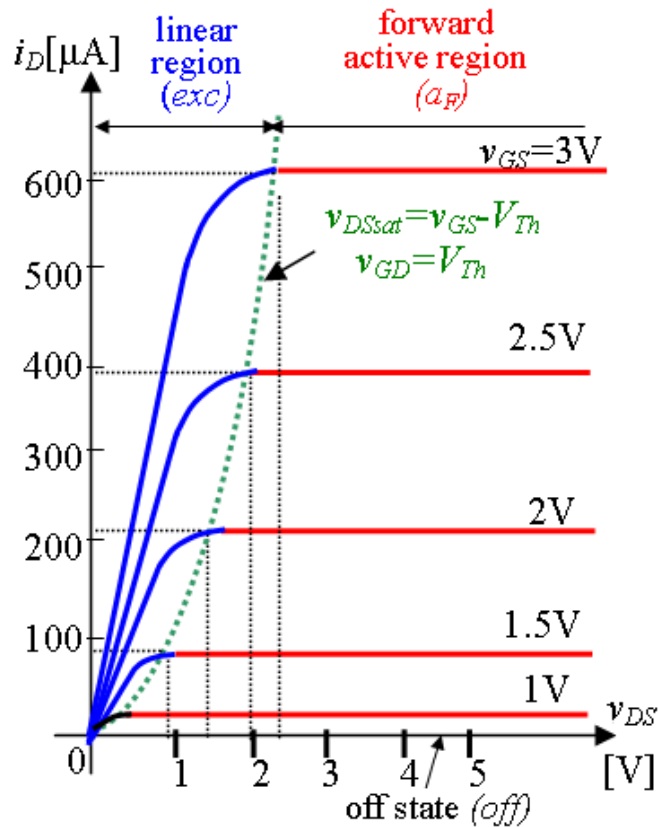

• Saturation region (aF)

$v_{DS} > V_{DSsat}$ $i_D = \beta(v_{GS} - V_{Th})^2$

i_D – quadratic dependence on v_{GS}

• Linear region (exc)

$v_{DS} < V_{DSsat}$ $i_D = \beta[2(v_{GS} - V_{Th})v_{DS} - v_{DS}^2]$


i_D – linear dependence on v_{GS}

- also influenced by the output voltage v_{DS}

Quiescent point Q = a point on the output characteristic $i_D(v_{DS})$ of MOSFET

- Q is defined by V_{DS} and I_D
- $Q(V_{DS}, I_D)$ is at the intersection between the load line and the output characteristic corresponding to v_{GS}

Load line:
 $v_{DS} = V_{PS} - R_D i_D$

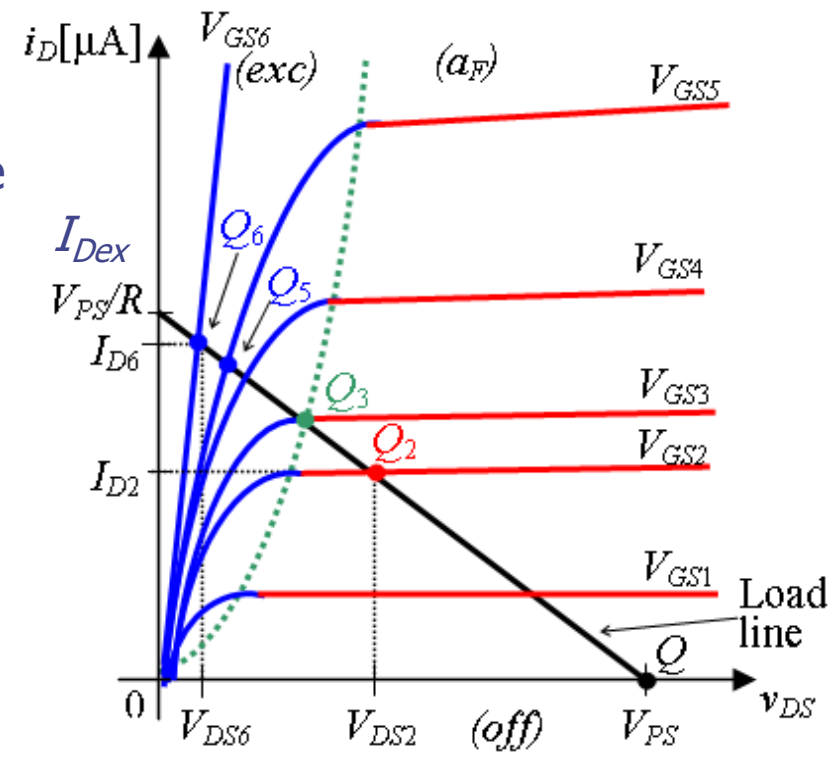

T – (off): $V_{GS} < V_{Th}$

$$i_D = 0$$


T – (a_F): $V_{Th} < V_{GS} < V_{GS3}$

$$i_D = \beta (v_{GS} - V_{Th})^2$$

Boundary (a_F) - (exc): $v_{DS,sat} = v_{GS} - V_{Th}$

T – (exc): $V_{GS} > V_{GS3}$
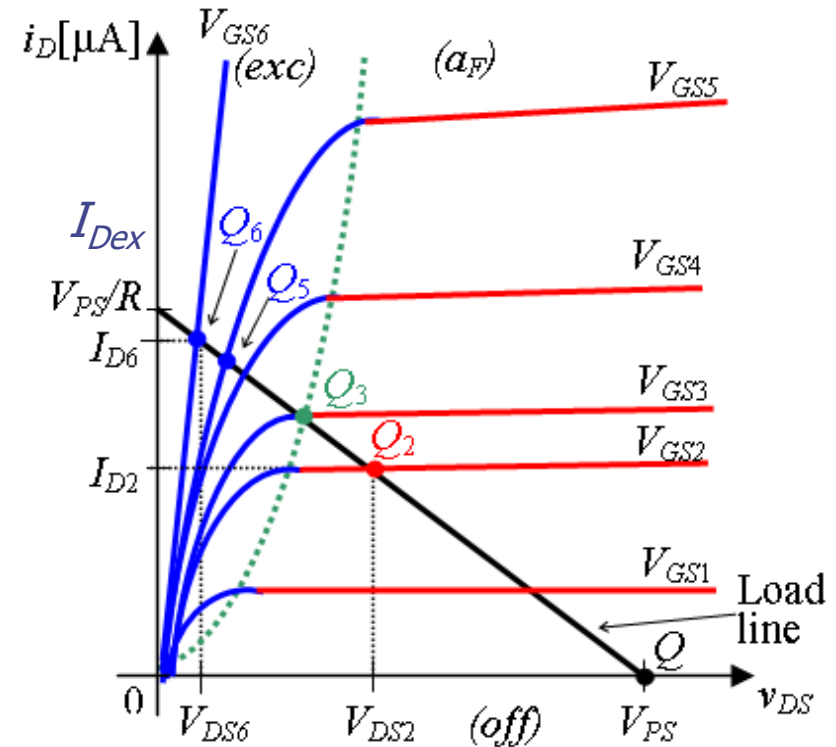
$$i_D = \beta [2(v_{GS} - V_{Th})v_{DS} - v_{DS}^2]$$



- Modes of use
 - switching mode: (off) / (exc)
 - as an amplifier: (a_F)
 - voltage-controlled linear resistance (small v_{DS})

Linear region (exc):

$$i_D = \beta [2(v_{GS} - V_{Th})v_{DS} - v_{DS}^2]$$

β – parameter of the MOSFET - beta factor
 - measured in $\mu\text{A}/\text{V}^2$, mA/V^2 , A/V^2
 - constructive parameter

Saturation (active) region (a_F):

$$i_D = \beta (v_{GS} - V_{Th})^2$$

For integrated transistors:

$$\beta = \frac{K}{2} \frac{W}{L}$$

$$i_D = \frac{K}{2} \frac{W}{L} (v_{GS} - V_{Th})^2$$

In the active region

K – transconductance parameter [$\mu\text{A}/\text{V}^2$]
 W - the width of the channel [μm]
 L - the length of the channel [μm]




➤ Example - 1

Compute the values of V_{GS} , I_D , V_{DS} , V_{GD} , V_{DSsat} for:

- i) $v_{Co} = 0.5 \text{ V}$;
- ii) $v_{Co} = 2.5 \text{ V}$;
- iii) $v_{Co} = 2.75 \text{ V}$.

Place the quiescent points $Q(V_{DS}, I_D)$ in the plan of output characteristics.

Find the operating regions of T.

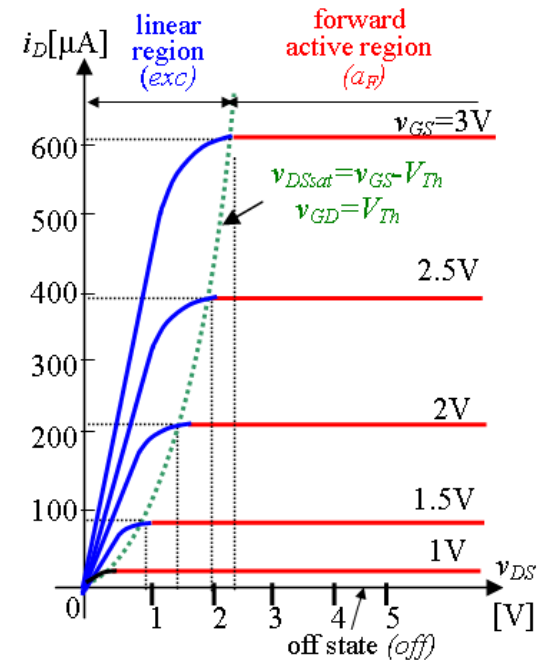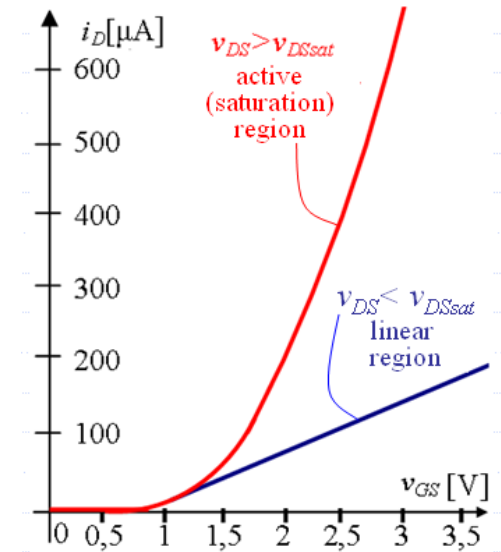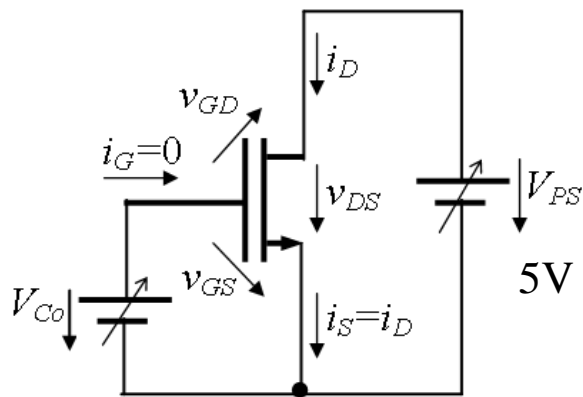


➤ Example - 2

a) What is the operating region of T for:

- i) $v_{GS} = 0.8 \text{ V}$;
- ii) $v_{GS} = 2.5 \text{ V}$;
- iii) $v_{GS} = 4 \text{ V}$.

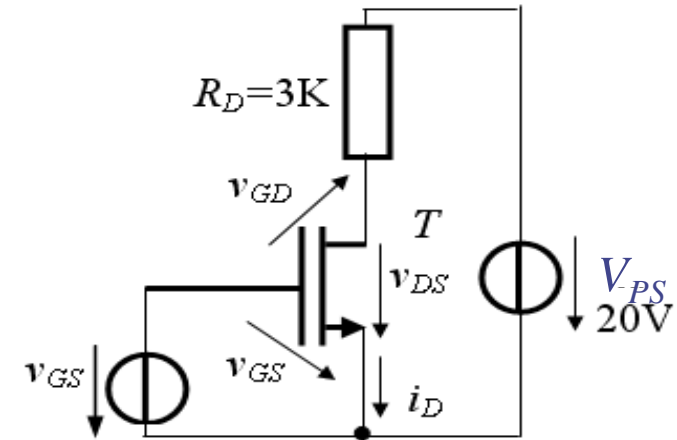b) What is the minimum value of v_{GS} so that T stays in (exc)?



$$B = 2 \text{ mA/V}^2$$

$$V_{Th} = 1 \text{ V}$$

➤ Example - 2


Solution:

a)

i) Because $v_{GS} < V_{Th}$ \Rightarrow T - (off)

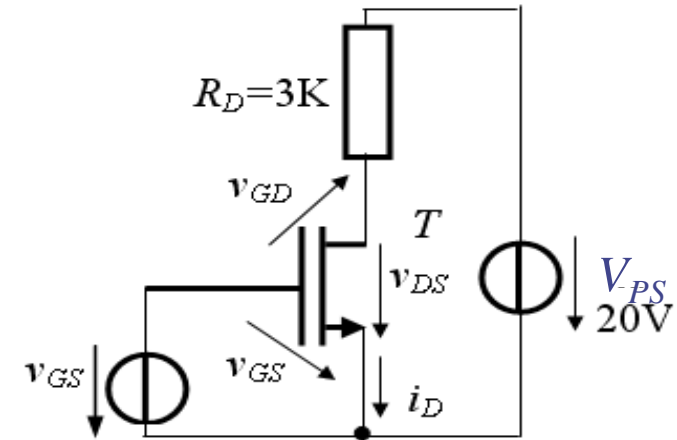ii) $v_{GS} > V_{Th} \Rightarrow$ T is on, in (a_F) or in (exc)

- Assume T in (a_F), so that $i_D = \beta(v_{GS} - V_{Th})^2$
- Compute v_{DS}
- Compare v_{DS} with v_{DSsat} :
 - If $v_{DS} > v_{DSsat}$ the assumption was **true**, and T is in (a_F)
 - If $v_{DS} < v_{DSsat}$ the assumption was **false**, and T is in (exc)



$$B = 2 \text{ mA/V}^2$$

$$V_{Th} = 1 \text{ V}$$

➤ Example - 2

Solution:

a) ii)

$$i_D = 2(2.5 - 1)^2 = 4.5 \text{ mA}$$


$$v_{DS} = V_{PS} - R_D i_D$$

$$v_{DS} = 20 - 3 \cdot 4.5 = 6.5 \text{ V}$$

$$v_{DS \text{ sat}} = v_{GS} - V_{Th} = 2.5 - 1 = 1.5 \text{ V}$$

$v_{DS} > v_{Dssat}$ T is in (a_F)
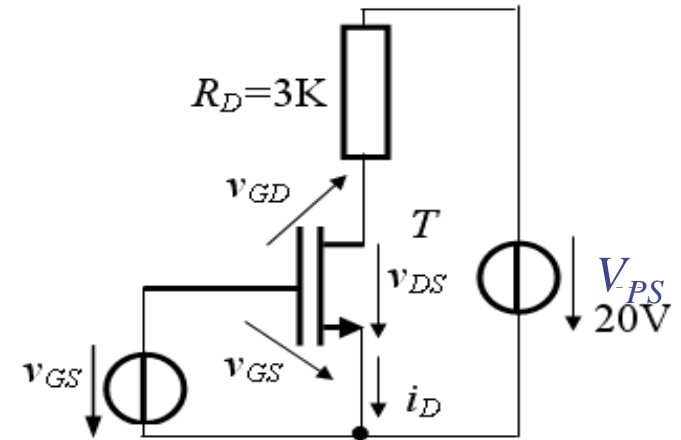
$$v_{GD} = v_{GS} - v_{DS} = 2.5 - 6.5 = -4 \text{ V} < V_{Th}$$




$$B = 2 \text{ mA/V}^2$$

$$V_{Th} = 1 \text{ V}$$

➤ Example - 2

Solution:

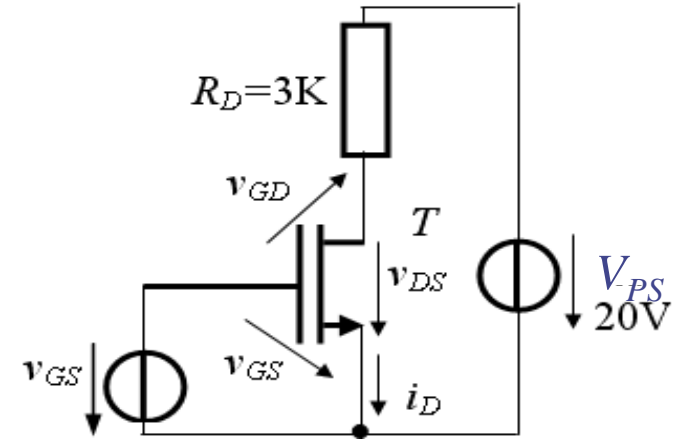

$$B = 2 \text{ mA/V}^2$$

$$V_{Th} = 1 \text{ V}$$

a) iii) $v_{GS} > V_{Th} \Rightarrow T$ is on, in (a_F) or in (exc)

- Assume **T** in (a_F), so that $i_D = \beta(v_{GS} - V_{Th})^2$

$$i_D = 2(4 - 1)^2 = 18 \text{ mA}$$

- Compute v_{DS} $v_{DS} = 20 - 3 \cdot 18 = -34 \text{ V}$

- Compare v_{DS} with v_{DSsat} :

$$V_{DS \text{ sat}} = v_{GS} - V_{Th} = 4 - 1 = 3 \text{ V} \qquad v_{DS} < v_{Dssat}, \text{ T is in (exc)}$$

Alternative method: compare the value of i_D in (a_F) with i_{Dex}


$$i_{Dex} = \frac{V_{PS} - v_{DS,ex}}{R} \approx \frac{V_{PS}}{R} = \frac{20}{3} = 6.67 \text{ mA} \qquad i_D = 18 \text{ mA} > i_{Dex} = 6.67 \text{ mA} \Rightarrow T - \text{(exc)}$$

What is the actual value of i_D ?

➤ Example - 2

Solution:

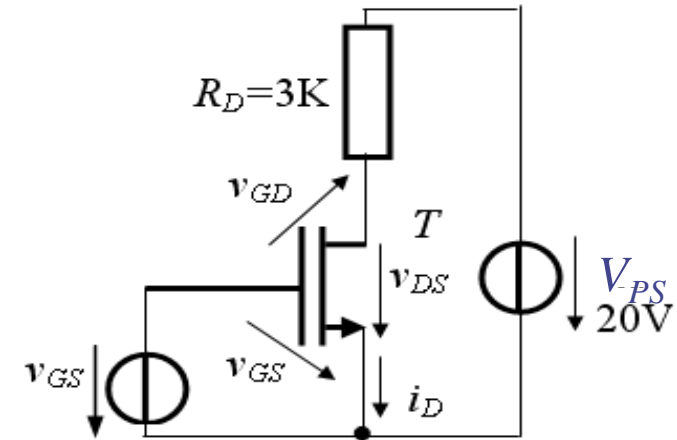b) Minimum value of v_{GS} so that T stays in (exc)



$$B = 2 \text{ mA/V}^2$$

$$V_{Th} = 1 \text{ V}$$

The operating point of T is placed on the v_{DSsat} curve:

$$v_{DSsat} = V_{PS} - R_D i_D \qquad V_{PS} - R_D i_D = v_{GSmin} - V_{Th}$$



$$v_{DSsat} = v_{GSmin} - V_{Th} \qquad i_D = \beta (v_{GSmin} - V_{Th})^2$$

$$R \beta (v_{GSmin} - V_{Th})^2 + (v_{GSmin} - V_{Th}) - V_{PS} = 0$$

Two solutions for v_{GSmin} , choose the convenient one: $v_{GSmin} > V_{Th}$

$$v_{GSmin} = 2.744 \text{ V}$$

➤ Example - 3

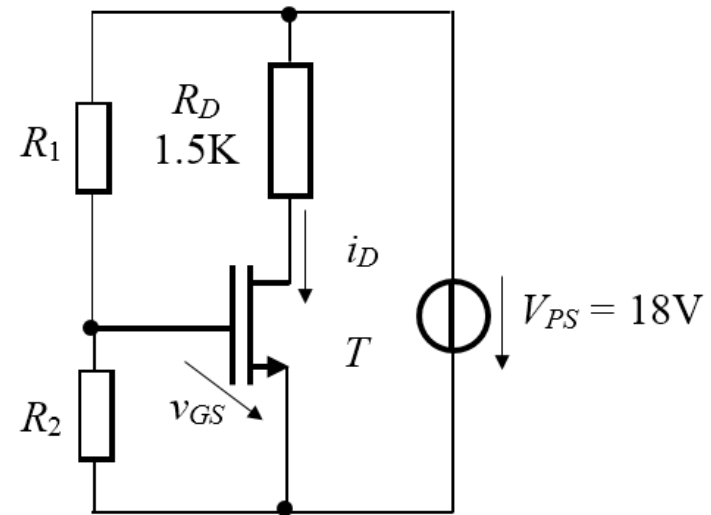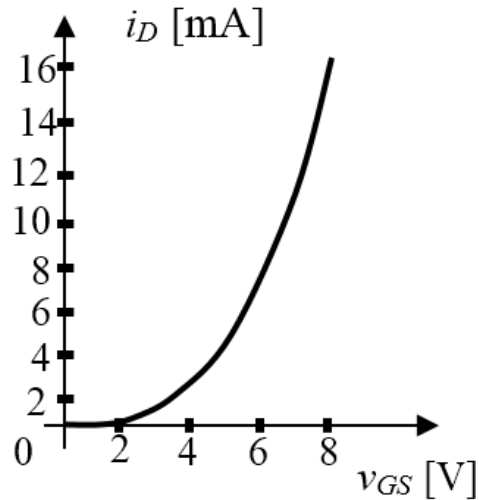

- a) Determine the operating region of the transistor for:
- $R_1 = 4.5 \text{ M}\Omega$; $R_2 = 0.5 \text{ M}\Omega$;
 - $R_1 = 12 \text{ M}\Omega$; $R_2 = 6 \text{ M}\Omega$;
- b) What can be the range for R_1 with $R_2 = 0.5 \text{ M}\Omega$ so that the transistor is (on)?

Summary

The MOSFET is no longer a random acronym, after digging into:

- Symbols
- Structure and physical operation
- Operating principle
- Transfer and output characteristics
- Quiescent point
- Operating regions
- Examples

Next week: Recap. Preparation for exam.

To do: Homework 10