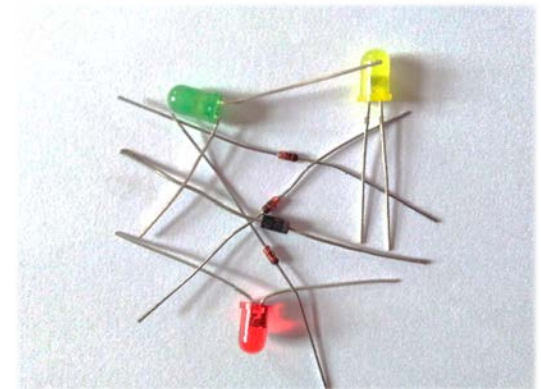




ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.



C2 – Diodes. DR circuits.




Contents

- Physical structure. Symbol.
- Current-voltage characteristic
- Operating regions
- Operating (quiescent) point
- Parameters of the diode
- Constant voltage drop model
- Analysis of two-port DR networks


Physical structure – *pn* junction

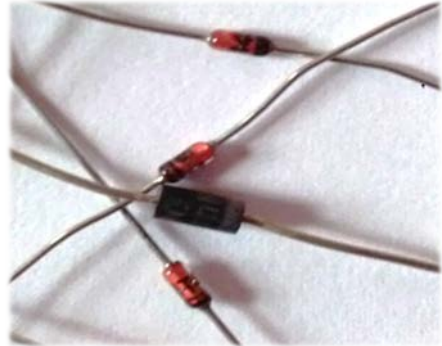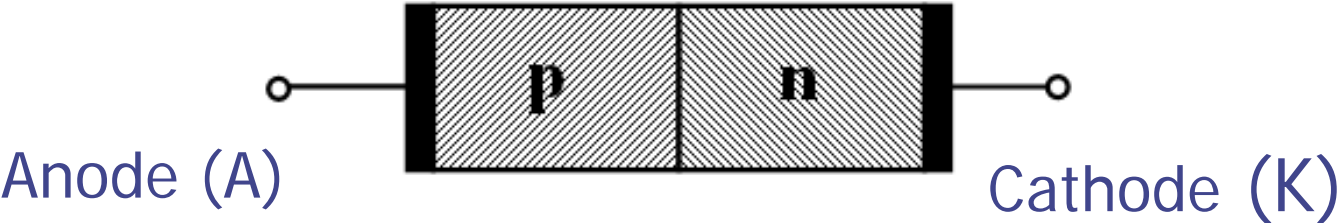

circuit symbol

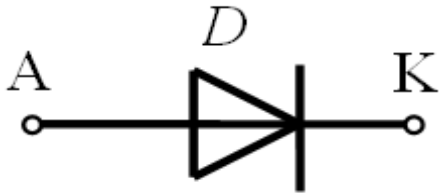


directions for current and voltage

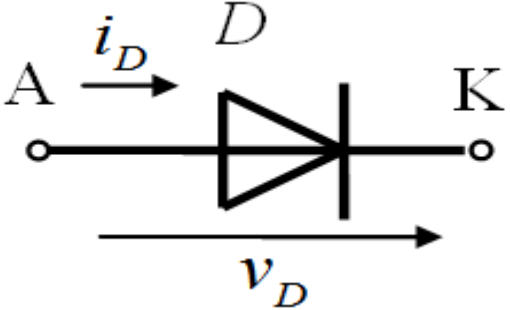

The arrow in the diode's symbol indicates the direction of the forward current flow.

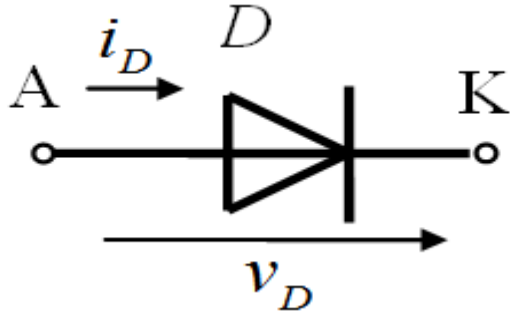The current flowing through the diode is controlled by the voltage drop across the diode itself – **nonlinear** semiconductor device



Diode equation – William Shockley (Bell Labs, 1950)

$$i_D = I_S \left(e^{\frac{v_D}{nV_T}} - 1 \right)$$

I_S - saturation current (~ nA - pA)

$n=2$ discrete diodes

$n=1$ integrated diodes

$$V_T = \frac{KT}{q}$$

thermal voltage

K - Boltzmann's constant


q - elementary charge (electric charge carried by a single electron)

T - absolute temperature measured in K

$$V_T = 25\text{mV} @ 20^\circ\text{C}$$

$$i_D = I_S \left(e^{\frac{v_D}{nV_T}} - 1 \right)$$

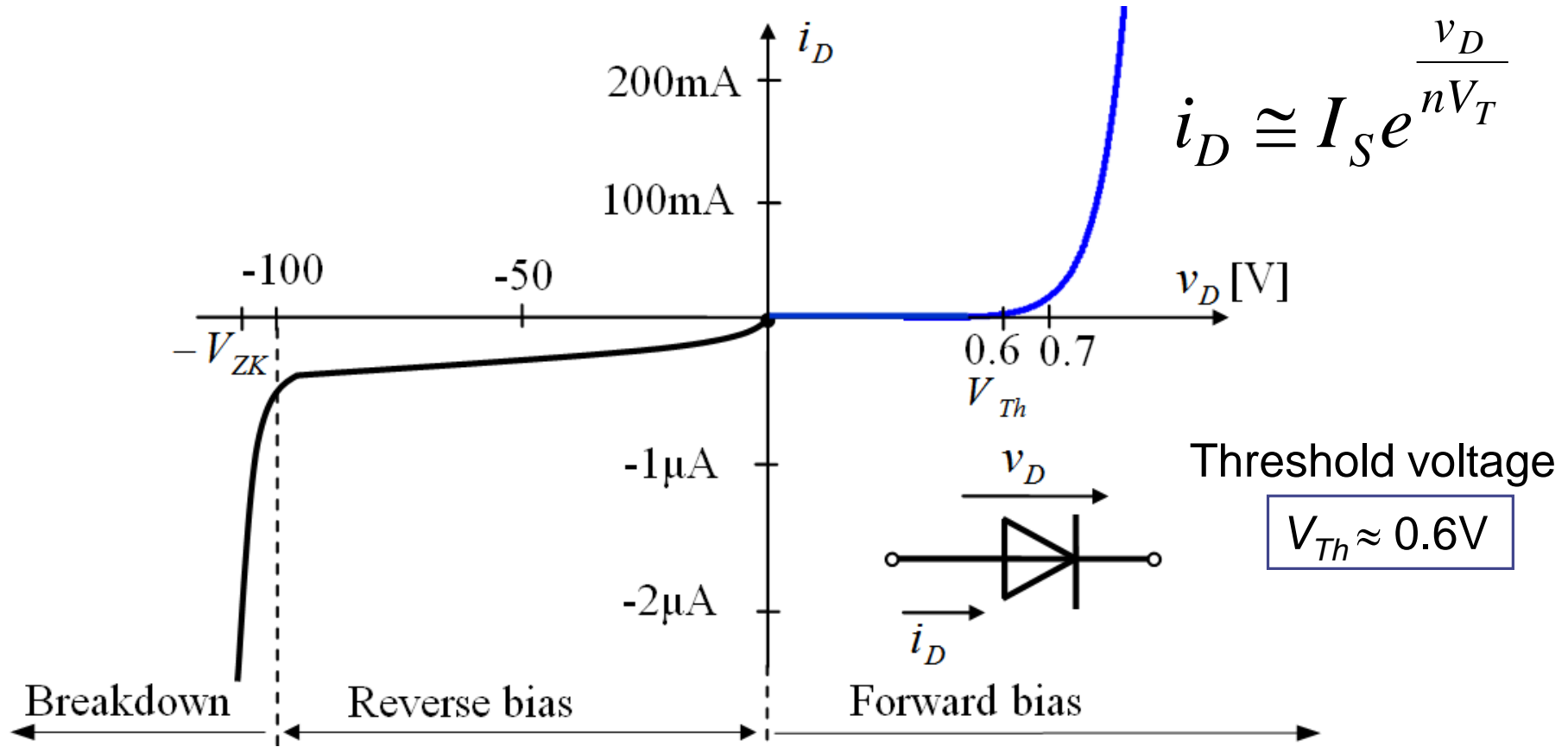
Exponential model of the diode
(valid in forward and reverse regions)



$$i_D \cong I_S e^{\frac{v_D}{nV_T}}$$

!Mind the scale for the Y-axis!

Numerical illustration

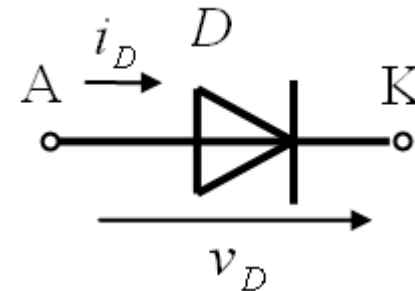

D is a rectifier diode, 1N400x with $I_S = 14 \text{ nA}$, $n = 2$



Assuming a voltage drop across the diode

$$v_D = 0.7 \text{ V}$$

the current through the diode results as:

$$i_D = 14 \cdot 10^{-9} \left(e^{\frac{700}{2 \cdot 25}} - 1 \right) = 16.8 \text{ mA}$$
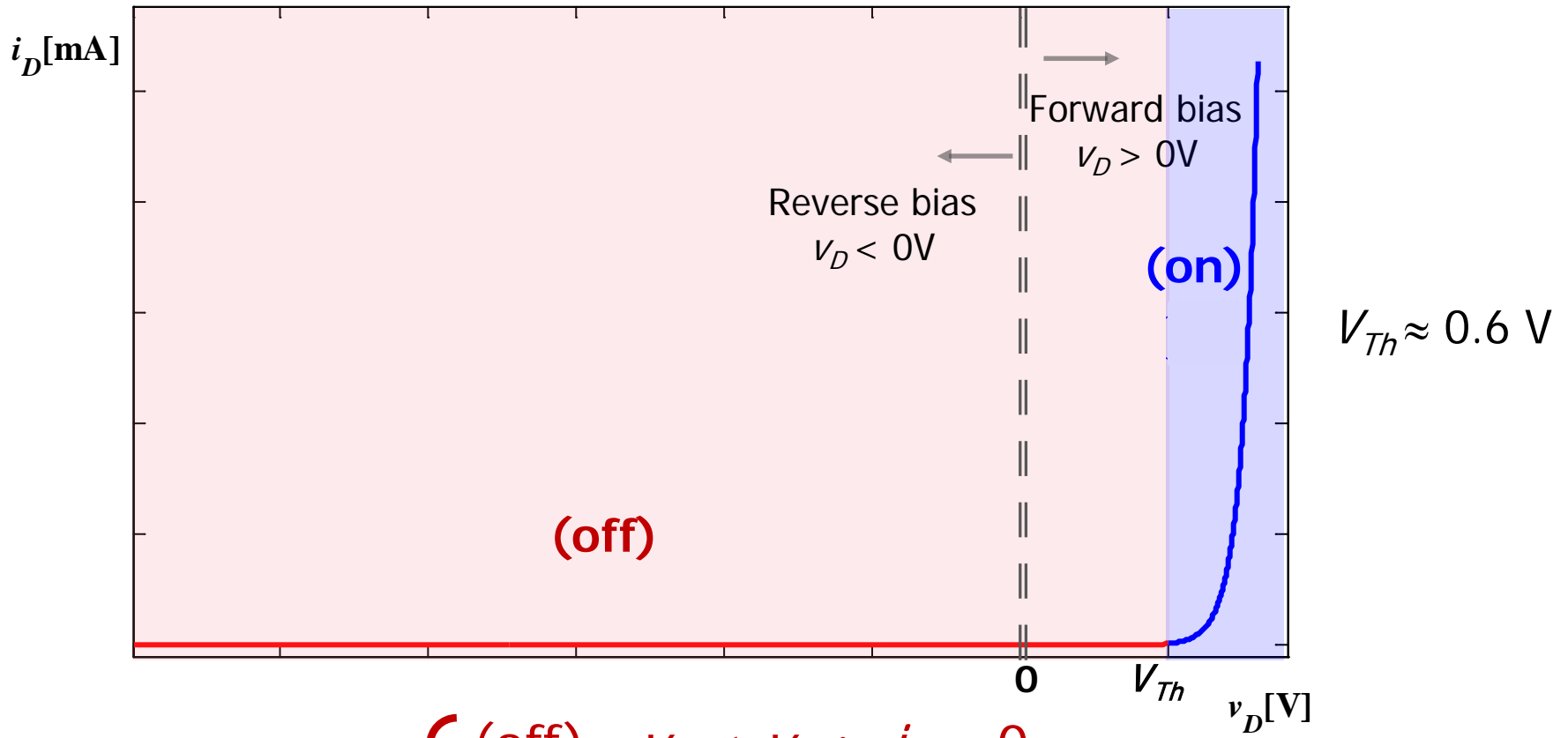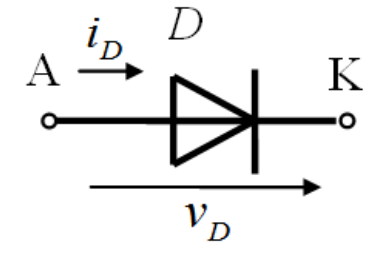
$$i_D = I_S \left(e^{\frac{v_D}{nV_T}} - 1 \right)$$



$$\left\{ \begin{array}{l} \text{(off)} \quad V_D < V_{Th}; \quad i_D = 0 \\ \text{(on)} \quad V_D > V_{Th}; \quad i_D > 0 \end{array} \right.$$

$$Q(V_D; I_D)$$


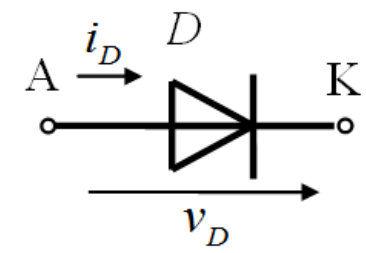


Illustration for 1N400x with $I_S = 14 \text{ nA}$, $n = 2$

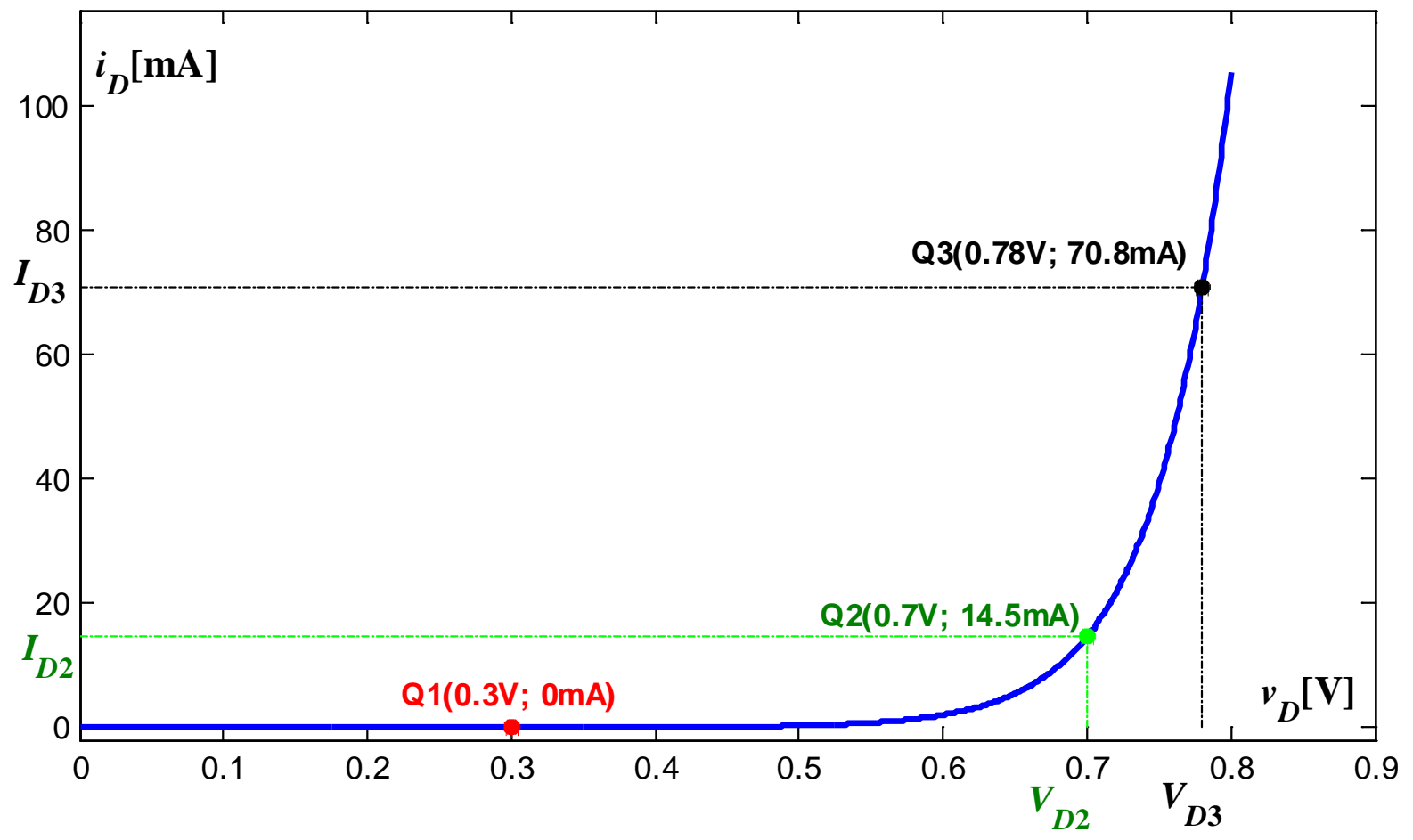


Temperature dependence

$$i_D \cong I_S e^{\frac{v_D}{nV_T}}$$

I_S , V_T - depend directly on the temperature

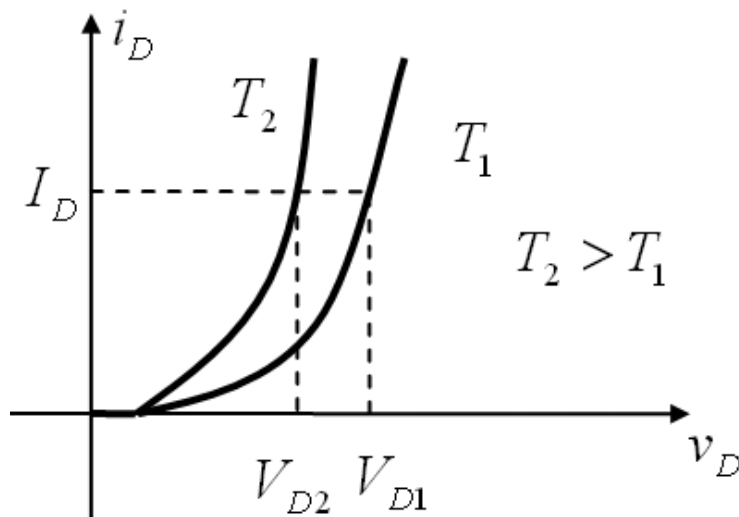At a **constant current**, the voltage across the diode **decreases** by ~ 2 mV for every 1°C increase in temperature



$TC = -2\text{mV}/^\circ\text{C}$ negative temperature coefficient

$$20^\circ\text{C} \quad v_D = 650\text{mV}$$

$$40^\circ\text{C} \quad v_D = 610\text{mV}$$

$$v_D(T_2) = v_D(T_1) + TC \cdot (T_2 - T_1) \Big|_{I_D = \text{cst}}$$

At a **constant voltage** across the diode, the current **increases** with the temperature

The parameters of the diode are defined (and computed) in the operating (quiescent) point, $Q(V_D, I_D)$

- **Static parameters** – defined in static regime (dc)
 - static resistance r_D

- **Dynamic parameters** – defined in variable regime (ac)
 - a.k.a. small signal parameters*
 - dynamic (small signal resistance) r_d

➤ Static parameters

$$r_D = \frac{V_D}{I_D} \Big|_Q \quad \text{static resistance}$$


$$g_D = \frac{1}{r_D} = \frac{I_D}{V_D} \Big|_Q \quad \text{static conductance}$$

Example:

$$Q_1(0.65\text{V}; 5.4\text{mA}) \quad r_{D1} = \frac{0.65}{5.4} = 120\Omega$$

$$Q_2(0.7\text{V}; 14.5\text{mA}) \quad r_{D2} = \frac{0.7}{14.5} = 48.3\Omega$$
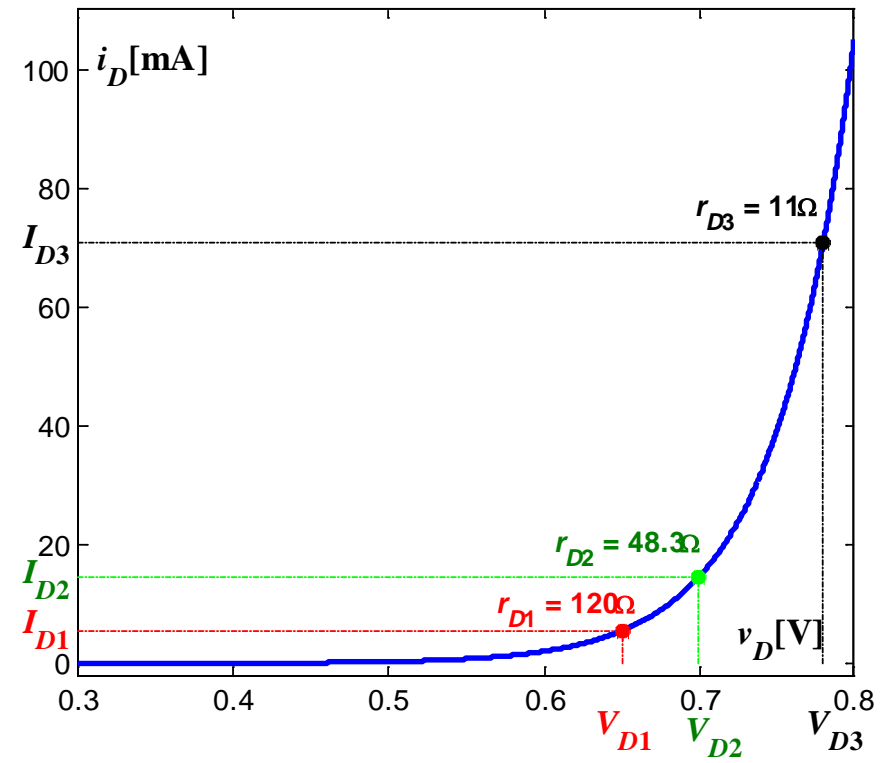
$$Q_3(0.78\text{V}; 70.8\text{mA}) \quad r_{D3} = \frac{0.78}{70.8} = 11\Omega$$



As the current increases, the diode goes in deeper conduction and its static resistance decreases.



OPTIONAL

➤ **Dynamic (small signal) parameters**

A small ac signal is superimposed on the dc quantities

$$V_D(t) = V_D + v_d(t)$$

$$i_D(t) = I_D + i_d(t)$$

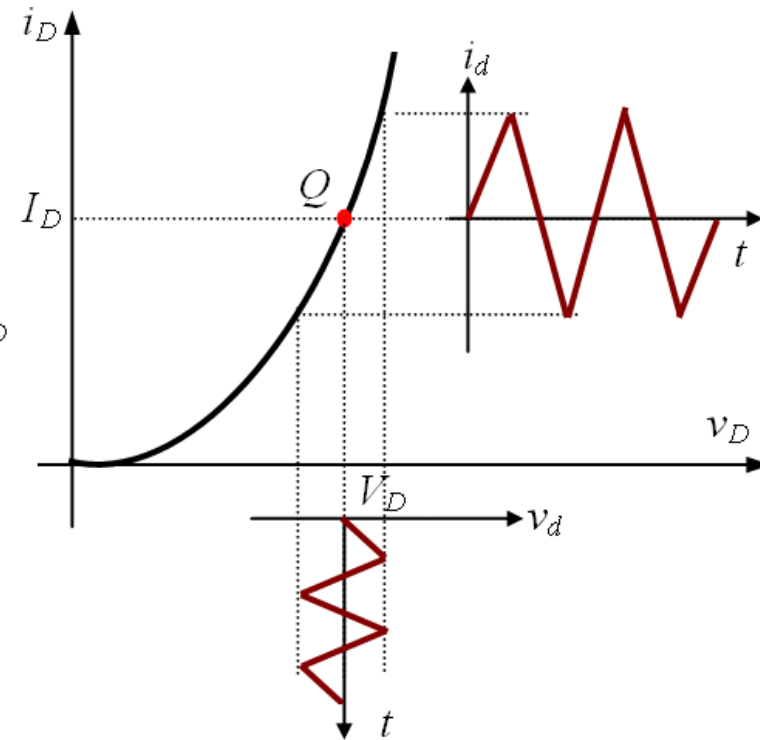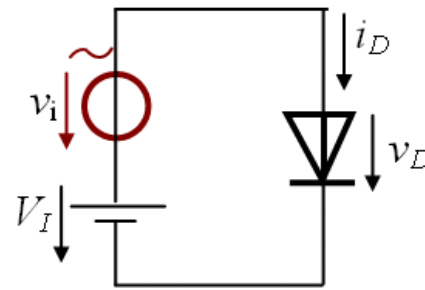

Dynamic (small signal) resistance:

$$r_d = \left. \frac{v_d}{i_d} \right|_Q \quad r_d = \left. \frac{\delta v_D}{\delta i_D} \right|_Q$$


Small signal approximation:

linear region around Q


$$r_d = \frac{nV_T}{I_D}$$

OPTIONAL


Interpretation of r_D and r_d

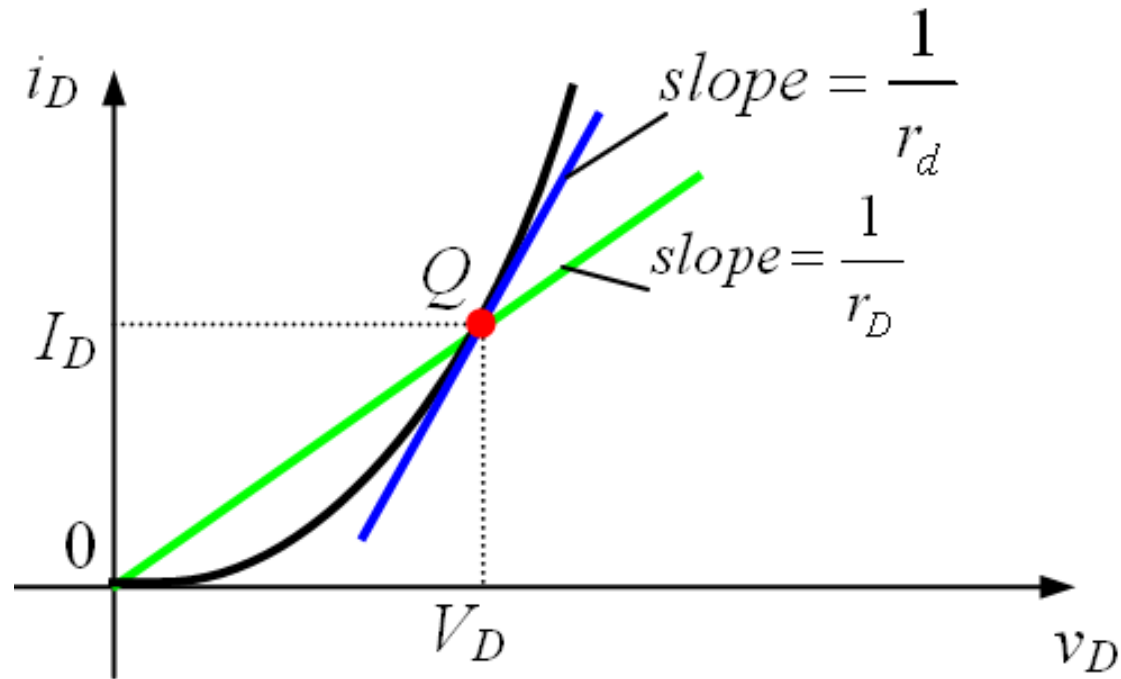

D modelling in the OP

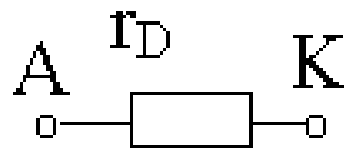


direct current

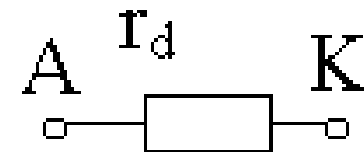



small signal variation

OPTIONAL

Example

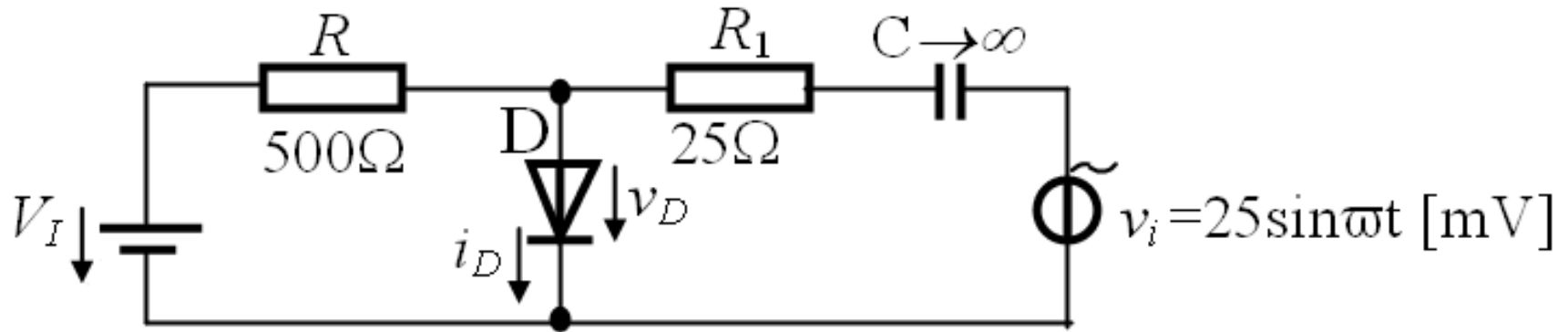

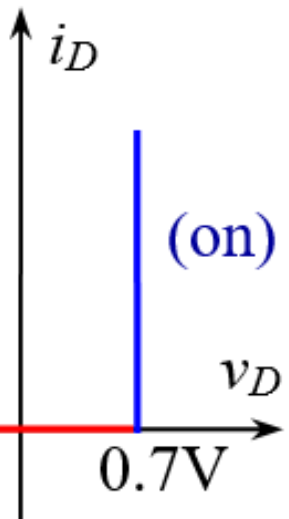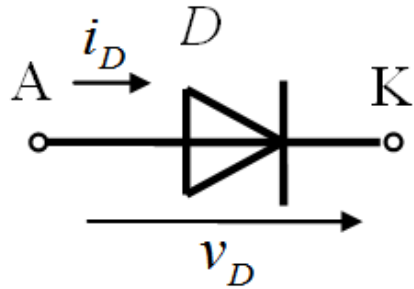- a) Draw the dc equivalent circuit.
- b) Assuming $Q(0,64V; 4,7mA)$, what is the value of the static resistance?
- c) Draw the small-signal equivalent circuit.
- d) What is the value of the small-signal resistance in Q ?



$v_D < 0.7 \text{ V}$

$D - \text{(off)}$


$\left\{ \begin{array}{l} v_D < 0.7 \text{ V} \\ i_D = 0 \end{array} \right.$

$v_D > 0.7 \text{ V}$

$D - \text{(on)}$

$\left\{ \begin{array}{l} v_D = 0.7 \text{ V} \\ i_D > 0 \end{array} \right.$

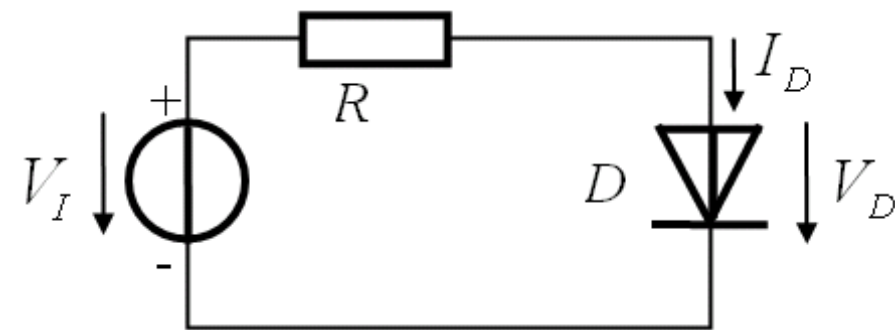- Circuit with a dc voltage source and a resistor



Compute $Q(V_D, I_D)$

Diode equation: $I_D = I_S e^{\frac{V_D}{nV_T}}$

KVL: $V_I = I_D R + V_D$


$$\left. \begin{array}{l} \text{Diode equation: } I_D = I_S e^{\frac{V_D}{nV_T}} \\ \text{KVL: } V_I = I_D R + V_D \end{array} \right\} \Rightarrow V_I - V_D = R I_S e^{\frac{V_D}{nV_T}}$$

Transcendental equation

Two solving methods:


1. Graphical method
2. Numerical method (successive approximation)

➤ Graphical method

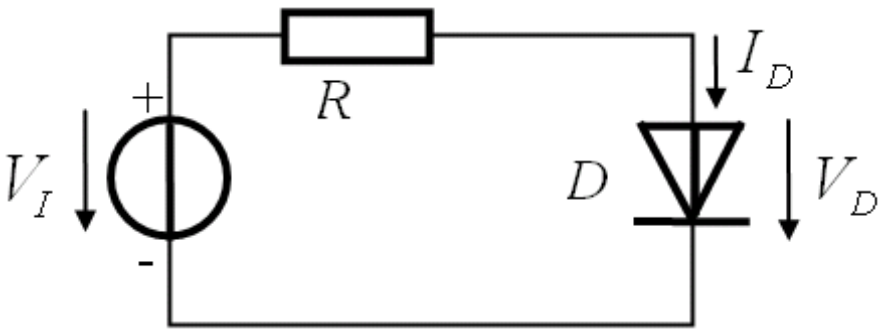


Diode equation: $I_D = I_S e^{\frac{V_D}{nV_T}}$

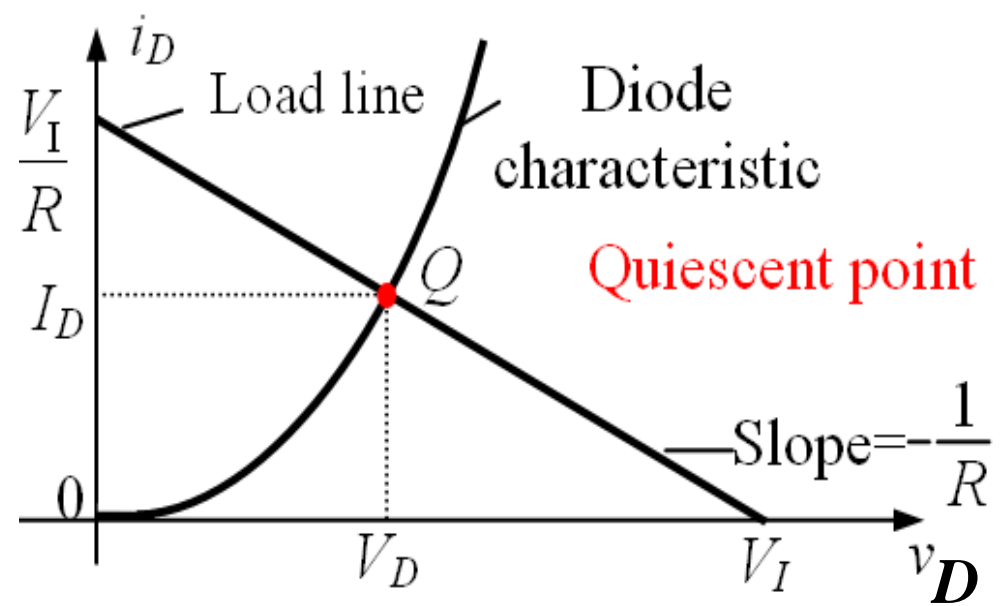KVL (load line equation): $V_I = I_D R + V_D$




➤ Graphical method

Effect of R on the quiescent point, Q

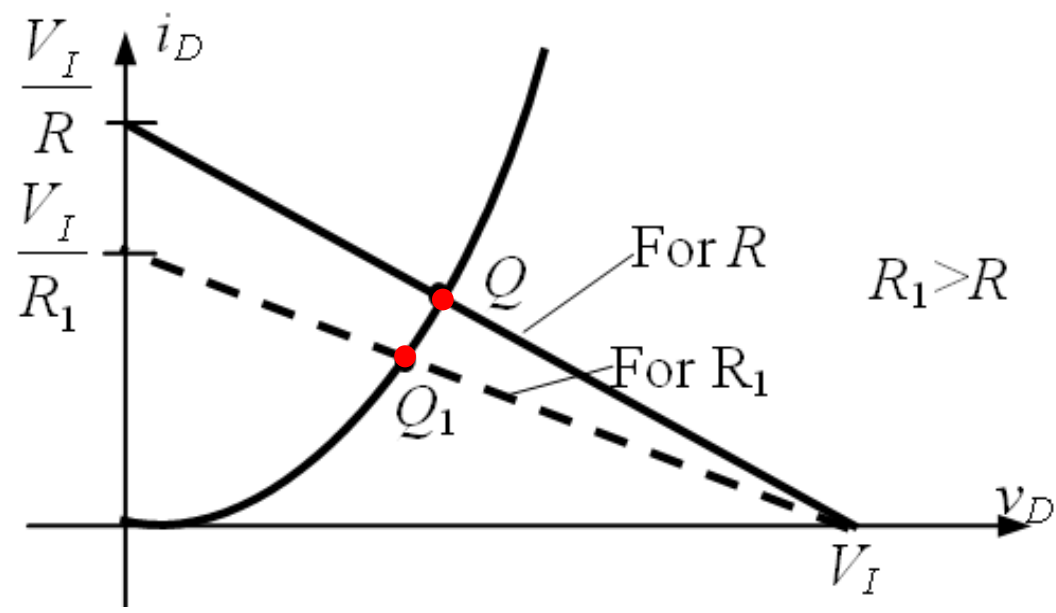

➤ Numerical method - simplified

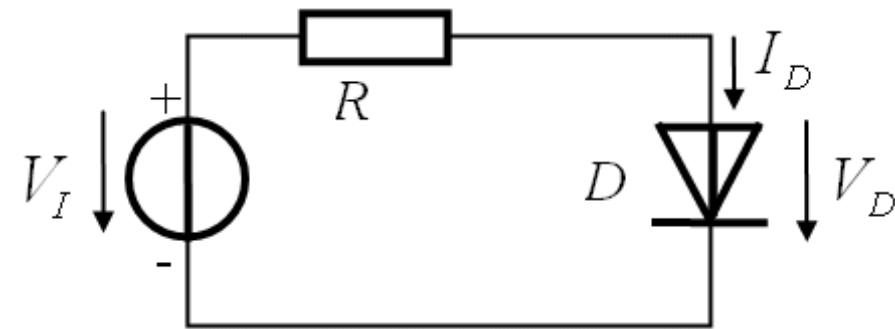


Assume the voltage drop across the diode $V_D = 0.7 \text{ V}$ and **compute** the current I_D using the load line equation

$$V_D = 0.7V$$

$$I_D = \frac{V_I - V_D}{R}$$

Example

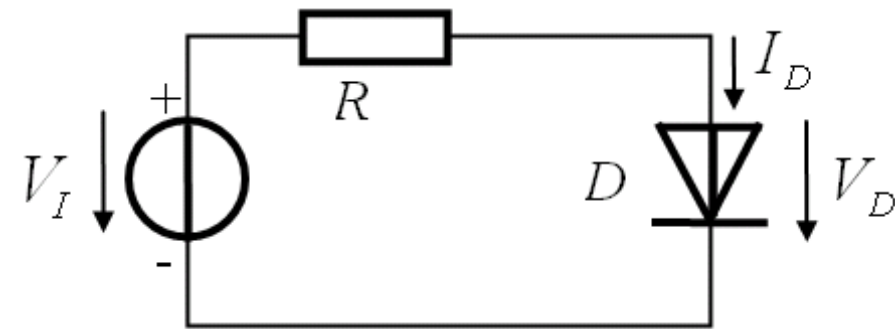

$$V_I = 9 \text{ V}, \quad R = 0.5 \text{ k}\Omega$$

What is the operating (quiescent) point Q of the diode D ?

$$V_D > 0.6 \text{ V} \quad D - (\text{on})$$

Assume $V_D = 0.7 \text{ V}$ across the conducting diode

$$I_D = \frac{V_I - V_D}{R} \quad I_D = \frac{9 - 0.7}{0.5} = 16.6 \text{ mA}$$

$$Q(0.7 \text{ V}, 16.6 \text{ mA})$$

OPTIONAL

➤ Numerical method - iterative

1. Consider an **initial value** of diode voltage, eg. $V_D^{(0)} = 0.7 \text{ V}$ and compute current $I_D^{(0)}$ using the load line equation

$(V_D^{(0)}, I_D^{(0)})$ – **initial solution**

2. Using $I_D^{(0)}$, compute voltage $V_D^{(1)}$ from diode equation, then current $I_D^{(1)}$ from the load line equation

$(V_D^{(1)}, I_D^{(1)})$ – **solution after first iteration**


Repeat step **2** if more accurate values are required.

For quick, first order analysis of the circuit,

the **initial solution** is considered!

OPTIONAL

Example

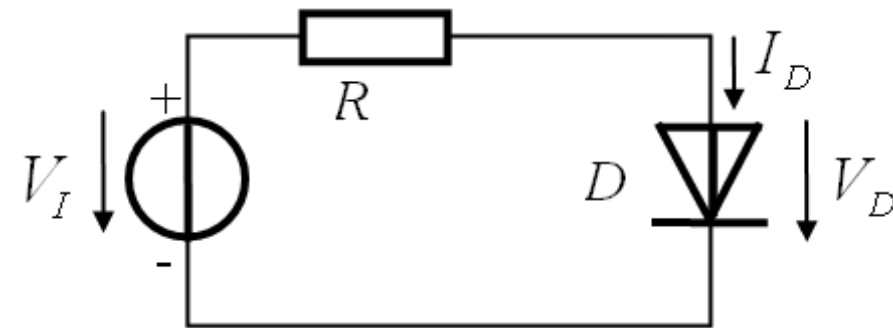

$$V_I = 3 \text{ V}, \quad R = 0.5 \text{ k}\Omega,$$

$$D \text{ is } 1\text{N}400\text{x}, \quad I_S = 14 \text{ nA}, \quad n = 2.$$

What is the operating (quiescent) point Q of diode D ?

Quick, first order analysis:

$$V_D > 0.6 \text{ V} \quad D - (\text{on})$$

Assume $V_D = 0.7 \text{ V}$ across the conducting diode

$$I_D = \frac{V_I - V_D}{R} \quad I_D = \frac{3 - 0.7}{0.5} = 4.6 \text{ mA} \quad Q(0.7 \text{ V}, 4.6 \text{ mA})$$

OPTIONAL

Example

Detailed analysis

$$I_D = \frac{V_I - V_D}{R} \quad I_D = I_S e^{\frac{V_D}{nV_T}} \quad V_D = nV_T \ln \frac{I_D}{I_S}$$

Step 1 $V_D^{(0)} = 0.7\text{V}$ $I_D^{(0)} = \frac{3 - 0.7}{0.5} = 4.6\text{mA}$

Step 2 $V_D^{(1)} = n \cdot V_T \cdot \ln \frac{I_D^{(0)}}{I_S} = 2 \cdot 0.025 \cdot \ln \frac{4.6\text{mA}}{14\text{nA}} = 0.635\text{V}$

$$I_D^{(1)} = \frac{V_I - V_D^{(1)}}{R} = \frac{3 - 0.635}{0.5} = 4.73\text{mA}$$

Step 3 $V_D^{(2)} = n \cdot V_T \cdot \ln \frac{I_D^{(1)}}{I_S} = 2 \cdot 0.025 \cdot \ln \frac{4.73\text{mA}}{14\text{nA}} = 0.637\text{V}$

$$I_D^{(2)} = \frac{V_I - V_D^{(2)}}{R} = \frac{3 - 0.637}{0.5} = 4.726\text{mA}$$

$$Q(0.637\text{V}; 4.726\text{mA})$$

Summary

Our first encounter with the diode revealed details regarding:

- Physical structure. Symbol.
- Current-voltage characteristic
- Operating regions
- Operating (quiescent) point
- Parameters of the diode
- Constant voltage drop model
- Analysis of two-port DR networks

Next week: DR switching circuits.