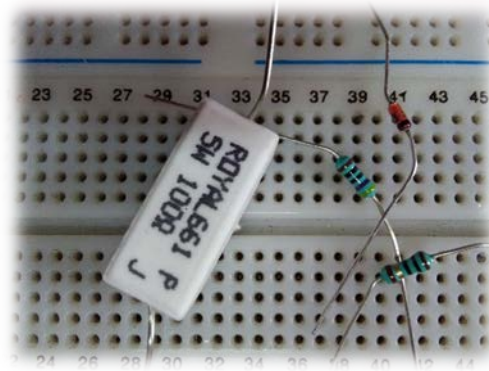





# ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

## C3 – DR switching circuits



Previously on ED (C2):

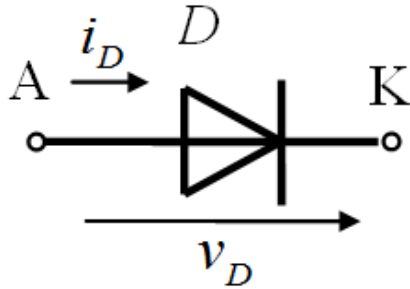

Exponential model

$$i_D \cong I_S e^{\frac{v_D}{nV_T}}$$

Constant voltage drop model

$v_D < 0.7 \text{ V}$

**D – (off)**

$v_D < 0.7 \text{ V}$

$$\begin{cases} v_D < 0.7 \text{ V} \\ i_D = 0 \end{cases}$$

$v_D > 0.7 \text{ V}$


**D – (on)**

$i_D > 0$

$$\begin{cases} v_D = 0.7 \text{ V} \\ i_D > 0 \end{cases}$$
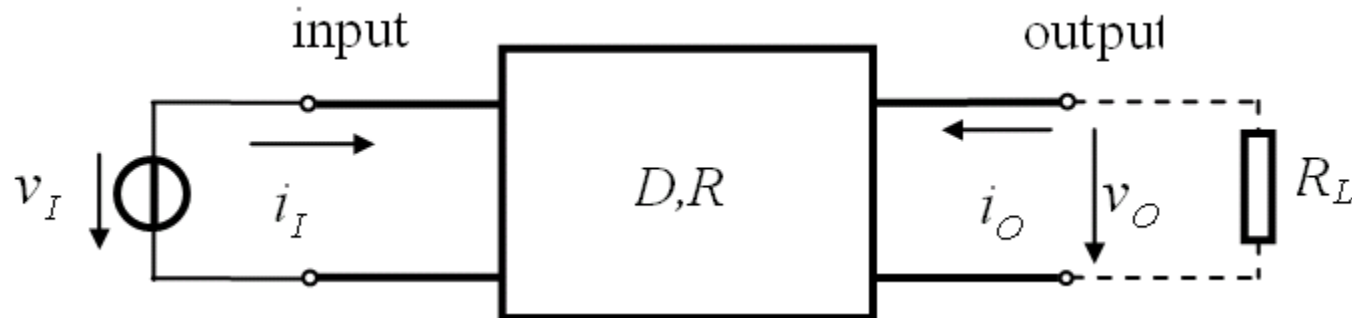
# Contents

- Two-port DR networks. DR switching circuits.
- Voltage transfer characteristic (VTC)
- Two-port DR networks analysis
- Applications of two-port DR networks
  - Half-wave rectifier
  - Pulses selector
  - Voltage limiter
  - Maximum multi-port networks
  - Minimum multi-port networks




**Two-port** network = circuit w/ two ports – input, output

Two-port **DR** network = DR circuit w/ two ports – input, output

**Switching** two-port DR network = DR circuit w/ two ports,  $D$  – (on), (off)

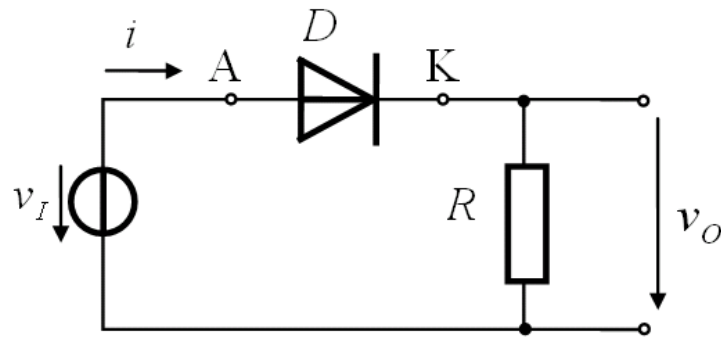The **analysis** of switching two-port DR networks works with the **constant voltage drop model** of the diode.




Voltage transfer characteristic (VTC)

graphical illustration of  $v_O(v_I)$

Steps for deducing the VTC:

- ❖ Take into account **all possible situations** that result from the combination of diode states (*on*, *off*)
- ❖ For each situation,
  - draw** the equivalent circuit
  - find**  $v_O$
  - determine** the range of  $v_I$
- ❖ **Plot** the VTC.

## Example

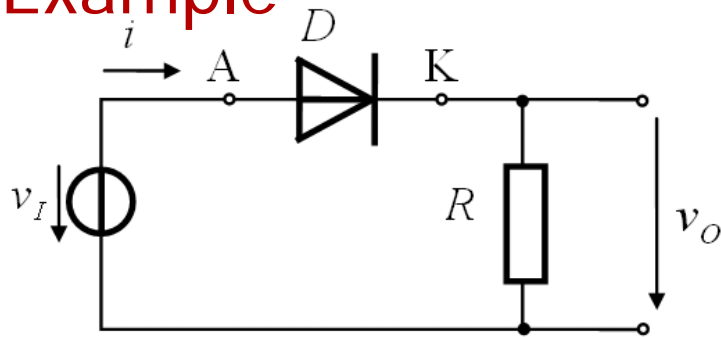

Deduce and plot VTC  $v_O(v_I)$


**Step 1.** Write down KVL and Ohm's law for the circuit (circuit's equations)

**Step 2.** Draw the equivalent circuits for D-(on) and D-(off)

**Step 3.** Find  $v_O$  and the range for  $v_I$  by replacing the diode's equations in the circuit's equations.

**Step 4.** Write down the complete expression of VTC  $v_O(v_I)$  and plot it, for D-(on) and D-(off).

## Example

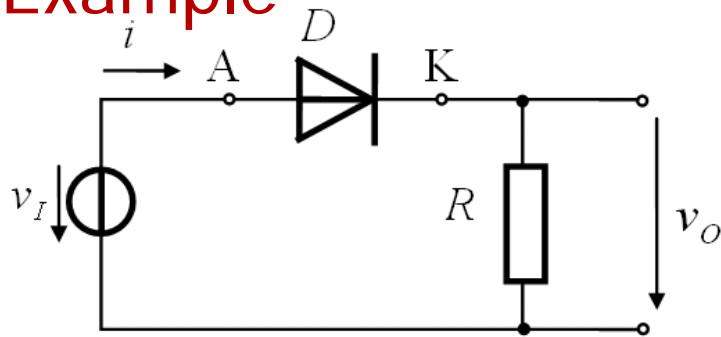


Deduce and plot VTC  $v_O(v_I)$

**Step 1.** Write down KVL and Ohm's law for the circuit (circuit's equations)

$$\begin{aligned} -v_I + v_D + v_O &= 0 \\ v_O &= i_D R \end{aligned}$$

**! Always valid, regardless of the state of the diode!**


### Example

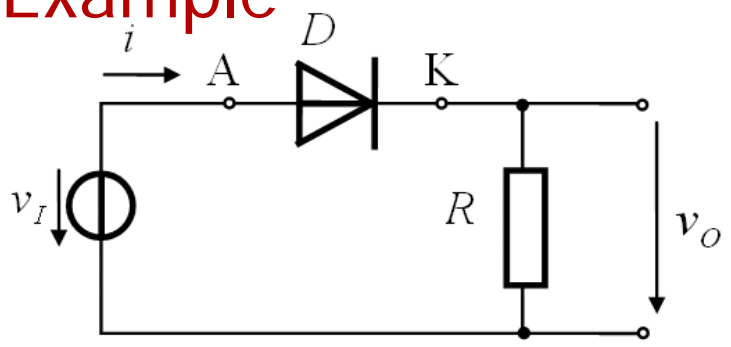


Deduce and plot VTC  $v_O(v_I)$

Step 2. Draw the equivalent circuits for D-(on) and D-(off)

#### D – (off)

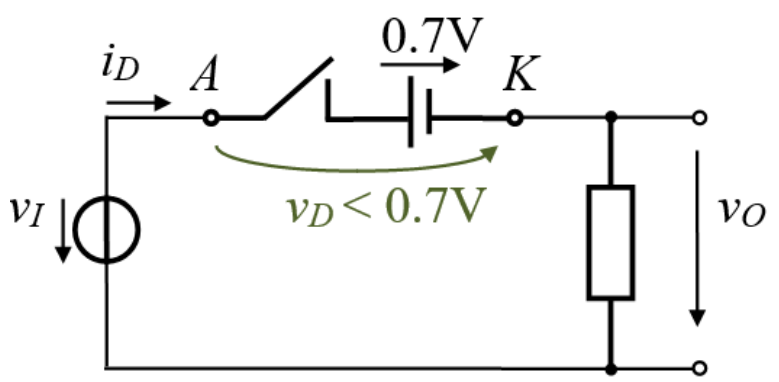


#### D – (on)

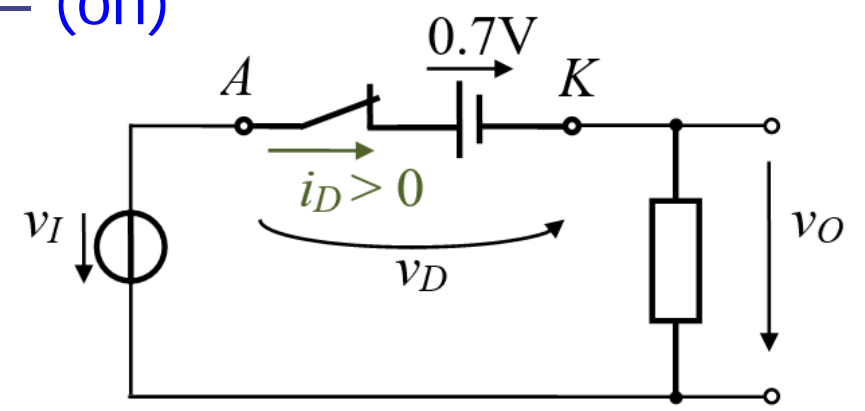



Example

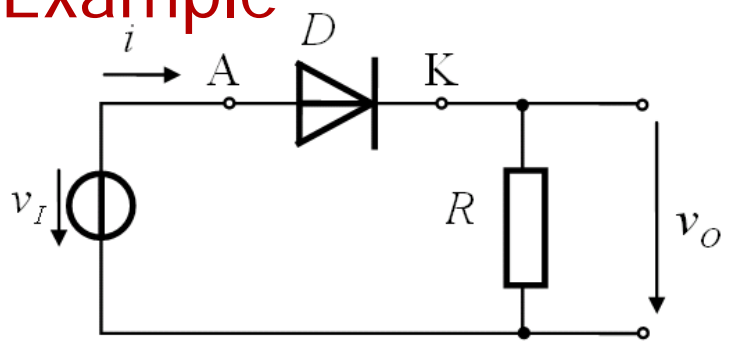

Deduce and plot VTC  $v_O(v_I)$


Step 3. Find  $v_O$  and the range for  $v_I$  by replacing the diode's equations in the circuit's equations.

$$-v_I + v_D + v_O = 0$$

$$v_O = i_D R$$

$D - \text{(off)}$
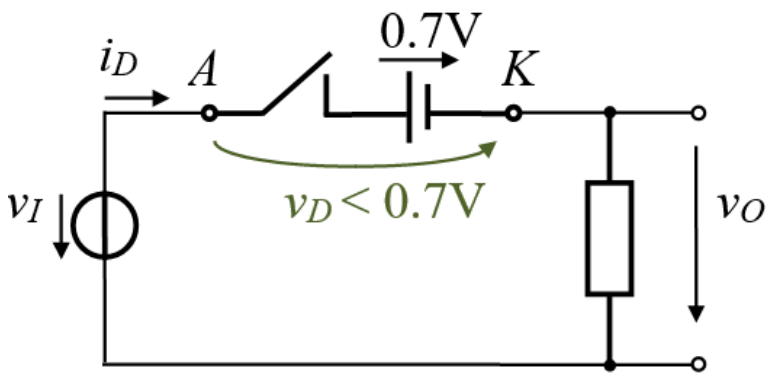
$$\begin{cases} v_D < 0.7V \\ i_D = 0A \end{cases}$$



$$v_O = i_D R = 0$$

$$v_O = 0$$

$$v_D = v_I - v_O$$


$$v_D < 0.7$$

$$v_I - v_O < 0.7$$

$$v_I - 0 < 0.7$$

$$v_I < 0.7V$$

Example

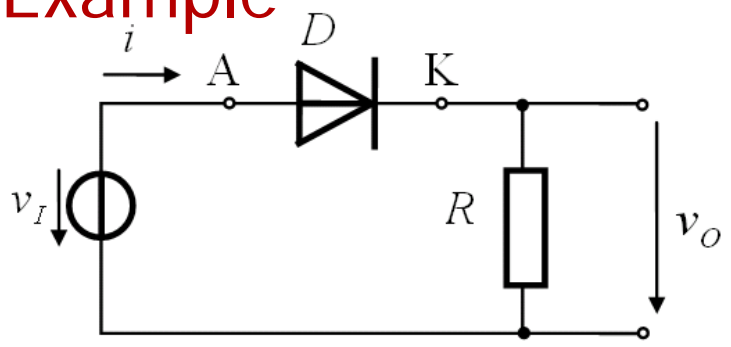

Deduce and plot VTC  $v_O(v_I)$


Step 3. Find  $v_O$  and the range for  $v_I$  by replacing the diode's equations in the circuit's equations.

$$-v_I + v_D + v_O = 0$$

$$v_O = i_D R$$

$D - (\text{on})$
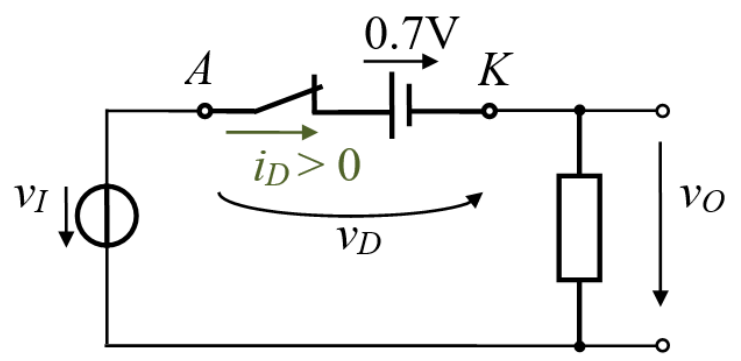
$$\begin{cases} v_D = 0.7V \\ i_D > 0A \end{cases}$$



$$-v_I + 0.7 + v_O = 0$$

$$v_O = v_I - 0.7$$


$$i_D = \frac{v_O}{R} \quad \frac{v_O}{R} > 0$$

$$v_O > 0$$

$$v_I - 0.7 > 0$$

$$v_I > 0.7V$$


### Example

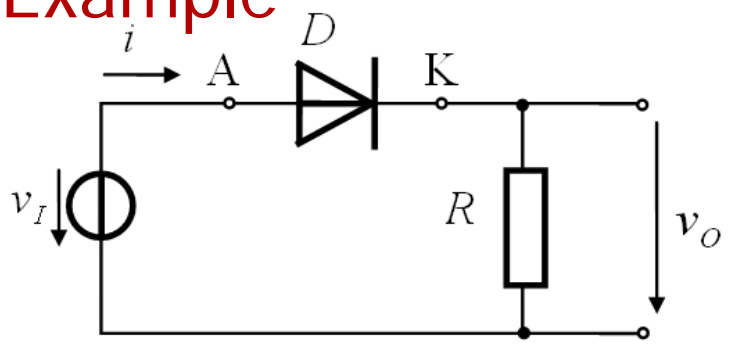

Deduce and plot VTC  $v_O (v_I)$


**Step 4.** Write down the complete expression of VTC  $v_O (v_I)$  and plot it, for D-(on) and D-(off).
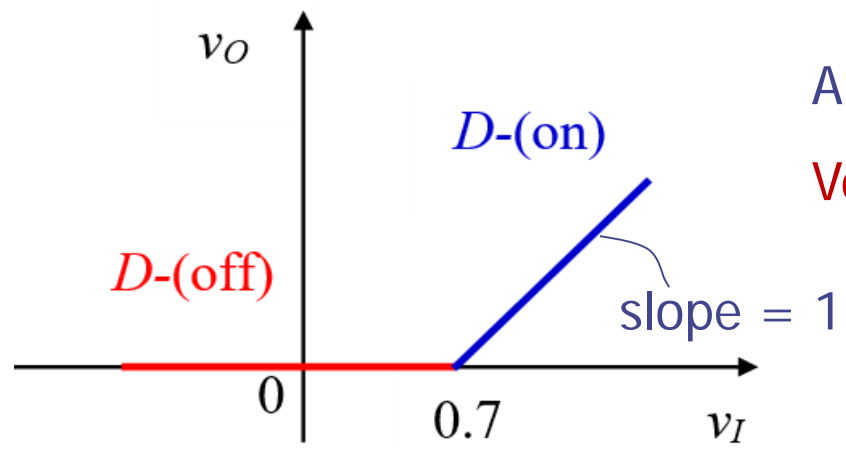
$$v_O = \begin{cases} 0, & v_I < 0.7V \\ v_I - 0.7V, & v_I > 0.7V \end{cases}$$





Application:  
**Voltage rectifier**

## Example




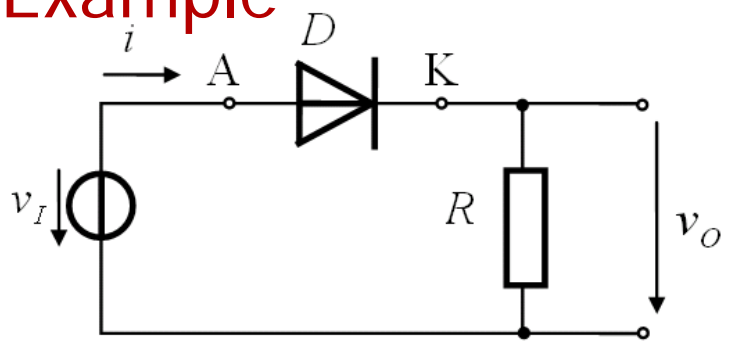


$$v_O = \begin{cases} 0, & v_I < 0.7\text{V} \\ v_I - 0.7\text{V}, & v_I > 0.7\text{V} \end{cases}$$

## Waveforms

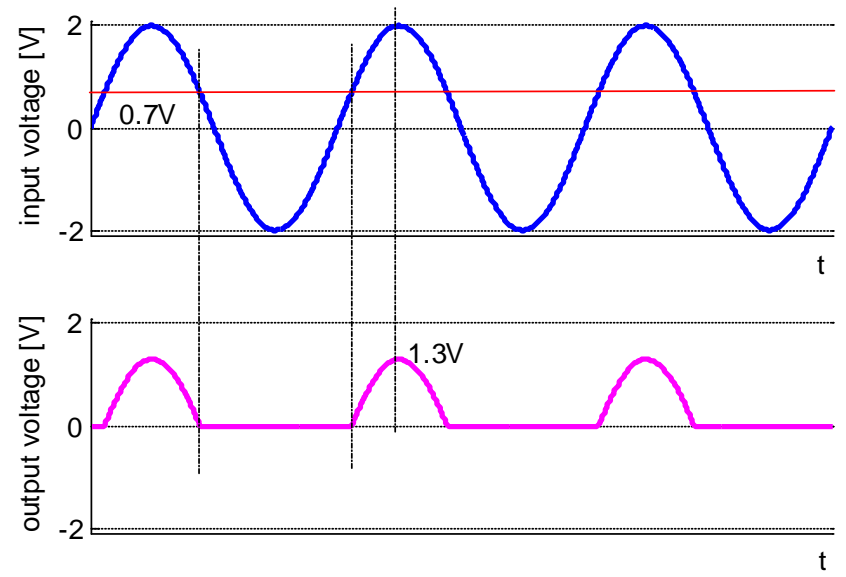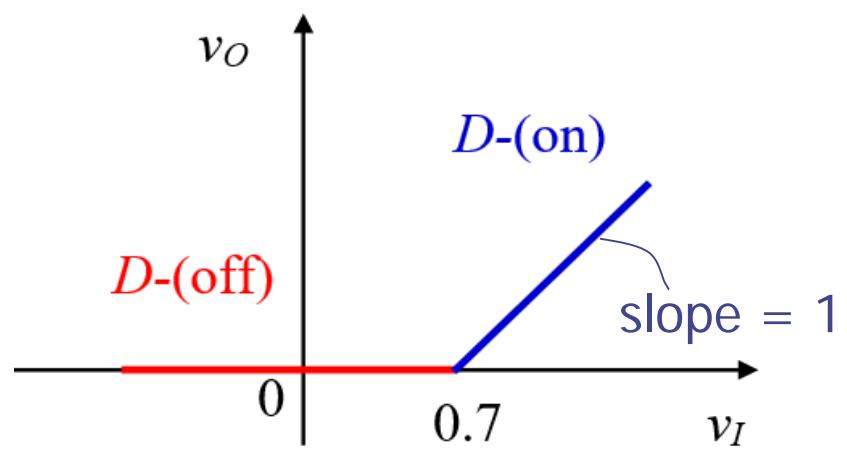


## Influence of $V_{Th}$ and $V_{D,on}$

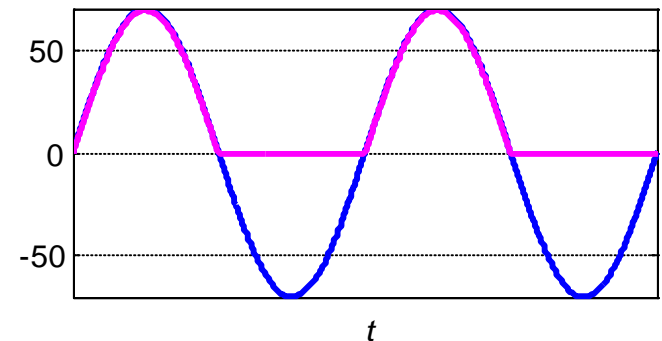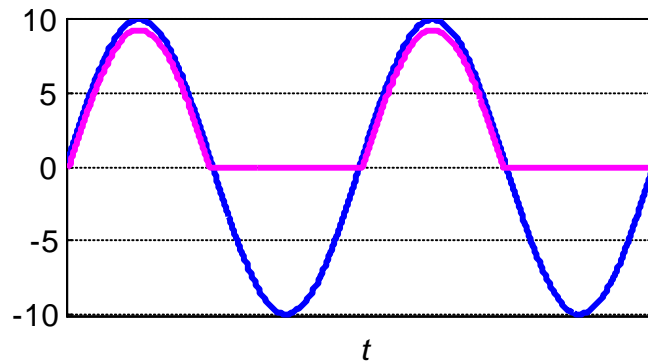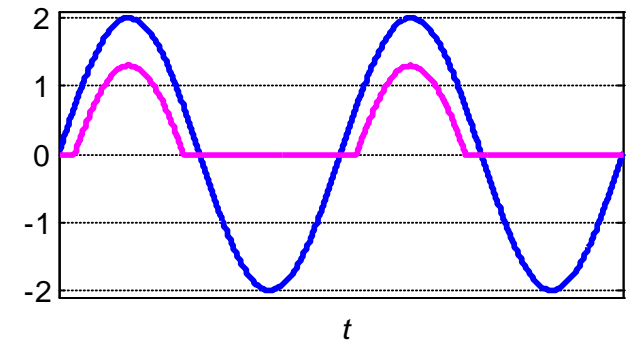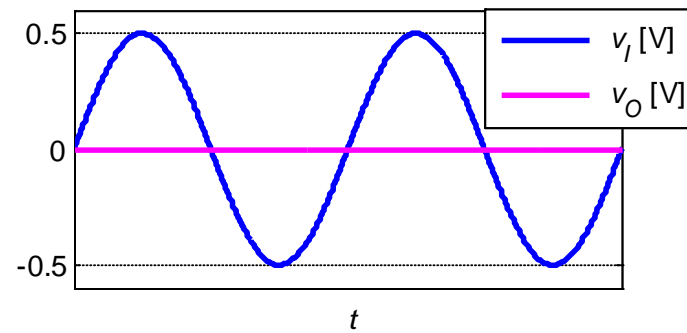

If the input voltage is large enough ( $\gg 0.7$  V)

- $V_{Th}$  can be considered 0 V
- $V_{D,on}$  can be neglected, meaning that for  $D - (on)$ ,  $v_O = v_I$

## Example

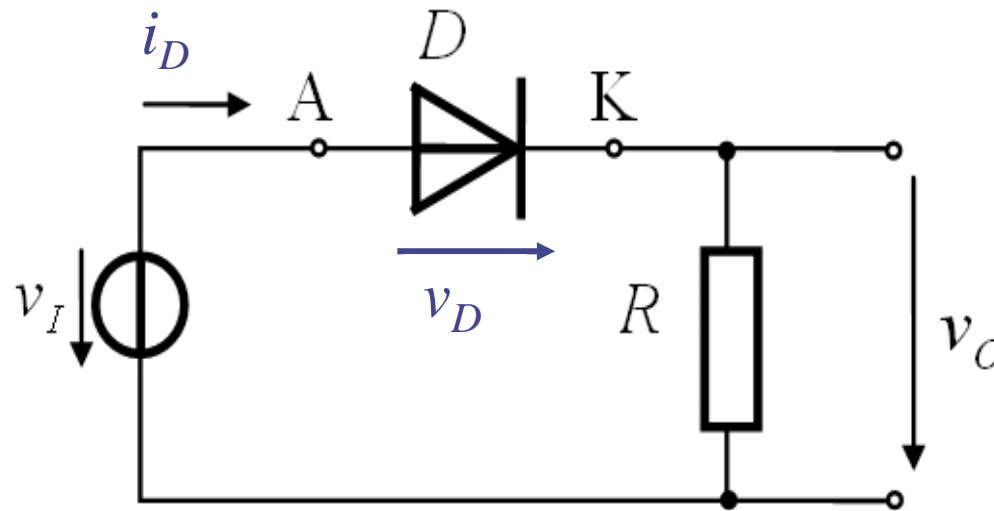


- How does the output voltage look like if the input is a sine wave, 3 V amplitude and 2 V offset?
- What is the peak forward current through diode for  $R = 2 \text{ k}\Omega$ ?
- What is the peak reverse voltage  $V_{DR}$  across  $D$  ( $V_{DR} = -v_D$ )?
- Repeat a) and b) if the offset of the input voltage becomes -4 V.
- Repeat the above points, assuming the diode is reversed in the circuit.

## Other series connections



- Reverse the diode
- Change the places of D and R (output voltage collected from D)

*!Forbidden connection!*

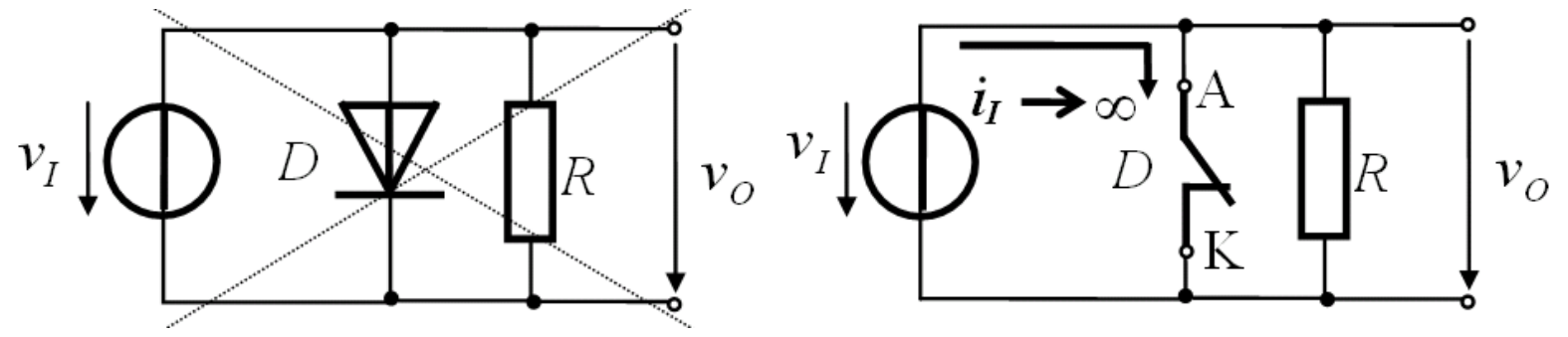

Never connect a voltage source so that during normal operation, the source can be short-circuited.



# Loaded two-port networks

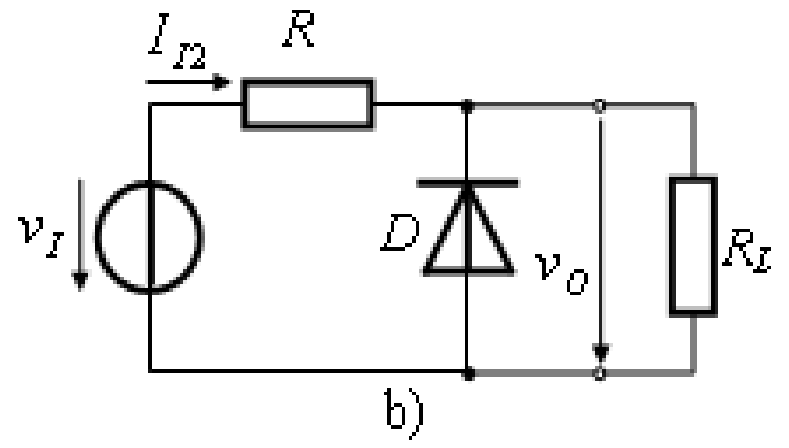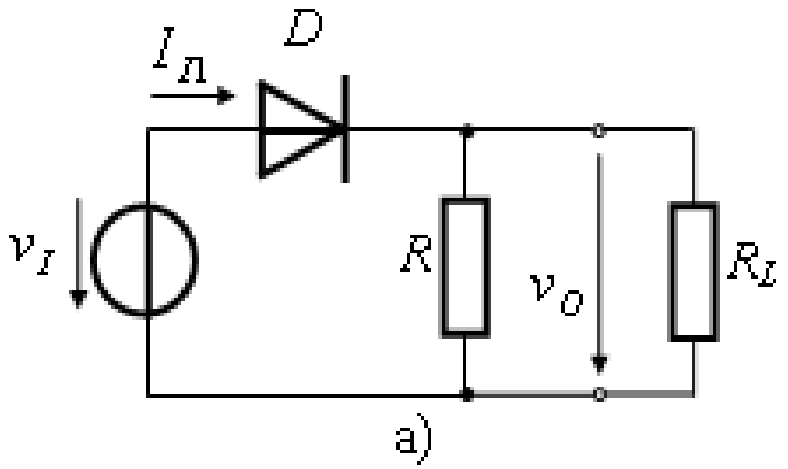



What are the effects of  $R_L$  on the VTC and on the output voltage?



➤ Half-wave rectifier

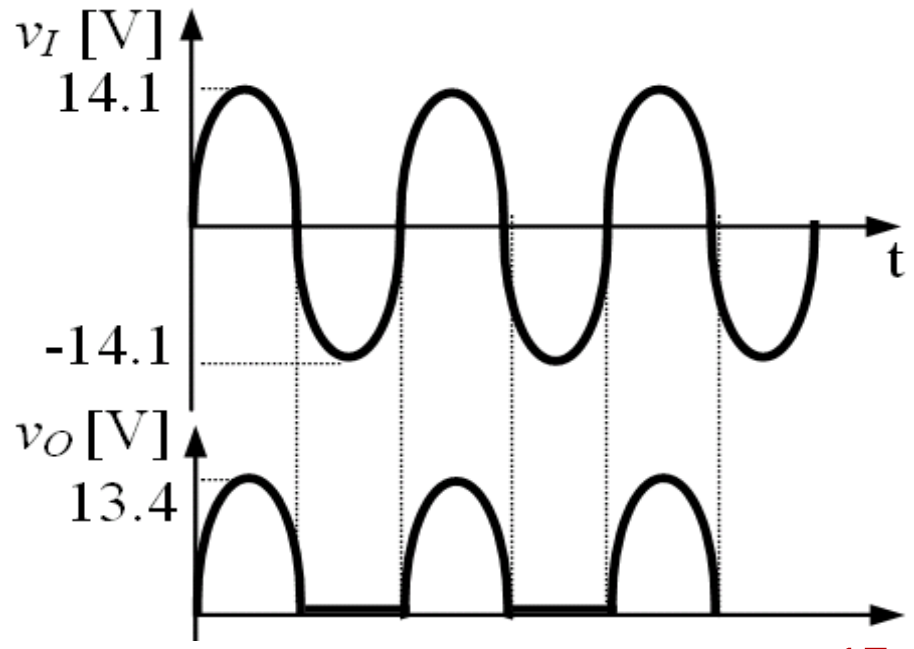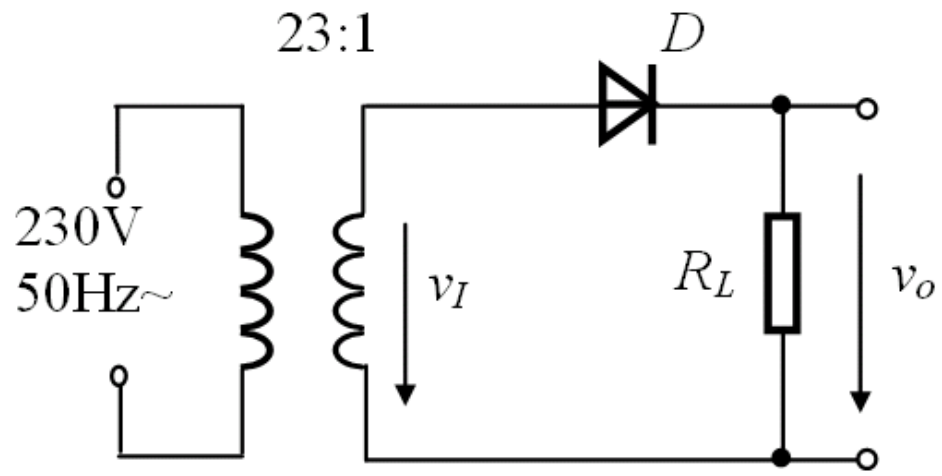


➤ Pulses selector

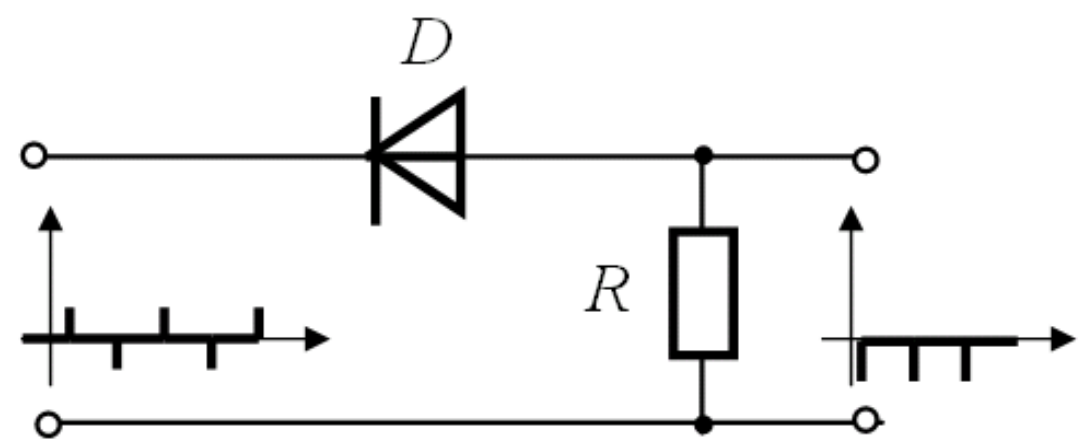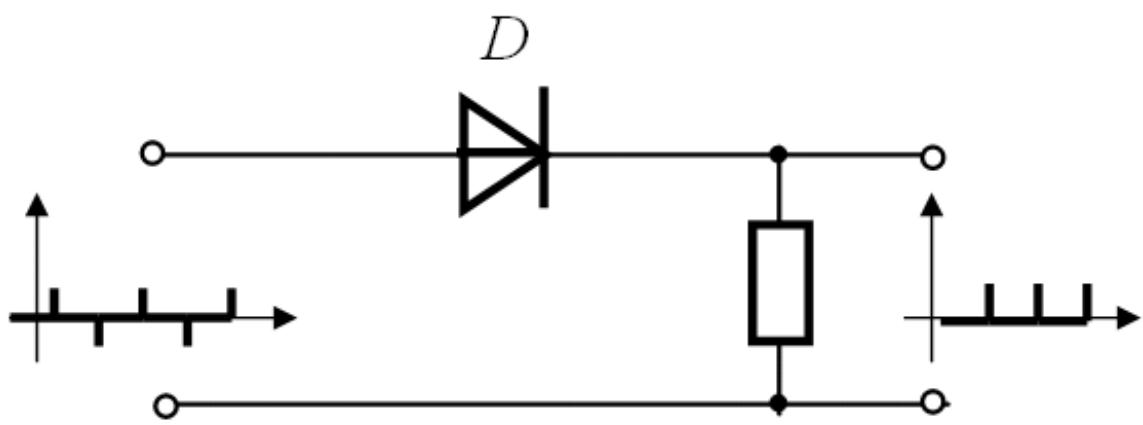



### ➤ Voltage limiters (clamp networks)

Reverse engineering:  
Use the waveforms to deduce and plot VTC  $v_O(v_I)$ .


simple

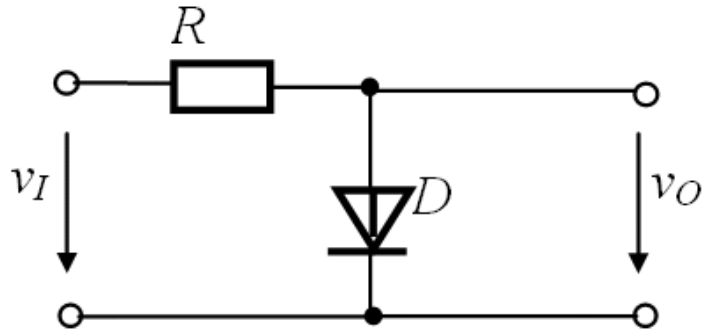

double

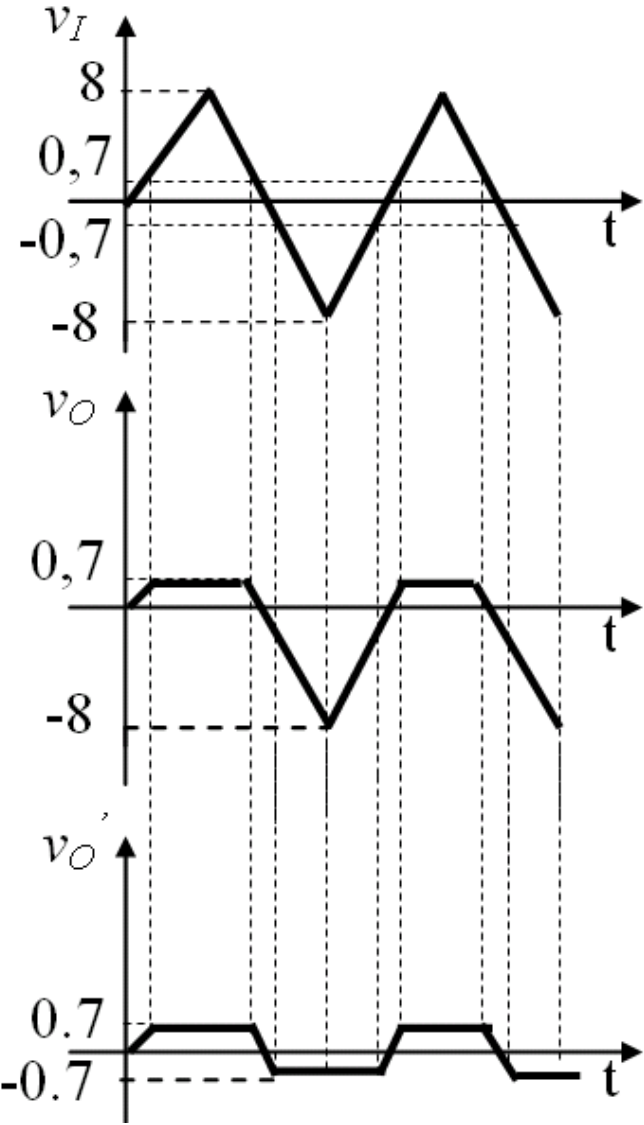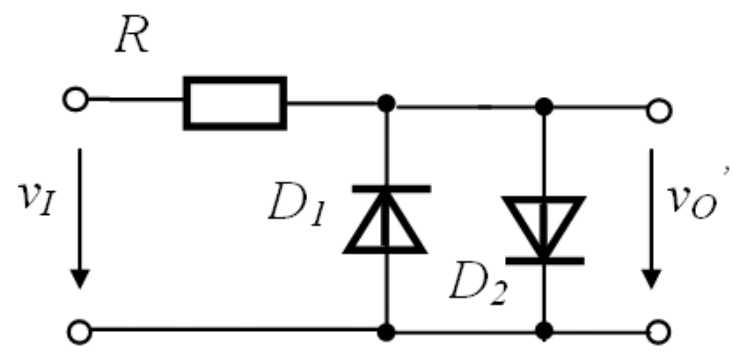

## ➤ Maximum multi-port networks

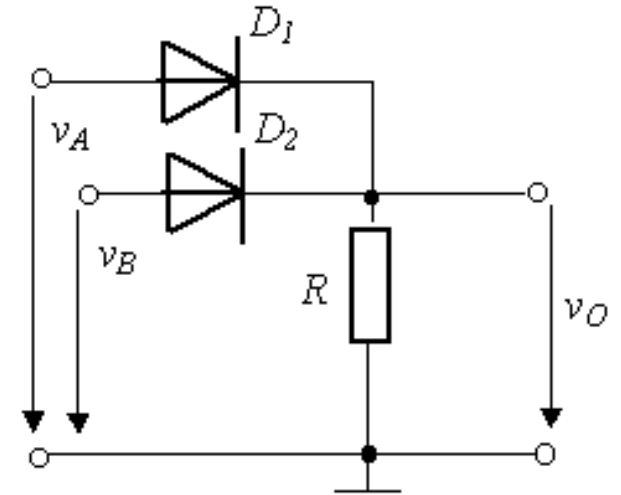


$$\begin{cases} v_A > v_B \\ v_A > 0.7\text{V} \end{cases} \quad D_1 - (\text{on}), D_2 - (\text{off}); \quad v_O = v_A - 0.7\text{V}$$

$$\begin{cases} v_B > v_A \\ v_B > 0.7\text{V} \end{cases} \quad D_1 - (\text{off}), D_2 - (\text{on}); \quad v_O = v_B - 0.7\text{V}$$

$$\begin{cases} v_A < 0.7\text{V} \\ v_B < 0.7\text{V} \end{cases} \quad D_1 - (\text{off}), D_2 - (\text{off}); \quad v_O = 0$$

$$v_O = \max(v_A - 0.7\text{V}; v_B - 0.7\text{V}; 0\text{V})$$


➤ Maximum multi-port networks

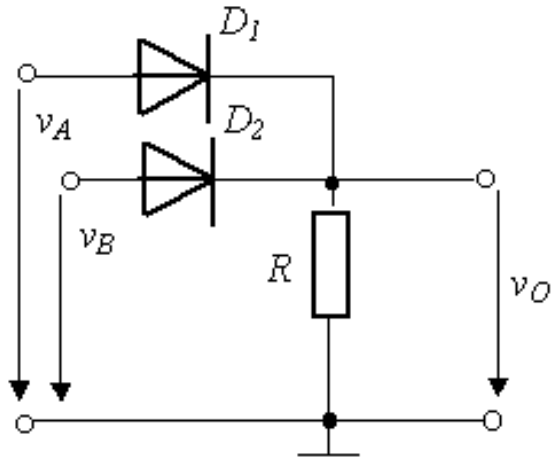


$v_O = \max(v_A - 0.7 \text{ V}; v_B - 0.7 \text{ V}; 0)$  -----

$v_O = \max(v_A; v_B; 0)$  neglecting 0.7 V —————

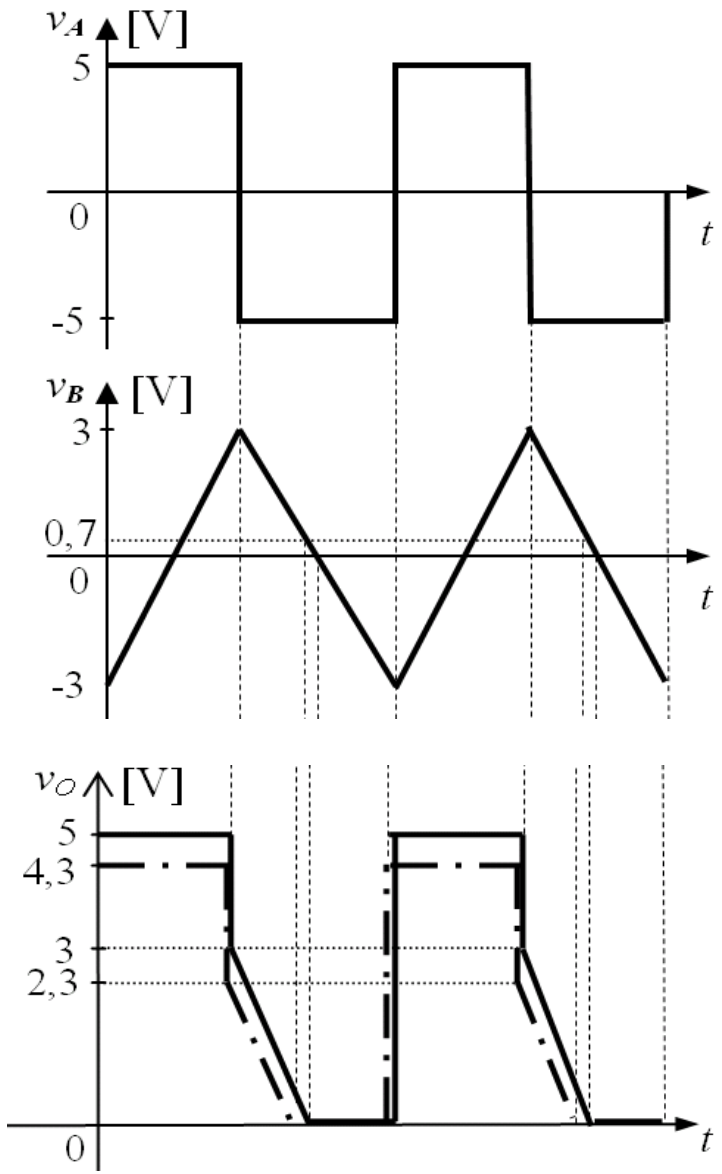- What is the peak value of the current through each circuit element if  $R=5 \text{ k}\Omega$ ?
- What is the range of values for  $R$ , if the peak forward current through each diode is 200 mA?




➤ Minimum multi-port networks

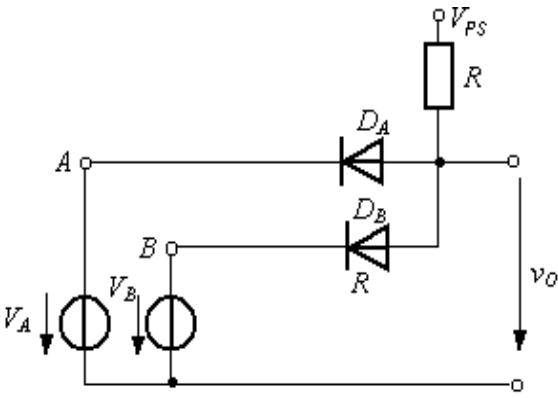


$$v_O = \min(v_A + 0.7 \text{ V}; v_B + 0.7 \text{ V}; V_{PS})$$

$$v_O = \min(v_A; v_B; V_{PS}) \text{ neglecting } 0.7 \text{ V}$$

- Plot  $v_O(t)$ .

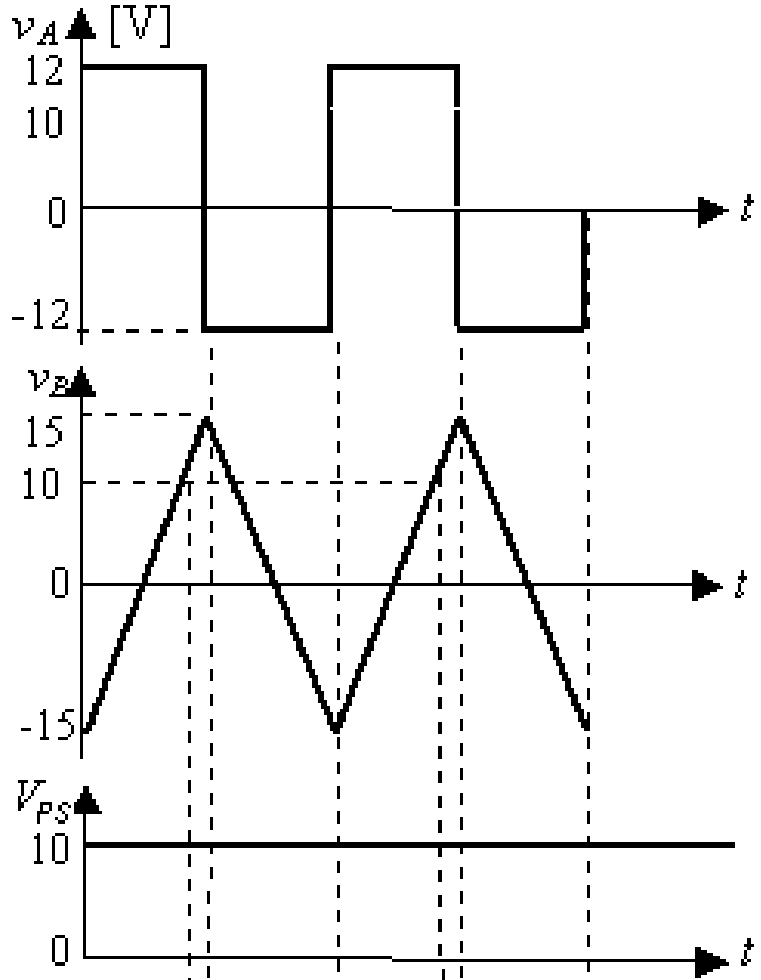

➤ Back-up supply from a 9 V battery

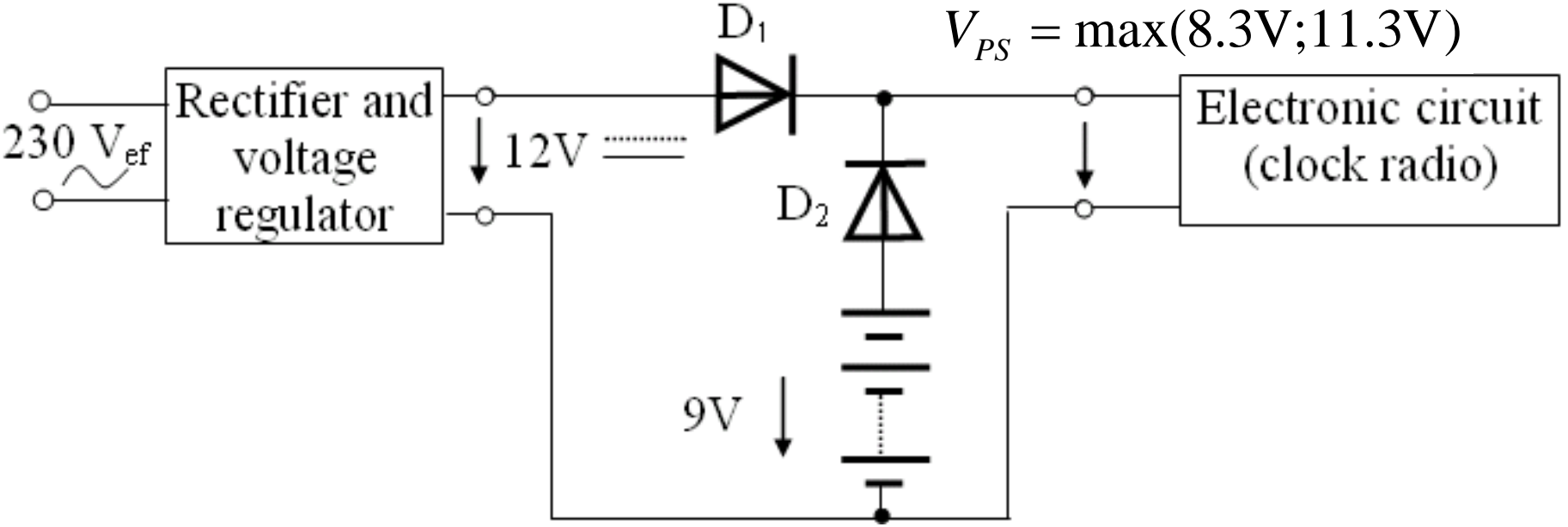

# Summary

Although the war is not over, today we won the battle against:

- Two-port DR networks. DR switching circuits.
- Voltage transfer characteristic (VTC)
- Two-port DR networks analysis
- Applications of two-port DR networks

Next week: Full-wave DR rectifiers. DC switching circuits. DRC rectifiers. LEDs.

## To do: Homework 1