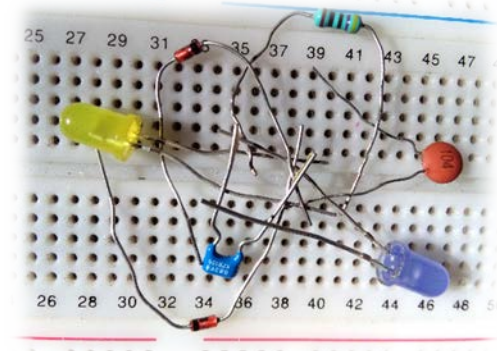




# ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.



**C4 – Full-wave DR rectifiers.  
DC switching circuits.  
DRC rectifiers. LEDs.**



# Contents

- Full-wave DR rectifiers
- Two-port DC networks
  - Positive/negative peak detector
  - Translation networks
  - Voltage doubler
- DRC rectifiers (power supply filtering)
- LEDs and photodiodes

➤ Full-wave rectifier – diode bridge

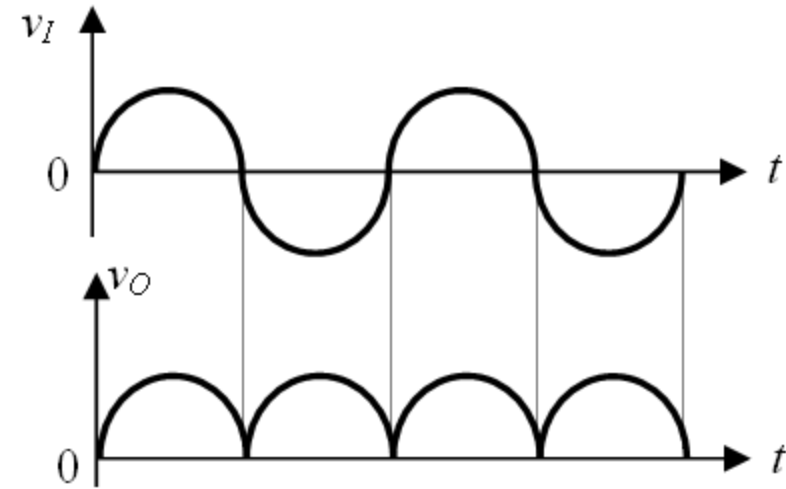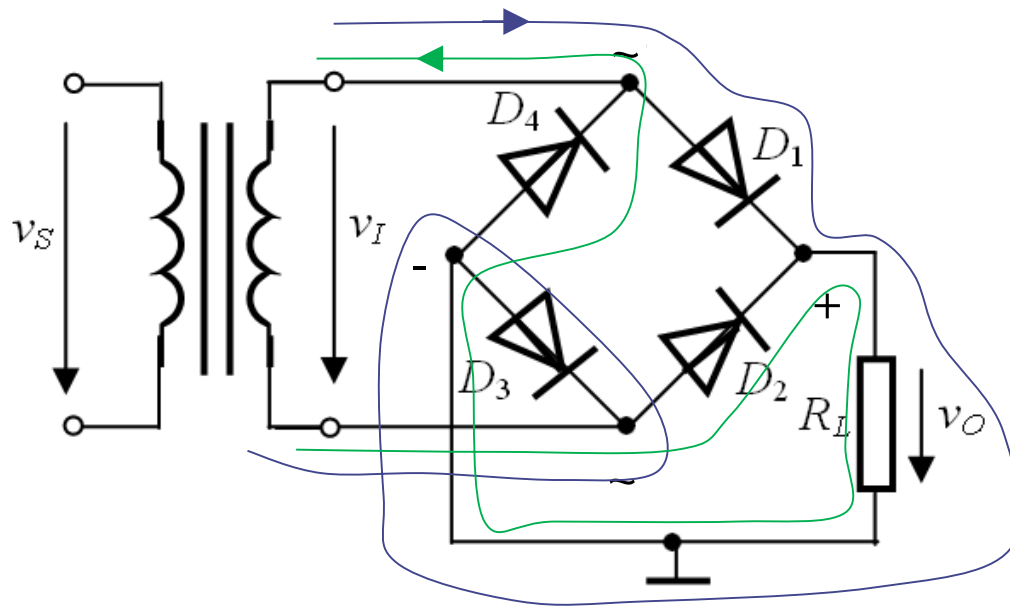


neglecting 0.7 V


➤ positive half,  $v_I > 0$   
 $D_1, D_3$  – (on)  $D_2, D_4$  – (off)

➤ negative half,  $v_I < 0$   
 $D_1, D_3$  – (off)  $D_2, D_4$  – (on)

➤ Full-wave rectifier – center-tapped transformer

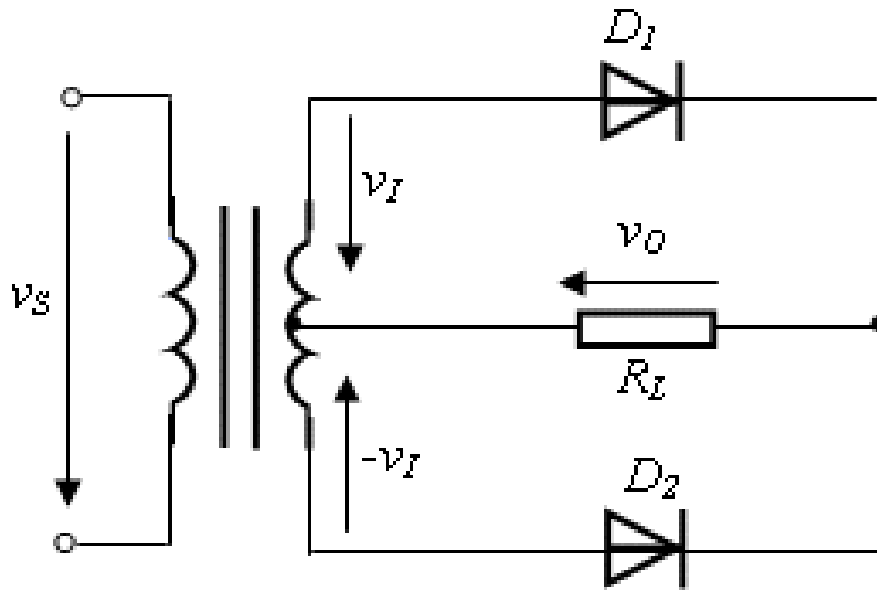


neglecting 0.7 V

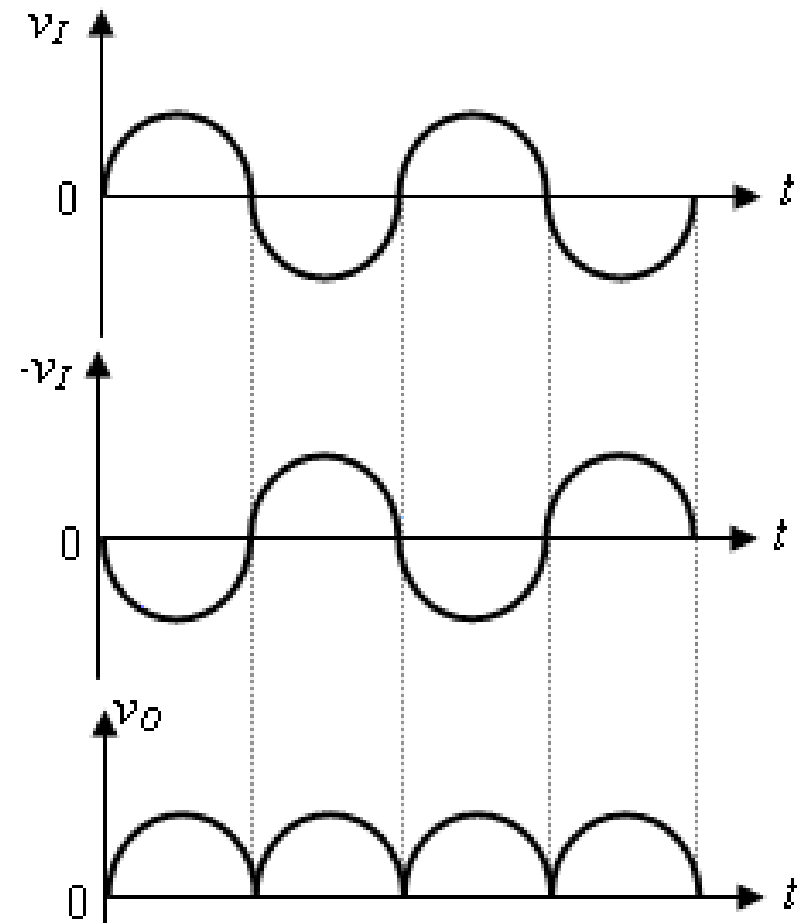

### Example

$$v_I(t) = \hat{V}_I \sin \omega t$$

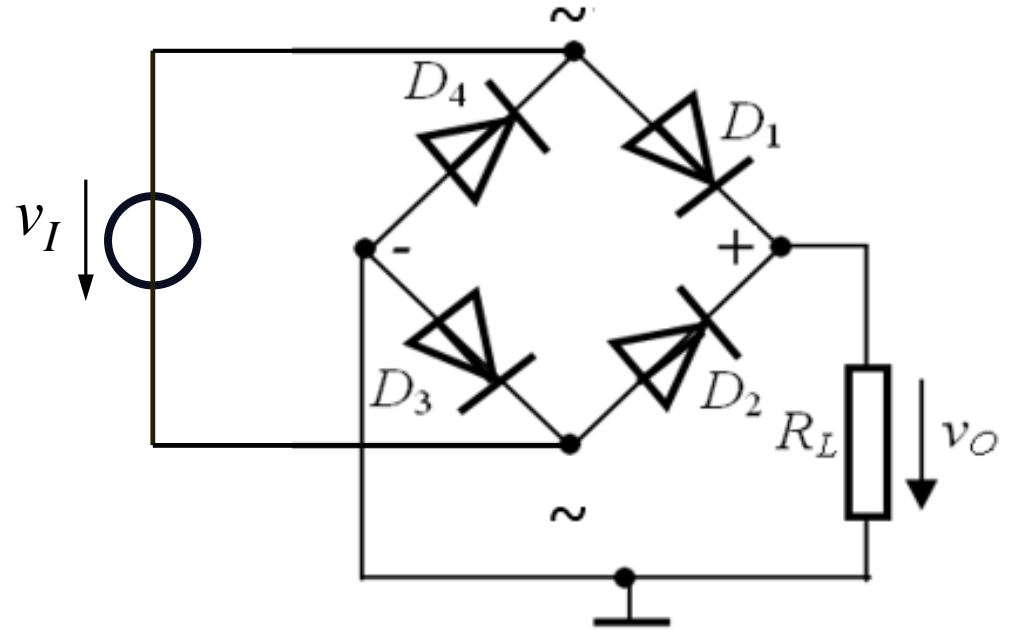


For the circuit in the figure,  $R_L=50\Omega$ . Assume  $\hat{V}_I = 7V$ .

- a) Plot  $v_o(t)$  and  $i_o(t)$
- b) Compute the values of the maximum reverse voltage  $V_{DR}$  across each diode and the maximum forward current through each diode.
- c) Repeat a) and b) assuming  $\hat{V}_I = 100V$ .
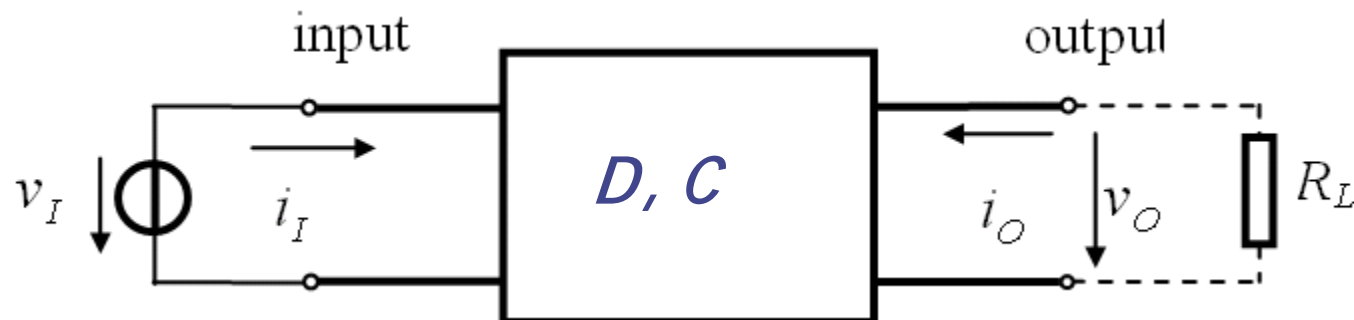
## Preamble


The steady-state properties (i.e. the **VTC**) of two-port DC networks **are of no interest** in applications.

The focus is on the **time-domain behavior** – how does  $v_O$  look for variable  $v_I$ ?



The **analysis** of switching two-port DC networks works with the **constant voltage drop model** of the diode.

➤ Temporal extreme two-port DC networks

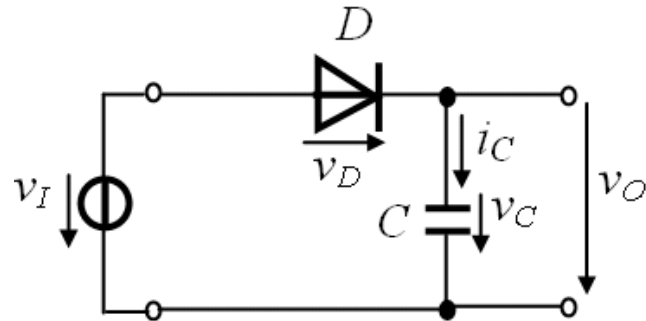

$$v_D(t) = v_I(t) - v_O(t)$$

$$v_O(t) = v_C(t)$$

Based on the states of the diodes, there are two possible cases:


1. If  $v_D$  tends to be  $> 0.7$  V,  $D$  – (on)

$v_D = 0.7$  V,  $i_C(t) > 0$ ,  $v_C(t)$  increases (C charges)

2. If  $v_D < 0.7$  V,  $D$  – (off)

$i_C(t) = 0$        $v_C(t) = \text{constant}$

➤ Temporal extreme two-port DC networks

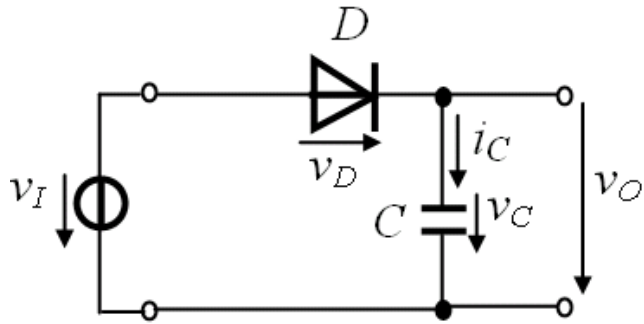


$$v_D(t) = v_I(t) - v_O(t)$$

$$v_O(t) = v_C(t)$$


Application:  
**Positive peak detector**

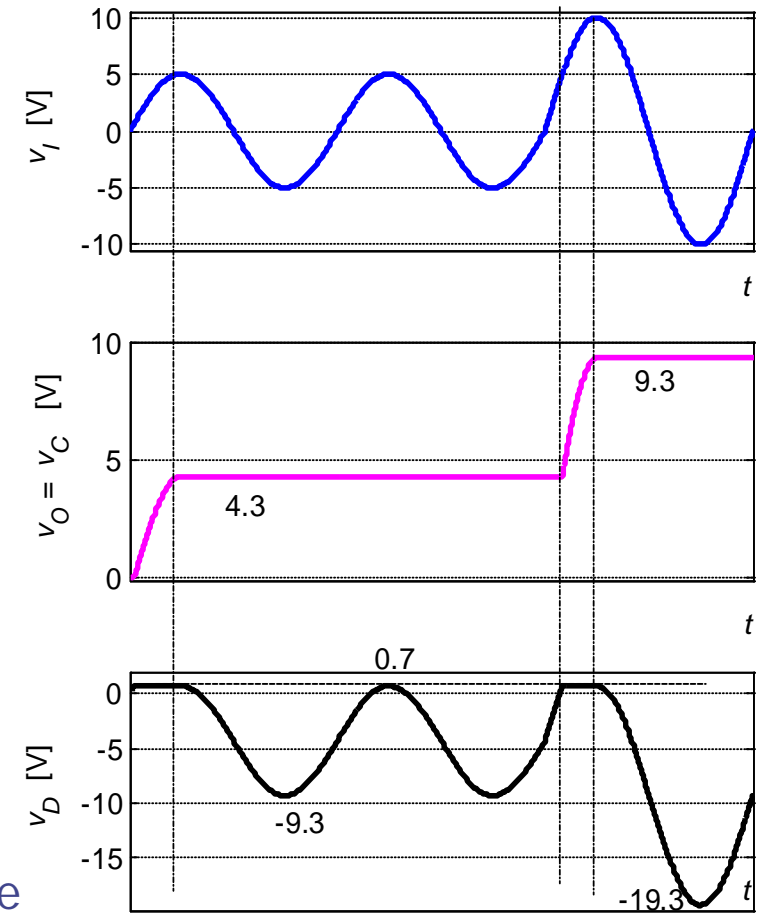- Plot  $v_O(t)$ ,  $v_D(t)$  if  $v_I(t)$  is a 6 V amplitude sine wave with a dc component of:
  - 0 V; ii) +2 V; iii) -7 V
- Change the circuit, in order to obtain a negative peak detector.





➤ Translation two-port DC networks

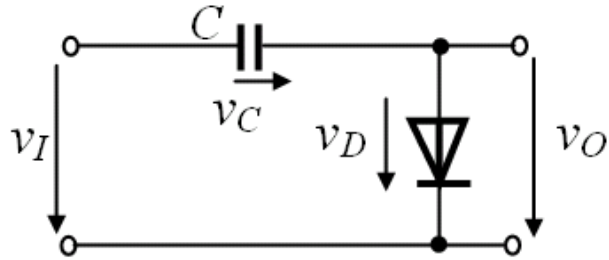


$$v_D(t) = v_I(t) - v_C(t)$$


$$v_O(t) = v_D(t)$$

Application:

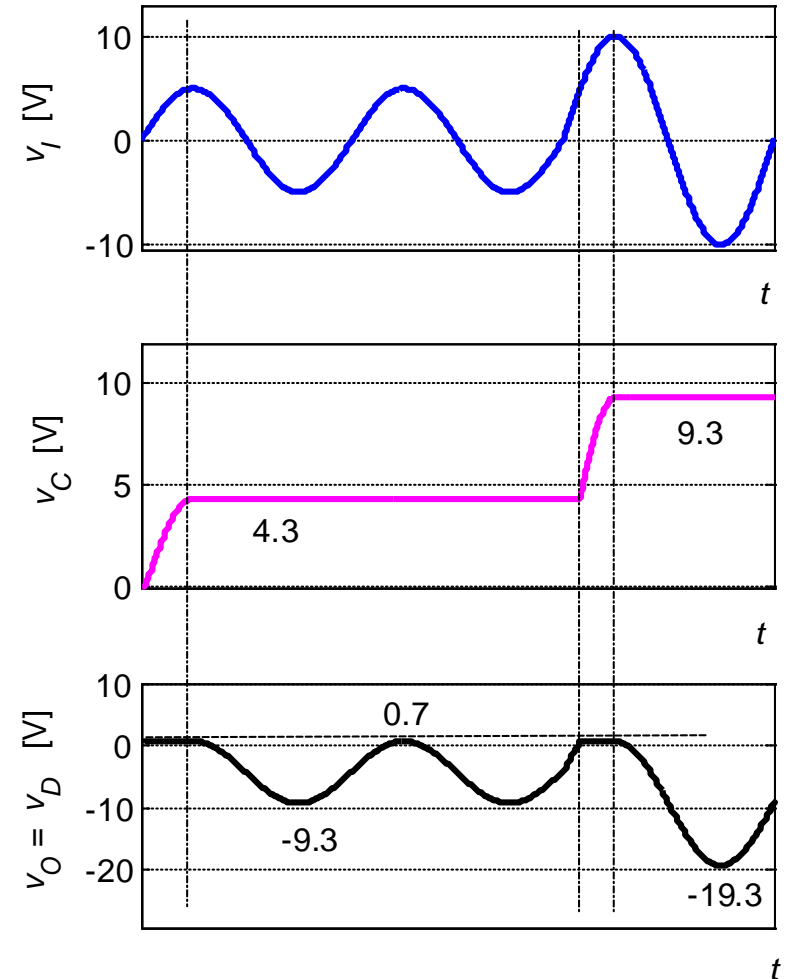Translation towards negative values (downward)



➤ Translation two-port DC networks

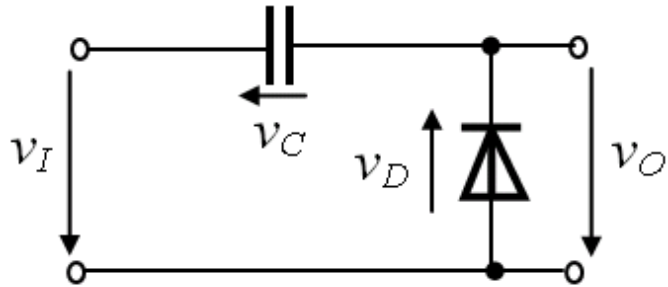


$$v_D(t) = -v_I(t) - v_C(t)$$

$$v_O(t) = -v_D(t)$$

Application:

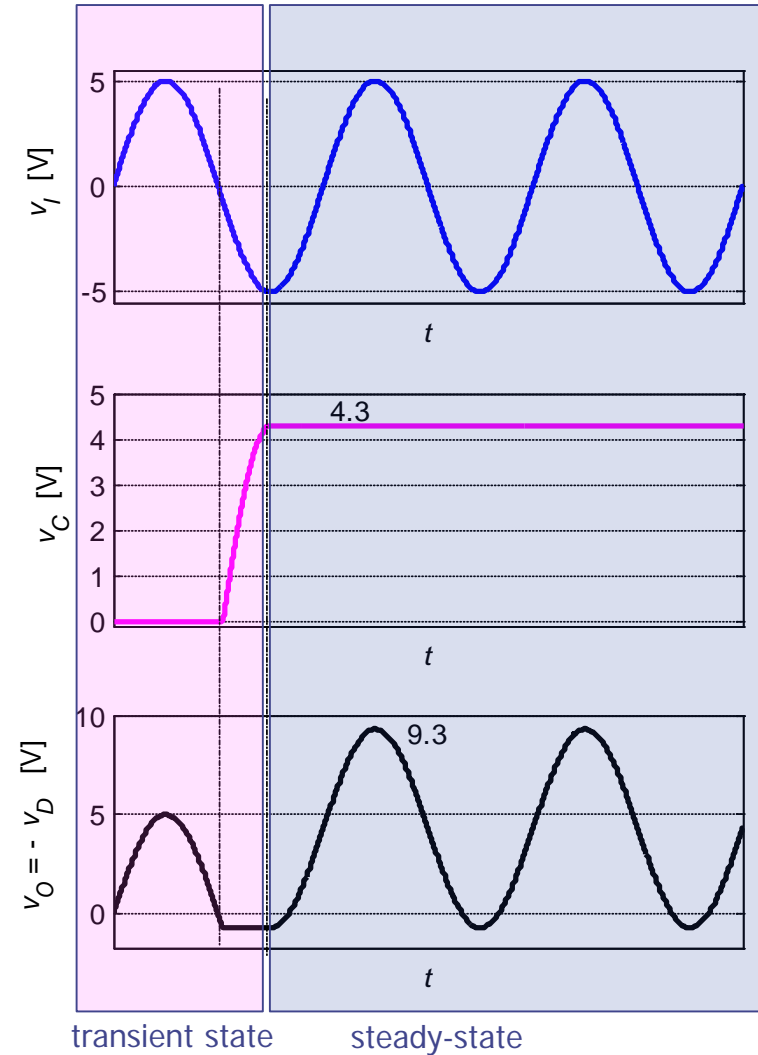
Translation towards positive values (upward)


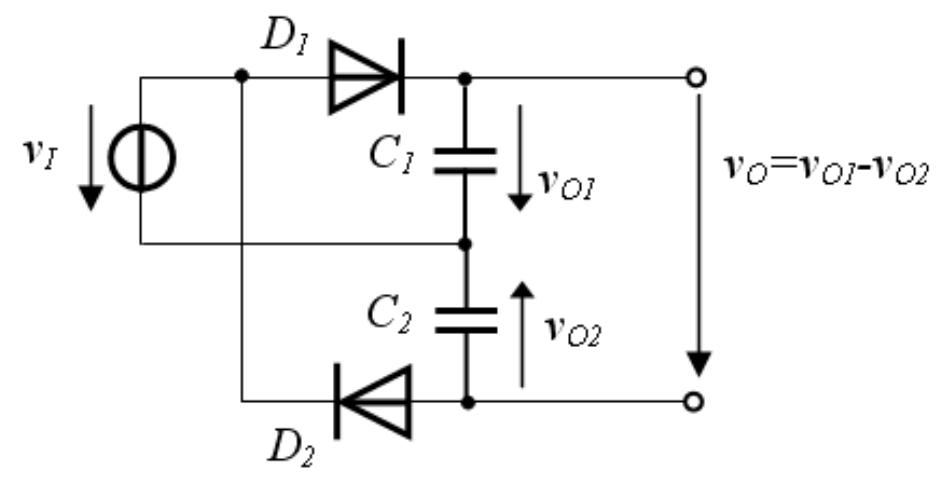
## ➤ Voltage doubler

- variable (ac) input voltage
- dc output voltage
- output voltage is (almost) twice the amplitude of the input voltage


❑ **Solution 1:** series connection of a **positive** peak detector and a **negative** peak detector



$$v_{O1}(t) = \hat{V}_I$$
$$v_{O2}(t) = -\hat{V}_I$$
$$v_O(t) = \hat{V}_I - (-\hat{V}_I) = 2\hat{V}_I$$

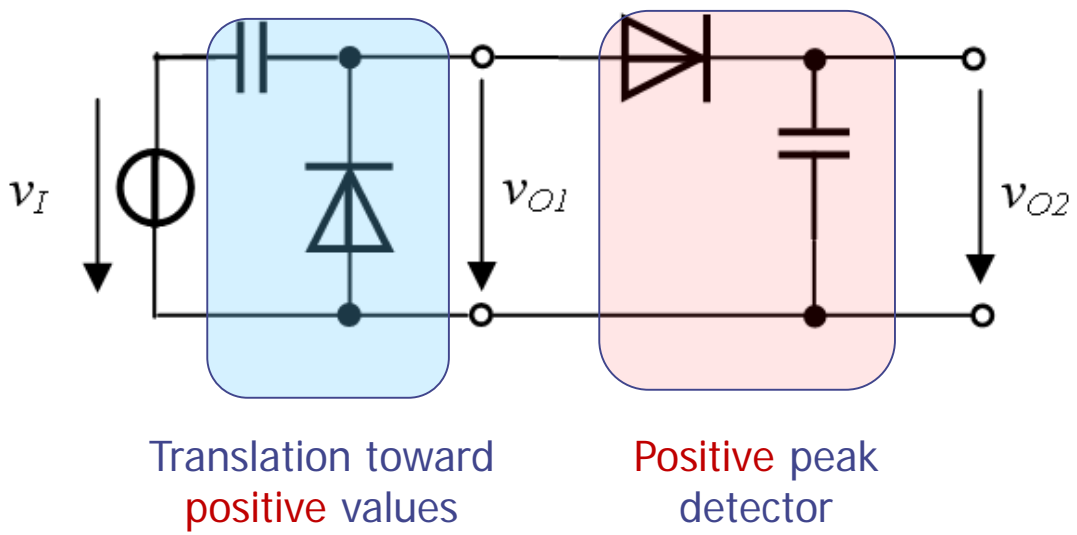
## ➤ Voltage doubler

❑ **Solution 2:** chain connection of an **upward** translation circuit and a **positive** peak detector





$$v_O \approx 2\hat{V}_I \text{ neglecting } 0.7 \text{ V}$$

$$v_O = 2\hat{V}_I - 1.4 \text{ V}$$

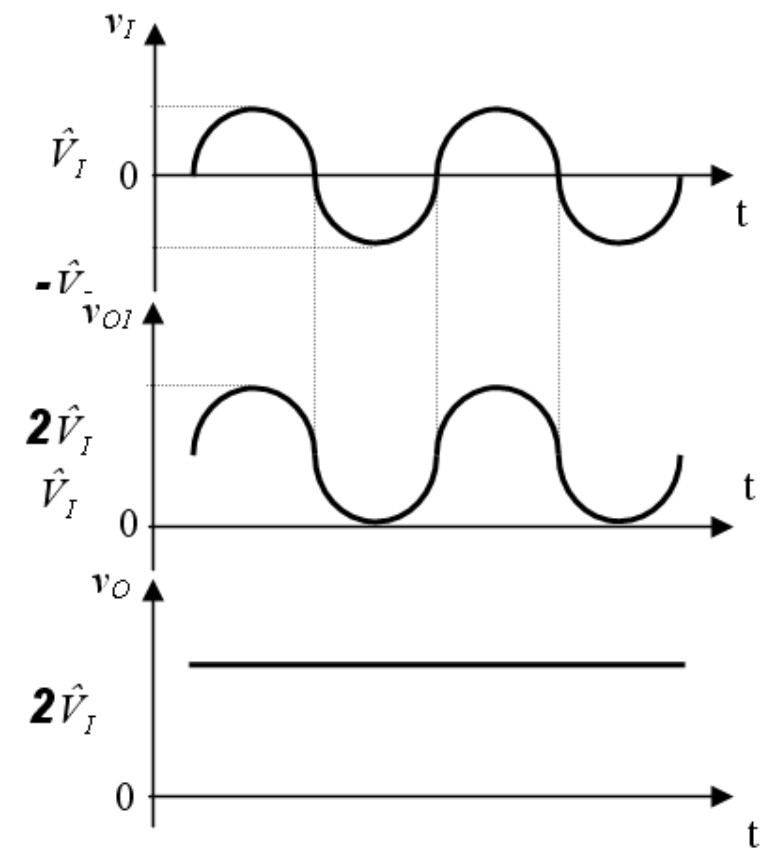


steady-state regime waveforms

## ➤ Voltage doubler

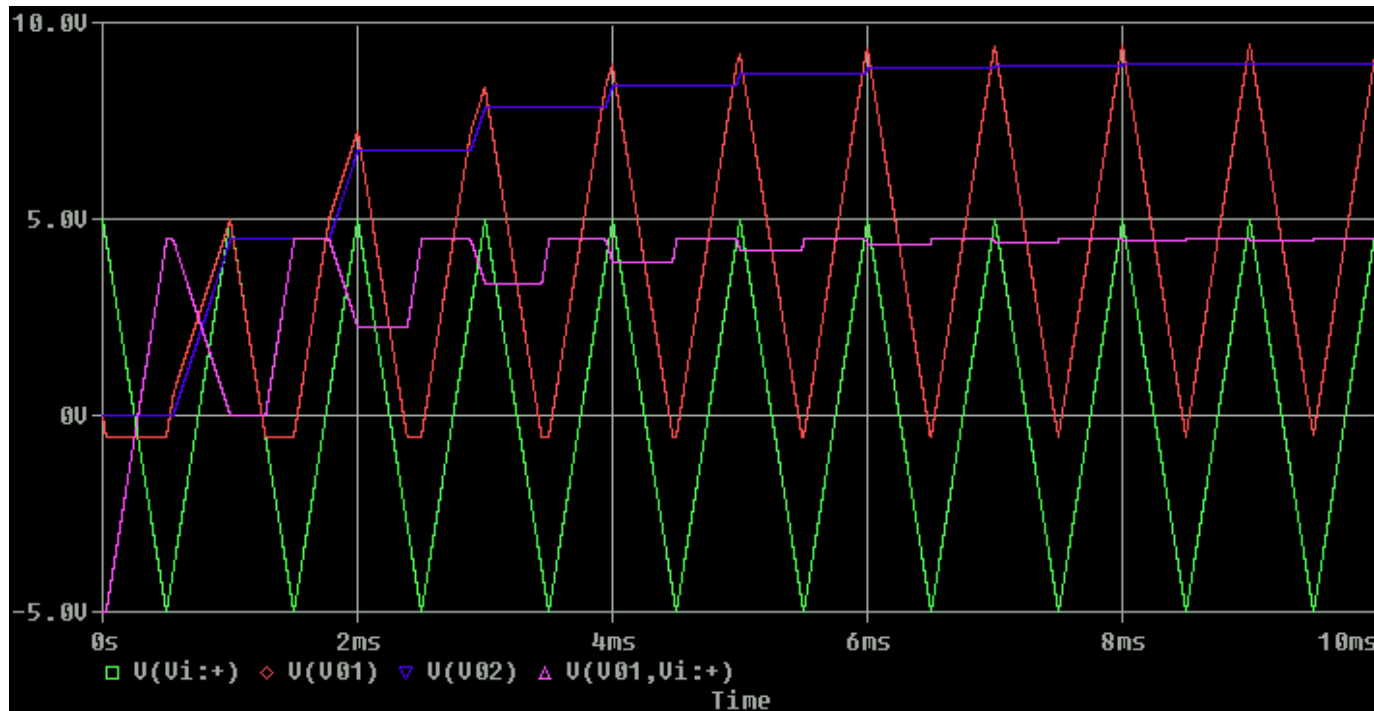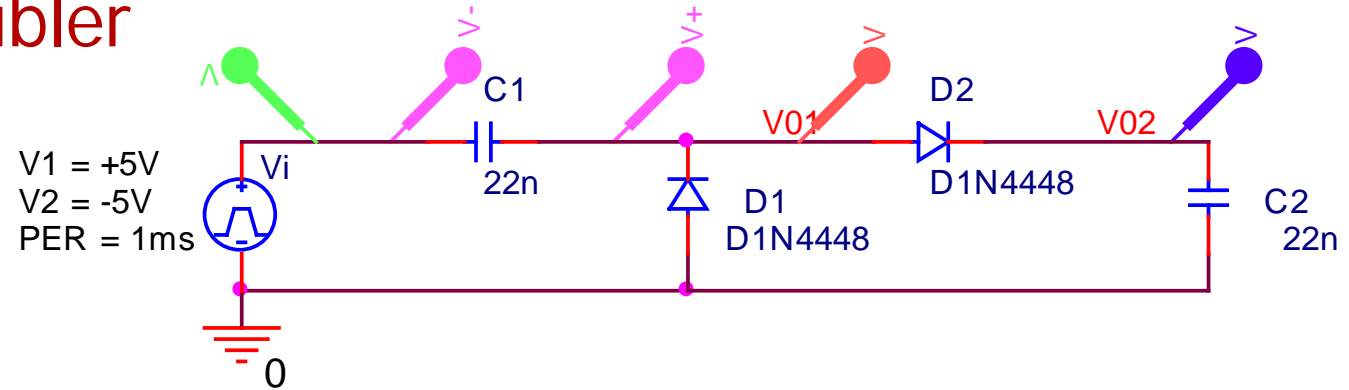


*OPTIONAL*

➤ Voltage tripler

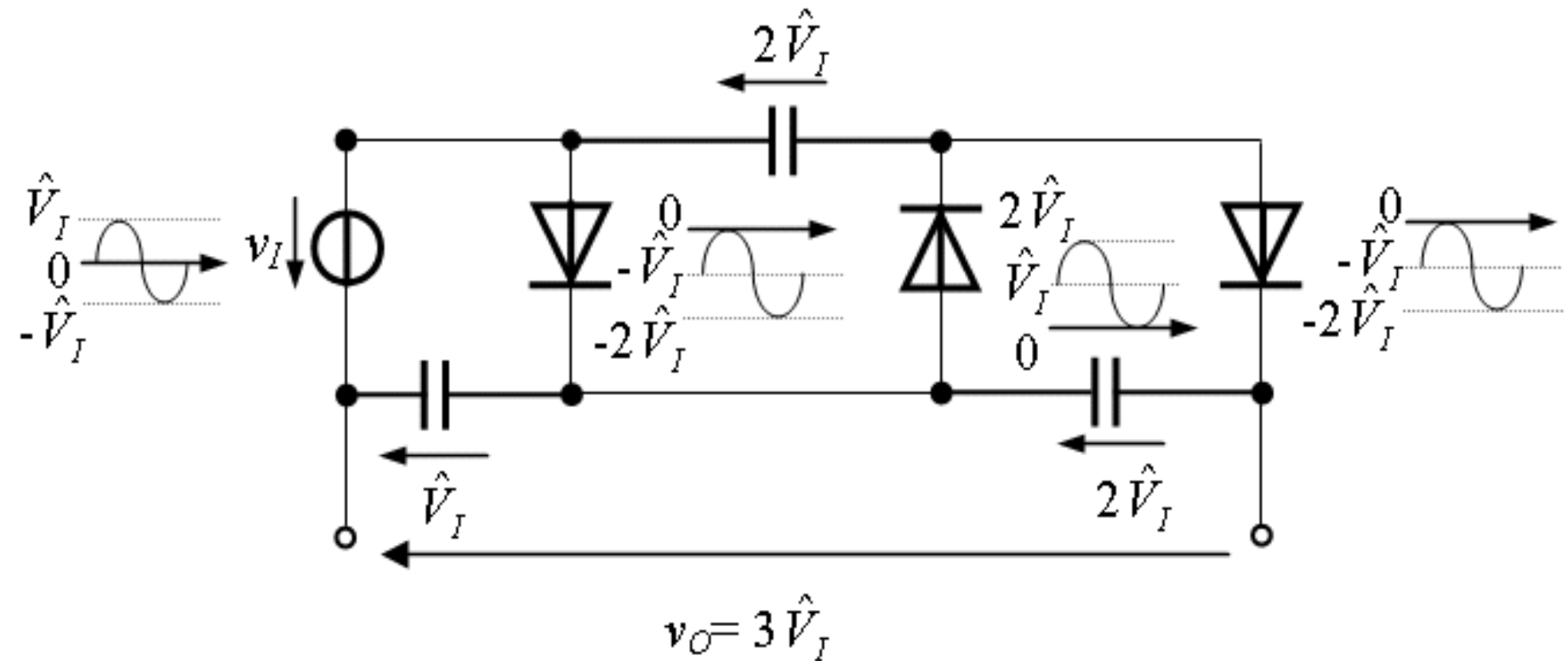

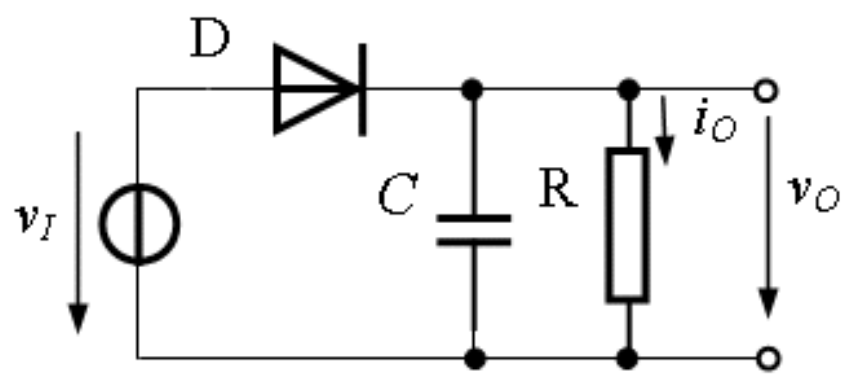
## ➤ Half-wave rectifier w/ capacitive filter (loaded positive peak detector)

- $v_I$  is the voltage in a secondary winding of a step-down line transformer.
- It is required to obtain an almost dc voltage (on a load resistor)



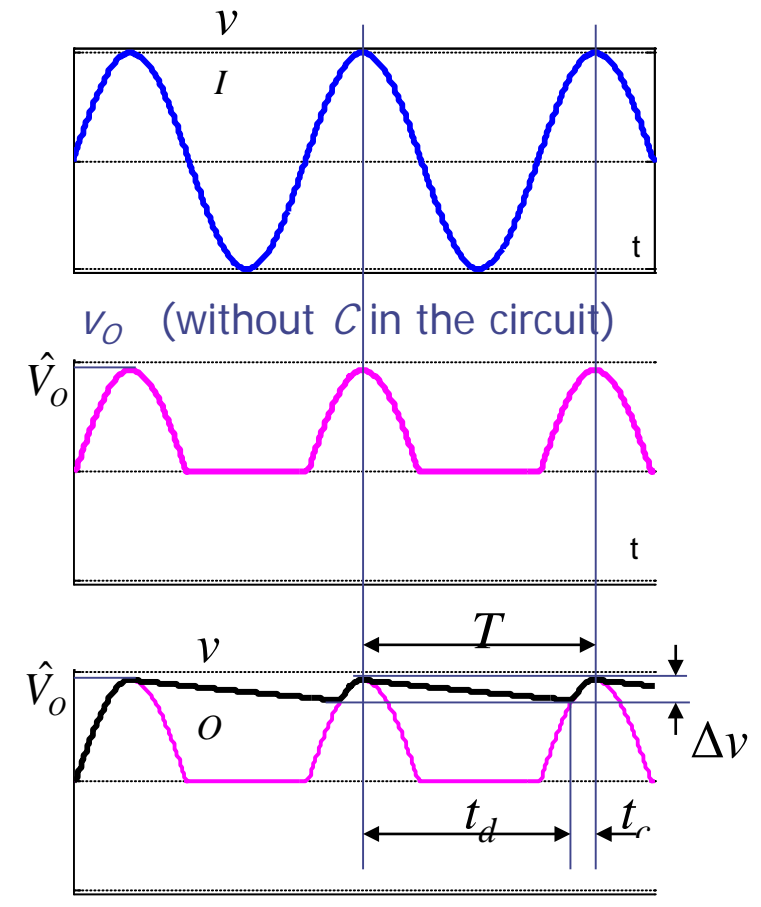How can the voltage ripple  $\Delta v$  be computed?



## ➤ Half-wave rectifier w/ capacitive filter (loaded positive peak detector)

Between two successive voltage peaks,  $D$  – (off) and  $C$  discharges through  $R$

$$v_c(t) = (1 - e^{-\frac{t}{RC}})V_\infty + V(0)e^{-\frac{t}{RC}}$$

If  $RC \gg T \Rightarrow$  the capacitor discharge during  $t_d$  can be approximated with a linear variation of the output voltage (across the capacitor)




$$C\Delta v = I\Delta t$$

$$\Delta t = t_d = T - t_c \approx T$$

The discharging current is assumed to be constant

$$I = \frac{\hat{V}_o}{R}$$

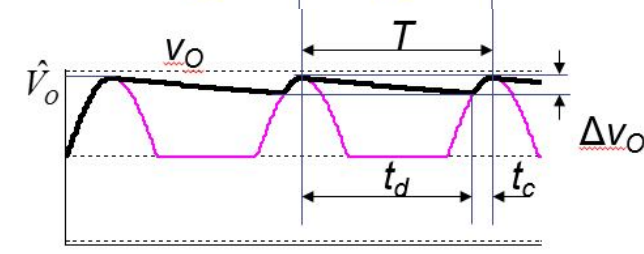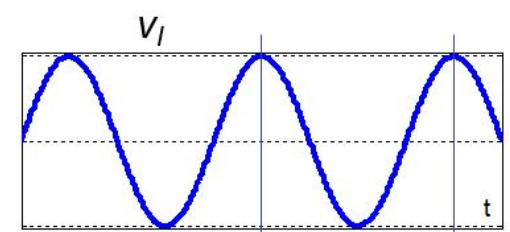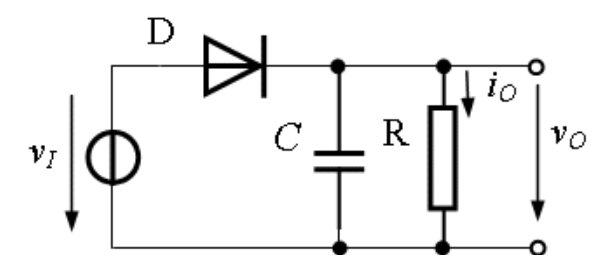
$$\Delta v = \frac{T}{C} I = \hat{V}_o \frac{T}{RC} = \frac{1}{f} \frac{\hat{V}_o}{RC}$$




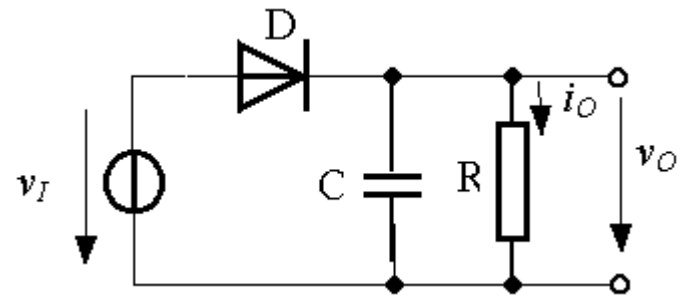
## Example

$\hat{V}_I = 10.7\text{V}$     $f=50\text{Hz}$     $R_L = 100\Omega$     $\Delta v < 1.5\text{V}$     $C = ?$



$$\hat{V}_O = \hat{V}_I - 0.7\text{V} = 10\text{V}$$


$$\Delta v = \frac{\hat{V}_O}{fRC} < 1.5\text{V}$$

$$C > \frac{\hat{V}_O}{1.5VfR} = \frac{10}{1.5 \cdot 50 \cdot 100} = 1333\mu\text{F} \quad C > 1333\mu\text{F}$$


Solution: electrolytic capacitor,  $C = 1500 \mu\text{F}/25 \text{ V}$

- What is the actual value of the output ripple?
- What should be a new value of  $C$ , in order to reduce the output ripple to half of the initial value?
- Solve again, assuming full-wave rectification.

## AM demodulator


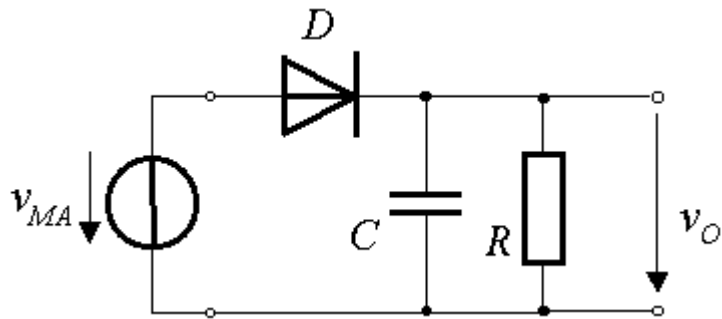


Envelope detector

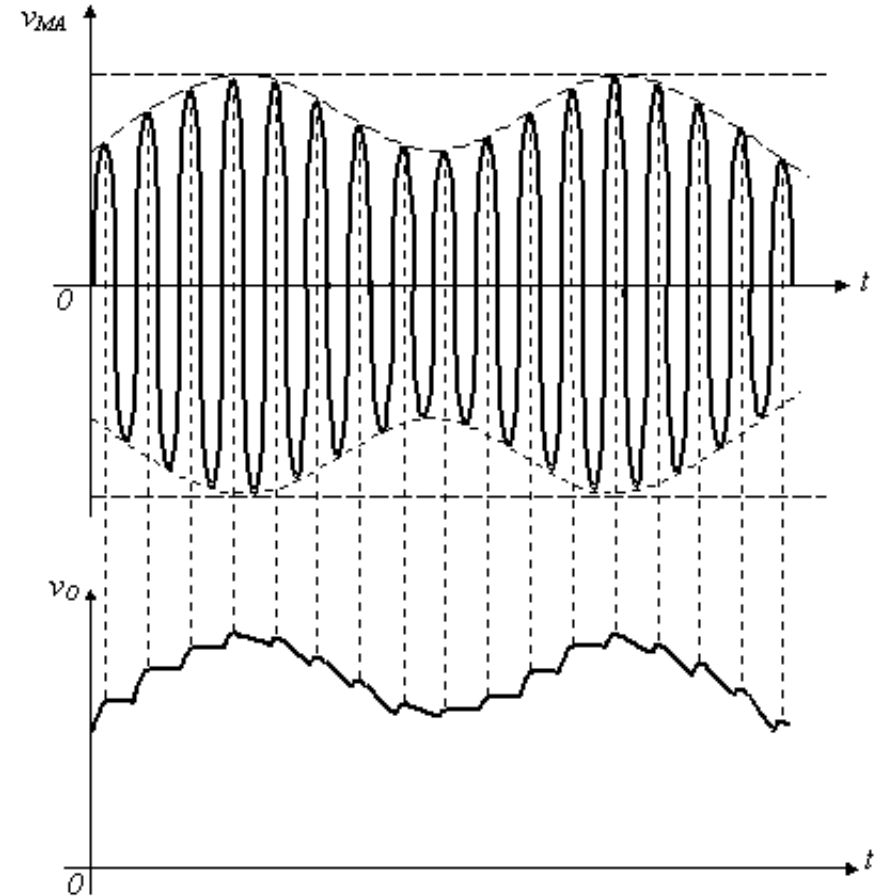

OPTIONAL

# DC component restoration


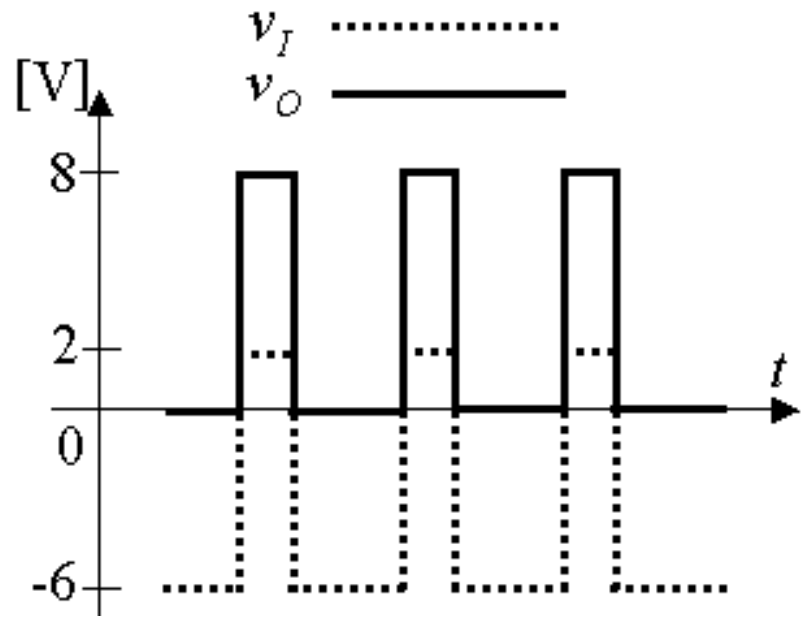
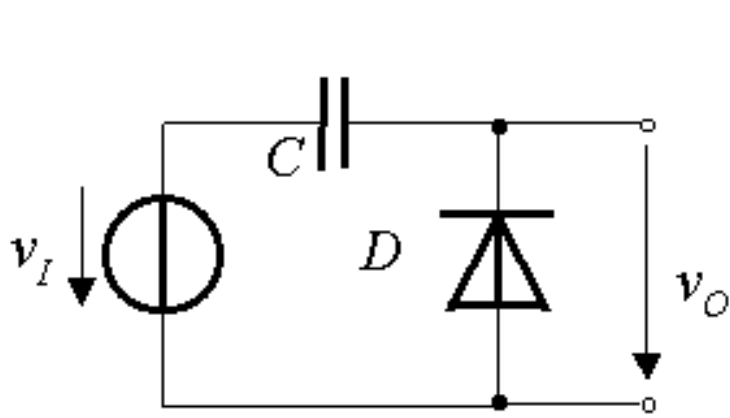


Consider a rectangular wave, transmitted on a line w/ capacitive coupling.

The signal loses its initial dc level.

The upward translation circuit provides a well determined dc component: *dc restoration*.

## ➤ LED – light emitting diode

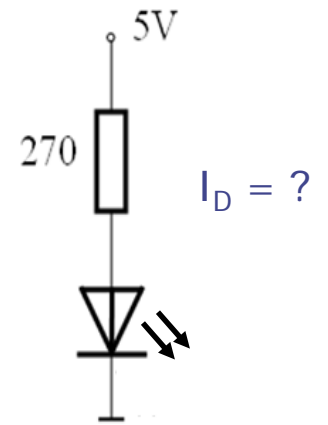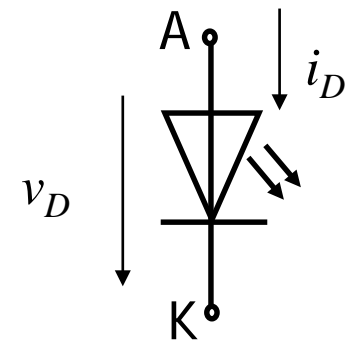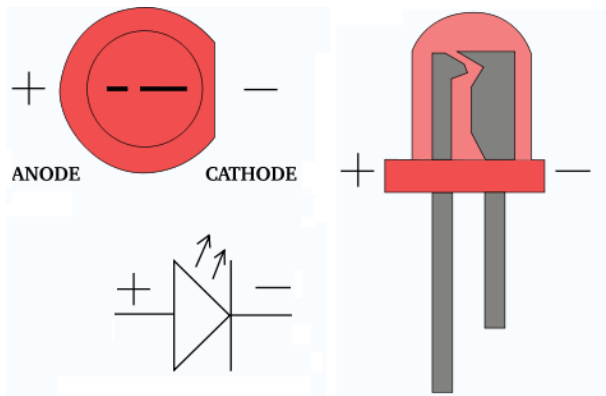

- behavior similar to conventional diodes
- 1.5 V to 3 V forward voltage drop
- in forward bias the LED lights up:
  - red, yellow, green, blue, white
  - IR – remote control
- emits radiation in the visible, infrared, or laser range
- typically 5 mA to 20 mA
- *power LED*: 3.5V @ 500 mA



➤ LED – excerpt from datasheet

**APPLICATIONS**

- Status lights
- Off/on indicator
- Background illumination
- Readout lights
- Maintenance lights
- Legend light



**TLHR440., TLHO440., TLHY440., TLHG440., TLHP440.**  
www.vishay.com Vishay Semiconductors

**High Efficiency LED in Ø 3 mm Tinted** **PRODUCT GROUP AND PACKAGE DATA**


- Product group: LED
- Package: 3 mm
- Product series: standard
- Angle of half intensity: ± 30°

<b>PARTS TABLE</b>														
PART	COLOR	LUMINOUS INTENSITY (m cd)			at I <sub>F</sub> (mA)	WAVELENGTH (nm)			at I <sub>F</sub> (mA)	FORWARD VOLTAGE (V)			at I <sub>F</sub> (mA)	TECHNOLOGY
		MIN.	TYP.	MAX.		MIN.	TYP.	MAX.		MIN.	TYP.	MAX.		
TLHR4400	Red	1.6	13	-	10	612	-	625	10	-	2	3	20	GaAsP on GaP
TLHO4400-MS12Z	Soft orange	1.6	13	-	10	598	-	611	10	-	2.4	3	20	GaAsP on GaP
TLHY4400	Yellow	1.6	10	-	10	581	-	594	10	-	2.4	3	20	GaAsP on GaP
TLHG4405	Green	6.3	15	-	10	562	-	575	10	-	2.4	3	20	GaP on GaP
TLHP4401	Pure green	1	4	-	10	555	-	565	10	-	2.4	3	20	GaP on GaP


<b>ABSOLUTE MAXIMUM RATINGS</b> (T <sub>amb</sub> = 25 °C, unless otherwise specified) <b>TLHR440., TLHO440., TLHY440., TLHG440., TLHP440.</b>				
PARAMETER	TEST CONDITION	SYMBOL	VALUE	UNIT
Reverse voltage		V <sub>R</sub>	6	V
DC forward current		I <sub>F</sub>	30	mA
Surge forward current	t <sub>p</sub> ≤ 10 μs	I <sub>FSM</sub>	1	A
Power dissipation	T <sub>amb</sub> ≤ 60 °C	P <sub>V</sub>	100	mW

# ➤ LED strips



## Single Color LED Strip

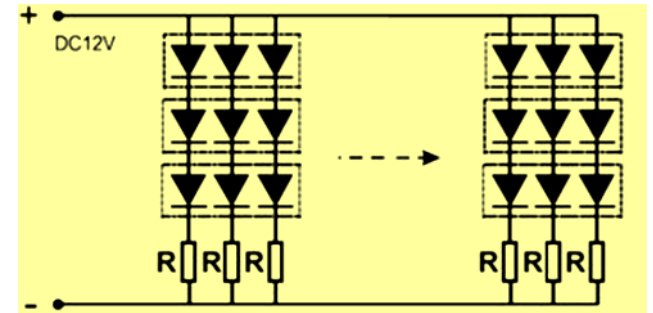

## RGB LED Strip

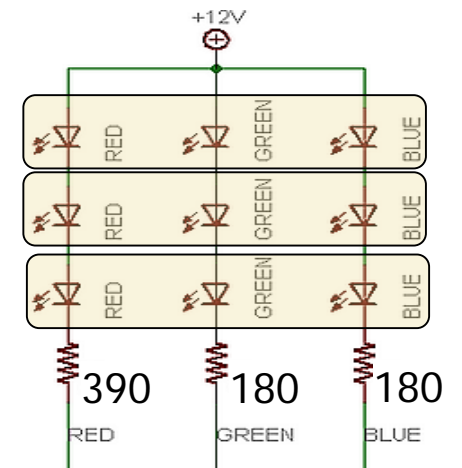

## ➤ Photodiodes

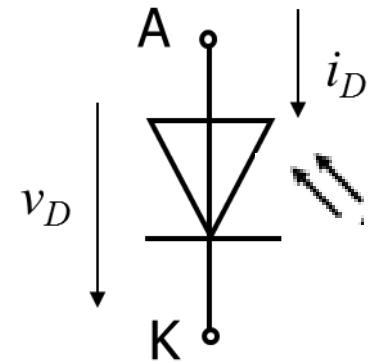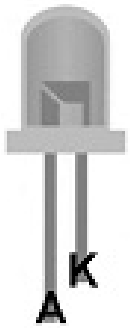

- photosensitive pn-junction
- transforms light into electrical signal (current)
- used in reverse bias

# ➤ Photodiodes - excerpt from datasheet



EVERLIGHT ELECTRONICS CO., LTD.

DEVICE NUMBER : DPD-033-071    REV : 1.0  
ECN : \_\_\_\_\_    PAGE : 1/7

**5mm Silicon PIN Photodiode, T-1 3/4**  
MODEL NO : PD333-3C/H0/L2

- **Features :**
- Fast response time
  - High photo sensitivity
  - Small junction capacitance

■ **Description :**  
 PD333-3C/H0/L1 is a high speed and high sensitive PIN photodiode in a standard 5  $\phi$  plastic package. The device is spectrally matched to infrared emitting diode.

- **Applications :**
- High speed photo detector
  - Camera
  - Infrared remote controller for TVs VCR, audio equipment, air conditioner, etc.

■ **Absolute Maximum Ratings at Ta = 25°C**

Parameter	Symbol	Rating	Unit	Notice
Reverse Voltage	V <sub>R</sub>	32	V	
Power Dissipation	P <sub>d</sub>	150	mW	
Lead Soldering Temperature	T <sub>sol</sub>	260	°C	4mm from mold body less than 5 seconds
Operating Temperature	T <sub>opr</sub>	-25 ~ +85	°C	
Storage Temperature	T <sub>stg</sub>	-40 ~ +85	°C	



# Summary

Only now we can safely say diodes are not a secret anymore, after studying:

- Full-wave DR rectifiers
- Two-port DC networks
- DRC rectifiers (power supply filtering)
- LEDs and photodiodes

**Next week:** Zener diodes. Operational amplifiers. Simple comparators with OpAmp.

**To do: Homework 2**