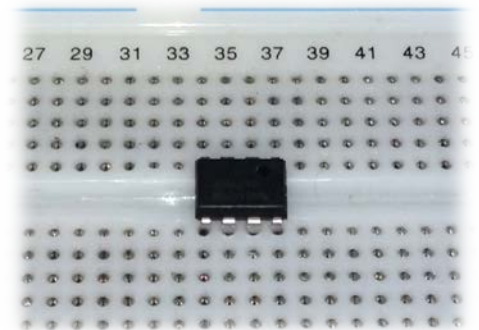




# ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

## C6 – Simple comparators with OpAmp



# Contents

## ➤ Simple comparators with OpAmp

- Simple comparators with  $V_{Th} = 0 \text{ V}$
- Simple comparators with  $V_{Th} \neq 0 \text{ V}$
- Applications

## Relation between output and input voltages


$$V_O = a v_D = \infty \cdot v_D$$

I. Utilization as **comparator**, in switching mode

$$v_O \in \{V_{OL}; V_{OH}\}$$

$v_D > 0$ ,  $v_O \rightarrow +\infty$ ,  $v_O$  limited by the positive supply  $v_O = V_{OH} \approx +V_{PS}$

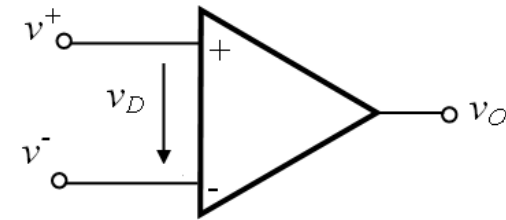$v_D < 0$ ,  $v_O \rightarrow -\infty$ ,  $v_O$  limited by the negative supply  $v_O = V_{OL} \approx -V_{PS}$



II. Utilization as **amplifier**

$$v_O \in (V_{OL}; V_{OH})$$

It is mandatory that  $v_D = 0$ , so then  $v_O = a \cdot v_D = \infty \cdot 0$  - indetermination

$v_D$  is kept at 0 by means of external components (R)

## OpAmp comparators


OpAmp in switching mode => OpAmp comparator

**Voltage comparator** = circuit that signalizes the **relative state** of two input voltages, through two **different states** of the **output** voltage

? **relative state** of two **input** voltages = ?

? two **different states** of the **output** voltage = ?

## OpAmp comparators

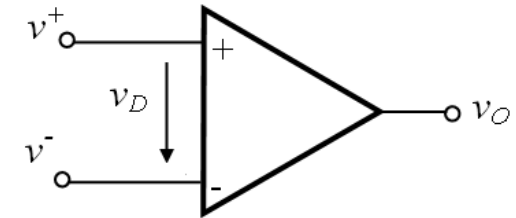

Voltage comparator = circuit that signalizes the **relative state** of two input voltages, through two **different states** of the **output** voltage

**relative state** of two **input** voltages = one input voltage is bigger/smaller than the other  
= their difference is positive/negative

For OpAmp comparators, a single input is considered, namely  $v_D = v^+ - v^-$

two **different states** of the **output** voltage = low/high




$$V_O \in \{V_{OL}, V_{OH}\}$$

$$v_D > 0, \text{ meaning } v^+ > v^-, v_O = V_{OH} \approx +V_{PS}$$

$$v_D < 0, \text{ meaning } v^+ < v^-, v_O = V_{OL} \approx -V_{PS}$$

# OpAmp comparators

OpAmp model in switching regime

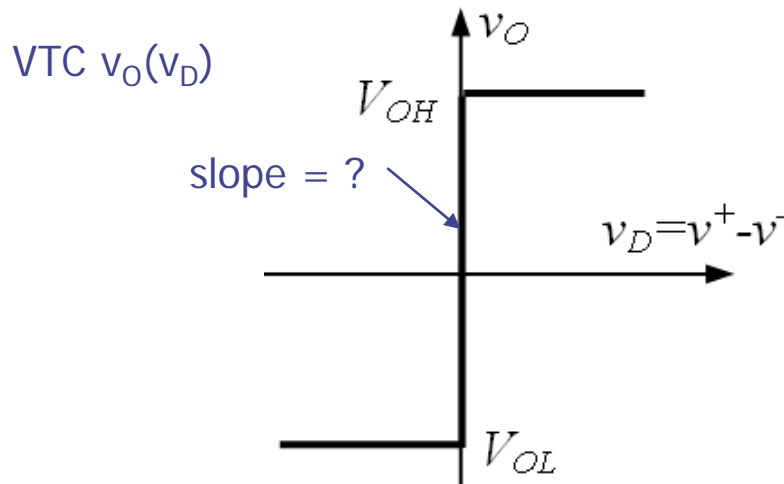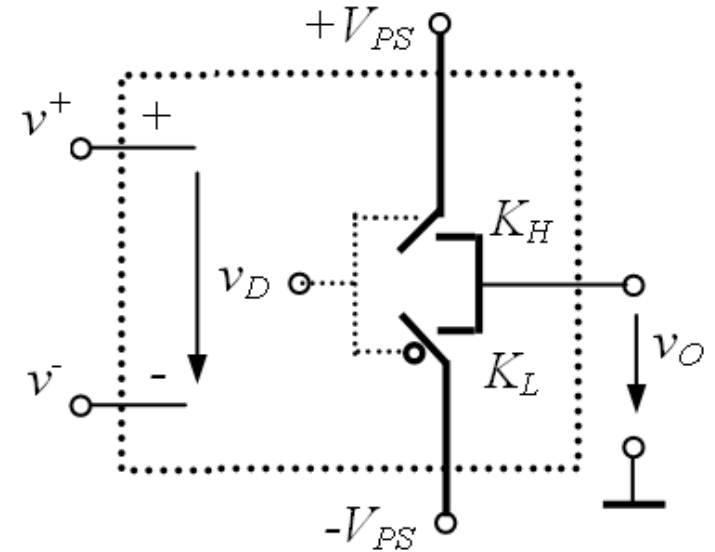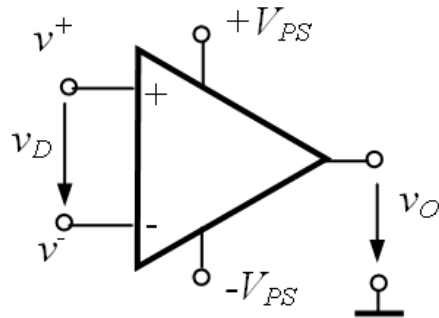

$v_D$	$K_H$	$K_L$	$v_O$
$> 0$	on	off	$V_{OH} = +V_{PS}$
$< 0$	off	on	$V_{OL} = -V_{PS}$

Suitable for rail-to-rail op-amp

## OpAmp comparators

Types of voltage comparators:

- Simple comparators – **without** feedback, **one** threshold voltage
- Hysteresis comparators – **positive** feedback, **two** threshold voltages

**Threshold voltage**  $V_{Th}$  = particular value(s) of the input voltage, for which the output voltage switches (changes states) (hence  $v_D = 0$ )

$$V_{Th} = v_I |_{v_D=0}$$

**Feedback** = (backward) connection, between output and input

- positive feedback = output is connected to non-inverting input
- negative feedback = output is connected to inverting input

## Simple comparators

= comparators without feedback, one threshold voltage

Threshold voltage  $V_{Th}$  = particular value(s) of the input voltage  $v_I$ , for which the output voltage switches (changes states) (hence  $v_D = 0$ )

$$V_{Th} = v_I |_{v_D=0}$$


Steps for finding  $V_{Th}$ :

- **Step 1:** write down the expressions for  $v^+$  and  $v^-$  (Ohm's law, KVL, voltage divider, Millman)
- **Step 2:** write down  $v_D = v^+ - v^-$
- **Step 3:** set  $v_D$  to 0 and replace  $v_I$  with  $V_{Th}$
- **Step 4:** compute the numerical value of  $V_{Th}$



➤ Simple comparators with  $V_{Th} = 0\text{ V}$

▪ Non-inverting

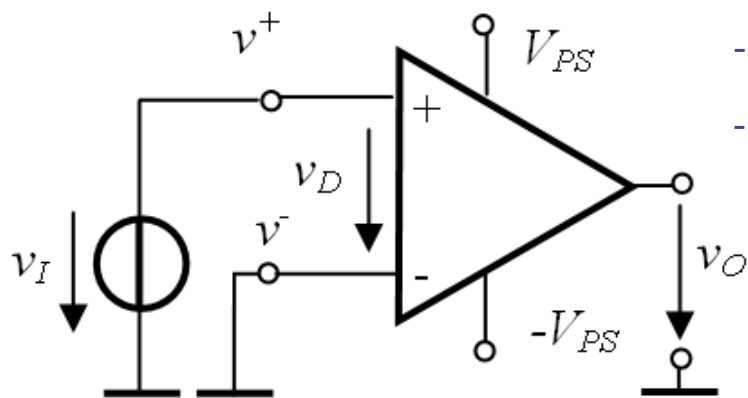

- $v_I$  is applied at the non-inverting input ( $v^+$ )
- the inverting input ( $v^-$ ) is connected to ground ( $0\text{ V}$ )


$$v_D = v^+ - v^-$$

$$v^+ = v_I; \quad v^- = 0$$

$$v_D = v_I$$

$$v_D = 0; \quad V_{Th} = 0$$

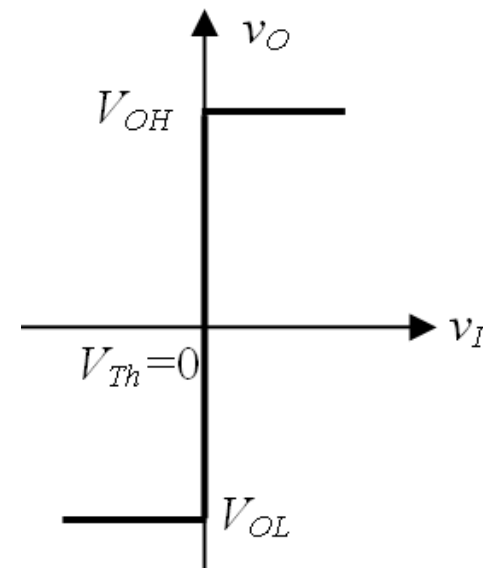
$$v_O = \begin{cases} V_{OH} & \text{if } v_D > 0, \text{ this is } v_I > 0 \\ V_{OL} & \text{if } v_D < 0, \text{ this is } v_I < 0 \end{cases}$$



Plot the input and output voltages, if the input voltage is a sine wave with 5 V amplitude and the supply is  $\pm V_{PS} = \pm 15\text{ V}$ .

## ➤ Simple comparators with $V_{Th} = 0\text{ V}$

### ▪ Inverting

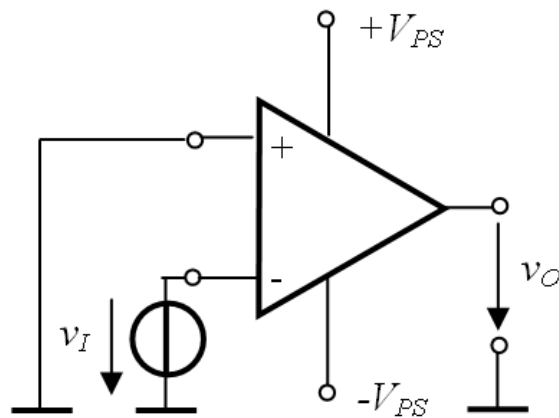

- $v_I$  is applied at the inverting input ( $v^-$ )
- the non-inverting input ( $v^+$ ) is connected to ground (0 V)


$$v_D = v^+ - v^-$$

$$v^+ = 0; \quad v^- = v_I$$

$$v_D = -v_I$$

$$v_D = 0; \quad V_{Th} = 0$$

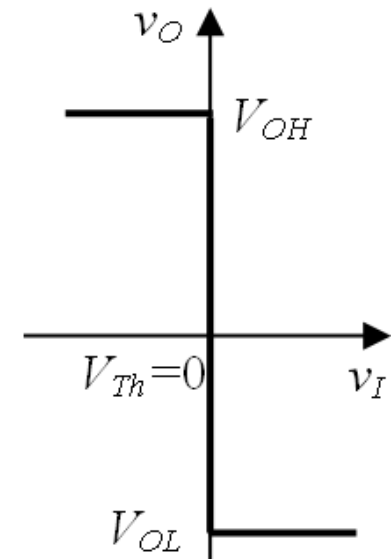
$$v_O = \begin{cases} V_{OH} & \text{if } v_D > 0, \text{ this is } v_I < 0 \\ V_{OL} & \text{if } v_D < 0, \text{ this is } v_I > 0 \end{cases}$$



Plot the input and output voltages, if the input voltage is a sine wave with 5 V amplitude and the supply is  $\pm V_{PS} = \pm 15\text{ V}$ .

## ➤ Simple comparators with $V_{Th} \neq 0 V$

### ▪ Non-inverting

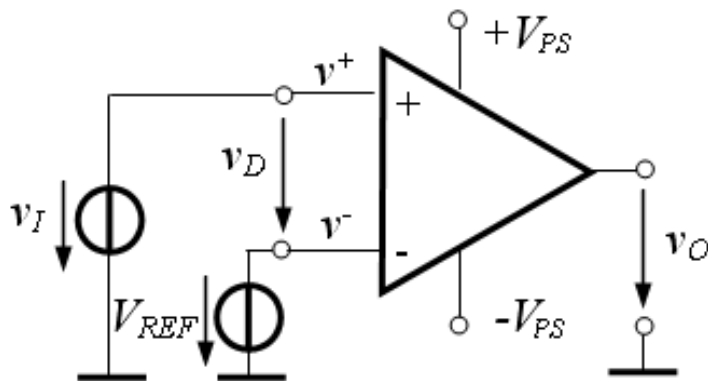


-  $v_I$  is applied at the non-inverting input ( $v^+$ )

$$v_D = v^+ - v^-$$

$$v_D = v_I - V_{REF}$$



$$v_D = 0; \quad V_{Th} = V_{REF}$$

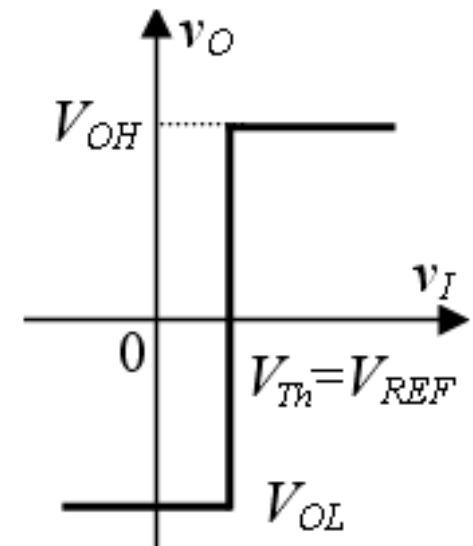

How can  $V_{REF}$  be obtained, using the already available dc supplies?

➤ Simple comparators with  $V_{Th} \neq 0 V$

- Non-inverting

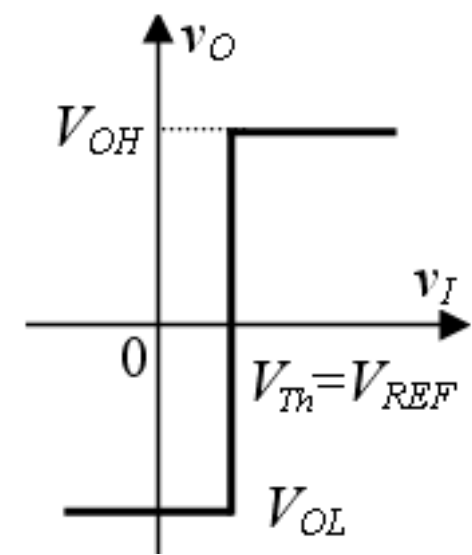
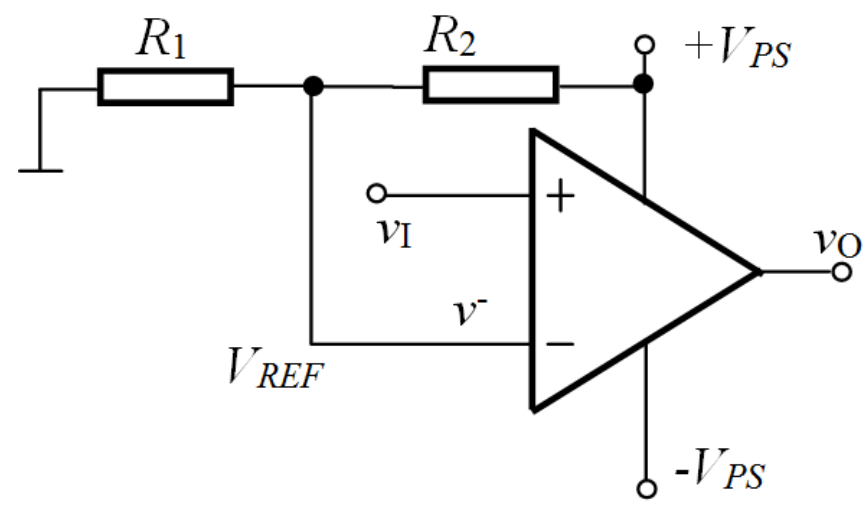


$$V_{REF} = \frac{R_1}{R_1 + R_2} V_{PS}$$

Negative  $V_{REF}$ ?

## ➤ Simple comparators with $V_{Th} \neq 0 V$




### ▪ Example

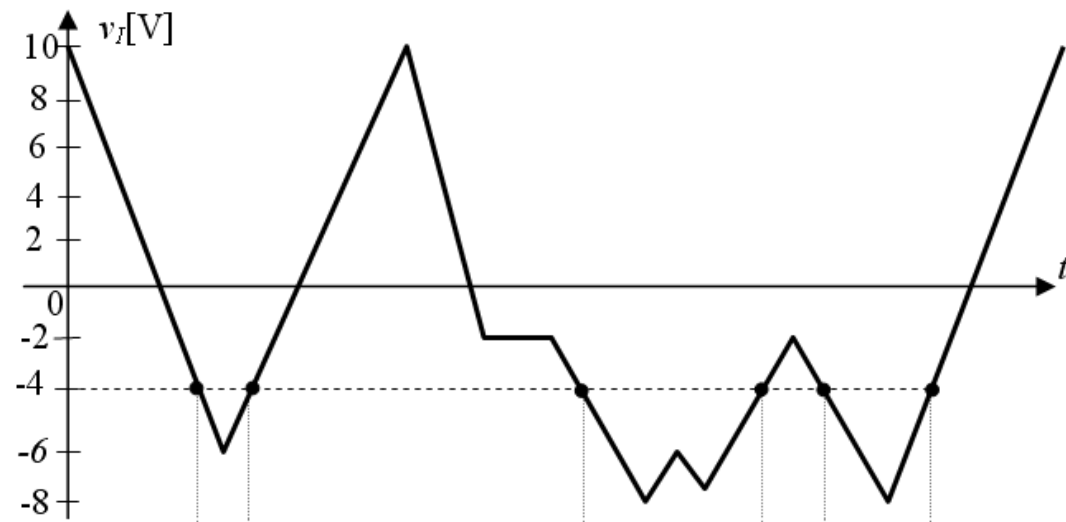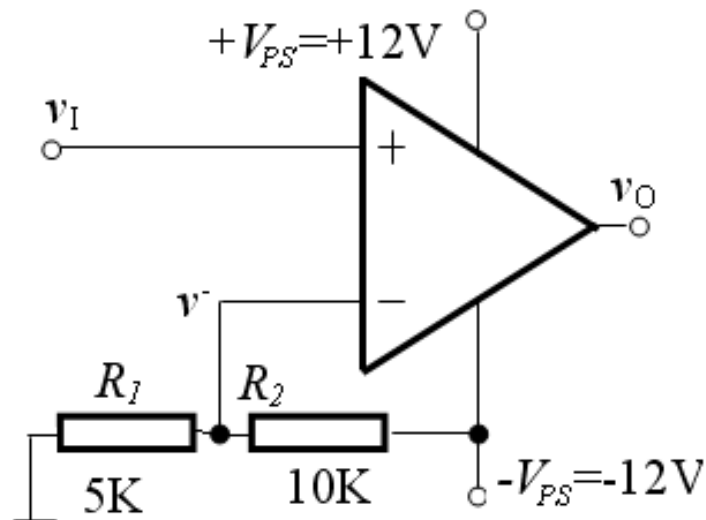

- Deduce and plot VTC  $v_O(v_I)$ . What is the application of the circuit?
- Plot  $v_O(t)$  for the given  $v_I(t)$ .
- Change the circuit, so that it becomes an inverting comparator, with  $V_{Th} = 6 V$ .


➤ Simple comparators with  $V_{Th} \neq 0 V$

▪ Example

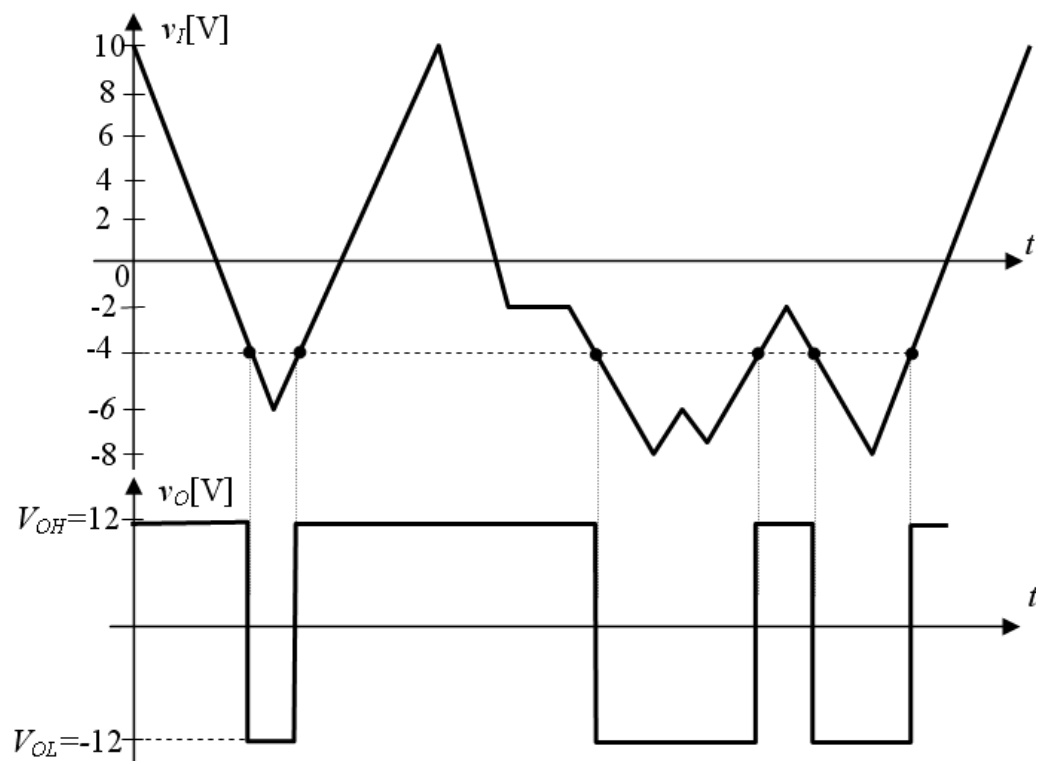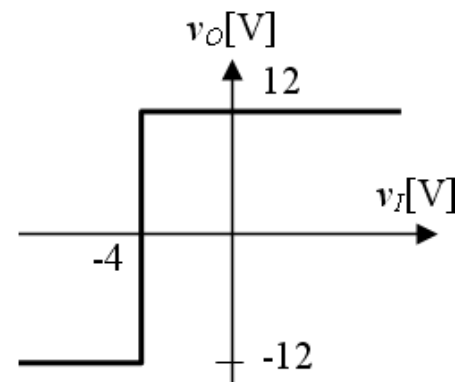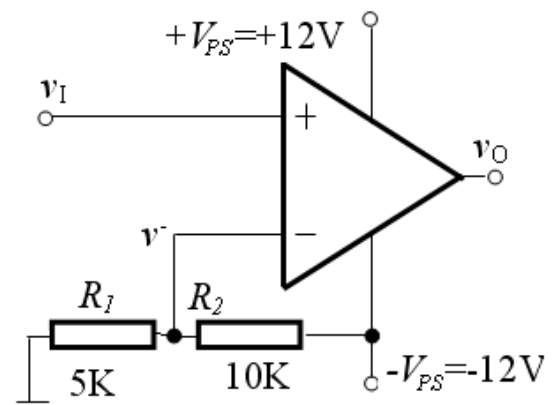

➤ Simple comparators with  $V_{Th} \neq 0 V$

▪ Inverting


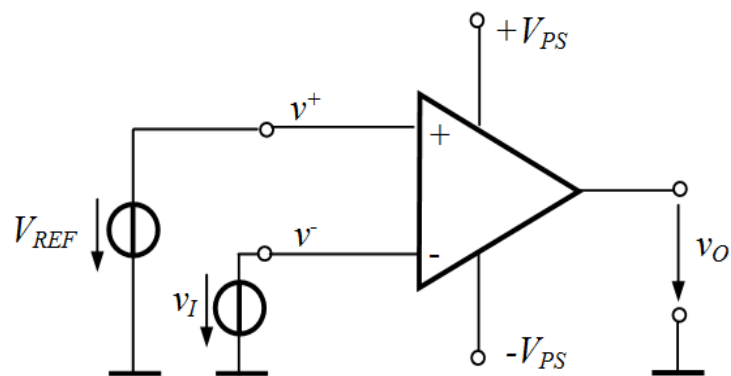


-  $v_I$  is applied at the inverting input ( $v^-$ )

$$v_D = v^+ - v^-$$

$$v_D = V_{REF} - v_I$$

$$v_D = 0; \quad V_{Th} = V_{REF}$$

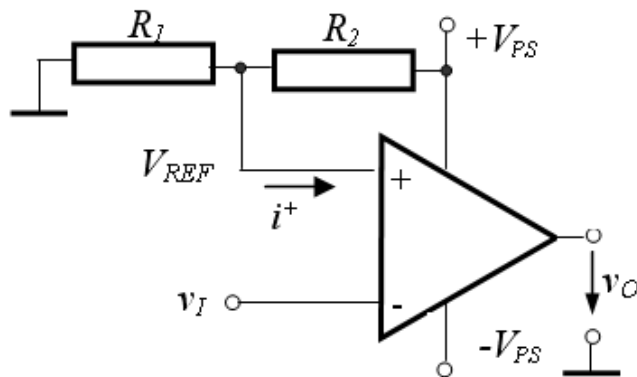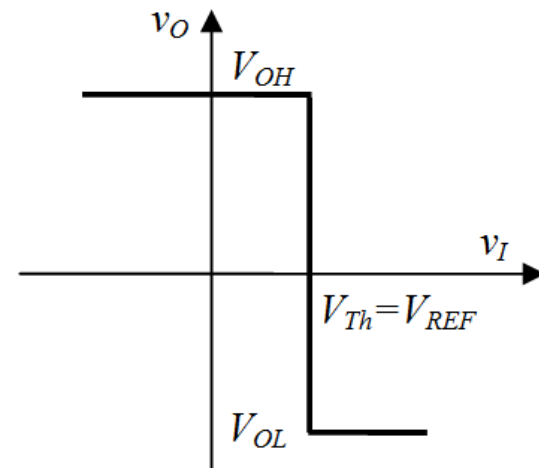

$i^+ \ll$  current through  $R_1, R_2$  divider ( $i^+ \approx 0$ )

$$V_{REF} = \frac{R_1}{R_1 + R_2} V_{PS}$$

## ➤ Applications

- **general-purpose** OpAmps are often used as comparators
- **special class** of ICs, intended for use as comparators:

*LM 306, LM 311, LM 399, LM 393, LM 339*

- high differential input voltage
- high-speed response (high slew-rate)
- open collector (open drain)
- many comparators have a ground terminal that is not present in usual OpAmps





## ➤ Applications

- Logic circuits
- Interface between analog and logic circuits
- Obtaining rectangular signal from sinusoidal (triangular) signal
- Optical indicator for voltage level (L10)
- Pulse width modulation
- Signalizing and control circuits
- Analog to digital converters, etc


## ➤ Applications

- Optical indicator for voltage level

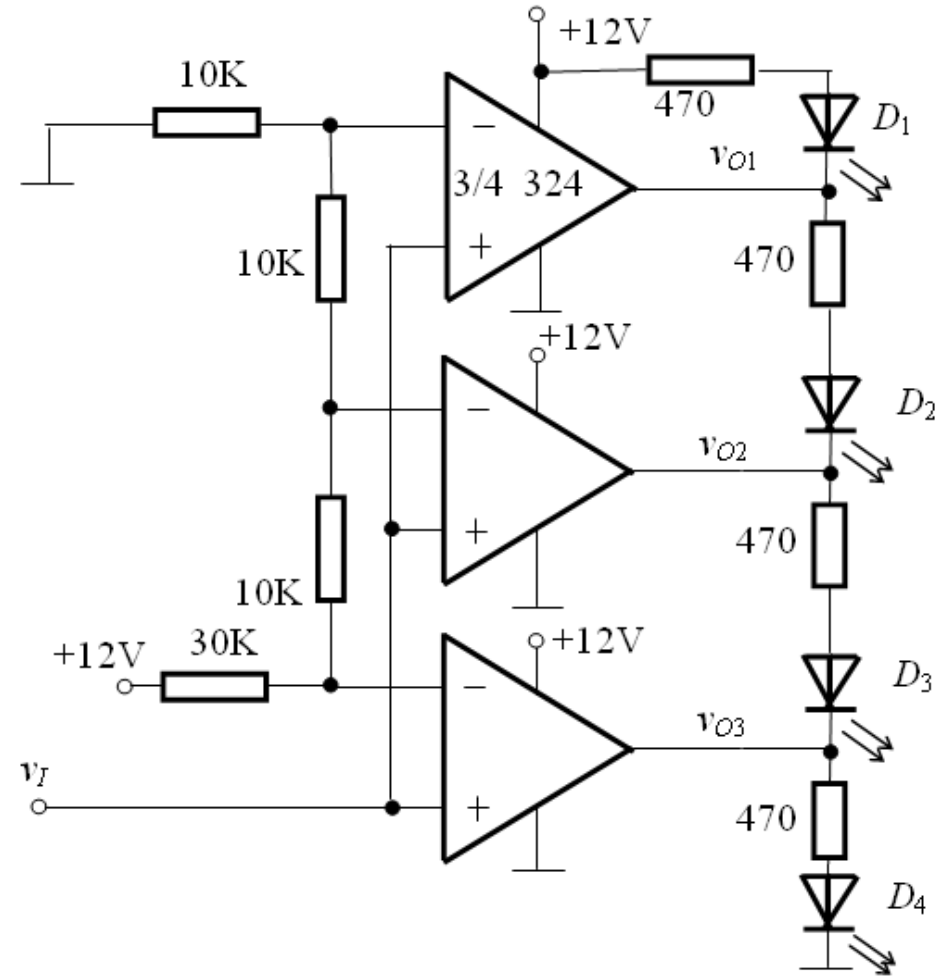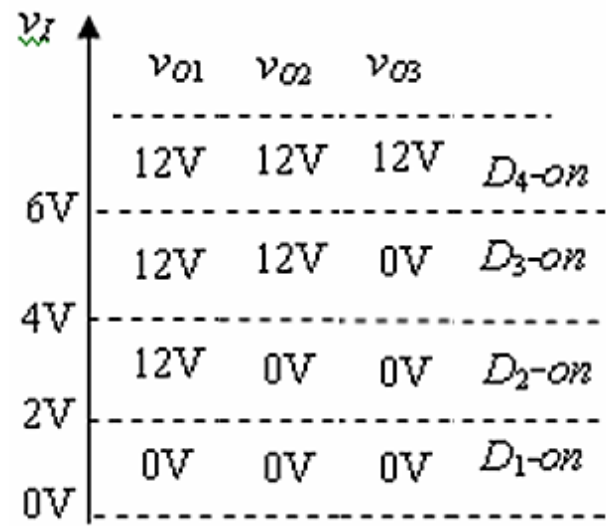

## ➤ Applications

- Light sensor circuit

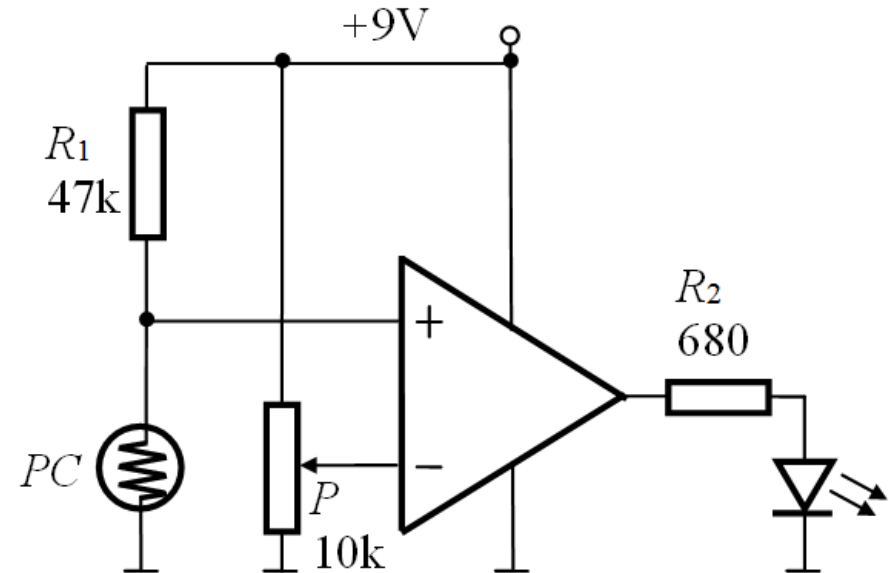

PC : CdS Photoconductive Photocells

PDV-P8001



LDR - light dependent resistor

Dark resistance:  $R_D > 200 \text{ k}\Omega$

Illuminated Resistance:  $R_I \in (3; 11) \text{ k}\Omega$

## ➤ Applications

- Analog to logic circuits interfacing

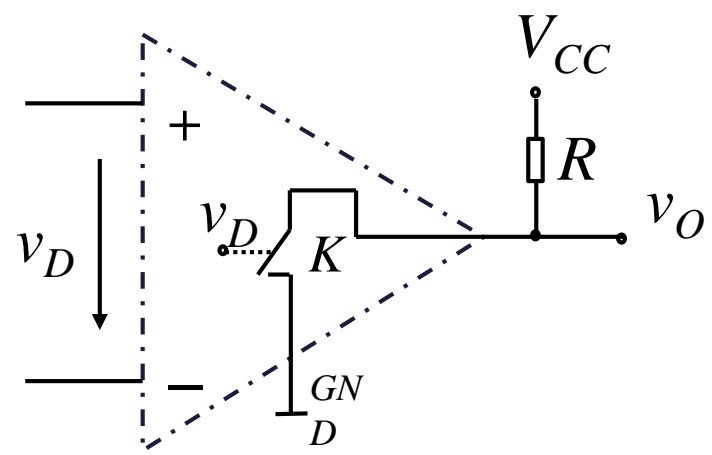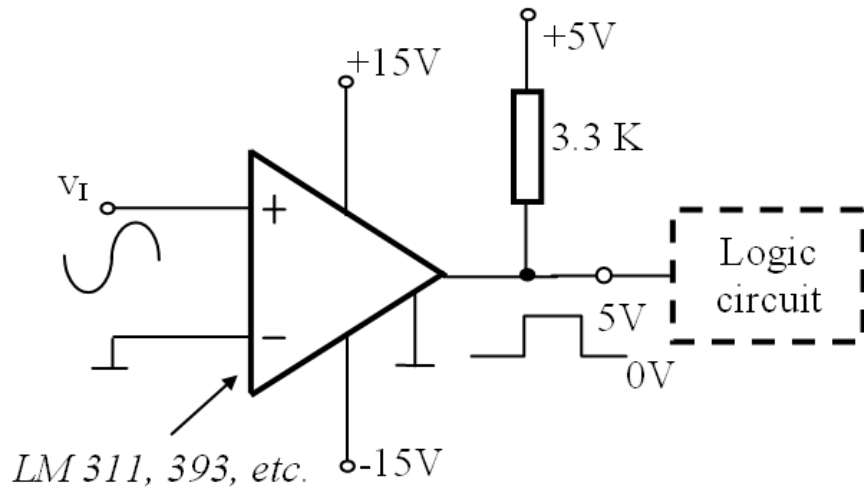

Comparator model

$v_D > 0$	K – (off)	$v_O = V_{CC}$
$v_D < 0$	K – (on)	$v_O = 0$

# Summary

- Simple comparators with OpAmp
  - Simple comparators with  $V_{Th} = 0\text{ V}$
  - Simple comparators with  $V_{Th} \neq 0\text{ V}$
  - Applications

**Next week:** Hysteresis comparators with OpAmp.

**To do: Homework 4**