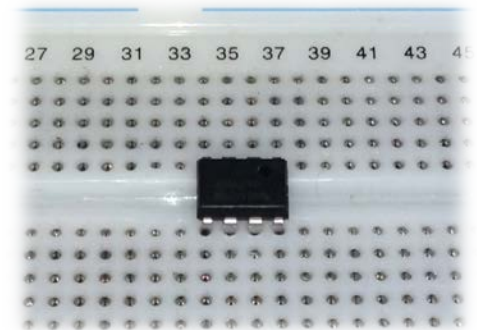




ELECTRONIC DEVICES

Assist. prof. Laura-Nicoleta IVANCIU, Ph.D.

C8 – Electronic amplifiers. Amplifiers with OpAmp.



Contents

➤ Electronic amplifiers


- Types of supply
- Power transfer and power balance
- Types of amplifiers
- VTC
- Modeling the voltage amplifier
- Amplifier performances
- Frequency response

➤ Amplifiers with OpAmp

- Non-inverting amplifier
- Inverting amplifier

Electronic amplifiers

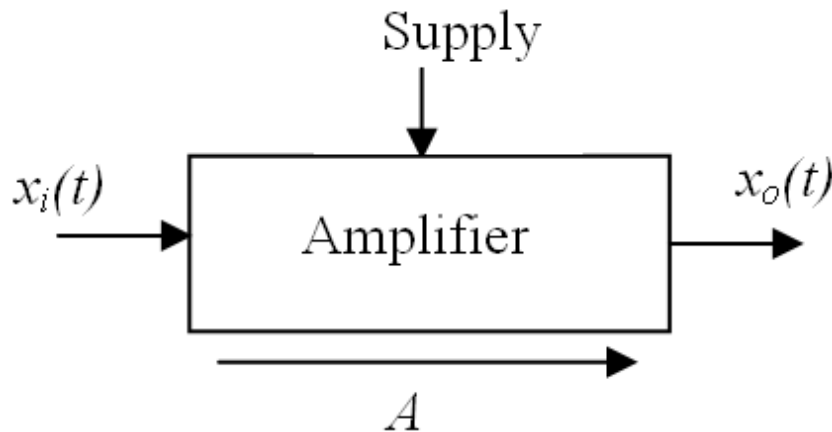Amplifier = active three-port network that delivers an output signal $x_o(t)$ (voltage or current) with the **same shape** as the input signal $x_i(t)$ and can provide **more power**, on an adequate load.



$$x_o(t) = Ax_i(t)$$

A – amplification, gain

$A < 0$ inverting


$A > 0$ non-inverting

Linear circuit: x_o proportional with x_i


➤ Types of supply

The supply is provided by dc voltage and/or current sources. Voltage sources are most commonly used.

Single source supply

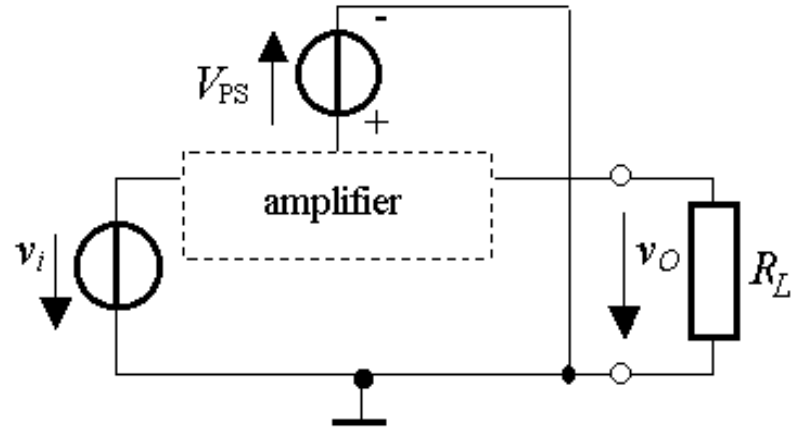

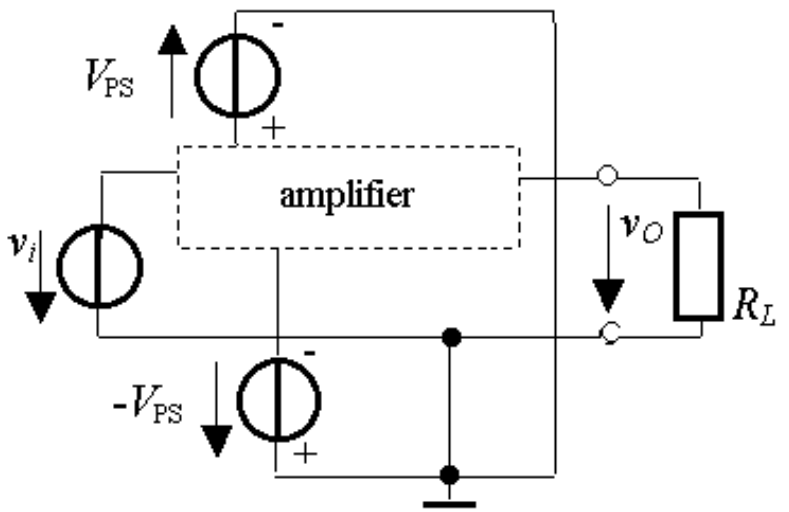Two source supply (symmetric differential)




➤ Power transfer and power balance

The average power of the output signal is **greater than** the average power of the input signal:

$$P_{out} > P_{in}$$

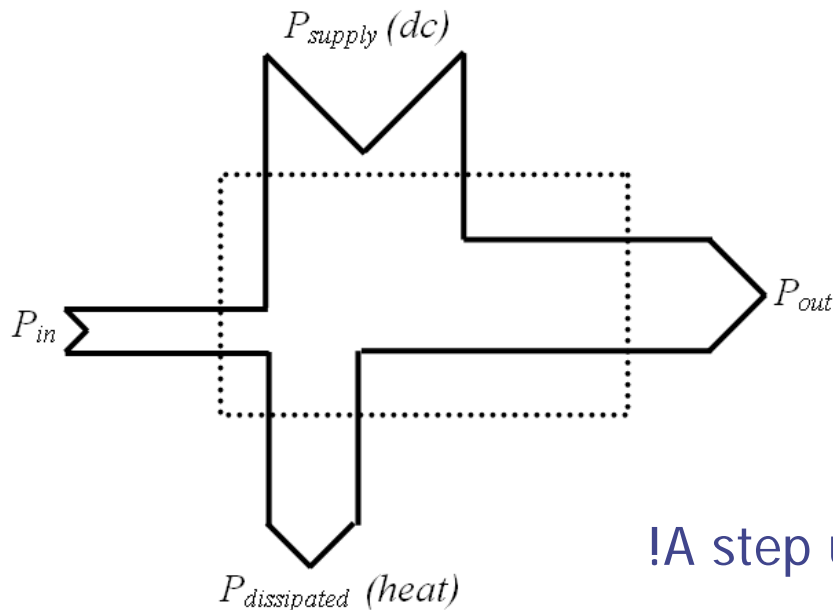The excess of the output power is taken **from the supply sources**.



$$P_{supply} + P_{in} = P_{out} + P_{dissip}$$

$$P_{supply} \approx P_{out} + P_{dissip}$$

$$\text{Efficiency: } \eta = P_{out} / P_{supply}$$

!A step up transformer **is not** an amplifier!

➤ Types of amplifiers

Based on the types of input/output signals (voltage/current):

- voltage amplifier $A_v = v_o/v_i$ - dimensionless
- current amplifier $A_i = i_o/i_i$ - dimensionless
- transconductance amplifier $A_{i/v} = i_o/v_i - [S], [mS]$
- transresistance amplifier $A_{v/i} = v_o/i_i - [\Omega], [k\Omega]$


➤ VTC

voltage-to-voltage, non-inverting amplifier, symmetric differential supply

- amplification (active) region:

$$v_I \in \left(\frac{V_{OL}}{A_v}; \frac{V_{OH}}{A_v} \right);$$

$$v_O \in (V_{OL}; V_{OH})$$

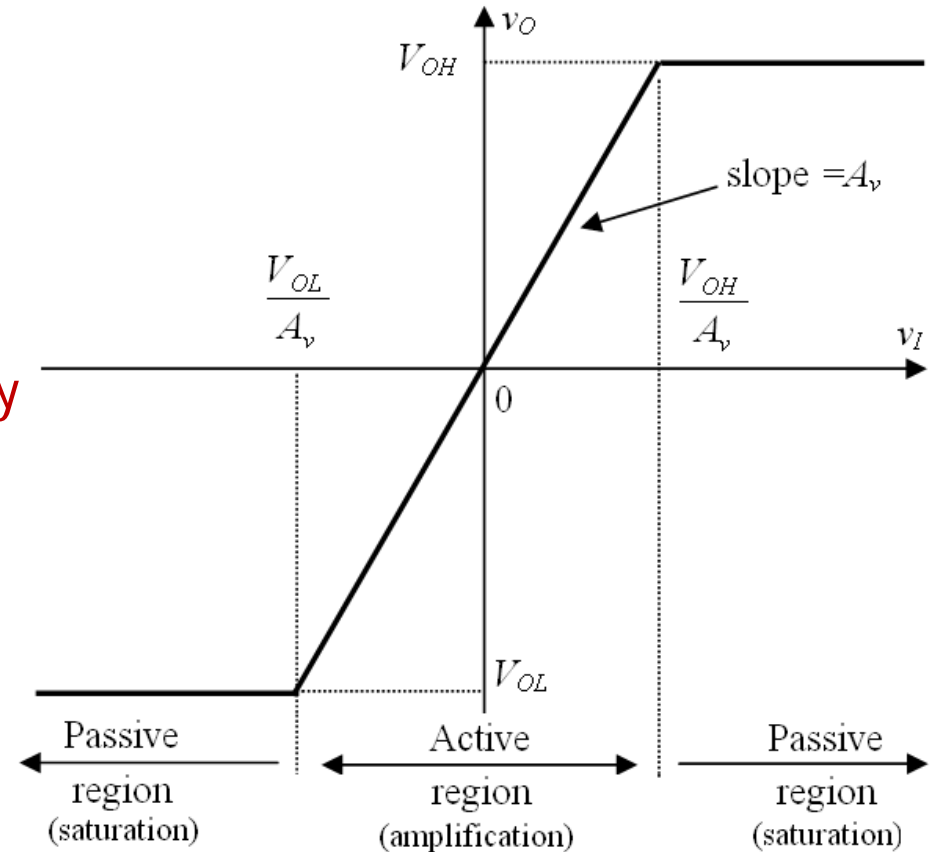


- ideal amplifier: $V_{OL} = -V_{PS}; V_{OH} = +V_{PS}$

- general-purpose OpAmp $v_O \in (-V_{PS} + 1V...2V; +V_{PS} - 1V...2V)$

- rail-to-rail OpAmp: $v_O \in (-V_{PS}; +V_{PS})$

➤ VTC

Signal transfer

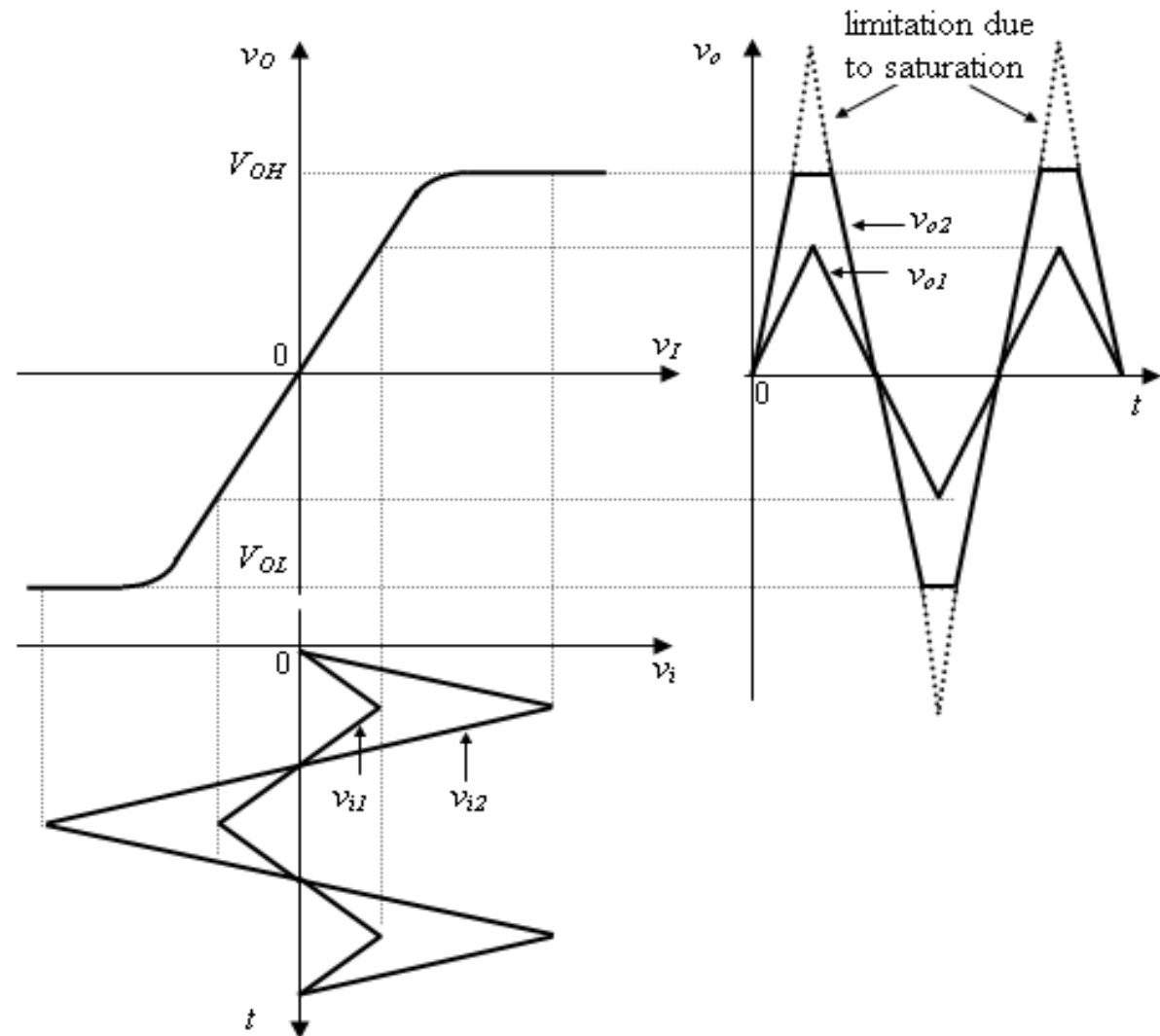

Note: if the input signal is low enough for the amplifier to work in a linear region around the OP: **small signal approximation**

➤ Modeling the voltage amplifier


- **two-port** networks: only the behavior of the **input** and **output** ports is explicitly taken into account, and the **input-output signal transfer**
- valid **regardless of the internal complexity** of the amplifiers
- valid in the **bandpass** frequency domain

Linear controlled sources

- active two-port network
- only one finite, non-zero parameter: forward transfer parameter (gain)
- the output signal is **controlled** by the input signal
- pseudo-sources


VCVS (voltage controlled voltage source)

$$v_O = a_v v_i$$

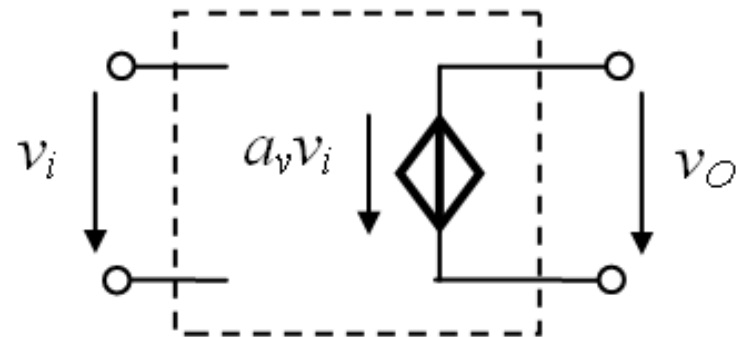

➤ Modeling the voltage amplifier


Amplifier model

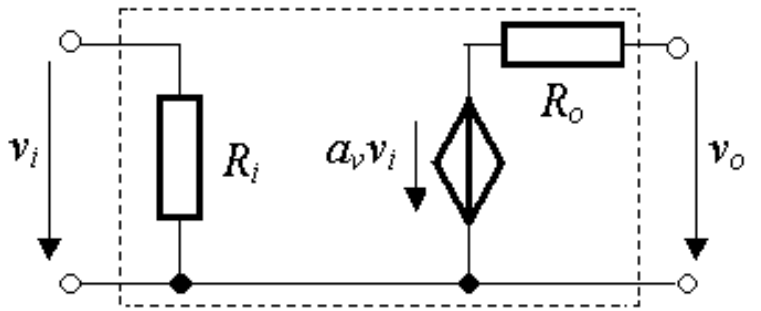

$$a_v = \frac{v_o}{v_i}$$

a_v – open circuit gain
 R_i – draws current from v_i
 R_o – deteriorates v_o in the presence of load

Amplifier model connected in a circuit

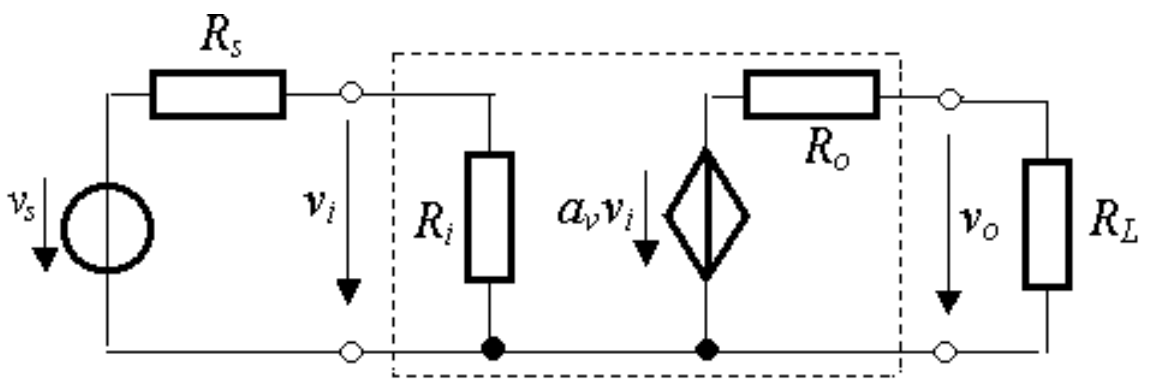


$$A_v = \frac{v_o}{v_s}$$

$$A_v = \frac{R_i}{R_s + R_i} \frac{R_L}{R_L + R_o} a_v$$

Ideal amplifier?

➤ Modeling the voltage amplifier

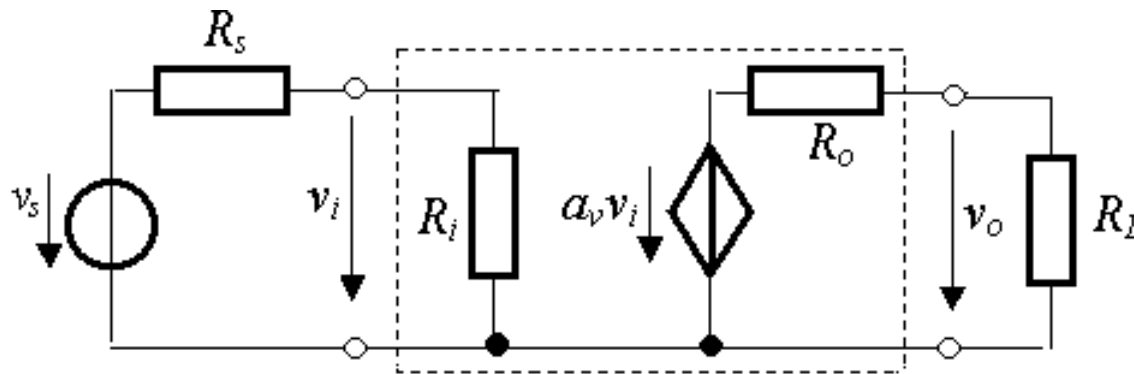

$$A_v = \frac{v_o}{v_s}$$

$$A_v = \frac{R_i}{R_s + R_i} \frac{R_L}{R_L + R_o} a_v$$

A_v is closer to the open circuit gain a_v when the voltage losses at the input (across R_s) and at the output (across R_o) are reduced.

- $R_i \gg R_s$ – the source voltage is transferred to the input

$$v_i \approx v_s$$

- $R_o \ll R_L$ – the voltage of the VCVS is transferred to the output

$$v_o \approx a_v v_i$$

Ideal voltage amplifier: $R_i = \infty$; $R_o = 0$


➤ Amplifier performances

▪ Gain (forward transfer factor)

- Analyze the circuit, by using circuit theorems and equation (Kirchhoff, Ohm, Millman)
- Express the output signal as a function of the input signal, then compute the gain

▪ Input resistance

$$R_i = \frac{v_i}{i_i}$$

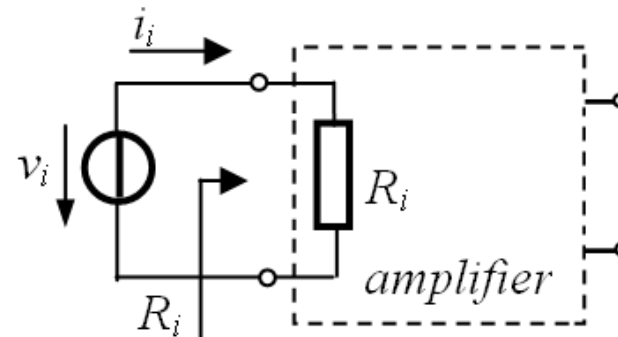


➤ Amplifier performances

■ Output resistance



- Set the input signal source to zero
- Connect a test source at the output

#1

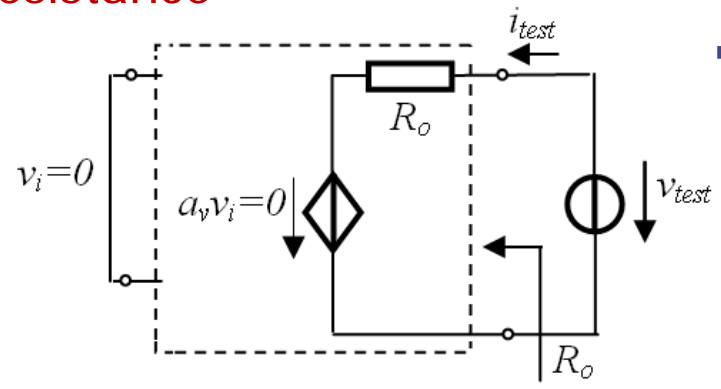

$$R_o = \frac{v_{test}}{i_{test}}$$

#2

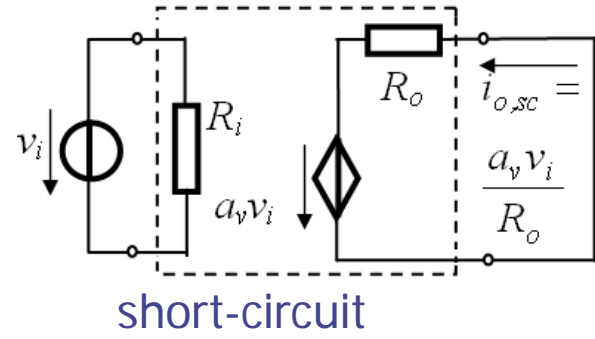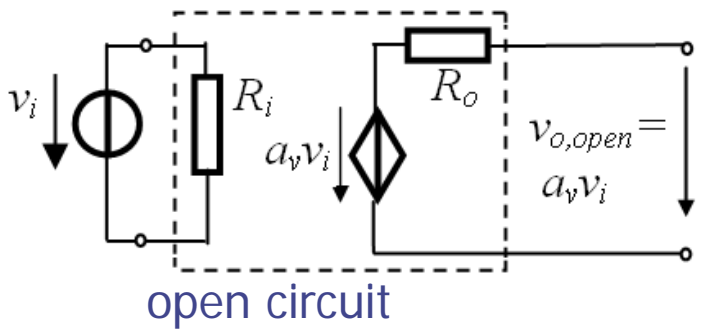


$$R_o = \frac{v_{o,open}}{i_{o,sc}}$$

➤ Frequency response

- analyze the equivalent model of the amplifier including capacitive components too, by means of their complex impedances: $1/j\omega C$

- complex transfer function for the gain: $A(j\omega) = \frac{v_o(j\omega)}{v_i(j\omega)}$

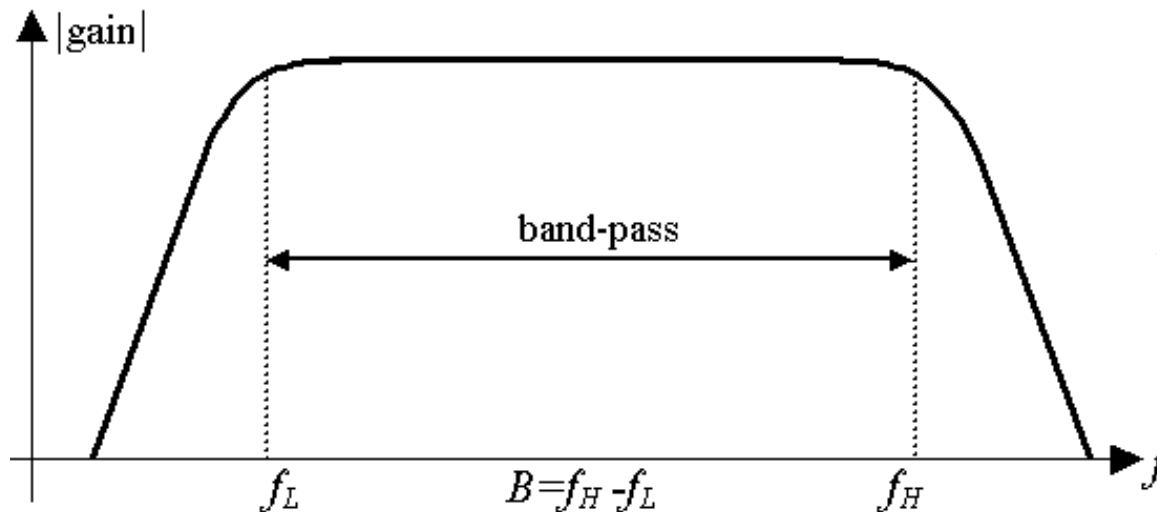
- input and output impedances are now complex $Z_i(j\omega)$ $Z_o(j\omega)$



Band-pass amplifier

Why does the gain decrease at low/high frequencies?

➤ Frequency response

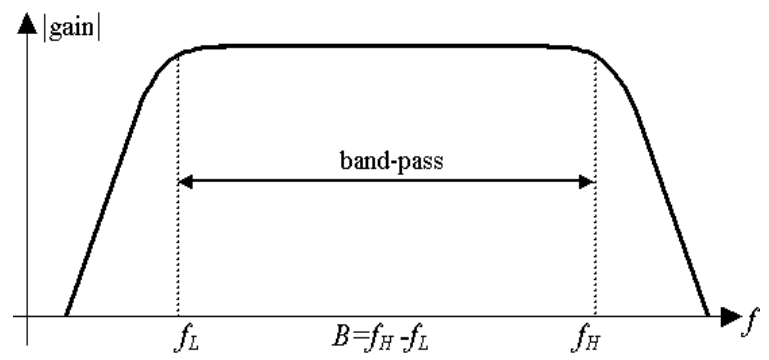


internal capacitances (parasitic) of active devices


$\Rightarrow Av \searrow @ f \nearrow$

coupling/decoupling capacitors (tens of μF)

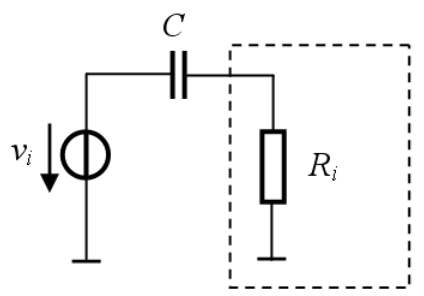$\Rightarrow Av \searrow @ f \searrow$ (zero dc gain)




capacitive coupling at input

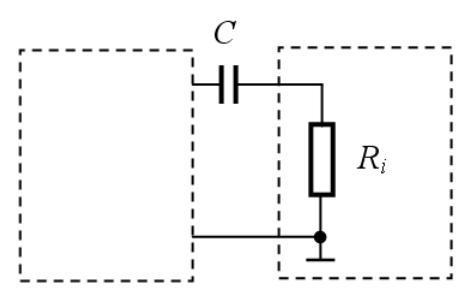


capacitive coupling of two amplifier stages

Direct coupling amplifier (LPF)

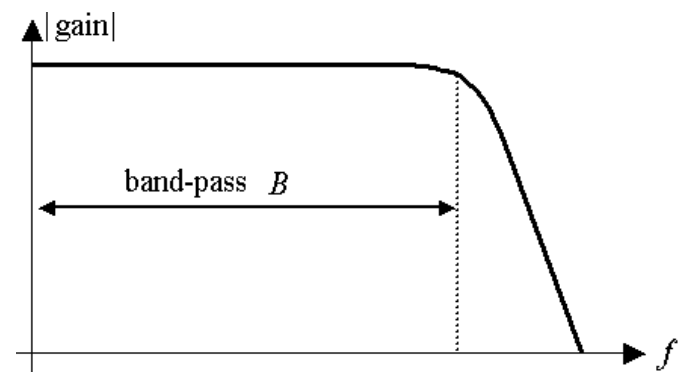

Amplifiers with OpAmp

$$v_O = a v_D = \infty \cdot v_D$$

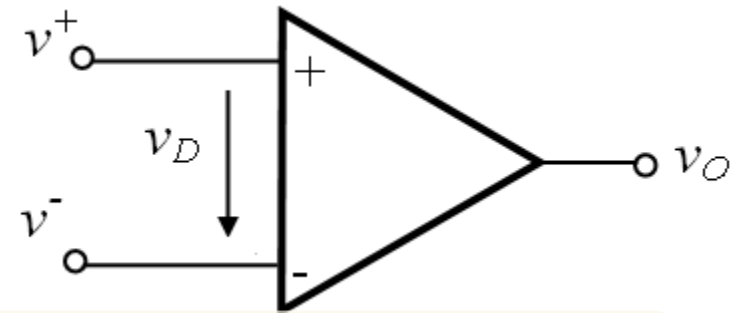

I. Utilization as **comparator**, in switching mode

$$v_O \in \{V_{OL}; V_{OH}\}$$

C6 + C7

$v_D > 0$, $v_O \rightarrow +\infty$, v_O limited by the positive supply $v_O = V_{OH} \approx +V_{PS}$

$v_D < 0$, $v_O \rightarrow -\infty$, v_O limited by the negative supply $v_O = V_{OL} \approx -V_{PS}$


II. Utilization as **amplifier**

$$v_O \in (V_{OL}; V_{OH})$$

It is mandatory that $v_D = 0$, so then $v_O = a \cdot v_D = \infty \cdot 0$ - indetermination

v_D is kept at 0 by means of external components (R) arranged in a negative feedback **(NF)** configuration

Amplifiers with OpAmp

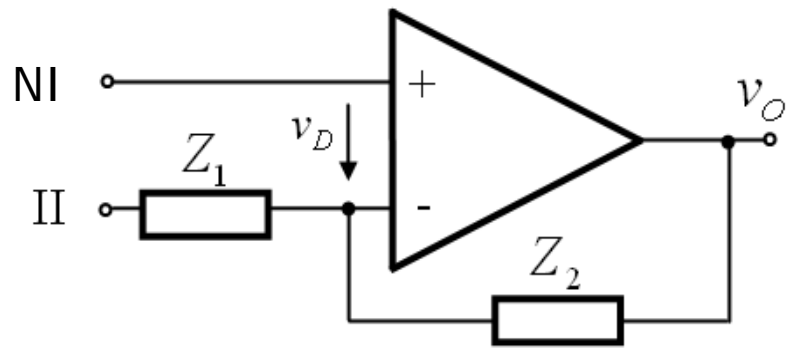


$$v_O = a v_D$$

$v_D = 0$ $v_D \uparrow$, $v_O \uparrow$, $v^- \uparrow$, $v_D \downarrow$

NF automatically keeps v_D at zero

NI	II	Amplifier
v_1	ground	non-inverting
ground	v_1	inverting
V_{I1}	V_{I2}	differential


➤ Non-inverting amplifier

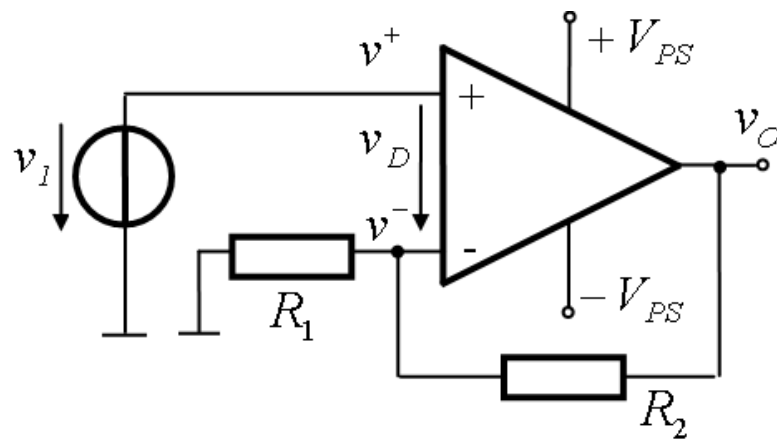

$$v^- = \frac{R_1}{R_1 + R_2} v_O$$

$$v_D = v^+ - v^- = v_I - \frac{R_1}{R_1 + R_2} v_O = 0$$

$$v_I = \frac{R_1}{R_1 + R_2} v_O$$

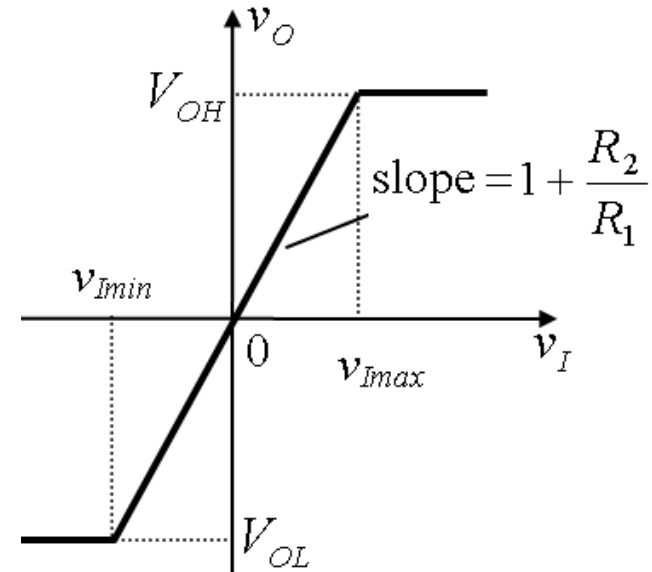

$$A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$


➤ Non-inverting amplifier

Alternative method for computing A_v

$$\left. \begin{array}{l} v_D = 0 \\ v^+ = v_I \end{array} \right\} \Rightarrow v^- = v_I$$

The same current goes through R_1 and R_2
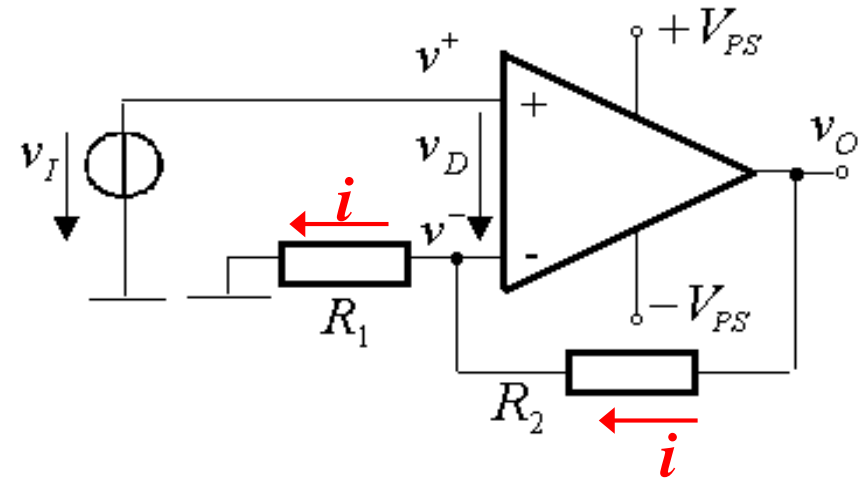
$$\frac{v_I}{R_1} = \frac{v_O - v_I}{R_2} \quad A_v = \frac{v_O}{v_I} = 1 + \frac{R_2}{R_1}$$




Direct consequences of NF for an OpAmp with very high intrinsic gain ($a \rightarrow \infty$ for ideal op-amp):

- gain is set only by the **ratio of two resistors** (external components)
- the gain value: **precise and stable**
- the gain is **independent of the OpAmp**, it is not influenced by the technological spread of the OpAmp's parameters

➤ Non-inverting amplifier

Input and output resistances

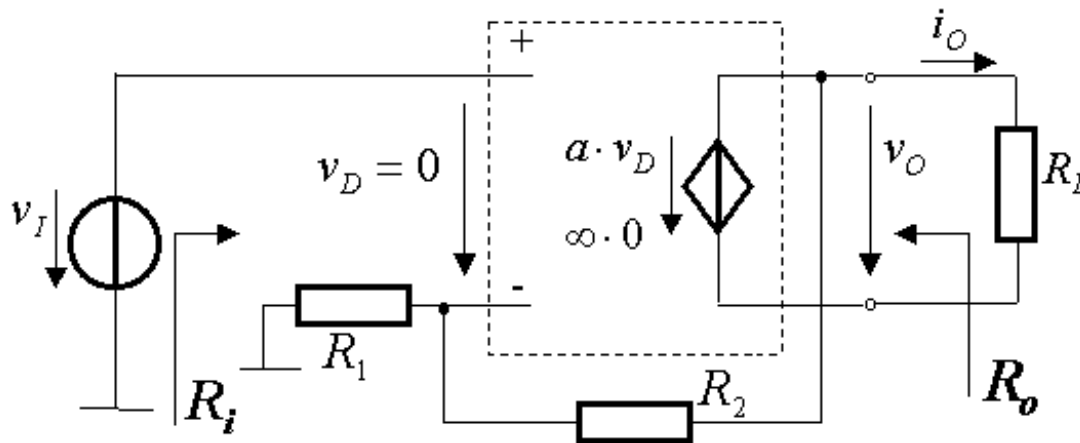





Computed on the equivalent model

v_i sees an open circuit, so $R_i = \infty$

$$R_o = \frac{v_{O_{open}}}{i_{O_{sc}}} = \frac{v_{O_{open}}}{\infty} = 0$$

➤ Non-inverting amplifier



Example

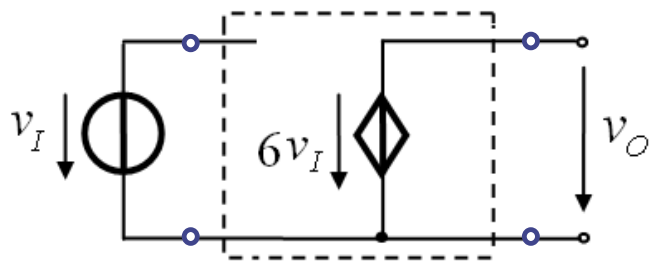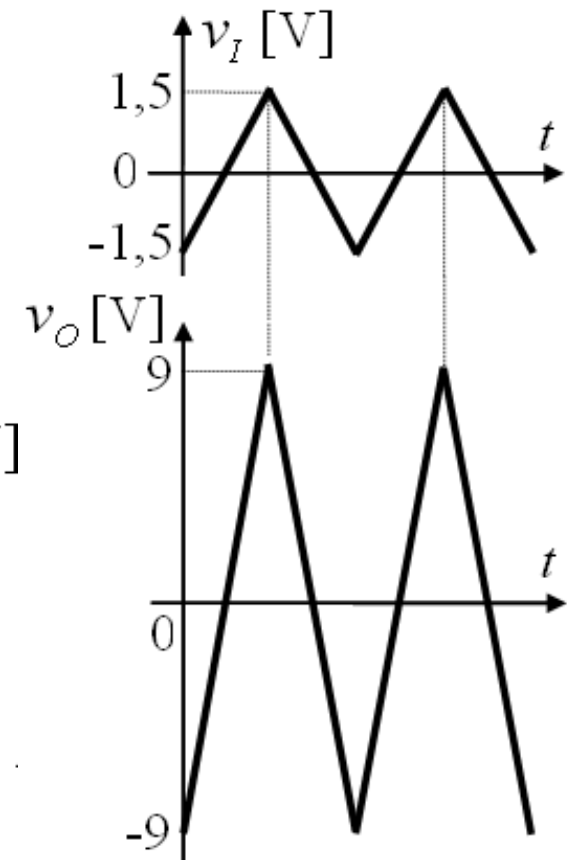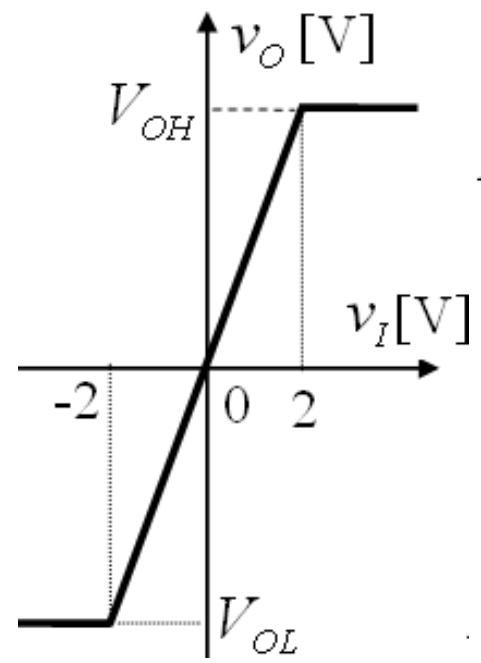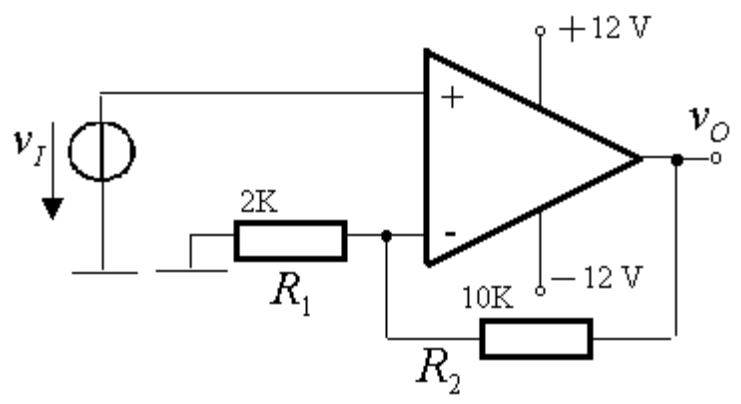

- $v_o(t)$ for triangular $v_i(t)$, 3 V amplitude, zero dc component


➤ Non-inverting amplifier

Adjustable gain

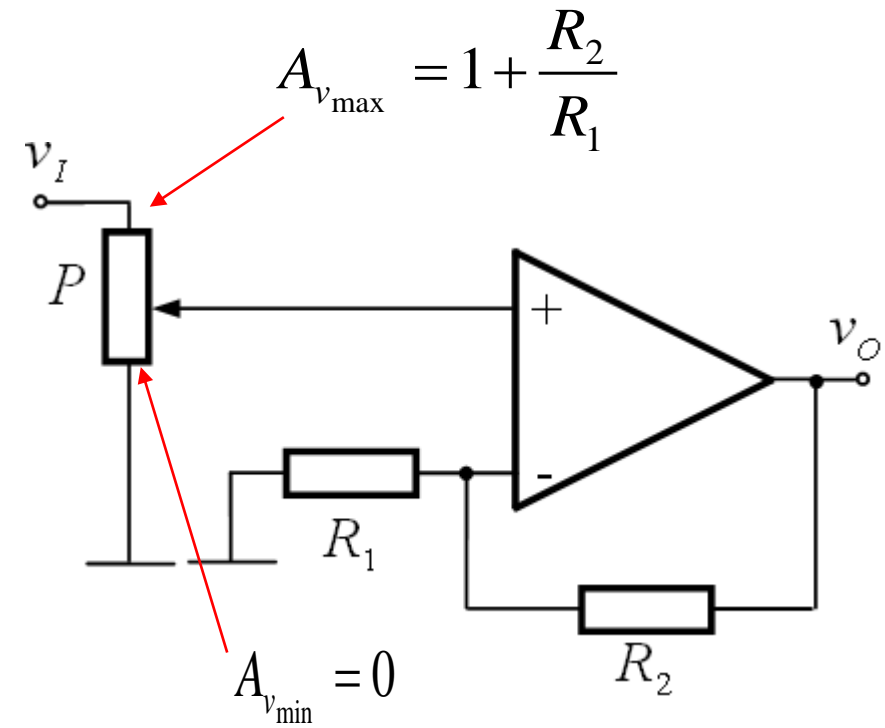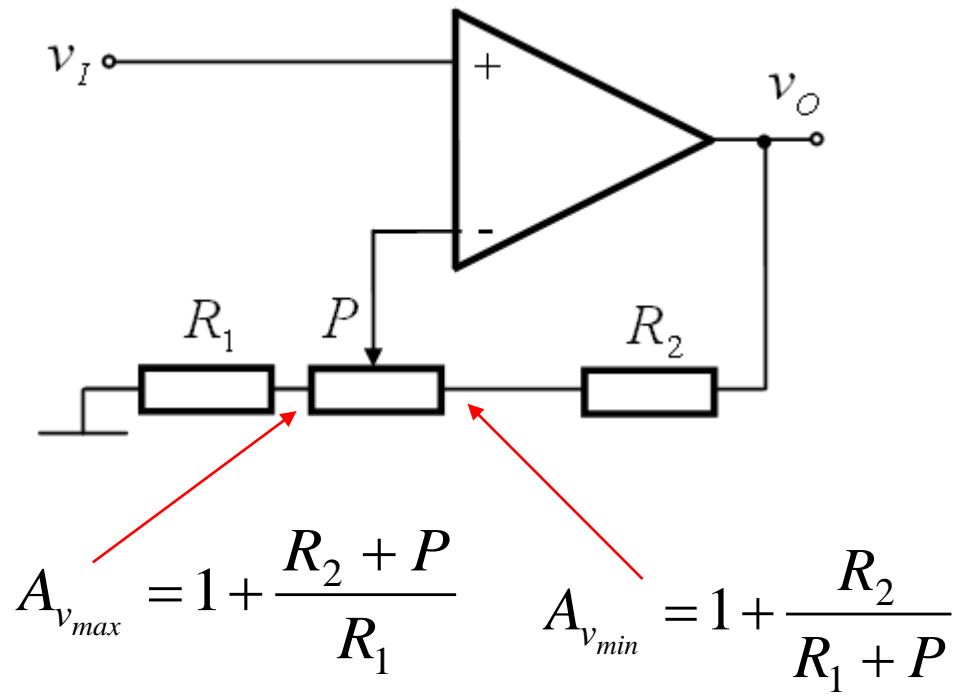

➤ Non-inverting amplifier

Voltage follower

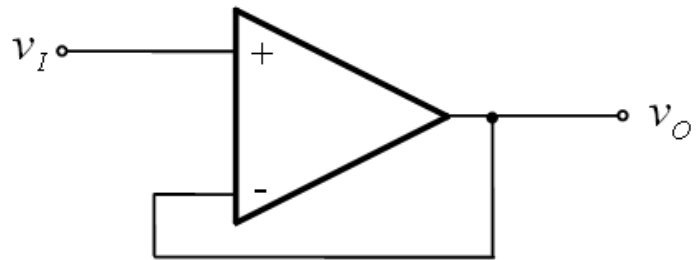


$$v_O = v_I$$

the output voltage **follows**
the input voltage

- total (full) NF
- no voltage gain ($A_v = 1$)
- infinite current gain ($A_i = \infty$)

Voltage followers are used as a **buffer stages** between a source (or the output of a circuit) with **high R_O** (can only supply low current) to a **low R_L** (needs high current) – impedance matching.


➤ Inverting amplifier

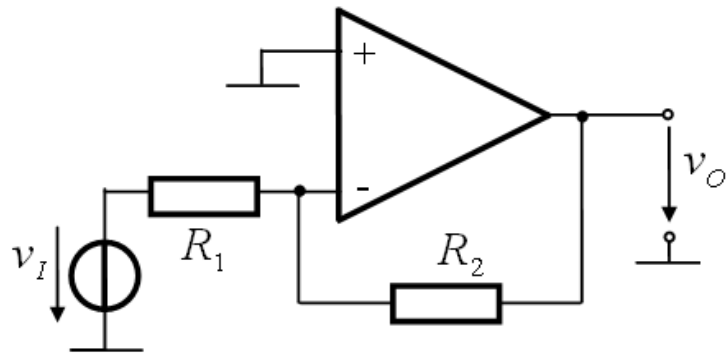

$$v^+ = 0$$

$$v^- = \frac{R_2}{R_1 + R_2} v_I + \frac{R_1}{R_1 + R_2} v_O$$
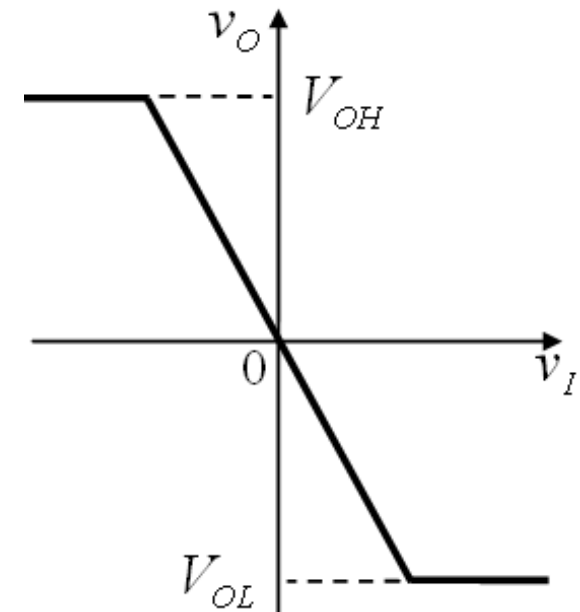
$$v_D = v^+ - v^- = 0 - \frac{R_2}{R_1 + R_2} v_I - \frac{R_1}{R_1 + R_2} v_O = 0$$



$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$

➤ Inverting amplifier

Alternative method for computing A_v

$$\text{NF} \Rightarrow v_D = 0$$


$$\begin{aligned} v^+ &= v^- \\ v^+ &= 0 \end{aligned} \Rightarrow v^- = 0$$

virtual ground

$$i_1 = i_2 \quad i_1 = \frac{v_I - 0}{R_1} \quad i_2 = \frac{0 - v_O}{R_2}$$


$$\frac{v_I}{R_1} = -\frac{v_O}{R_2}$$
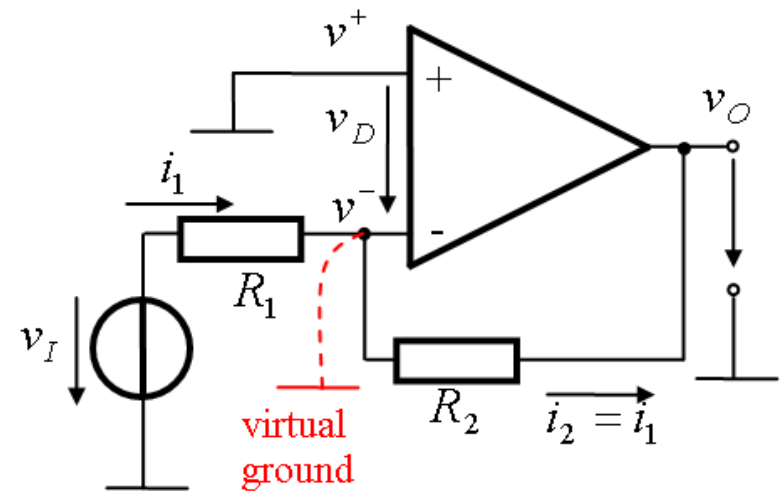
$$A_v = \frac{v_O}{v_I} = -\frac{R_2}{R_1}$$



➤ Inverting amplifier

Input and output resistances

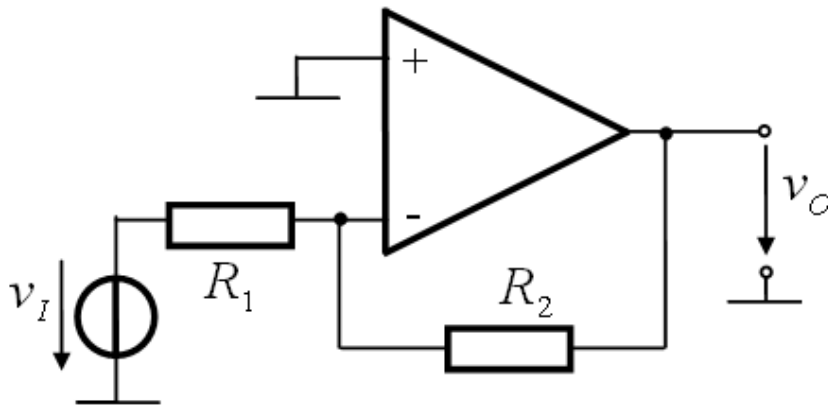

The input source “sees” only R_1 (the inverting input is virtual ground)

$$R_i = R_1$$


$$R_o = 0$$

- Noninverting amplifier: $R_i \rightarrow \infty$
- Inverting amplifier: $R_i \rightarrow$ finite (units, tens of $k\Omega$)

➤ Inverting amplifier

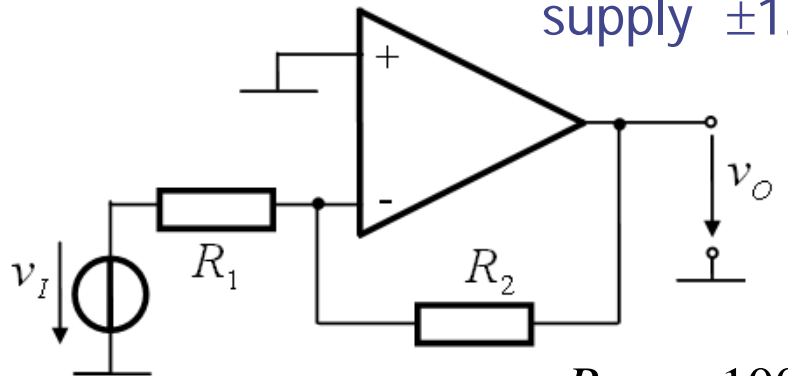Example


$R_1 = 10\text{ K}$, $R_2 = 100\text{K}$,
supply $\pm 12\text{ V}$




$$R_i = R_1 = 10\text{k} \quad A_v = -\frac{R_2}{R_1} = -\frac{100}{10} = -10$$

$$R_o = 0$$

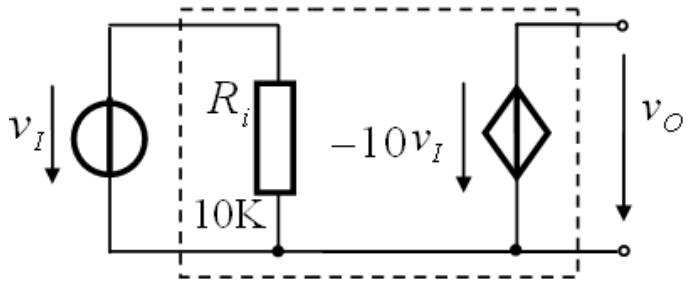v_i range: $(-1.2\text{V}; +1.2\text{V})$




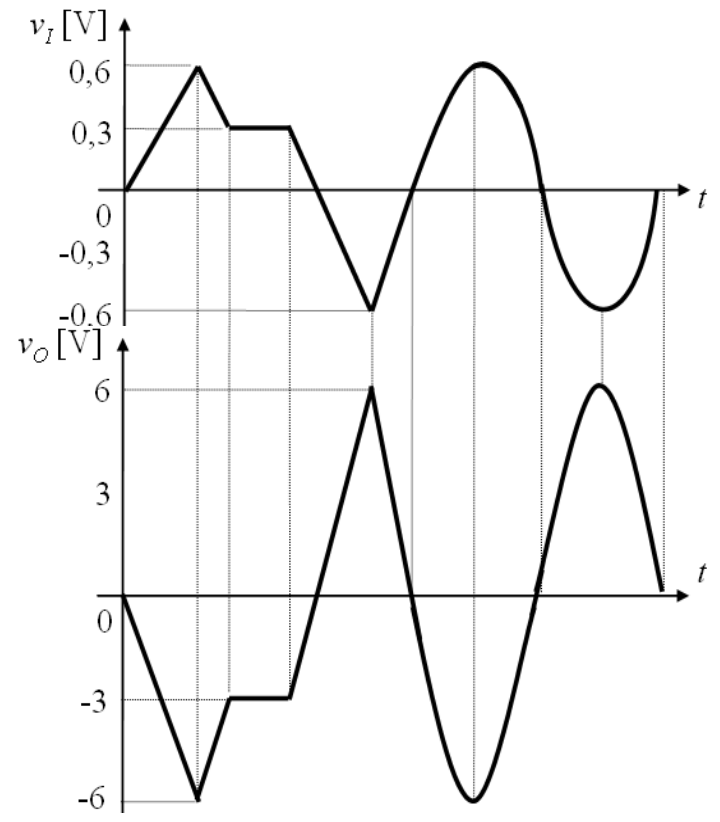- ✓ R_i , R_o , A_v
- ✓ v_i range for active region
- ✓ equivalent model



➤ Inverting amplifier


Voltage follower

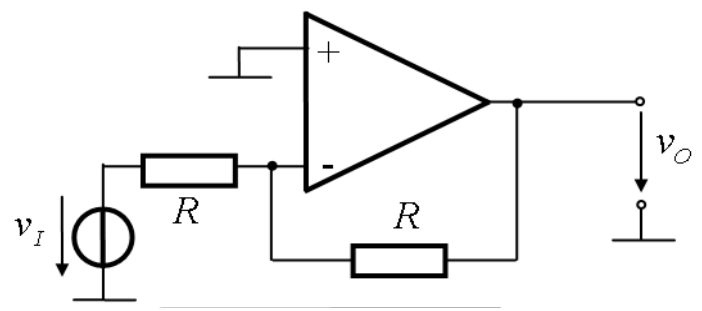

$$v_O = -v_I$$


$$A_v = \frac{v_O}{v_I} = -1$$

$$R_i = R$$

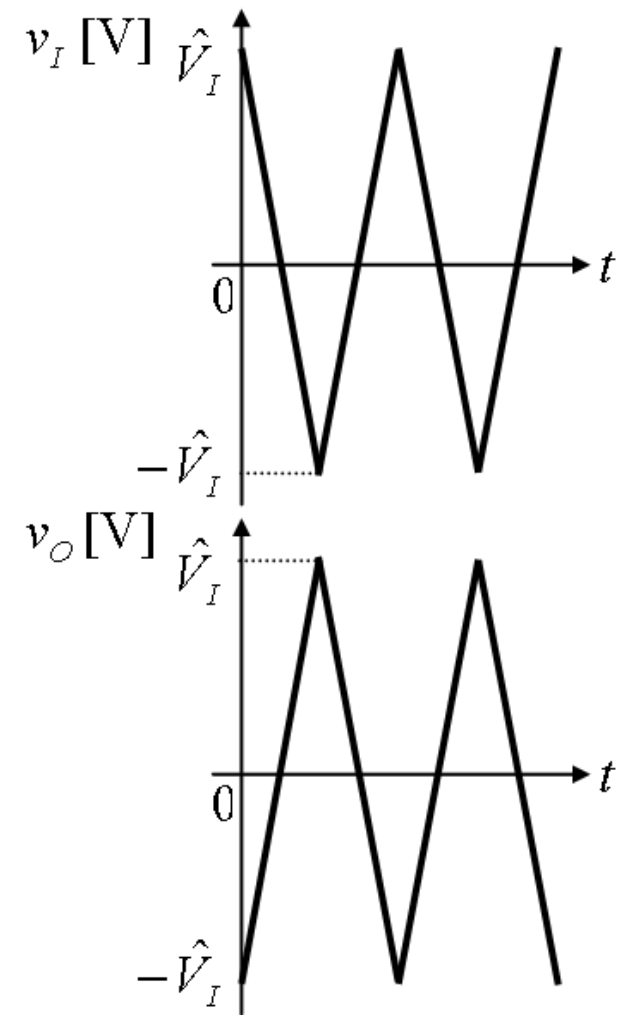

➤ Design example

Design an inverting amplifier with $R_i > 8 \text{ k}\Omega$ and $|A_v|$ adjustable in the range $[10, 18]$.

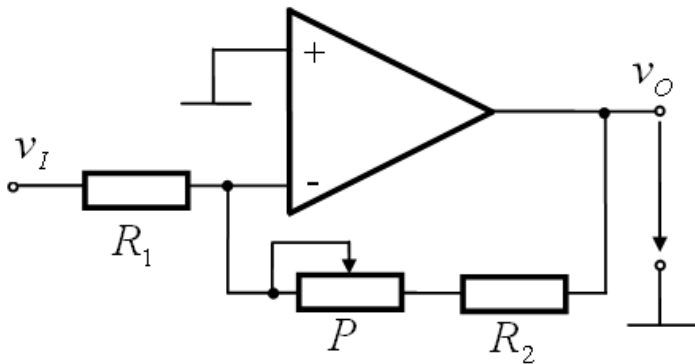

$$|A_v|_{\min} = \frac{R_2}{R_1} = 10$$

$$|A_v|_{\max} = \frac{R_2 + P}{R_1} = 18$$

$$R_2 = 10R_1 \quad R_2 + P = 18R_1$$

What next?

➤ Design example

Design an inverting amplifier with $R_i > 8 \text{ k}\Omega$ and $|A_v|$ adjustable in the range $[10, 18]$.

$$R_2 = 10R_1 \quad R_2 + P = 18R_1$$

Solution 1

$$R_i = R_1 \geq 8 \text{ k}\Omega \quad \text{Choose} \quad R_1 = 10 \text{ k}\Omega$$

$$P = 18 \cdot 10 - 100 = 80 \text{ k}\Omega$$

$$R_2 = 10 \cdot 10 = 100 \text{ k}\Omega$$

$P = 100 \text{ k}\Omega$ will be used. Keeping $R_2 = 100 \text{ k}\Omega$ will result in:

$$R_1 = \frac{R_2 + P}{18} = \frac{100 + 100}{18} = 11,1 \text{ k}\Omega$$

$$R_2 = 100 \text{ k}\Omega \quad P = 100 \text{ k}\Omega$$

$$\text{Verification:} \quad |A_v|_{\min} = 9.1 \quad |A_v|_{\max} = 18 \quad \text{Acceptable?}$$

➤ Design example

Design an inverting amplifier with $R_i > 8 \text{ k}\Omega$ and $|A_v|$ adjustable in the range $[10, 18]$.

$$R_2 = 10R_1 \quad R_2 + P = 18R_1$$

Solution 2

Select $P = 100 \text{ k}\Omega$

$$\begin{cases} R_2 = 10R_1 \\ R_2 + 100 \text{ k} = 18R_1 \end{cases} \quad \begin{cases} R_1 = 12.5 \text{ k}\Omega \\ R_2 = 125 \text{ k}\Omega \end{cases}$$

$$R_i = R = 12.5 \text{ k}\Omega > 8 \text{ k}\Omega$$

Verification: $|A_v|_{\min} = 10 \quad |A_v|_{\max} = 18$

What if we began w/
 $P = 10 \text{ k}\Omega$?

OPTIONAL

➤ High gain and high input resistance

$$R_i = R_1$$


- same current through R_1 and R_{21}
- same voltage across R_3 and R_{21}

$$A_v = \frac{v_O}{v_I} = - \left(\frac{R_{21} + R_{22}}{R_1} + \frac{R_{21}R_{22}}{R_1R_3} \right)$$

For $R_1 = 1\text{k}$, $R_{21} = 10\text{k}$
 $R_{22} = 10\text{k}$, $R_3 = 0.1\text{k}$

$$A_v = - \left(\frac{10 + 10}{1} + \frac{10 \cdot 10}{1 \cdot 0.1} \right) = -1020$$

$$R_i = 1\text{k}$$

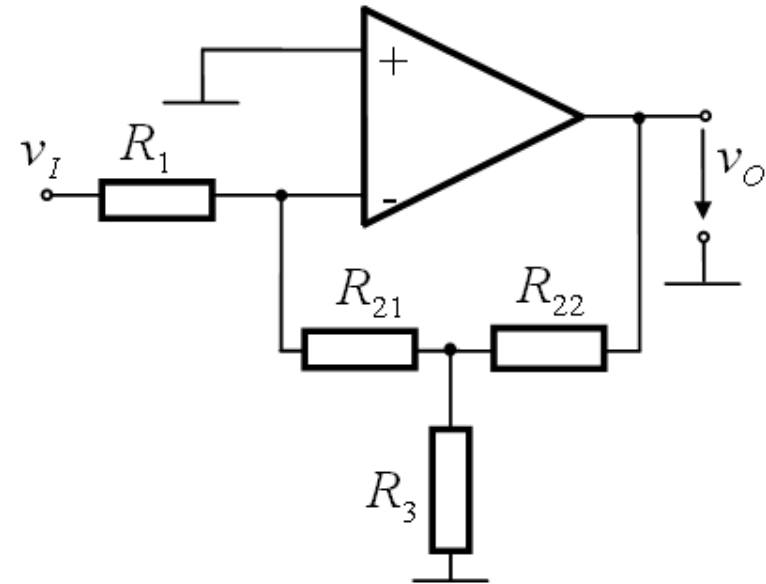

Summary

The *little black bug* (OpAmp) is also able to make:

- Amplifiers with OpAmp
 - Non-inverting amplifiers
 - Inverting amplifiers

Next week: Summing and differential amplifiers with OpAmp.

To do: Homework 6