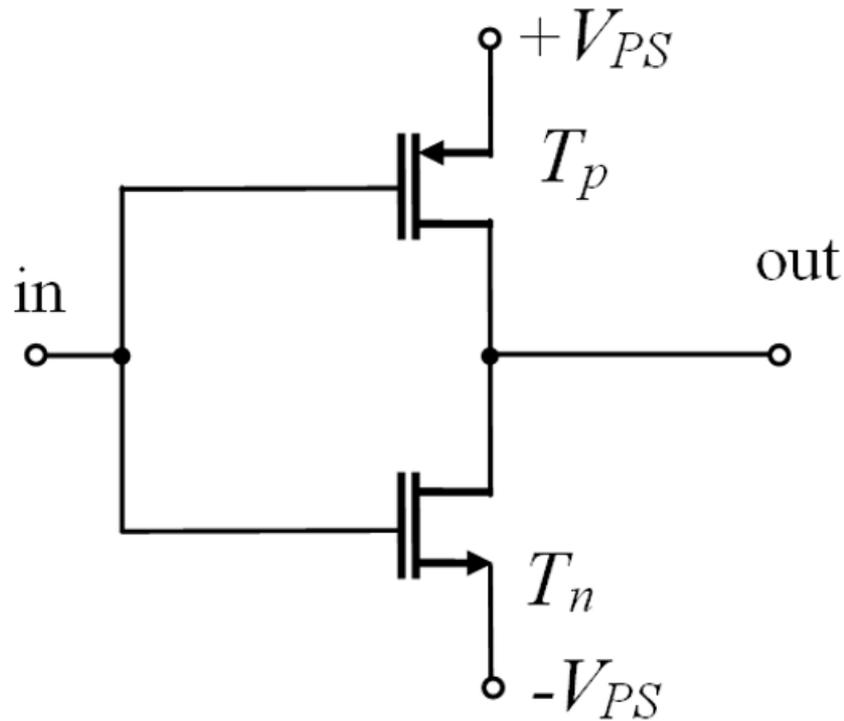


Class D Power Amplifiers


- A Class D amplifier is a **switching amplifier** based on pulse-width modulation (**PWM**) techniques
- Purpose: high efficiency, 80% - 95%.
- The reduction of the power dissipated by the amplifying transistors is due to the switching operation mode
- Increase in efficiency and reduction of the physical dimensions of the heatsink
- Class D amplifiers are involved in portable equipment, battery operated equipment, equipment with space constraints, etc.

Amplifying (power) stage

- The amplifying transistors are complementary, operating in switching mode (logic inverter)
- **Current gain**



Block Diagram. Operation Principle


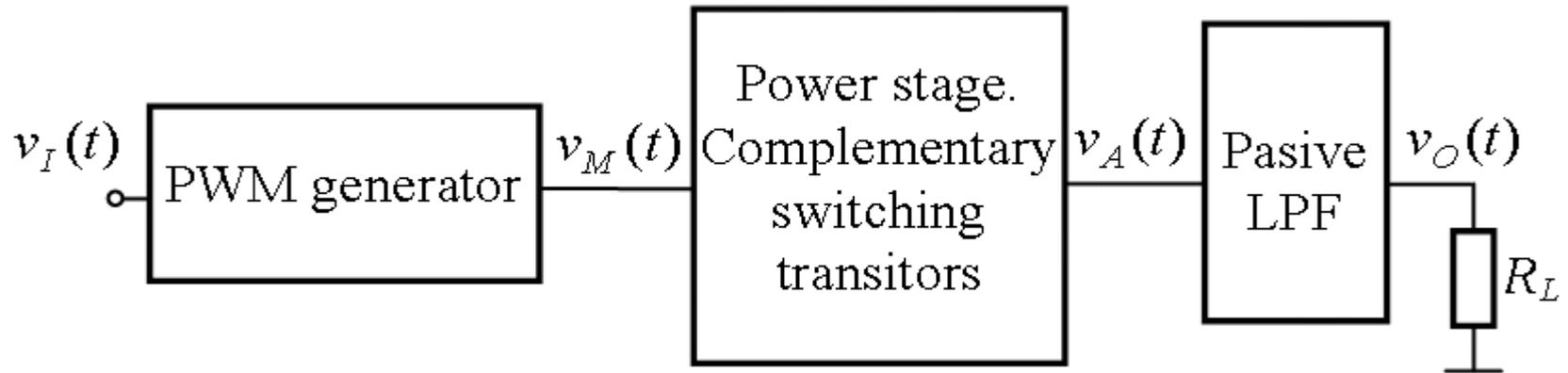


- The input signal (v_I) is converted into a pulse-width-modulated (PWM) signal (v_M) with a much higher frequency (switching frequency).
- v_M has a constant period but variable duty-cycle, modulated by the instantaneous value of the input signal.

Reconstruction of the useful signal



LP filtering: the fundamental frequency is extracted from the amplified PWM signal (v_A) while the switching frequency and superior harmonics and components are removed.

PWM Generator

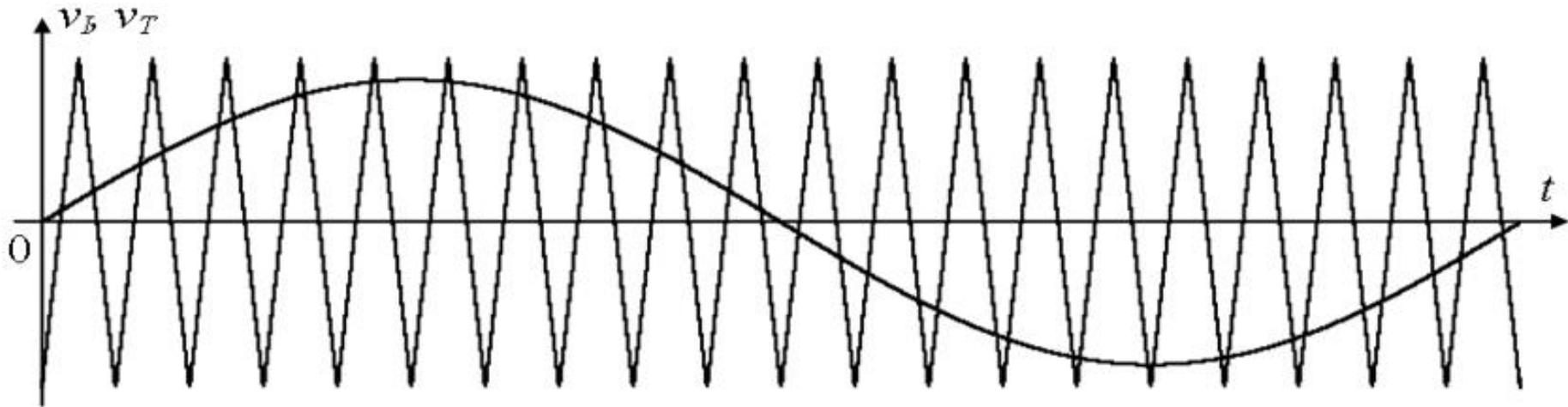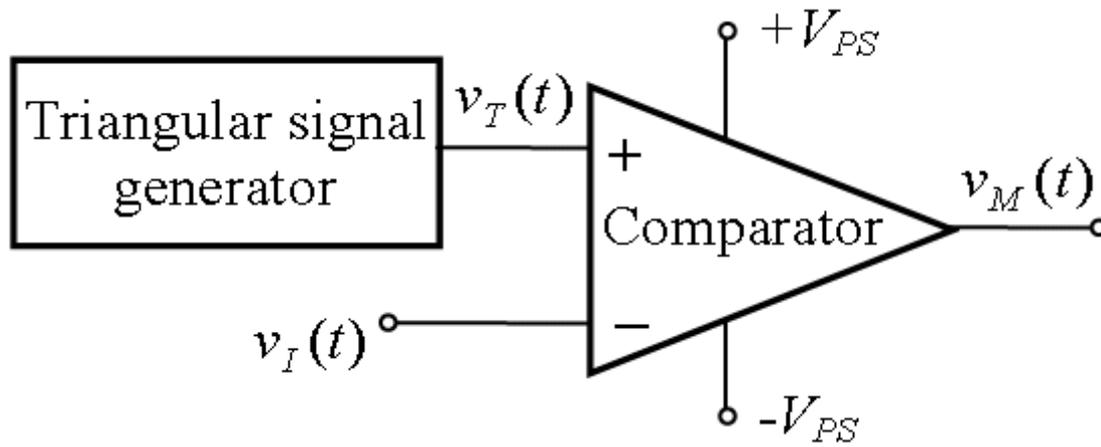


$v_M(t)$?

PWM Generator

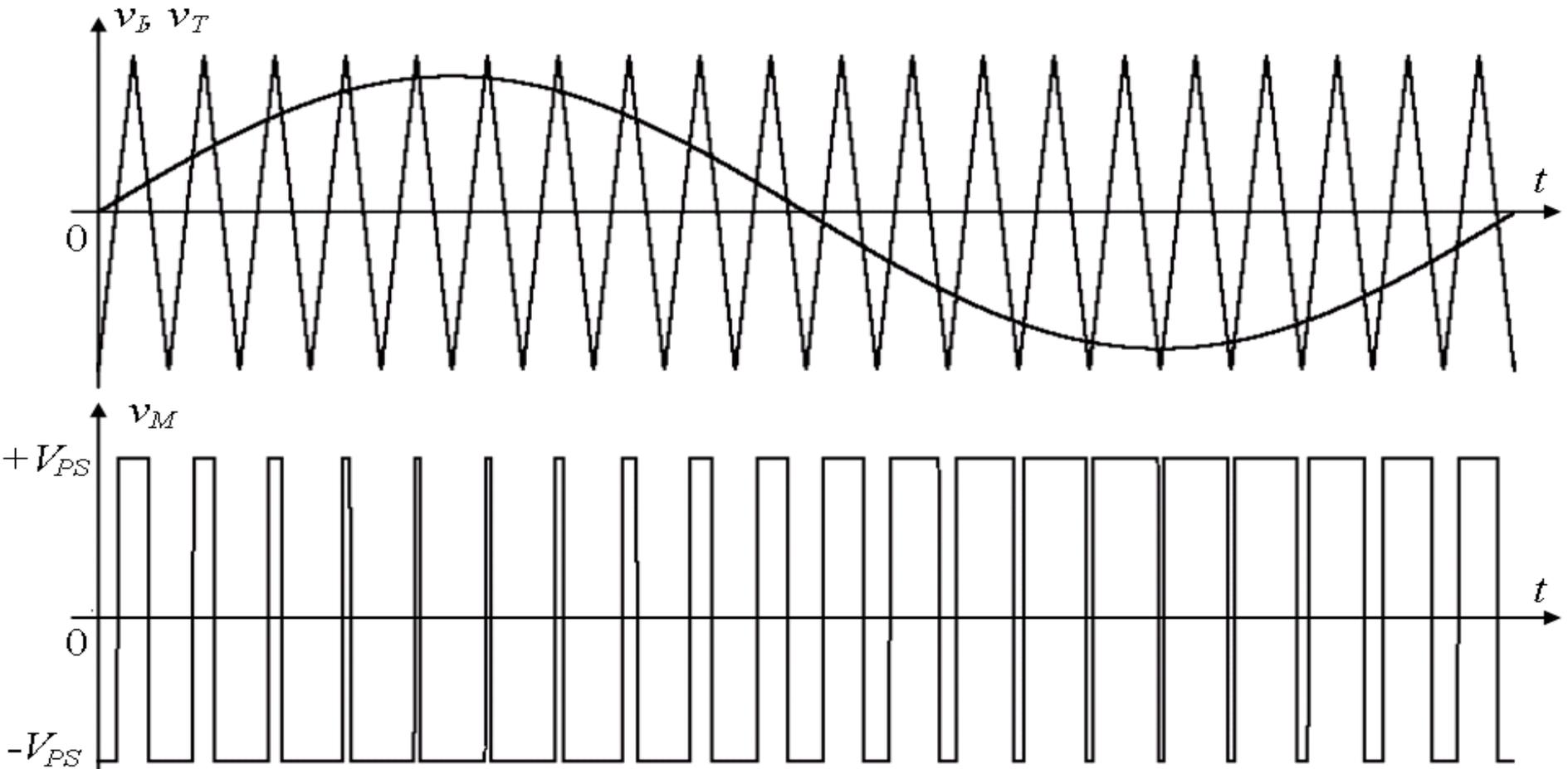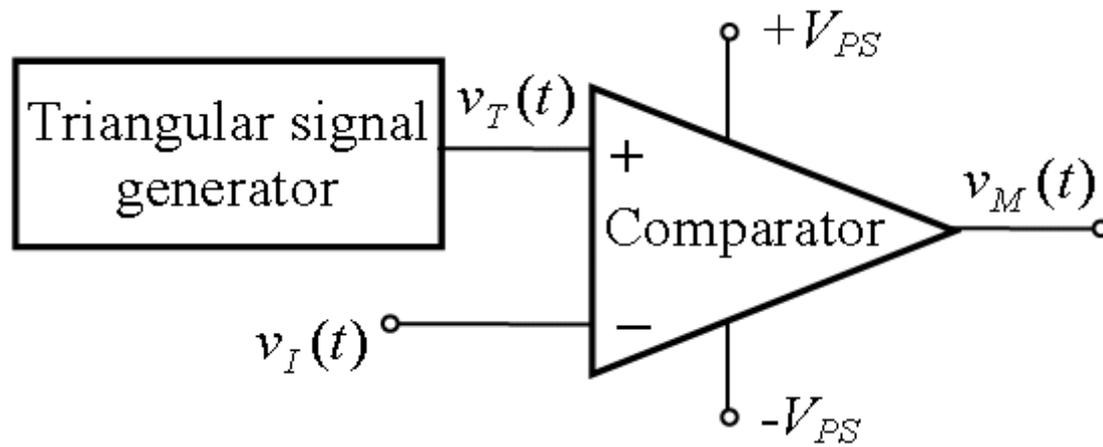

Power stage

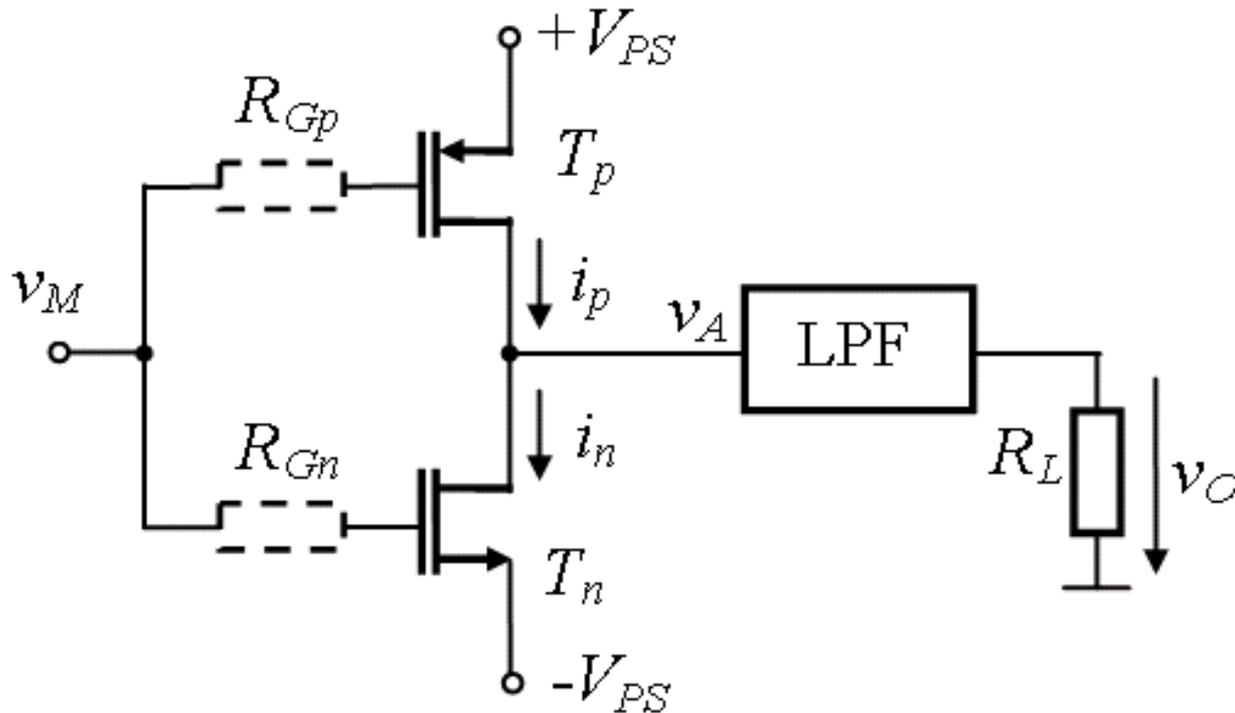

$$v_{M_L} = -V_{PS} \quad T_p \text{ (on), } T_n \text{ (off)} \quad v_A = +V_{PS}$$

$$v_{M_H} = +V_{PS} \quad T_p \text{ (off), } T_n \text{ (on)} \quad v_A = -V_{PS}$$

Inverting current amplifier


Each transistor commutation happens in a finite time.

During the commutation there is some (small) power dissipation across the transistors.

At the frequencies of the input signal, the equivalent LPF impedance should be sufficiently low (zero).

- The **conducting transistor can not be turned off instantaneously**; some time is necessary to turn off the transistor.
- There is a time interval when **both transistors are on**. A high current pulse flows between supply sources, through the conducting transistors.
- This (large) current pulse can lead to transistor failure.

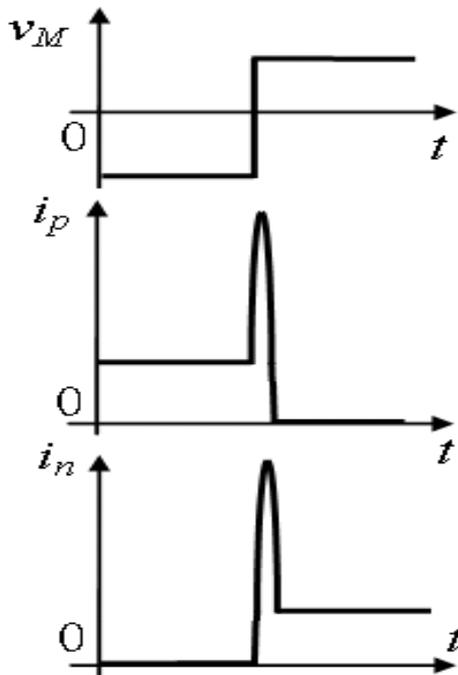
Solution: The control signal for (off) \rightarrow (on) must be delayed in comparison with the control signal for (on) \rightarrow (off)



Current commutation for

T_p : (on) \rightarrow (off)

T_n : (off) \rightarrow (on)

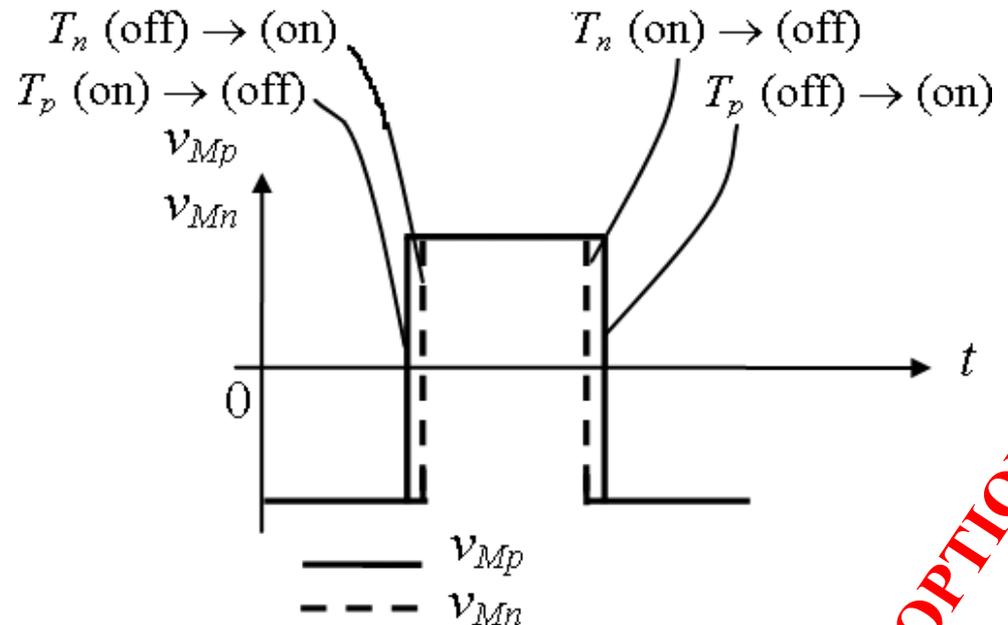


Control of the transistors using different control signals

OPTIONAL

Frequency Spectrum

The frequency spectrum of the pulse-width-modulated signals contains: input signal frequency (f_i), switching frequency (f_T), and harmonics:

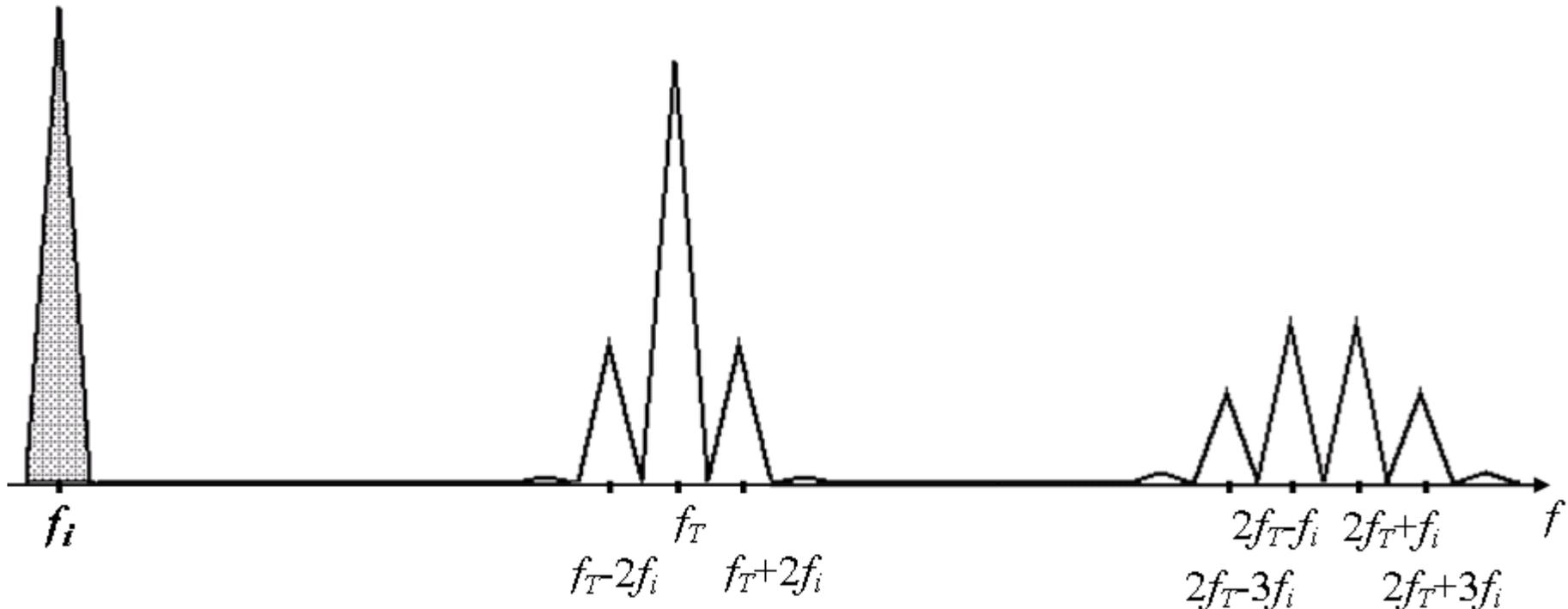
$$f_i, f_T, f_T \pm 2f_i, 2f_T \pm f_i, 2f_T \pm 3f_i$$



A LPF should be used to remove the switching frequency and harmonics, thus reconstructing the amplified signal

Low Pass Filter

A single stage, second order LC filter

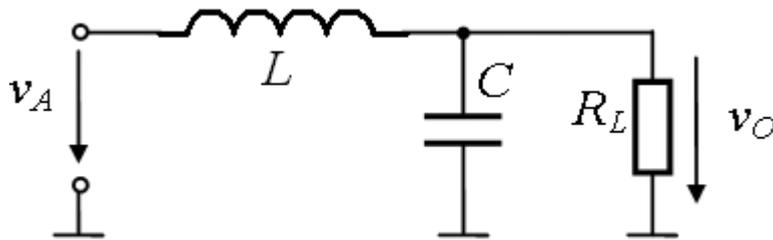

$$F(j\omega) = \frac{v_O(j\omega)}{v_I(j\omega)} = \frac{1}{1 + j\omega LC \frac{1}{R_L C} + (j\omega)^2 LC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \omega_0 R_L C$$

$$F(j\omega) = \frac{1}{1 + j \frac{\omega}{\omega_0} \frac{1}{Q} + \left(j \frac{\omega}{\omega_0} \right)^2}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Greater than the frequency of useful signal to avoid its attenuation


The filter should highly attenuate the f_T frequency

$$f_0 < (1/10) f_T \quad \text{For at least 40dB attenuation at } f_T$$

Switching frequency should be at least 10 times greater than the maximum signal frequency.

$Q=0.707$ provides a frequency response that introduces -3dB at corner frequency.

Class D Power Amplifier - Example

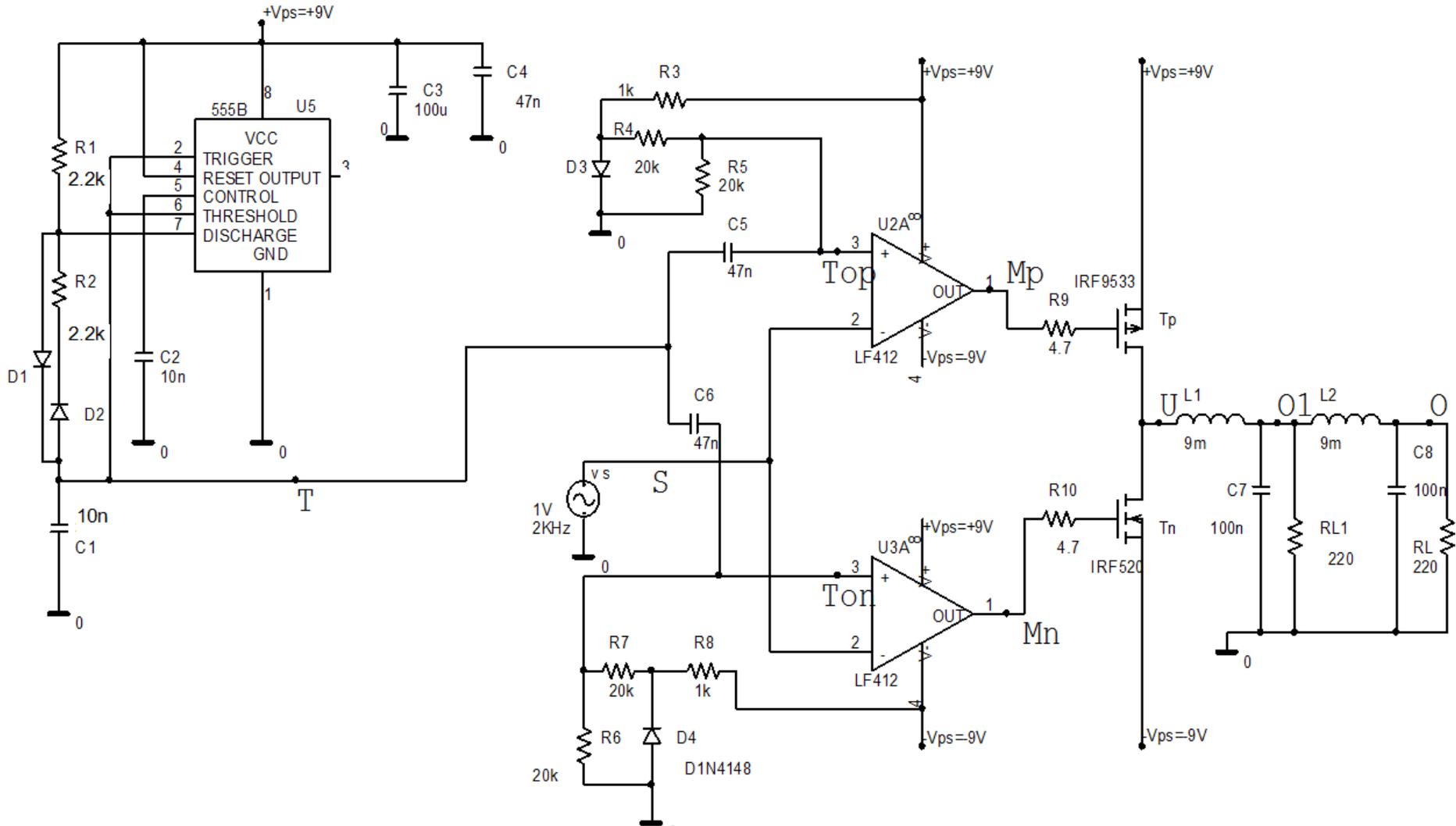

Specialised Integrated Circuits

- **LX1721/1722: Class-D Stereo Power Amplifier Controller**
 - controlere pentru amplificatoare audio în clasă D, stereo; conține toate componentele pentru comanda tranzistoarelor etajului de putere.
- **LX1725 : 15W X 2 30W BTL CLASS-D AUDIO AMPLIFIER**
 - amplificator audio de putere în clasă D cu două canale. Poate fi utilizat atât ca amplificator stereo cât și ca amplificator mono în configurație punte. Puterea maximă este de 15Wx2 (configurația stereo) și 30W (punte), pe sarcină de 8Ω. Randamentul este de peste 90%. Etajul de putere (tranzistoare MOS) este integrat în circuit, în exterior se mai conectează doar filtrul LC și difuzoarele. Principale aplicații: televizoare, CD/DVD Combo Player, sisteme Home theater, sistem audio pentru calculatoare, etc.
- **LX1708: 15W+15W STEREO FILTERLESS CLASS-D AMPLIFIER**
 - amplificator audio CMOS în clasa D, 15Wx2 stereo ce nu necesită filtrare. Este optimizat pentru funcționare cu eficiență maximă la cost minim. Utilizează trei niveluri de modulare PWM, ceea ce permite eliminarea filtrului. Principale aplicații: televizoare, sisteme de navigare pentru automobile, sisteme audio pentru calculatoare, sisteme de sunet portabile, etc.