

BUCK AND BUCK-BOOST DC-DC CONVERTERS

I. OBJECTIVES

- a) To visualize the waveforms for the voltages and currents from the dc-dc converter circuits (Buck and Buck-boost).
- b) To determine the parameters of the output voltages for the dc-dc converters.

II. COMPONENTS AND INSTRUMENTATION

We use the experimental assembly from Fig. 3, equipped with an IRF9130 transistor (enhanced p – channel MOS transistor), a diode, an inductor, resistors and capacitors of different values. The positive voltage supply is applied from a dc voltage supply, and the command voltage is obtained from the signal generator. We use a dual channel oscilloscope to visualize the signals, and a multimeter to measure the dc values.

III. PREPARATION

P1. Buck converter (Step – down)

The output voltage of the Buck converter is lower than the input voltage.

- For the circuit in Fig.1, supplied with $V_I=10V$, controlled with a rectangular signal v_{cmd} from the function generator, with an amplitude of 10V, frequency 33KHz and a duty cycle $\delta=50\%$, draw the waveforms of the following signals:

- $v_I(t)$, $v_{cmd}(t)$, $v_{D3}(t)$, $v_O(t)$;
- $i_I(t)$, $i_{D3}(t)$, $i_{L1}(t)$, $i_{C1}(t)$.

- Write the relationship between V_O and V_I and find the value of V_O for $V_I=10V$ and duty cycle $\delta=50\%$. The duty cycle is computed as $\delta=T_L/T$, where T_L represents the time during which the control signal is 0V (control transistor M1 is in conduction state) and T is the period of the signal.

P2. Buck-Boost converter (Step – down/step – up)

The output voltage of a Buck – Boost converter has an inverted polarity compared with the input voltage.

- For the circuit in Fig. 2, supplied with $V_I=10V$, controlled with a rectangular signal v_{cmd} from the function generator, with an amplitude of 10V, frequency 20KHz and a duty cycle $\delta=50\%$, draw the waveforms of the following signals:

- $v_I(t)$, $v_{cmd}(t)$, $v_{L2}(t)$, $v_O(t)$;
- $i_I(t)$, $i_{D3}(t)$, $i_{L2}(t)$, $i_{C2}(t)$.

- Write the relationship between V_O and V_I and find the value of V_O for $V_I=10V$ and duty cycle $\delta=50\%$.

IV. EXPLORATIONS AND RESULTS

1. Buck converter

1.1. Waveforms

Exploration

- Supply the circuit in Fig.1 with $V_I=10V$ and connect a load resistance $R_{L1}=50\Omega$. You will do this by connecting $J2$ with $J3$, $J4$ with $J5$, $J7$ with $J8$, $J11$ with $J12$ and $R1$ closed.

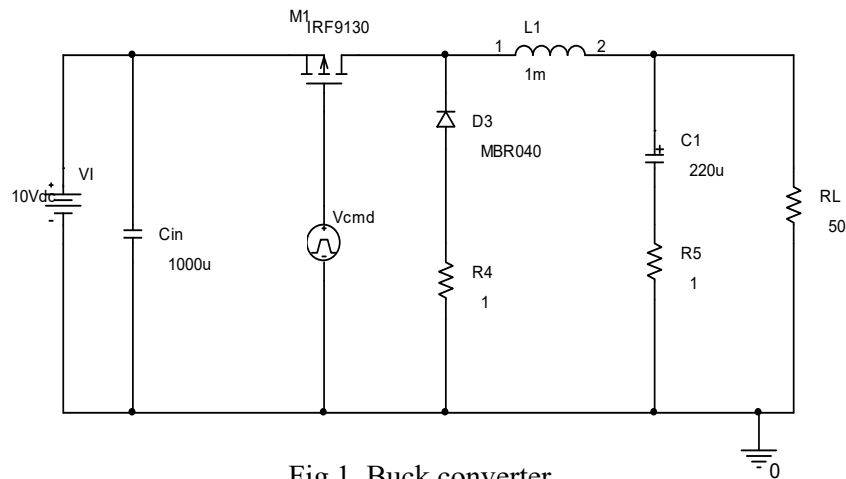


Fig.1. Buck converter

- In the gate terminal of the control transistor M_1 , apply a rectangular signal v_{cmd} from the function generator, with an amplitude of 10V, frequency 33KHz and a duty cycle $\delta=50\%$.

- Visualize the waveforms of the following signals:
 - the control voltage $v_{cmd}(t)$ and the voltage on R_4 , $v_{R4}(t)$, between $J13$ and GND (R_4 acts like a current transducer for $i_{D3}(t)$);
 - the control voltage $v_{cmd}(t)$ and the voltage on R_5 , $v_{R5}(t)$ between $J14$ and GND (R_5 acts like a current transducer for $i_{C1}(t)$);
 - the control voltage $v_{cmd}(t)$ and the output voltage $v_o(t)$. The output voltage is measured between OUT and GND , for $J14$ connected to the ground.

Results

- Draw the waveforms for $v_{cmd}(t)$, $v_o(t)$, $v_{L2}(t)$, $i_{RL}(t)$, $i_{C1}(t)$, $i_{L1}(t)$, $i_{D3}(t)$ and $i_I(t)$.

1.2. Verifying the relationship between the input and the output voltage

Exploration

- Visualize the control voltage $v_{cmd}(t)$ and the output voltage $v_o(t)$, for $R_{L1}=50\Omega$ and compute V_o/V_I .
- Modify the value of the input voltage and the amplitude of the control voltage to 8V. Measure once again the output voltage and the variation of the output voltage, Δv_o , and recompute V_o/V_I .

Results

- The value of V_o/V_I for $V_I=10V$.
- The value of V_o/V_I for $V_I=8V$.

1.3. Variation of the output voltage ripple Δv_o with load resistance

Exploration

- For the circuit in Fig.1. with R_{L1} apply once again v_{cmd} with a duty cycle $\delta=50\%$. Copy the values for v_o and Δv_o obtained in section 1.2.
- At the output, replace the load resistance R_{L1} with $R_{L2} = 75\Omega$, by disconnecting $R1$ and connecting the jumper on the $R2$ position. Visualize the control and the output voltages, measure the output voltage v_o , as well as the variation of the output voltage, Δv_o .

Results

- The values of V_O and Δv_O for $\delta=50\%$ (copied from section 1.2.)
- Draw the waveforms for $v_{cmd}(t)$ and $v_O(t)$, for R_{L2} .
- The values of V_O and Δv_O for R_{L2} .

2. Buck-Boost converter

2.1. Waveforms

Exploration

- Supply the circuit in Fig.2 with $V_I=10V$ and connect a load resistance $R_{L1}=200\Omega$. You will do this by disconnecting all the jumpers and connecting $J1$ with $J2$, $J5$ with $J6$, $J8$ with $J9$, $J10$ with $J11$ and $R3$ closed.

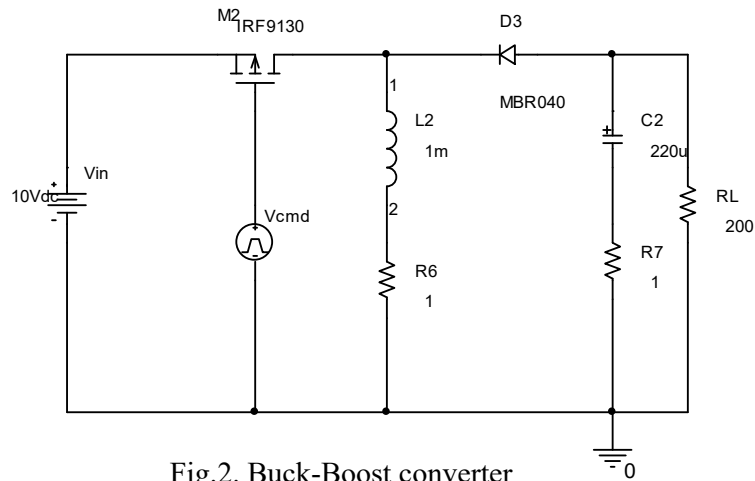


Fig.2. Buck-Boost converter

- In the gate terminal of the control transistor M_2 , apply a rectangular signal v_{cmd} from the function generator, with an amplitude of 10V, frequency 20KHz and a duty cycle $\delta=50\%$.
- Visualize the waveforms of the following signals:
 - the control voltage $v_{cmd}(t)$ and the voltage on R_6 , $v_{R6}(t)$, between $J13$ and GND (R_6 acts like a current transducer for $i_{L2}(t)$);
 - the control voltage $v_{cmd}(t)$ and the voltage on R_7 , $v_{R7}(t)$ between $J14$ and GND (R_7 acts like a current transducer for $i_{C2}(t)$);

- the control voltage $v_{cmd}(t)$ and the output voltage $v_o(t)$. The output voltage is measured between *OUT* and *GND*, for *J14* connected to the ground.

Results

- Draw the waveforms for $v_{cmd}(t)$, $v_o(t)$, $v_{L2}(t)$, $i_{RL}(t)$, $i_{C2}(t)$, $i_{D3}(t)$, $i_{L2}(t)$ and $i_i(t)$.

2.2. Verifying the relationship between the output and the input voltage

Exploration

- Visualize the control voltage $v_{cmd}(t)$ and the output voltage $v_o(t)$, for $R_{L1}=200\Omega$ and compute V_o/V_i .
- Modify the value of the input voltage and the amplitude of the control voltage to 8V. Measure once again the output voltage and the variation of the output voltage, Δv_o , and recompute V_o/V_i .

Results

- The value of V_o/V_i for $V_i=10V$.
- The value of V_o/V_i for $V_i=8V$.

2.3. Variation of the output voltage ripple Δv_o with load resistance

Exploration

- For the circuit in Fig.2 with R_{L1} apply once again v_{cmd} with a duty cycle $\delta=50\%$. Copy the values for v_o and Δv_o obtained in section 2.2.
- At the output, replace the load resistance R_{L1} with $R_{L2} = 250\Omega$, by disconnecting *R3* and connecting the jumper on the *R4* position. Visualize the control and the output voltages, measure the output voltage v_o , as well as the variation of the output voltage, Δv_o .

Results

- The values of V_o and Δv_o for $\delta=50\%$ (copied from section 2.2.)
- Draw the waveforms for $v_{cmd}(t)$ and $v_o(t)$, for R_{L2} .
- The values of V_o and Δv_o for R_{L2} .

REFERENCES

1. Oltean, G., Circuite Electronice, UT Pres, Cluj-Napoca, 2007, ISBN 978-973-662-300-4
2. D. Petreuş, Ş. Lungu - Surse în comutație – îndrumător de laborator, Ed. Mediamira, Cluj-Napoca, 1999.
3. <http://www.bel.utcluj.ro/dce/didactic/fec/fec.htm>

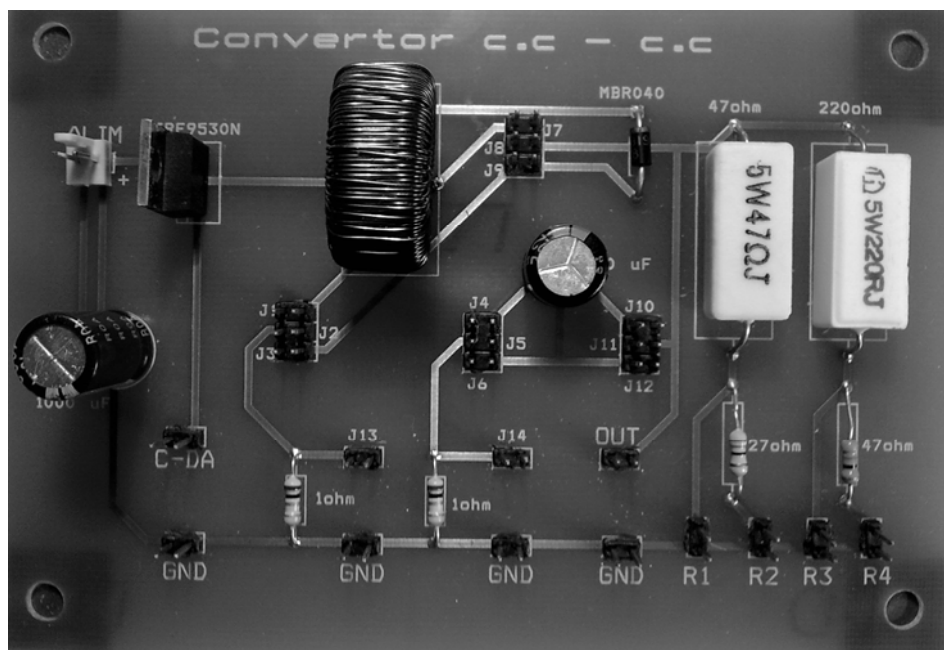


Fig. 3. Experimental assembly