

# MOSFET LOGIC CIRCUITS

## I. OBJECTIVES

- a) Finding out the logic function of some circuits with MOSFET

## II. COMPONENTS AND INSTRUMENTATION

You will use the experimental assembly built with n-channel IRFZ24N MOSFETs and resistors. Because you will apply and measure both dc and ac voltages you will need a dc regulated voltage supply, a signal generator, a digital multimeter and a dual channel oscilloscope

## III. PREPARATION

### 1.P. Logic inverter with MOSFET

The following logic convention is used: the high level of the voltage – “1” logic, the low level of the voltage – “0” logic.

For the n-channel IRFZ24N MOSFET, what is the value of the threshold voltage,  $V_{Th}$ , and of  $\beta$ , according with the datasheet?

#### 1.1.P Logic function

- Find the logic function of the circuit from Fig. 1.

#### 1.2.P VTC

- Plot the VTC  $v_Y(v_A)$  for the circuit in Fig. 1.

### 2.P. NAND logic circuit

- What is the electrical operating table for the circuit in Fig. 2?  $v_A, v_B \in \{0V, 5V\}$ . What are the states (off or extreme conduction) of transistors  $T_A$  and  $T_B$  for all possible combinations of values of  $v_A$  and  $v_B$ ?
- What is the truth table for the circuit in Fig. 2?

### 3.P. AND logic circuit

- What is the electrical operating table for the circuit in Fig. 3?  $v_A, v_B \in \{0V, 5V\}$ . What are the states (off or extreme conduction) of transistors  $T_A$  and  $T_B$  for all possible combinations of values of  $v_A$  and  $v_B$ ?
- What is the truth table for the circuit in Fig. 3?

### 4.P. NOR logic circuit

- What is the electrical operating table for the circuit in Fig. 4?  $v_A, v_B \in \{0V, 5V\}$ . What are the states (off or extreme conduction) of transistors  $T_A$  and  $T_B$  for all possible combinations of values of  $v_A$  and  $v_B$ ?
- What is the truth table for the circuit in Fig. 4?

### 5.P. OR logic circuit

- What is the electrical operating table for the circuit in Fig. 5?  $v_A, v_B \in \{0V, 5V\}$ . What are the states (off or extreme conduction) of transistors  $T_A$  and  $T_B$  for all possible combinations of values of  $v_A$  and  $v_B$ ?
- What is the truth table for the circuit in Fig. 5?

## IV. EXPLORATION AND RESULTS

### 1. Logic inverter with MOSFET

#### 1.1. Logic function

##### Exploration

Build the circuit in Fig. 1.

- At input A, apply a TTL signal with 1kHz frequency obtained from the signal generator.
- Using the calibrated oscilloscope in the Y-t mode you will visualise  $v_A(t)$  and  $v_Y(t)$ .

##### Results

- $v_A(t)$ ,  $v_Y(t)$ .
- The truth table in which A and Y are the input and output logic variables.
- What is the logic function of the circuit?

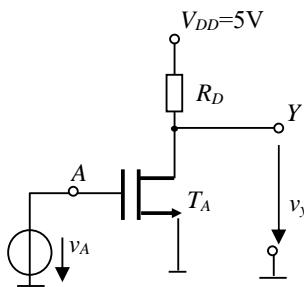


Fig. 1. Logic inverter with MOSFET

#### 1.2. VTC

##### Exploration

Use the circuit in Fig. 1.

- $v_A(t) = 5 \sin(2\pi 1000t)$  [V] [Hz]
- Using the oscilloscope in the Y-X mode you will visualise the VTC  $v_Y(v_A)$

##### Results

- VTC  $v_Y(v_A)$ . What is the value of the threshold voltage, based on the VTC from the oscilloscope?

### 2. NAND logic circuit

##### Exploration

Build the circuit in Fig. 2.

- $v_A, v_B \in \{0V; 5V\}$  in all possible combinations
- Measure  $v_Y$  with the dc voltmeter for all possible combinations of the two input voltages.

##### Results

- Electrical operating table containing  $v_A$ ,  $v_B$ ,  $v_Y$ , the off or exc states of  $T_A$  and  $T_B$  for the 4 possible combinations of  $v_A$  and  $v_B$  values from  $\{0V; 5V\}$
- Truth table with A, B logic inputs and Y logic output
- Is the logic function the same as the one determined at 2.P.?

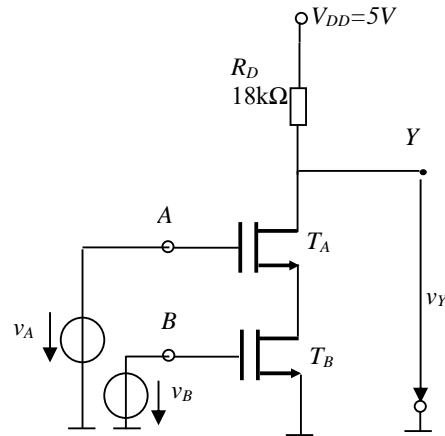


Fig. 2. NAND logic circuit

### 3. AND logic circuit

#### Exploration

Build the circuit in Fig. 3.

- $v_A, v_B \in \{0V; 5V\}$  in all possible combinations
- Measure  $v_Y$  with the dc voltmeter for all possible combinations of the two input voltages.

#### Results

- Electrical operating table containing  $v_A, v_B, v_Y$ , the off or exc states of  $T_A, T_B, T_C$  for the 4 possible combinations of  $v_A$  and  $v_B$  values from  $\{0V; 5V\}$
- Truth table with A, B logic inputs and Y logic output
- Is the logic function the same as the one determined at 3.P.?

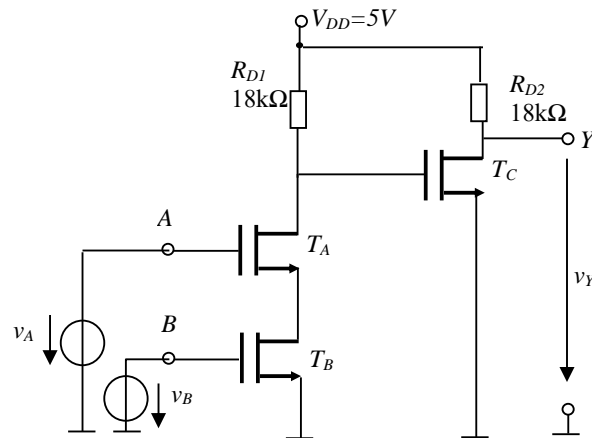


Fig. 3. AND logic circuit

### 4. NOR logic circuit

#### Exploration

Build the circuit in Fig. 4.

- $v_A, v_B \in \{0V; 5V\}$  in all possible combinations
- Measure  $v_Y$  with the dc voltmeter for all possible combinations of the two input voltages.

#### Results

- Electrical operating table containing  $v_A, v_B, v_Y$ , the off or exc states of  $T_A$  and  $T_B$  for the 4 possible combinations of  $v_A$  and  $v_B$  values from  $\{0V; 5V\}$

- Truth table with A, B logic inputs and Y logic output
- Is the logic function the same as the one determined at 4.P.?

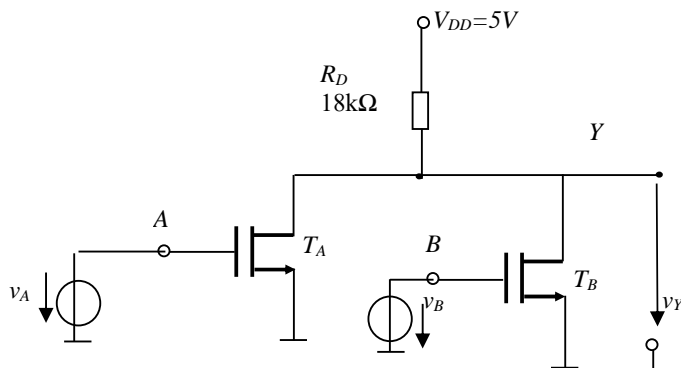


Fig. 4. NOR logic circuit

## 5. OR logic circuit

### Exploration

Build the circuit in Fig. 5.

- $v_A, v_B \in \{0V; 5V\}$  in all possible combinations
- Measure  $v_Y$  with the dc voltmeter for all possible combinations of the two input voltages.

### Results

- Electrical operating table containing  $v_A, v_B, v_Y$ , the off or exc states of  $T_A, T_B, T_C$  for the 4 possible combinations of  $v_A$  and  $v_B$  values from  $\{0V; 5V\}$
- Truth table with A, B logic inputs and Y logic output
- Is the logic function the same as the one determined at 5.P.?

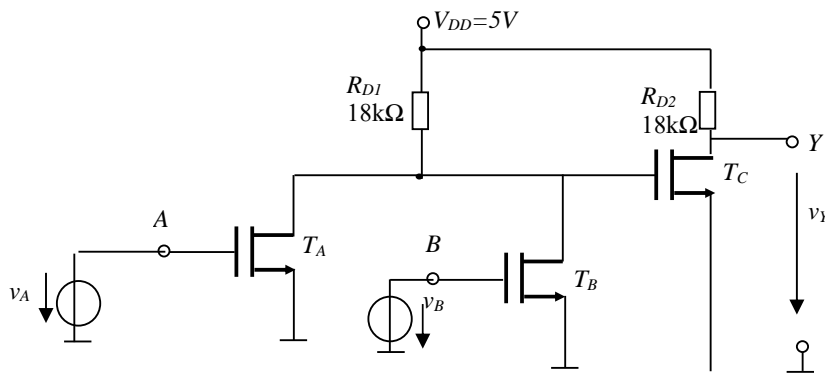


Fig. 5. OR logic circuit

### REFERENCES

1. Oltean, G., Electronic Devices, Editura U.T. Pres, Cluj-Napoca, ISBN 973-662-220-7, 2006
2. Sedra, A. S., Smith, K. C., Microelectronic Circuits, Fifth Edition, Oxford University Press, ISBN: 0-19-514252-7, 2004
3. <http://www.bel.utcluj.ro/dce/didactic/fec/>