

SINGLE-STAGE BJT AMPLIFIERS

I. OBJECTIVES

- Analyzing the CE, CB and CC configurations.
- Determining the effect of the finite load resistance on the parameters of the amplifier.

II. COMPONENTS AND INSTRUMENTATION

Use the breadboard, a 2N2222 BJT, some resistors and capacitors. The supply is obtained from the dc regulated voltage supply. The input voltage is obtained from the signal generator. To visualize the voltage waveforms, a dual-channel oscilloscope is used.

The terminals of the 2N2222 BJT are shown in Fig. 1.



Fig. 1. 2N2222 BJT – pinout diagram

III. PREPARATION

For the BJT, consider $\beta=75$, $V_{BE, on}=0.6V$.

1.P. DC equivalent circuit

- Draw the dc equivalent circuit, based on the schematic in Fig. 2.
- Compute the quiescent point, $Q(V_{CE}, I_C)$.

2.P. Small-signal equivalent circuit

- Draw the small signal equivalent schematic in midfrequency for this stage.
- Compute the values of the small signal model parameters of T: g_m ; r_{be} .
- What is the configuration of this stage? Justify your answer.

- Find the expressions and values of the voltage gain $A_v = v_o/v_i$, the input resistance R_i and the output resistance R_o .
- Plot $v_B(t)$, $v_O(t)$ and $v_o(t)$ for $v_i(t) = 20\sin\omega t$ [mV].
- Recompute any of the previously computed values that are subject to change when the load resistance $R_L = 470\Omega$ is added at the output of the circuit.

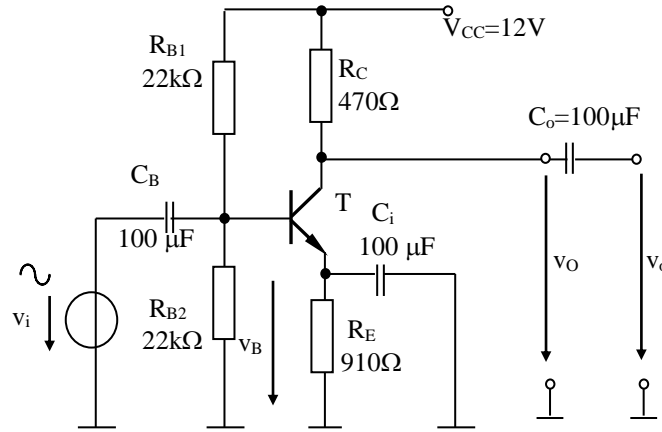


Fig. 2. CE BJT amplifier schematic

IV. EXPLORATION AND RESULTS

1. CE amplifier

Exploration

- Build the circuit in Fig. 2.
- The input voltage is $v_i(t) = 20\sin\omega t$ [mV], frequency of 5kHz.
- Visualize the input and output voltages on the oscilloscope, simultaneously, with both channels in AC mode.
- Is the amplifier inverting or non-inverting?
- Determine the gain $A_v = v_o/v_i$, by measuring the amplitudes of the input and output voltages.
- Set the output channel to DC mode. What is the value of the DC component of the output voltage?
- Increase the amplitude of the input voltage, until the output voltage reaches saturation.
- Starting from 5kHz, increase the frequency of the input voltage, until the output voltage starts to decrease.
- Come back to $v_i(t) = 20\sin\omega t$ [mV]. Add $R_L = 470\Omega$ at the output of the circuit. Determine the new value of the gain.

Results

- The waveforms of the input and output voltages, simultaneously, with both channels in AC mode.
- The amplitudes of the input and output voltages, and the gain.
- The waveforms of the input and output voltages, simultaneously, with the output channel in DC mode.
- The value of the DC component of the output voltage.
- The maximum value of the input voltage that can be amplified without reaching saturation.
- The maximum frequency of the input voltage, for which the output has the same amplitude as for 5kHz.
- The new value of the gain, after adding the finite load resistance in the circuit.

2. CB amplifier

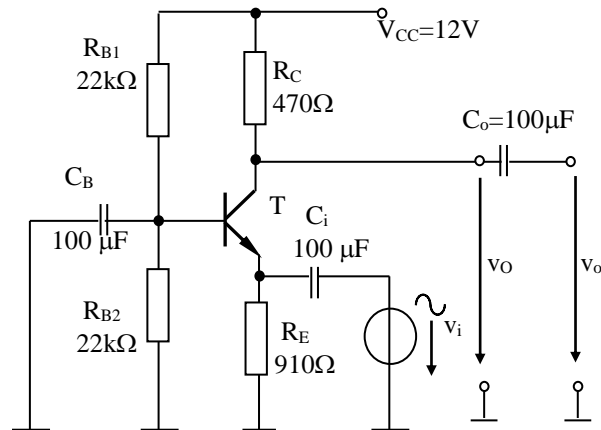


Fig. 3. CB BJT amplifier schematic

Exploration

- Build the circuit in Fig. 3.
- The input voltage is $v_i(t) = 20\sin\omega t$ [mV], frequency of 5kHz.
- Visualize the input and output voltages on the oscilloscope, simultaneously, with both channels in AC mode.
- Is the amplifier inverting or non-inverting?
- Determine the gain $A_v = v_o/v_i$, by measuring the amplitudes of the input and output voltages.
- Set the output channel to DC mode. What is the value of the DC component of the output voltage?
- Add $R_L = 470\Omega$ at the output of the circuit. Determine the new value of the gain.

Results

- The waveforms of the input and output voltages, simultaneously, with both channels in AC mode.
- The amplitudes of the input and output voltages, and the gain.
- The waveforms of the input and output voltages, simultaneously, with the output channel in DC mode.
- The value of the DC component of the output voltage.
- The new value of the gain, after adding the finite load resistance in the circuit.

3. CC amplifier

Exploration

- Build the circuit in Fig. 4.
- The input voltage is $v_i(t) = 20\sin\omega t$ [mV], frequency of 5kHz.
- Visualize the input and output voltages on the oscilloscope, simultaneously, with both channels in AC mode.
- Is the amplifier inverting or non-inverting?
- Determine the gain $A_v = v_o/v_i$, by measuring the amplitudes of the input and output voltages.
- Add $R_L = 470\Omega$ at the output of the circuit. Determine the new value of the gain.

Results

- The waveforms of the input and output voltages, simultaneously, with both channels in AC mode.
- The amplitudes of the input and output voltages, and the gain.
- The new value of the gain, after adding the finite load resistance in the circuit.

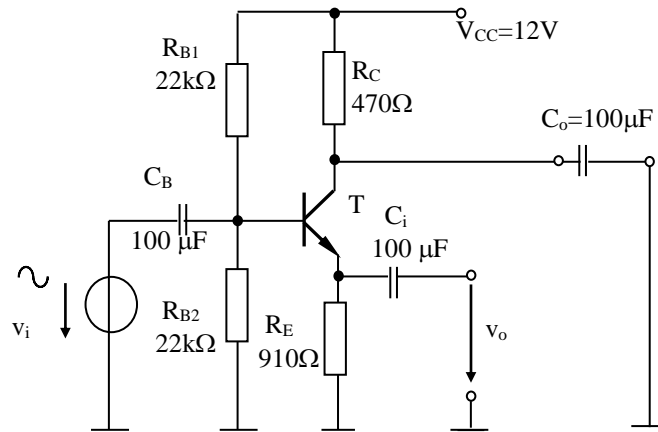


Fig. 4. CC BJT amplifier schematic

Table 1 – Results for the CE, CB, and CC amplifier

Amplifier Parameter	Common emitter CE		Common base CB	Common collector CC
	Computed	Measured	Measured	Measured
Gain $A_v = v_o/v_i$ (R_L - infinite)				
Gain $A_v = v_o/v_i$ ($R_L = 470 \Omega$)				

REFERENCES

1. Oltean, G., Electronic Devices, Editura U.T. Pres, Cluj-Napoca, ISBN 973-662-220-7, 2006
2. Sedra, A. S., Smith, K. C., Microelectronic Circuits, Fifth Edition, Oxford University Press, ISBN: 0-19-514252-7, 2004
3. <http://www.bel.utcluj.ro/dce/didactic/fec>