

# SINUSOIDAL OSCILLATORS

## I. OBJECTIVES

- a) The adjustment of the value of the forward transmission  $a$  in order to fulfill the Barkhausen criterion in Wien bridge oscillators.
- b) Understanding the amplitude stabilization mechanism of the oscillations, using amplitude stabilization circuits with diodes.

## II. COMPONENTS AND INSTRUMENTATION

For the experiments, we use a breadboard and a 741 operational amplifier, two 1N4148 diodes, resistors and capacitors. In order to supply the experimental assembly, we use a dc voltage source. We will also need a sine wave signal generator. To visualize the ac voltages we use a dual channel oscilloscope.

## III. PREPARATIONS

### P.1. The Wien bridge sinusoidal oscillator

The oscillator circuit is presented in Fig.2.

- Which is the frequency of the sine wave signal generated by the oscillator? What is the value of  $|r|$  at the frequency of oscillation? What about the phase of  $r$ ?
- What should be the value of the forward transmission (basic amplifier's gain)  $a$  in order to ensure the oscillation? What happens with the output signal  $v_o$  if  $a$  decreases under this value? What if  $a$  increases over this value?
- As you can see from the scheme in Fig. 2, the circuit doesn't have an input signal, only the power supply. Despite this, we will obtain a sine wave signal at the output of the circuit. Explain the mechanism by which the sine wave signal  $v_o$  at the output of the oscillator is generated.
- In order to obtain at the output of the oscillator a sine wave signal in the absence of an external input signal, is it sufficient to set  $a$  at the value specified in the Barkhausen criterion,  $a_0$ ? How must the value  $a$  be with respect to  $a_0$  after powering up the supply? Why? How does the waveform  $v_o(t)$  look like if  $a$  takes this value different from  $a_0$ ? How must the value  $a$

be modified after the oscillations have appeared in order to obtain at the output a sine wave signal?

- The condition for oscillation start-up and then for maintaining the oscillation after start-up implies the achievement of a:
  - Constant and infinite gain in the circuit.
  - Constant and finite gain, given by the Barkhausen criterion.
  - Larger gain than the one from the Barkhausen criterion, at start-up (after power up), followed by the decrease of the gain until it reaches the value from the Barkhausen criterion.

## **P.2. The amplitude stabilization in Wien bridge oscillators**

- On the oscillator with Wien Bridge from Fig.2, we will study now the amplitude stabilization mechanism.

In a sinusoidal oscillator with OpAmp there is no input signal, and the sinusoidal oscillation is generated when the circuit is powered up.

- For the circuit in Fig. 2, plot the waveform of the differential input signal  $v_{OUT\ WIEN}(t)$  after the circuit's power up. Also plot the output signal, if the basic amplifier's gain is  $a > a_0$ , where  $a_0$  is the basic amplifier's gain that fulfils the Barkhausen criterion.

### **P.2.1. Amplitude stabilization with diodes**

- The oscillator circuit with OpAmp and Wien Bridge, for which the amplitude stabilization is done using two anti-parallel diodes, is presented in Fig. 3.
- In what state (on or off) are the diodes  $D_1$  and  $D_2$  during the transient regime, just after the power up? Compute the gain of the basic amplifier  $a$ , in this case. Plot  $v_O(t)$  and  $v_{OUT\ WIEN}(t)$  in this case.
- In permanent regime, when we already have at the output a sine wave signal  $v_O(t)$ , are  $D_1$  and  $D_2$  on? Which is the condition for  $D_1$  and  $D_2$  to be on? Compute the basic amplifier's gain  $a$  in this case.
- Why is it necessary the use of two anti-parallel diodes in the circuit from Fig. 3?
- What is the role of the resistor  $R_5$  in parallel with  $D_1$  and  $D_2$  in the circuit?

## IV. EXPLORATIONS AND RESULTS

### 1. The Wien Bridge sinusoidal oscillator

#### Explorations

- Build the circuit from Fig. 1. Supply the assembly with  $\pm 15\text{V}$  dc.
- Apply at the input of the Wien bridge a sine wave signal  $v_I(t)$  from the signal generator,  $v_I(t) = 9\sin 2\pi v_0 t$  [V], where  $v_0 = 1.6\text{KHz}$ , frequency where the absolute value of the Wien Bridge transfer function is maximum ( $1/3$ ).
- Using the oscilloscope visualize the signals  $v_I(t)$  and  $v_O(t)$  (between OUT and the ground).
- Using potentiometer POT, adjust the value of the forward transmission  $a$  until the amplitude of the signal  $v_O(t)$ ,  $\hat{V}_O$ , equals the amplitude of the signal  $v_I(t)$ ,  $\hat{V}_I$ .

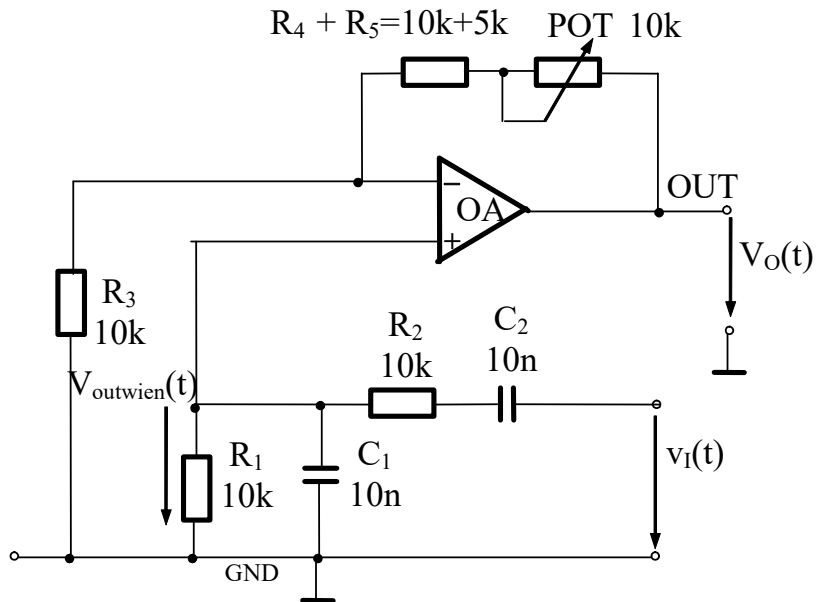


Fig. 1. OpAmp and Wien bridge circuit

- From this point on, no signal will be applied from the signal generator. The new circuit (Fig. 2) is obtained by connecting capacitor  $C_2$  with the output of the OpAmp – the feedback loop is now closed.
- Modify the position of the cursor of POT in order to obtain at the output a sine wave signal  $v_o(t)$ , visualizing simultaneously  $v_o(t)$  and  $v_{OUT\ WIEN}(t)$  on the oscilloscope.
- Plot the signals  $v_o(t)$  and  $v_{OUT\ WIEN}(t)$ . Measure and write down:
  - the amplitude and frequency of  $v_o(t)$ ;
  - the amplitude and frequency of  $v_{OUT\ WIEN}(t)$ .

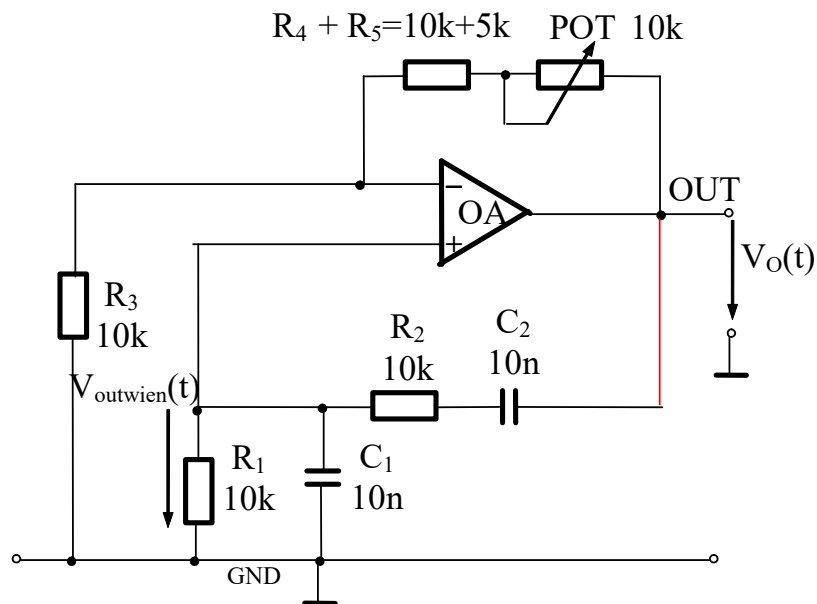


Fig. 2. Wien bridge oscillator

### Results

- Determine  $r$  from the plots of  $v_{OUT\ WIEN}(t)$  and  $v_o(t)$ .
- Determine the value of the phase shift between  $v_{OUT\ WIEN}(t)$  and  $v_o(t)$ . Using your measurements, check the fulfillment of the Barkhausen criterion.

## 2. The amplitude stabilization in Wien Bridge oscillators

### 2.1. Amplitude stabilization with diodes

#### Explorations

- Use the circuit in Fig. 3 by adding two diodes.
- Visualize  $v_o(t)$  on the oscilloscope. If needed, modify the cursor position of Pot until you obtain a sine wave on the output. Plot  $v_o(t)$  and measure the amplitude and frequency of  $v_o(t)$ ;
- Visualize and plot  $v_{OUT\ WIEN}(t)$ . Measure its amplitude and frequency.
- Now visualize  $v_o(t)$  while you decrease the value of Pot, and notice the change in  $v_o(t)$ . Plot  $v_o(t)$  for a randomly selected position of the cursor of POT, other than the one in the previous exploration step.
- Increase the value of POT and notice the change in  $v_o(t)$ . Redraw  $v_o(t)$  for a randomly selected value of Pot, other than the ones in the previous exploration steps.

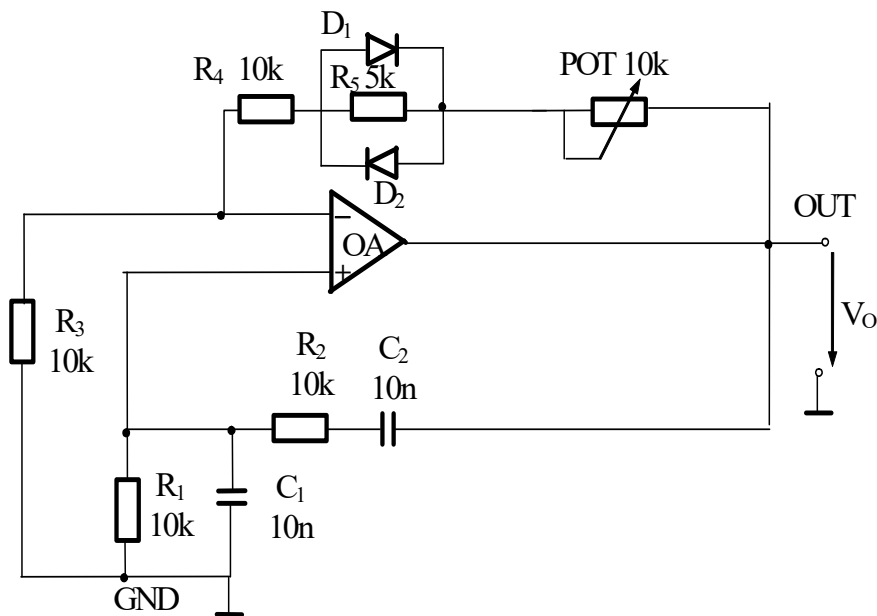


Fig. 3. Wien bridge oscillator: amplitude stabilization with diodes

## Results

- Compare the frequency  $\nu_0$  of the signal  $v_0(t)$  in this Wien Bridge oscillator with amplitude stabilization with the frequency of  $v_0(t)$  in the basic Wien bridge oscillator measured before.
- How can you modify  $v_0(t)$  amplitude,  $\hat{V}_0$  at the oscillator output? Give an approximate expression of  $\hat{V}_0$ .
- Is  $v_0(t)$  a “clean” sine wave (without any distortions)? Why?
- Find the value of the phase shift between  $v_{OUT\ WIEN}(t)$  and  $v_0(t)$ .
- How could you determine, using only the plots of  $v_0(t)$  and  $v_{OUT\ WIEN}(t)$ , the value of the forward transmission  $a$  of the circuit? Compute it.
- What process takes place in the circuit if the value of Pot decreases and how does it influence the output  $v_0(t)$ ? Answer the same question if the value of POT increases.

## REFERENCES

1. Oltean, G., Circuite Electronice, UT Pres, Cluj-Napoca, 2007, ISBN 978-973-662-300-4
2. Sedra, A. S., Smith, K. C., Microelectronic Circuits, Fifth Edition, Oxford University Press, ISBN: 0-19-514252-7, 2004
3. <http://www.bel.utcluj.ro/dce/didactic/fec/fec.htm>