



CONTENTS

Preface	9
1 FUNDAMENTALS	11
Introduction	11
1.1 Electric Signals	11
1.2 Relations and Theorems of Electric Circuits	14
1.2.1 Ohm's Law	14
1.2.2 Kirchhoff's Theorems	14
1.2.3 Resistor Connections	15
1.2.4 Resistive Dividers	17
1.2.5 Superposition Method	19
1.2.6 Thevenin's Theorem	22
1.2.7 Millman's Theorem	23
1.2.8 Power	25
1.3 The Capacitor and the Inductor	26
1.3.1 Current-Voltage Relation	27
1.3.2 Capacitor and Inductor Connections	28
1.3.3 The DC Behavior	28
1.3.3.1 RC Circuit with a Voltage Source	28
1.3.3.2 Charging the Capacitor at Constant Current	30
1.3.4 The AC Behavior	31
1.4 Generalization of Electric Circuit Theorems and Relations	32

1.5	Frequency Response	33
1.5.1	The Complex Transfer Function	33
1.5.2	Frequency Response Representation	34
2	DIODES	41
	Introduction	41
2.1	The Ideal Diode	42
2.2	Switching DR Two-Port Networks	44
2.2.1	Analysis of DR Two-Port Networks	44
2.2.2	The Constant-Voltage-Drop Model	50
2.2.3	DR Two-Port Networks with Biasing Voltage	53
2.2.4	Applications of the DR Two-Port Networks	55
2.3	Switching DR Multi-Port Networks	56
2.3.1	Maximum DR Multi-Port Networks	56
2.3.2	Minimum DR Multi-Port Networks	60
2.3.3	Applications of DR Multi-Port Networks	62
2.3.3.1	Full-Wave Rectifiers	62
2.3.3.2	Backup Supply	65
2.3.3.3	DR Logic Circuits	66
2.4	Switching DC Two-Port Networks	70
2.4.1	Temporal Extreme DC Two-Port Networks	70
2.4.2	Translation DC Two-Port Networks	72
2.4.3	Applications of DC Two-Port Networks	74
2.4.3.1	Voltage Multipliers	74
2.4.3.2	Power Supply Filtering	76
2.4.3.3	AM Demodulator	79
2.4.3.4	DC Restorer	80
2.5	Circuits with Diodes in Permanent Conduction	81
2.5.1	Diode Characteristics	81
2.5.2	Analysis of Diode Circuits	85
2.5.3	Parameters of the Diode	87
2.5.3.1	Static Parameters	87
2.5.3.2	Dynamic Parameters. The Small-Signal Model	88

2.5.4	The Zener Diode	92
2.5.5	Zener Diode Applications	95
2.5.5.1	Parametric Voltage Regulator	95
2.5.5.2	Voltage Reference	100
2.5.5.3	Double Voltage Limiters	100
2.5.5.4	Adjustment of the DC Component of a Variable Signal	101
3	THYRISTORS	102
	Introduction	102
3.1	Internal Structure	102
3.2	Operation. Current-Voltage Characteristics	103
3.3	Switching the Thyristor	106
3.3.1	Switching On	106
3.3.2	Switching Off	107
3.4	Thyristor Applications	108
3.4.1	Controlled Half-Wave Rectifier	108
3.4.2	Controlled Full-Wave Rectifier	110
4	OPERATIONAL AMPLIFIERS	112
	Introduction	112
4.1	Electronic Amplifiers	113
4.1.1	The Concept of Electronic Amplifier	113
4.1.2	The Amplifiers Supply	114
4.1.3	Power Transfer and Power Balance	114
4.1.4	Amplifier Types. Models	115
4.1.4.1	Linear Controlled Sources	116
4.1.4.2	Voltage Amplifiers	117
4.1.4.3	Current Amplifiers	119
4.1.4.4	Transconductance Amplifiers	120
4.1.5	Transfer Characteristics. Biasing	121
4.1.6	Determining the Amplifier Parameters	126
4.1.7	Frequency Response	128
4.2	The Operational Amplifier	130

4.2.1	The Op-Amp Terminals	130
4.2.2	Op-Amp Operation. The Ideal Op Amp	132
4.3	Op-Amp Comparators	133
4.3.1	Simple Comparators	135
4.3.2	Special Op Amp for Comparators	139
4.3.3	Simple Comparator Applications	140
4.3.4	Comparators with Hysteresis	143
4.3.5	Comparators with Hysteresis Applications	153
4.4	Op Amp as Amplifier	154
4.4.1	Op-Amp Amplifiers	155
4.4.1.1	Noninverting Amplifier	156
4.4.1.2	Inverting Amplifier	163
4.4.1.3	Differential Amplifier	170
4.4.2	Nonideal Performance of Op Amp	173
4.4.2.1	Finite Gain	173
4.4.2.2	Finite Bandwidth	176
4.4.2.3	Slew Rate	179
4.4.2.4	Offset Voltage	180
4.4.2.5	Bias Currents	182
4.4.2.6	Input and Output Resistances	183
4.4.3	Other Circuits using Op Amp as Amplifier	185
4.4.3.1	Current Sources	186
4.4.3.2	Active Rectifiers	189
4.4.3.3	Integrator – Active Low-Pass Filter	193
4.4.3.4	Negative Impedance Converter	195

5 TRANSISTORS **197**

Introduction	197
5.1 Operating Principle and Operating Regions	198
5.1.1 The Transistor as a Controlled Current Source	198
5.1.2 The Metal-Oxide-Semiconductor Field-Effect Transistor (MOSFET)	204
5.1.3 The Bipolar Junction Transistor (BJT)	212

5.2	Switching Transistors	221
5.2.1	Analog Switches	222
5.2.1.1	AS Implementation	225
5.2.2	Transistor Digital Circuits	229
5.2.2.1	CMOS Logic Gates	232
5.2.2.2	Bipolar Digital Circuits	236
5.3	Transistor as Amplifier	242
5.3.1	DC Biasing	243
5.3.1.1	MOSFET Biasing	246
5.3.1.2	BJT Biasing	250
5.3.2	Small-Signal Operation	254
5.3.2.1	Small-Signal Model of the MOSFET	254
5.3.2.2	Small-Signal Model of the BJT	258
5.3.3	Basic Amplifiers	261
5.3.3.1	Common-Source and Common-Emitter Amplifiers	262
5.3.3.2	Common-Gate and Common-Base Amplifiers	268
5.3.3.3	Common-Drain and Common-Collector Amplifiers	272
5.3.3.4	Emitter Degeneration Amplifier	276
5.3.3.5	Frequency Response of the Common-Source and Common-Emitter Amplifiers	277
5.3.4	Cascode Amplifiers	289
5.3.5	Current Sources and Current Mirrors	294
5.3.5.1	MOSFET Current Sources and Current Mirrors	294
5.3.5.2	BJT Current Sources and Current Mirrors	298
	APPENDIX 1 MOSFET – Structure and Physical Operation	302
	APPENDIX 2 BJT – Structure and Physical Operation	307
	References	313